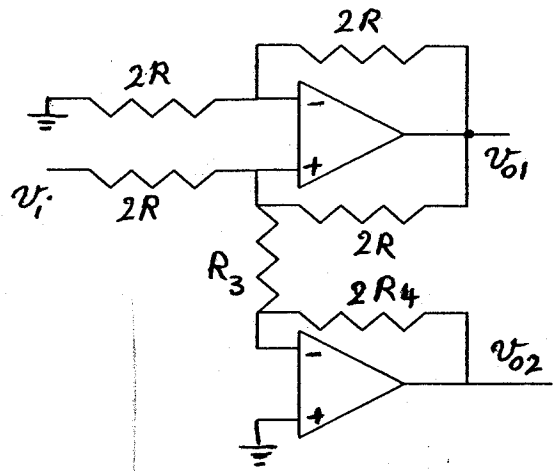


(ECE3455, Q3, Sum03) In the circuit shown,

- Find the gain V_o/V_i as a function of resistors.
- Find the gain V_o/V_i as a function of resistors.

(B)



solution:

(a) The voltage of node ① is half of the V_{o1} or $V_{o1}/2$

so the voltage of node ② is also $V_{o1}/2$, the voltage of node ③ is zero (0),

if we write a KCL at node ② we'll have

$$\frac{V_i - V_{o1}/2}{2R} = \frac{V_{o1}/2 - V_{o1}}{2R} + \frac{V_{o1}/2}{R_3}$$

$$\frac{V_i}{2R} - \frac{V_{o1}}{4R} = -\frac{V_{o1}}{4R} + \frac{V_{o1}}{2R_3}$$

$$\textcircled{1} \quad \boxed{\frac{V_{o1}}{V_i} = \frac{R_3}{R}}$$

so it is a non-inverting amp. with a gain similar to inverting form

(b) writing a node voltage eq. at node ③,

$$\frac{V_{o1}/2}{R_3} = \frac{0 - V_{o2}}{2R_4} \quad \text{or} \quad V_{o2} = -\frac{R_4}{R_3} V_{o1}$$

using eq ① $V_{o2} = -\frac{R_4}{R_3} \times \frac{R_3}{R} V_i = -\frac{R_4}{R} V_i$

$$\boxed{\frac{V_o}{V_i} = -\frac{R_4}{R}}$$