

Name: \_\_\_\_\_ (please print)

Signature: \_\_\_\_\_

**ECE 3455  
Final Exam  
August 11, 2010**

Exam duration: 180 minutes

- You may have one 8 ½ x 11 in. "crib" sheet, written on both sides, during the quiz. You may have any calculator you choose, but no computers. No other notes or materials will be allowed.
- Show all work necessary to complete the problem on these pages. A solution without the work shown will receive no credit.
- Show units in intermediate and final results, and in figures.
- If your work is sloppy or difficult to follow, points will be subtracted.

***This exam has 11 pages, including the cover sheet. Raise your hand if you are missing a page.***

1 \_\_\_\_\_ /45

2 \_\_\_\_\_ /35

3 \_\_\_\_\_ /45

4 \_\_\_\_\_ /35

5 \_\_\_\_\_ /40

Total \_\_\_\_\_ /200

*Note: the exam score will be normalized to 100.*

1. **(45 points)** Design an op-amp circuit that produces a triangle wave output with a period of 3 ms and an amplitude of 1.2 V. In addition, the triangle wave must have an adjustable dc offset between 0 and 2 V. As for components, assume the following.

- You have ideal dual-power-supply op amps that will function correctly as long as the power supplies are no smaller than  $\pm 3$  V and no larger than  $\pm 15$  V.
- You may use any number of op amps, resistors, capacitors, and inductors; these components may have any value.
- The only power supplies available are 9 V batteries that are otherwise ideal. You may use as many as you like.


2. (35 points) The transfer function for a particular amplifier is given below. The magnitude of  $T(\omega)$  at  $\omega = 4500$  rad/s is  $-15$  dB.  $K$  is not given, but it is known to be positive and real. All frequencies are in rad/s.

- i) Using the graph on the next page, plot the magnitude Bode plot for this amplifier.
- ii) Find the phase of  $T(\omega)$  as  $\omega \rightarrow \infty$ .
- iii) Find the phase of  $T(\omega)$  as  $\omega \rightarrow 0$ .


$$T(\omega) := K \cdot \frac{(j\omega + 2000)^2 \cdot (j\omega + 10000)^2}{j\omega \cdot (j\omega + 400)(j\omega + 50000) \cdot (j\omega + 100000)}$$

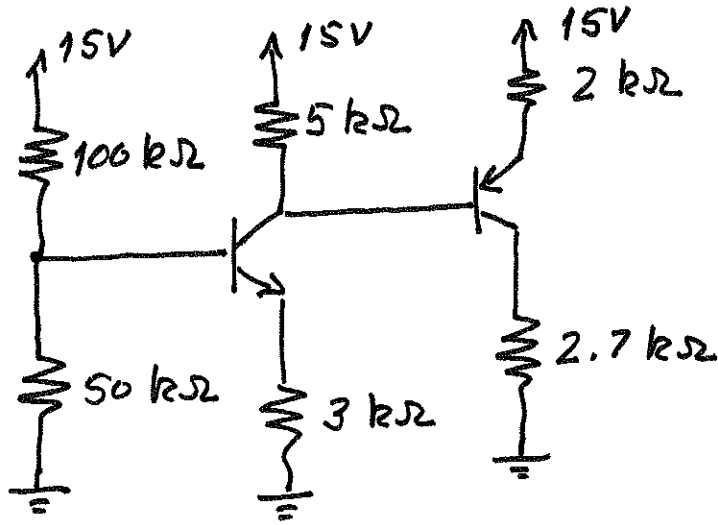
3. (45 points) For the circuit below, find the dc terminal voltages (at emitter, collector, and base) for each BJT. Be sure to test any assumptions you make about the operating region of the BJTs.

$V_{CESAT} = 0.3V$   
 $\beta = 100$   
 (both BJT's)



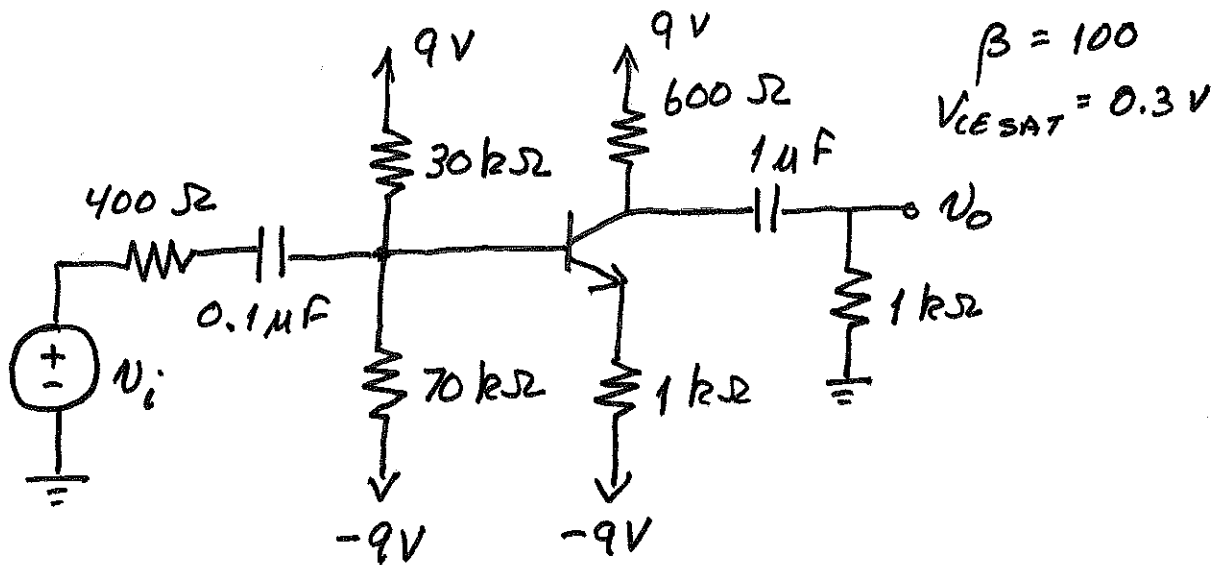
4. (35 points) For the circuit below, find the transfer function  $T(\omega) = V_o/V_i$ .




Room for extra work

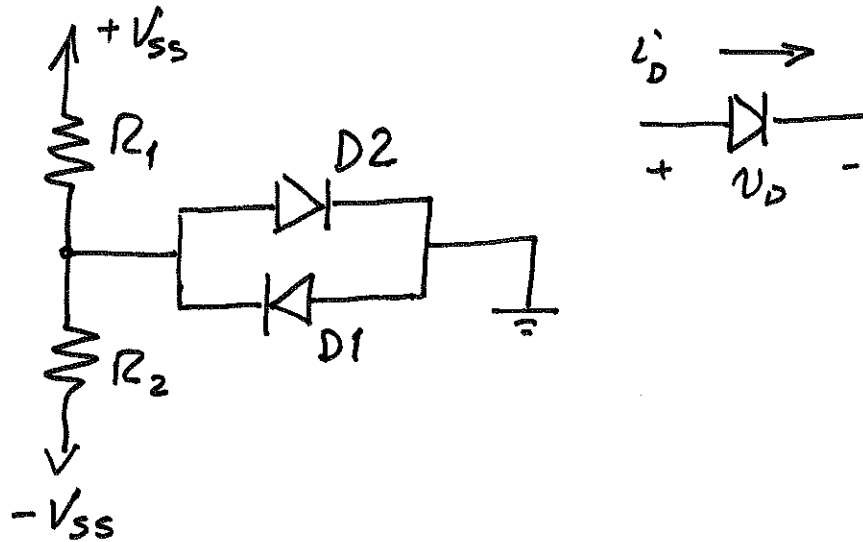5. (40 points) On the following page is shown the piecewise linear model for the diodes in the circuit below. The diodes are identical.

Choose resistors and a power supply value  $V_{SS}$  so that diode  $D_2$  is in region 1. In doing so, limit ~~the magnitude of  $V_{SS}$  to no more than 20 V,~~ and the resistor values to no more than 10 k $\Omega$ . Be sure to prove that diode  $D_1$  is the region you assume it to be.





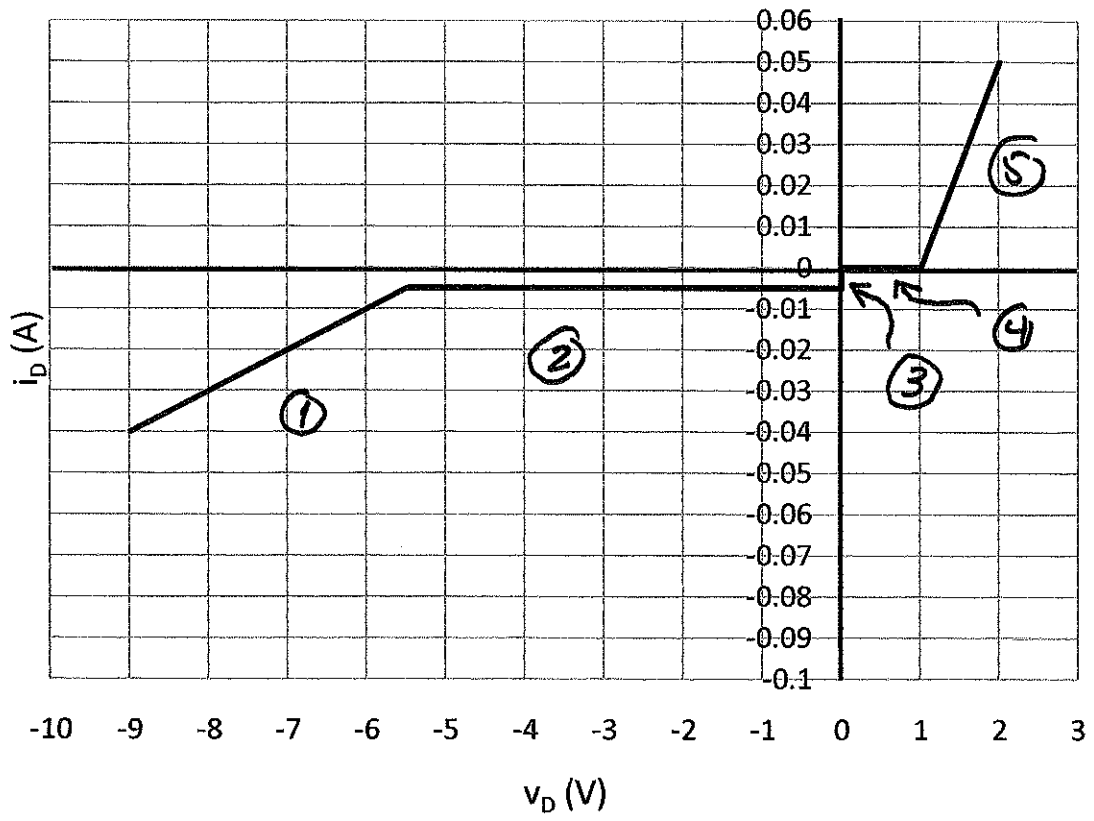

Name: SOLUTIONS (please print)

Signature: \_\_\_\_\_

ECE 3455  
Final Exam  
August 11, 2010

Exam duration: 180 minutes

- You may have one 8 ½ x 11 in. "crib" sheet, written on both sides, during the quiz. You may have any calculator you choose, but no computers. No other notes or materials will be allowed.
- Show all work necessary to complete the problem on these pages. A solution without the work shown will receive no credit.
- Show units in intermediate and final results, and in figures.
- If your work is sloppy or difficult to follow, points will be subtracted.

***This exam has 11 pages, including the cover sheet. Raise your hand if you are missing a page.***

1 \_\_\_\_\_ /45

2 \_\_\_\_\_ /35

3 \_\_\_\_\_ /45

4 \_\_\_\_\_ /35

5 \_\_\_\_\_ /40

Total \_\_\_\_\_ /200

*Note: the exam score will be normalized to 100.*

2. (35 points) The transfer function for a particular amplifier is given below. The magnitude of  $T(\omega)$  at  $\omega = 4500$  rad/s is  $-15$  dB.  $K$  is not given, but it is known to be positive and real. All frequencies are in rad/s.


- i) Using the graph on the next page, plot the magnitude Bode plot for this amplifier.  
 ii) Find the phase of  $T(\omega)$  as  $\omega \rightarrow \infty$ .  
 iii) Find the phase of  $T(\omega)$  as  $\omega \rightarrow 0$ .

$$T(\omega) := K \cdot \frac{(j\omega + 2000)^2 \cdot (j\omega + 10000)^2}{j\omega \cdot (j\omega + 400) \cdot (j\omega + 50000) \cdot (j\omega + 100000)}$$

Pole/Zero analysis:

- i)  $Z_1$  double at  $\omega = 2000$  rad/s     $Z_2$  double at  $\omega = 10,000$  rad/s  
 $P_1$  at 0     $P_2$  at  $\omega = 400$  rad/s  
 $P_3$  at  $\omega = 50,000$  rad/s     $P_4$  at  $\omega = 100,000$  rad/s.

Rough sketch:

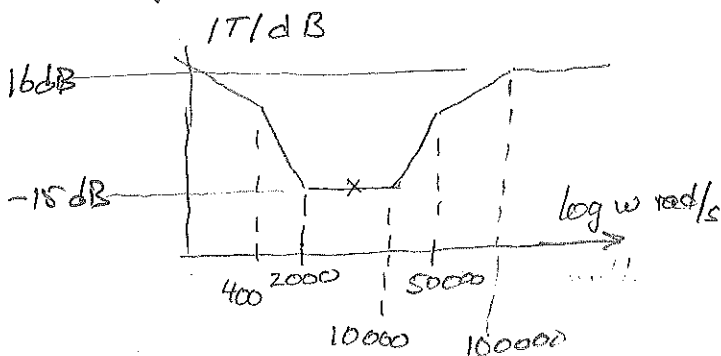

In principle, knowing  $|T(\omega = 4500 \text{ rad/s})|$  and all slopes, we do not need to know  $K$ . We will solve for it anyway...

$$-15 \text{ dB} \Rightarrow |T(\omega)| = 10^{-15/20} = 0.1778$$

$$|T(\omega)|_{\omega=4500 \text{ rad/s}} = K \cdot 0.02854 \Rightarrow K = \frac{0.1778}{0.02854} = 6.23$$

As  $\omega \rightarrow \infty \Rightarrow T(\omega) \rightarrow K \rightarrow 15.9 \text{ dB}$


ii)  $\omega \rightarrow \infty \Rightarrow T(\omega) \rightarrow K \rightarrow 0^\circ$

iii)  $\omega \rightarrow 0 \Rightarrow T(\omega) \rightarrow \frac{K'}{j\omega} \rightarrow -90^\circ$

3  
 magnitude:  
 axes: 2 x 2 ea = 4


Slopes: 6 x 2 ea. = 12  
 Breakpts: 6 x 2 ea. = 12

$|T(\omega)|$  dB

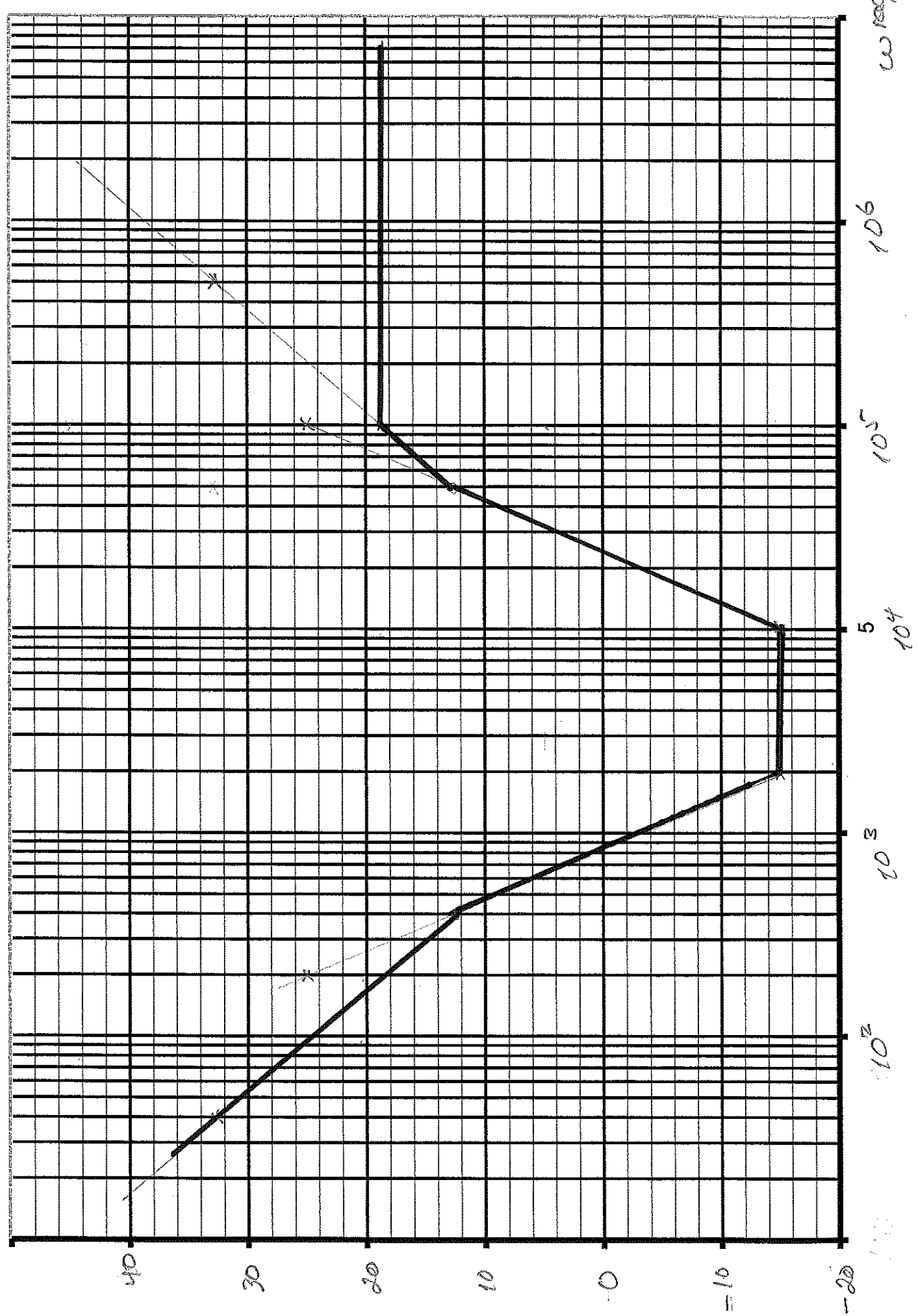


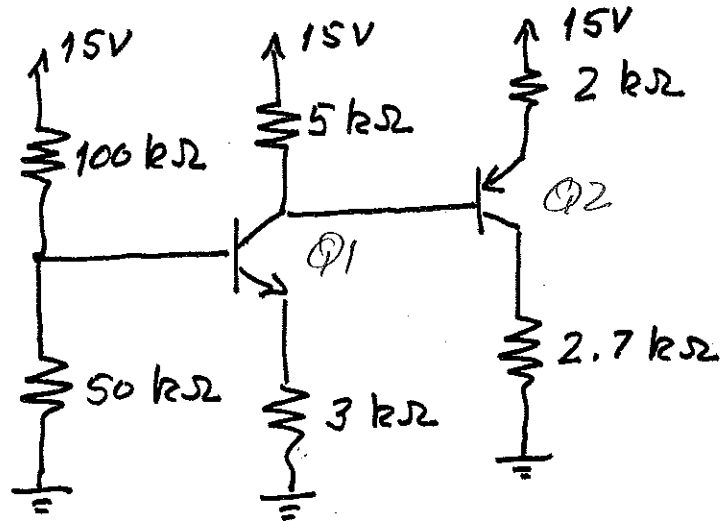3. (45 points) For the circuit below, find the dc terminal voltages (at emitter, collector, and base) for each BJT. Be sure to test any assumptions you make about the operating region of the BJTs.

$V_{CESAT} = 0.3V$   
 $\beta = 100$   
 (both BJT's)



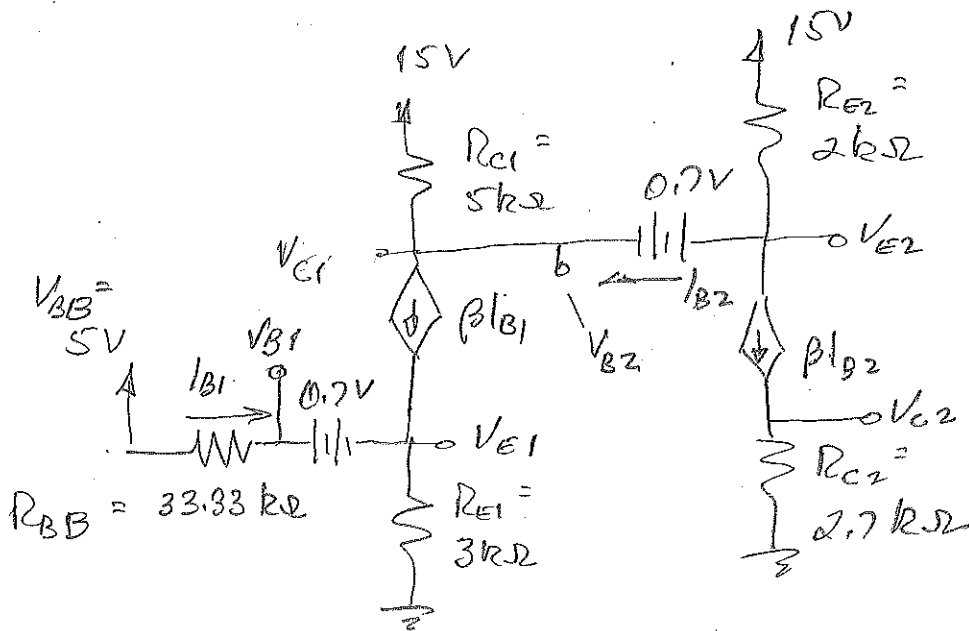We will guess linear region for both. Given 15V and 0 as shown, we expect current to be flowing top to bottom, which is linear region for both BJT's.



model #12

$$V_{BB} = 15 \cdot \frac{50}{150} = 5V$$

$$R_{BB} = 100k \parallel 50k = 33.33k\Omega$$

✓ ⇒ TEST

Room for extra work

$$\frac{V_{C1} - 15}{5000} + \beta I_{B1} + \frac{V_{C1} + 0.7 - 15}{2000} + \beta I_{B2} = 0 \quad (1)$$

$$-5 + 33.33 \times 10^3 I_{B1} + 0.7 + 101 I_{B1} \cdot 3000 = 0 \quad (2)$$

$$\Rightarrow I_{B1} = 12.78 \mu A \quad \checkmark$$

$$(\beta + 1) I_{B2} = \frac{15 - V_{CE2}}{2000} = \frac{15 - (V_{C1} + 0.7)}{2000} \quad (3)$$

$$\Rightarrow I_{B2} = \frac{1}{101} \cdot \frac{14.3 - V_{C1}}{2000}$$

$$(1) + (2) + (3) \Rightarrow \boxed{V_{C1} = 8.747 V} \quad +3$$

$$\Rightarrow I_{B2} = 27.49 \mu A \quad \checkmark \quad +2$$

$$\boxed{V_{CE1} = (\beta + 1) I_{B1} \cdot 3000 = 3.87 V} \quad +2$$

$$V_{C1} - V_{CE1} = 8.75 - 3.87 = 4.88 V \quad \checkmark$$

$$\boxed{V_{C2} = \beta I_{B2} \cdot 2700 = 7.42 V} \quad +2$$

$$\boxed{V_{CE2} = V_{C1} + 0.7 = 9.45 V} \quad +2$$

$$V_{C2} - V_{CE2} = 7.42 - 9.45 = -2.03 V \quad \checkmark$$

$$\boxed{V_{B1} = V_{BB} - I_{B1} \cdot R_{BB} = 4.57 V} \quad +2$$


$$\boxed{V_{B2} = V_{C1} = 8.747 V} \quad +2$$

So tests for  $I_{B1}$ ,  $I_{B2}$   
and  $V_{CE1}$ ,  $V_{CE2}$  are OK.

$V_s = +13$


Tests: +8

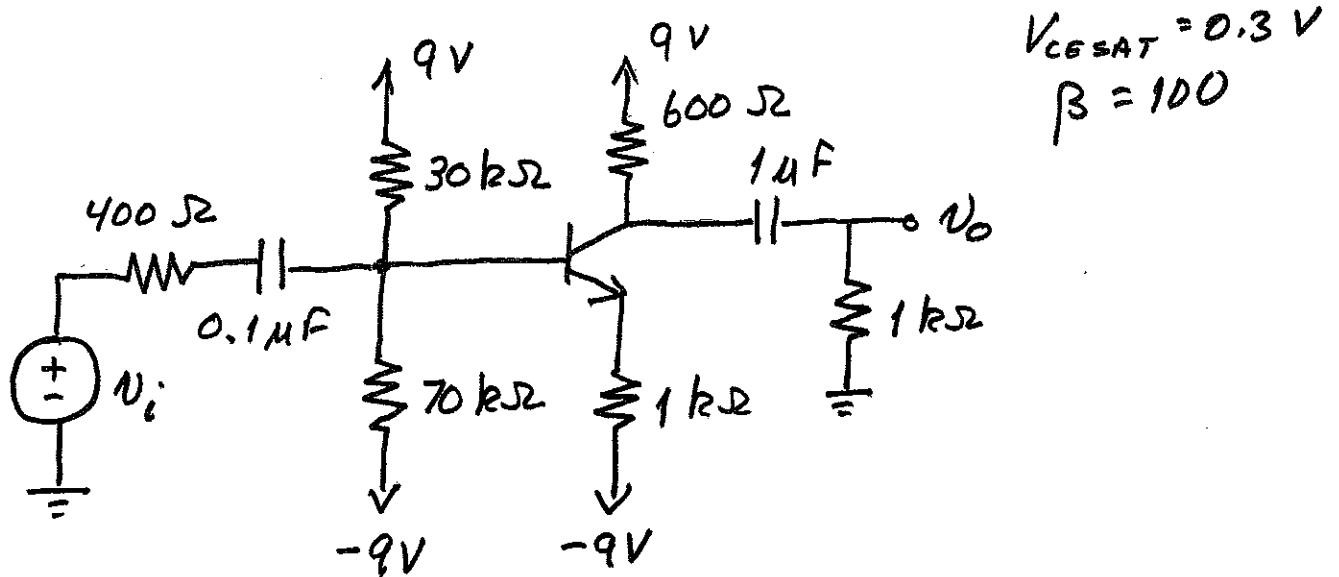4. (35 points) For the circuit below, find the transfer function  $T(\omega) = V_o/V_i$ .



We will assume active mode since the  $V_{CE}$ -resistor bias scheme shown seems to be designed for this region.

DC analysis:

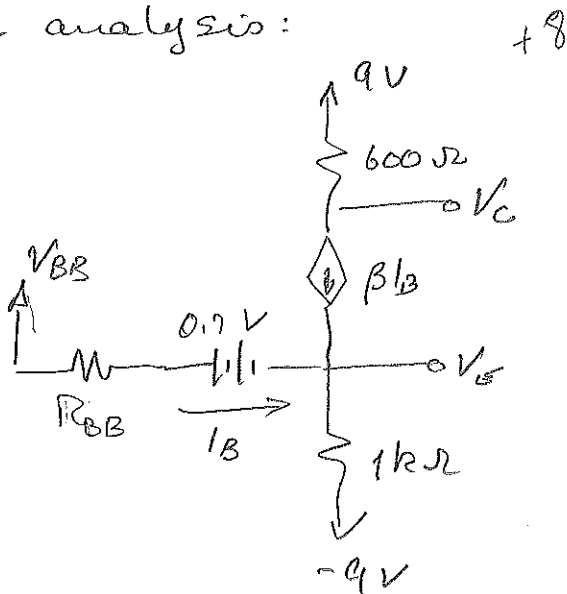

$$I_B = \frac{3.6 + 9 - 0.7}{21000 + 101(1000)}$$

$$= 97.54 \mu\text{A} \checkmark$$

$$V_C = 9 - (\beta I_B) \cdot 600 = 3.15 \text{ V}$$

$$V_E = 1000(\beta + 1)I_B - 9$$

$$= 0.85 \text{ V}$$

$$V_{CE} = 3.15 - 0.85 = 2.30 \text{ V} \checkmark$$

$$V_{BB} = 18 \cdot \frac{70}{70+30} - 9 = 3.6 \text{ V}$$


$$R_{BB} = 30\text{k} \parallel 70\text{k} = 21 \text{ k}\Omega$$

$$\Rightarrow r_{\pi} = \frac{V_T}{I_B} = \frac{0.025}{97.54 \times 10^{-6}}$$

$$= 256 \Omega$$

Room for extra work

+15

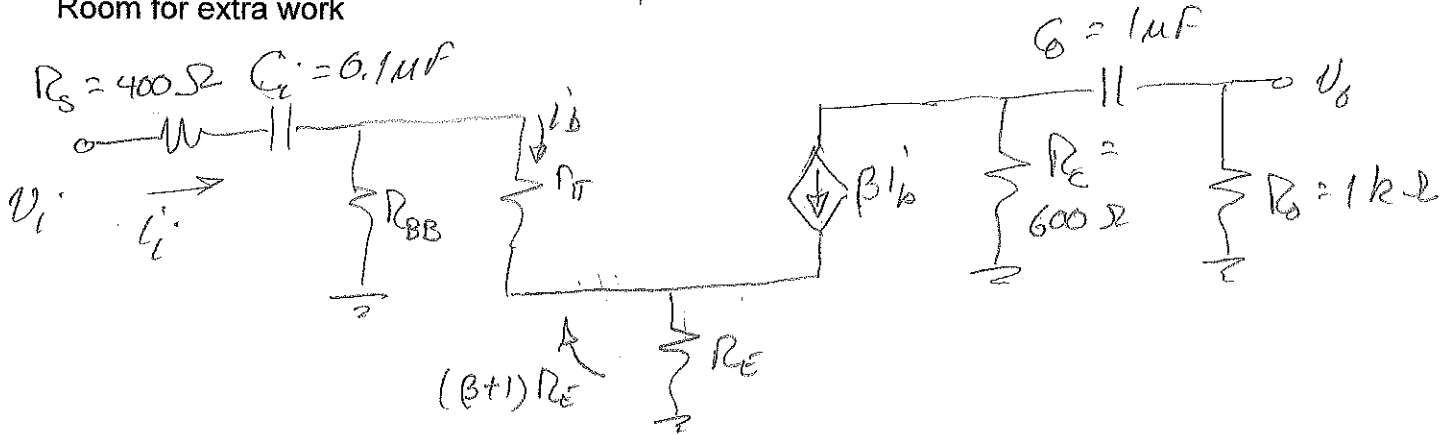

$$\bar{V}_o = -\beta \bar{I}_b \cdot \frac{R_c}{1 + j\omega C_0 (R_o + R_c)} = -\beta \bar{I}_b \cdot \frac{j\omega C_0 R_o \cdot R_c}{1 + j\omega C_0 (R_o + R_c)}$$

$$\bar{Z}_i = R_s + \frac{1}{j\omega C_i} + R_{BB} \parallel (r_{\pi} + (\beta+1)R_E)$$

$$\approx R_s + R_{BB} \parallel (\beta+1)R_E + \frac{1}{j\omega C_i}$$

$$\bar{I}_i = \frac{\bar{V}_i}{\bar{Z}_i} \quad \bar{I}_b = \bar{I}_i \cdot \frac{R_{BB}}{R_{BB} + (\beta+1)R_E + r_{\pi}} \approx 0$$


+12

$$\frac{\bar{V}_o}{\bar{V}_i} = \frac{-j\omega C_0 R_o R_c}{1 + j\omega C_0 (R_o + R_c)} \cdot \beta \frac{R_{BB}}{R_{BB} + (\beta+1)R_E} \cdot \frac{1}{R_s + R_{BB} \parallel (\beta+1)R_E + \frac{1}{j\omega C_i}}$$



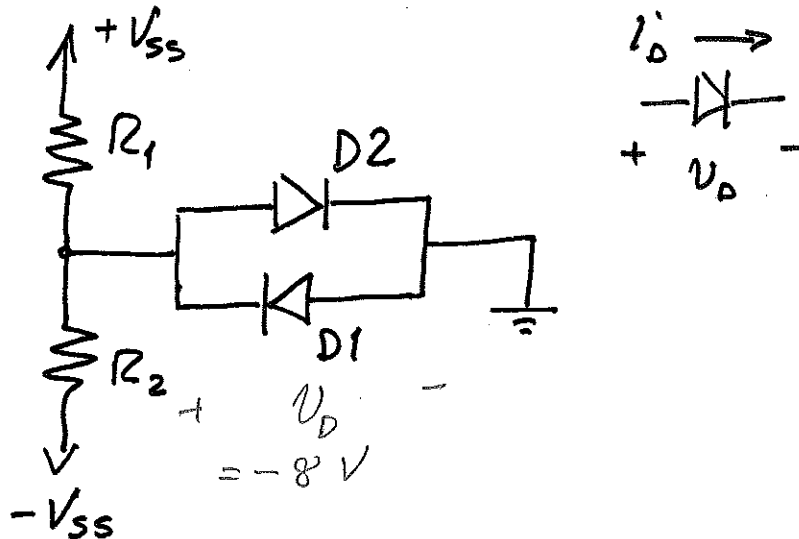
5. (40 points) On the following page is shown the piecewise linear model for the diodes in the circuit below. The diodes are identical.

Choose resistors and a power supply value  $V_{SS}$  so that diode  $D_2$  is in region 1. In doing so, limit ~~the magnitude of  $V_{SS}$  to no more than 20 V,~~ and the resistor values to no more than 10 k $\Omega$ . Be sure to prove that diode  $D_1$  is the region you assume it to be.




Since we require only that  $D_2$  be in region 1, we can simply choose an operating point in that region:

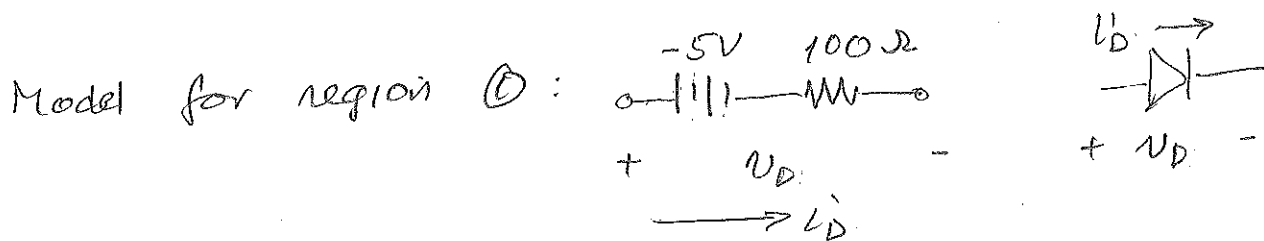$D_2: v_{D2} = -8V \quad i_{D2}' = -0.03A$  (arbitrary choice)



{ Extrapolating the  $i_D'$ - $v_D$  curve to the  $i_D' = 0$  axis  $\Rightarrow$  voltage source is  $-5V$ . Taking the inverse of the slope  $\Rightarrow$  resistance is  $\frac{\Delta V}{\Delta I} = \frac{1V}{10mA} = 100\Omega$ .

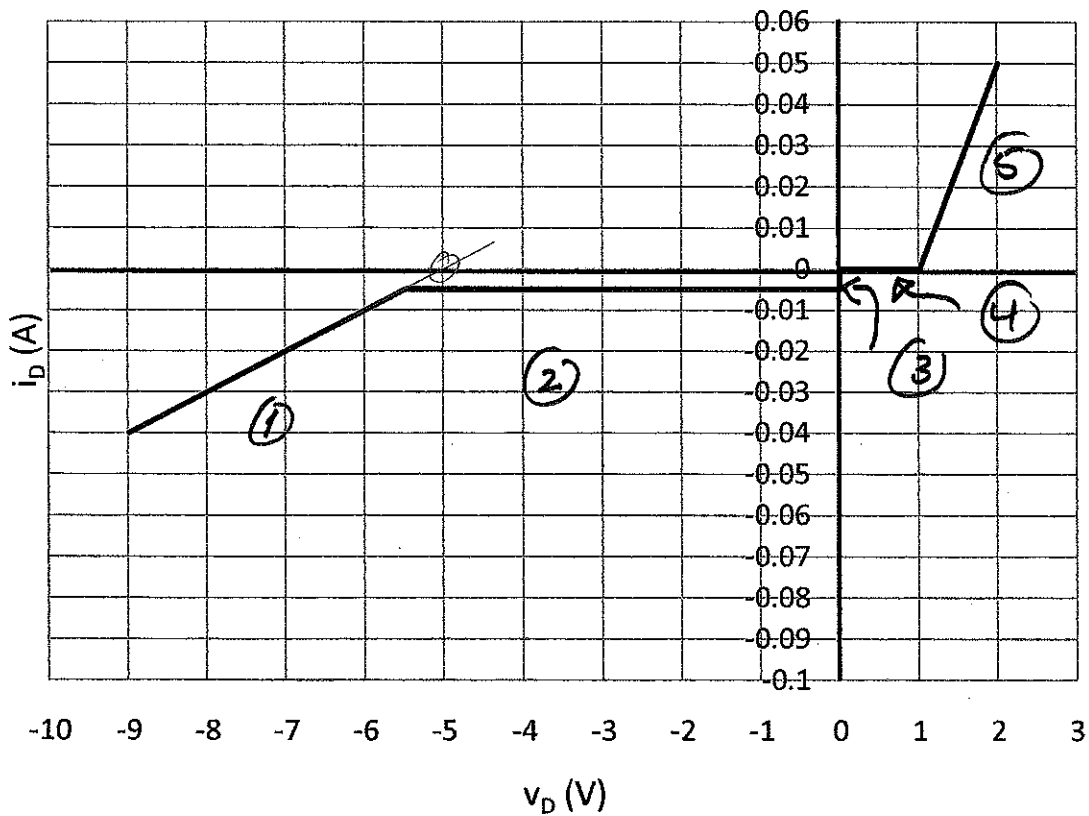
{ check:  $v_D = -8V \Rightarrow i_D' = -0.03A$ . Then according to the model,  $v_D = -5 + 100(-0.03) = -8V$  so this checks.



Now the Thevenin equivalent of the biasing circuit is

$$V_{Th} = 2V_{cc} \cdot \frac{R_2}{R_1 + R_2} - V_{ss}$$

$$R_{Th} = R_1 \parallel R_2$$

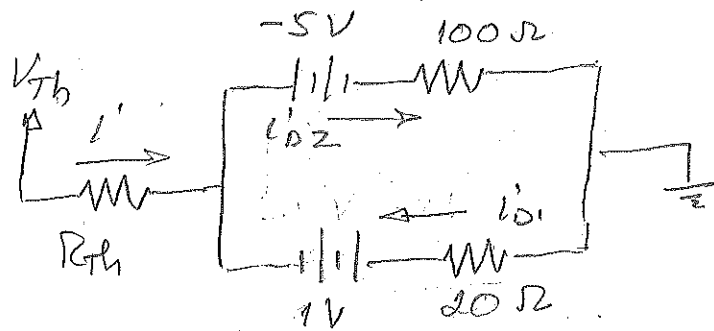

We have assumed  $i_D$  in region 5.

Also we have that  $v_D = -8V$  so

$$v_D = -8V$$

$$-V_{Th} + i' R_{Th} - 8 = 0$$

$$i' = i_{D2} - i_{D1}$$

to pg. 3  
→

Room for extra work

$$i'_{D2} = -0.03 \text{ A}$$

$$\Rightarrow i' = -0.38 \text{ A}$$

$$i'_{D1} = \frac{8 - 1}{20} = 0.35 \text{ A}$$

So we need to satisfy

$$V_{Th} = -0.38 R_{Th} - 8$$

$$\text{If } R_{Th} = 100 \Omega, V_{Th} = -46 \text{ V.} \Rightarrow$$

$$\frac{R_1 R_2}{R_1 + R_2} = 100 \quad \text{and} \quad 2V_{SS} \cdot \frac{R_2}{R_1 + R_2} - V_{SS} = -46$$

$$\Rightarrow \frac{R_2}{R_1 + R_2} = \frac{100}{R_1} \Rightarrow 2V_{SS} \cdot \frac{100}{R_1} - V_{SS} = -46$$

$$\text{If } V_{SS} = -100 \text{ V, } R_1 = 137 \Omega.$$

$$\Rightarrow R_2 = 370 \Omega.$$

$$\text{Check: } R_1 / R_2 = 137 / 370 = 100 \Omega \checkmark$$

$$V_{Th} = -200 \cdot \frac{R_2}{R_1 + R_2} + 100 = -46 \checkmark$$

D1 is clearly in  $\odot$  since  $i'_{D1} = 0.14 \text{ A}$ .