

Name: SOLUTIONS (please print)

Signature: \_\_\_\_\_

ECE 3455  
Mid-Term Exam  
July 13, 2010

Exam duration: 100 minutes

- You may have one 8 ½ x 11 in. “crib” sheet, written on both sides, during the quiz. You may have any calculator you choose, but no computers. No other notes or materials will be allowed.
- Show all work necessary to complete the problem on these pages. A solution without the work shown will receive no credit.
- Show units in intermediate and final results, and in figures.
- If your work is sloppy or difficult to follow, points will be subtracted.

***This exam has 10 pages, including the cover sheet. Raise your hand if you are missing a page.***

1 \_\_\_\_\_ /20

2 \_\_\_\_\_ /25



3 \_\_\_\_\_ /25

4 \_\_\_\_\_ /30

Total \_\_\_\_\_ /100

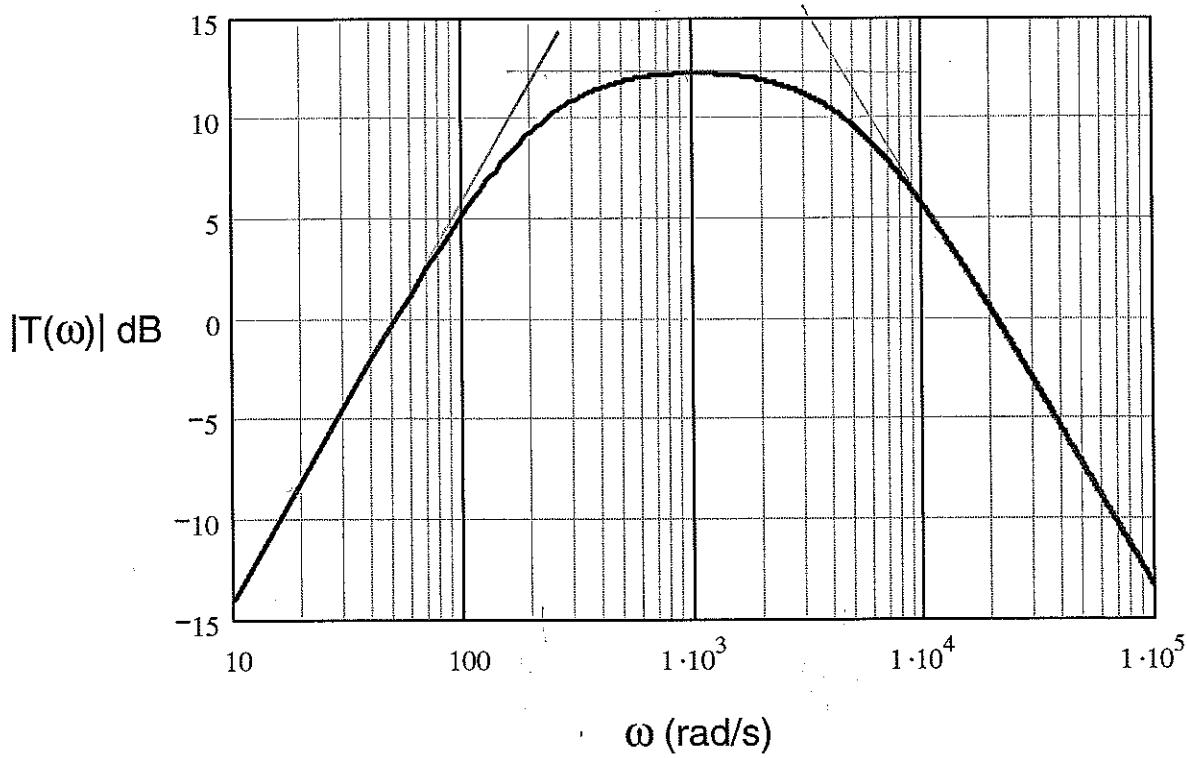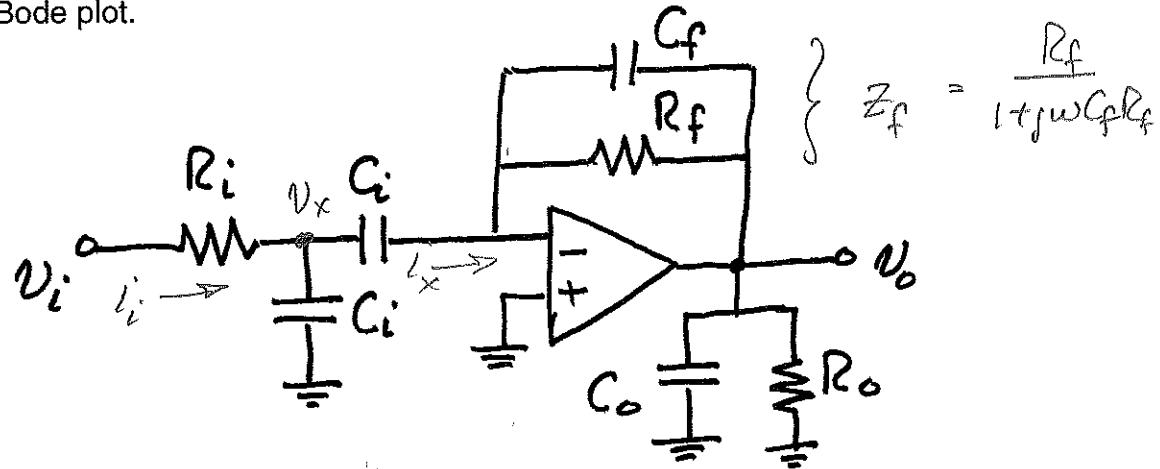1. (20 points) For the circuit shown below, do the following.


- Find the transfer function  $T(\omega) = V_o/V_i$ .
- The graph below is a magnitude Bode plot for the circuit; you can think of it as providing specifications for the circuit. Choose circuit component values to meet these specifications. Be sure your choices reproduce the important features of the Bode plot.



i)
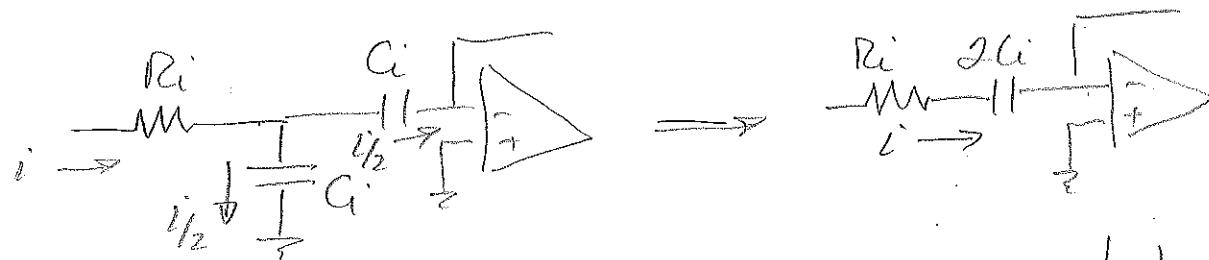
## Room for Extra Work

There is something interesting going on in the input of this circuit. It would appear that the capacitors  $C_i$  are in parallel so that all we need do is:



This correctly predicts the input impedance but it does not give the correct output. For that we need a more complete analysis. Looking at the original circuit:

$$\frac{\bar{V}_x}{j\omega C_i} + \frac{\bar{V}_x}{j\omega C_i} + \frac{\bar{V}_x - \bar{V}_i}{R_i} = 0 \Rightarrow \bar{V}_x = \frac{\bar{V}_i}{1 + j\omega 2C_i R_i}$$

$$\text{Thus } \bar{I}_x = j\omega C_i \bar{V}_x = \frac{j\omega C_i \bar{V}_i}{1 + j\omega 2C_i R_i} = \bar{I}_f$$

$$\text{So } \bar{V}_o = -\bar{I}_x Z_f = -\frac{j\omega C_i \bar{V}_i}{(1 + j\omega 2C_i R_i)(1 + j\omega C_f R_f)} R_f$$

+9

$$\boxed{T(\omega) = \frac{\bar{V}_o}{\bar{V}_i} = \frac{-j\omega C_i R_f}{(1 + j\omega 2C_i R_i)(1 + j\omega C_f R_f)}}$$

This is a factor of 2 less than if we had done a simple inverting configuration with the input impedance  $R_i + \frac{1}{j\omega 2C_i}$ . The reason is that the current in the feedback resistor has been reduced by half because of the capacitor to ground.

Room for extra work

In any case,  $C_0$  and  $R_0$  have no effect.

ii) From the graph we have two poles at

$$\omega_{z1} \approx 210 \text{ rad/s} \quad \omega_{z2} \approx 4300 \text{ rad/s.}$$

Our transfer function shows poles at

$$+\infty \quad \frac{1}{G_f R_f} = 4300 \text{ rad/s}, \quad \frac{1}{2C_i R_i} = 210 \text{ rad/s}$$

We have arbitrarily set the poles of  $T(w)$  equal to the poles indicated on the plot. The opposite assignment is also valid. So we have

$$C_f R_f = 2.33 \times 10^{-4} \quad R_i C_i = 2.38 \times 10^{-3}$$

But before we assign values, we note that

$$|T(w=10^3 \text{ rad/s})| = 12.5 \text{ dB} \rightarrow 4.22 \text{ V/V}$$

From our transfer function, we have

$$|T(w=10^3 \text{ rad/s})| = \left| \frac{j(1000)(2.38 \times 10^{-3}/R_i) \cdot R_f}{[1+j(1000)(2)(2.38 \times 10^{-3})][1+j(1000)(2.33 \times 10^{-4})]} \right|$$

$$\approx \left| \frac{j R_f / R_i \cdot 2.38}{(1+j 4.26)(1+j 0)} \right| \approx \frac{R_f}{R_i} \frac{4.26}{4.52} = \frac{1}{2} \frac{R_f}{R_i}$$

$$+2 \quad \boxed{\begin{array}{l} \text{So } R_i = 10 \text{ k}\Omega \quad C_i = 0.476 \mu\text{F} \\ \Rightarrow R_f = 84.4 \text{ k}\Omega \quad C_f = 2.76 \text{ nF} \end{array}} \Rightarrow R_f = 2(4.22)R_i$$

2. (25 points) On the next page you will find the phase Bode plot for a certain circuit. There are no breakpoints outside the frequency range shown. The magnitude Bode plot (not shown) increases with frequency at 20 dB/dec at very low frequencies, and has a constant value of 35 dB at  $\omega = 2,000 \text{ rad/s}$ . Find the transfer function for this circuit.

- +6 • Drop of  $90^\circ/\text{dec}$  at  $\omega = 2 \text{ rad/s} \Rightarrow$  double pole at  $\omega = 20 \text{ rad/s}$ .
  - +3 • Drop reduced to  $45^\circ/\text{dec}$  at  $40 \text{ rad/s} \Rightarrow$  zero at  $\omega = 400 \text{ rad/s}$ .
    - $\omega = 200 \text{ rad/s}$  : effect of double pole ends.
  - +3 • Increase of  $45^\circ/\text{dec}$  at  $\omega = 10^3 \text{ rad/s} \Rightarrow$  zero at  $\omega = 10^4 \text{ rad/s}$ .
    - $\omega = 4000 \text{ rad/s}$  : zero ends
    - $\omega = 10^5 \text{ rad/s}$  : zero ends.
- 

+5

$$T(\omega) = -K \cdot \frac{j\omega(j\omega + 400)(j\omega + 10^4)}{(j\omega + 20)^2}$$

+3

- The  $j\omega$  in the numerator accounts for the  $20 \text{ dB/dec}$  slope indicated in the magnitude Bode plot.

Also,  $|T(\omega)|_{\omega=2000 \text{ rad/s}} = 35 \text{ dB} \Rightarrow |T(\omega)|_{\omega=2 \text{ rad/s}} = 56.2$

+3 But  $|T(\omega)|_{\omega=2000 \text{ rad/s}} = 1.04 \times 10^4 K = 56.2$   
 $\Rightarrow K = \underline{5.4 \times 10^{-3}}$

- +2 Finally, we note that  $\angle T(\omega \rightarrow 0) \rightarrow 90^\circ$ , but the plot indicates  $\angle T(\omega \rightarrow 0) \rightarrow -90^\circ$ , so there must also be a '-' sign in  $T(\omega)$ .

$\angle T(\omega)$ , deg

-90


-135

-180

-225

-270

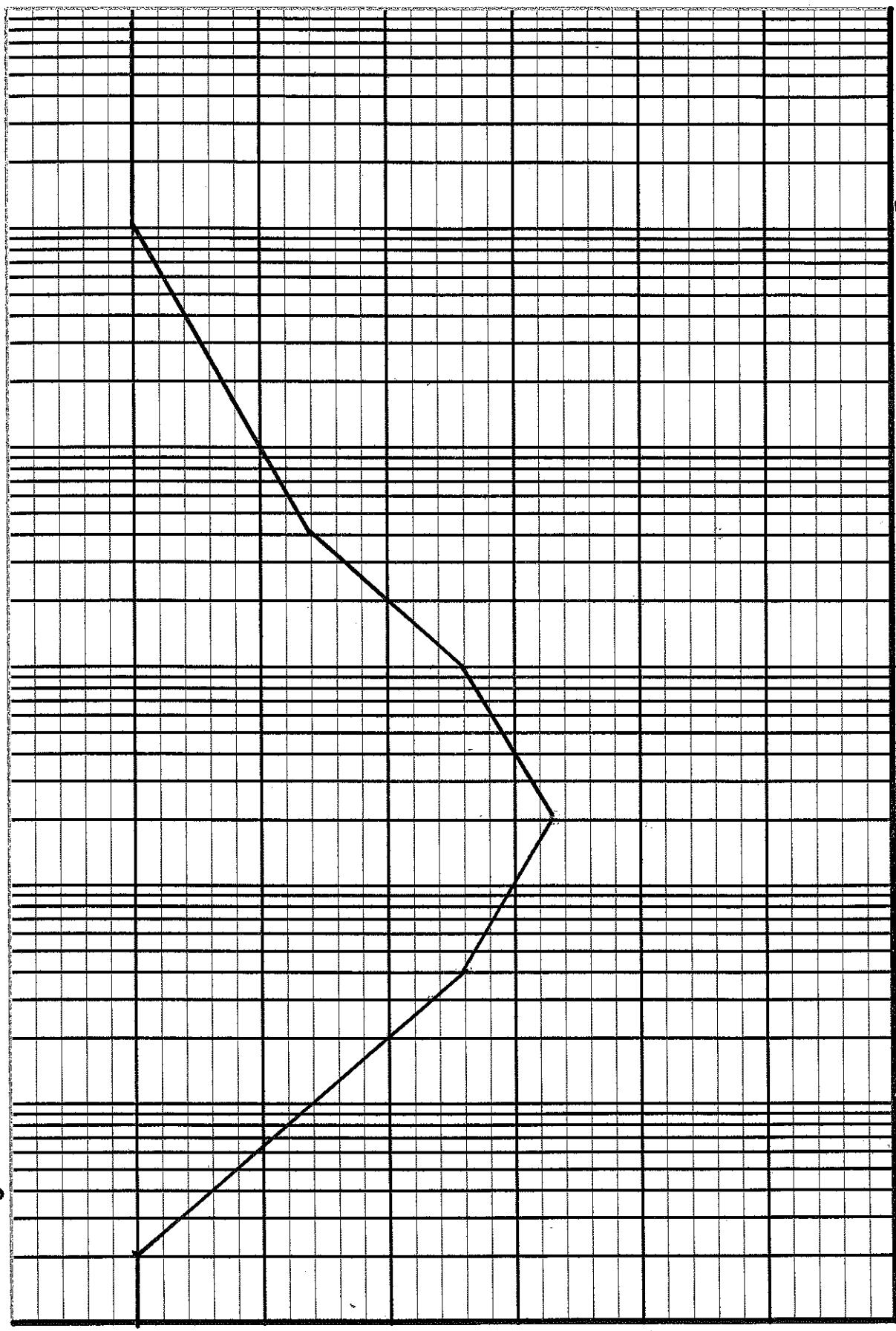$10^0 \quad 10^1 \quad 10^2 \quad 10^3 \quad 10^4 \quad 10^5$   
 $\omega$  (rad/s)




3. (25 points) For the circuit below, do the following.

- i. Choose component values to produce the output


$$v_o(t) = -2.5 \sin(\omega t) + V_{offset} \text{ [V]}$$

where  $V_{offset}$  is a dc offset voltage that ranges from +4 V to -4 V, and the potentiometer is a 10-turn,  $20\text{ k}\Omega$  potentiometer.

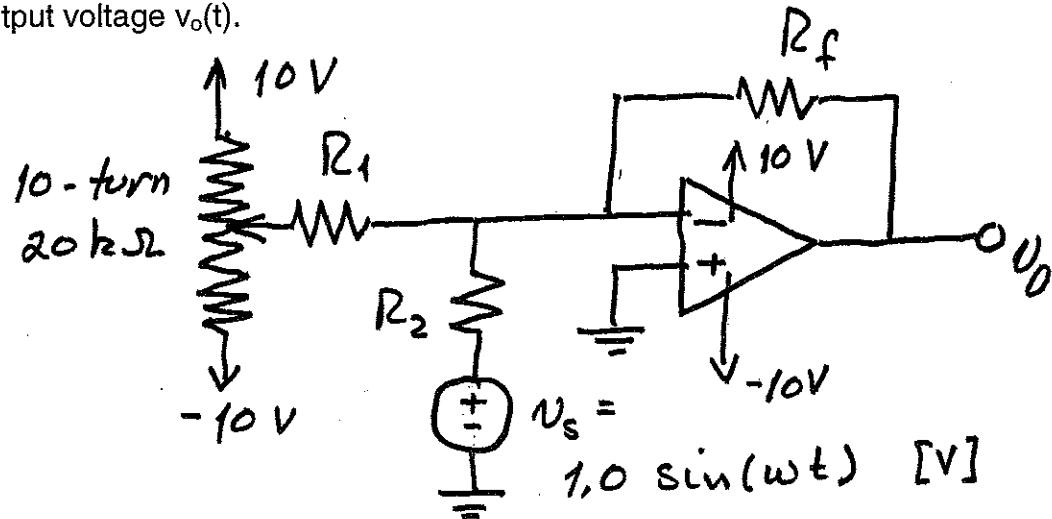- ii. The  $10\text{ k}\Omega$  potentiometer is set to 4 turns from its end value, with the smaller resistance above the wiper (as it is oriented in the figure). Write an expression for the output voltage  $v_o(t)$ .



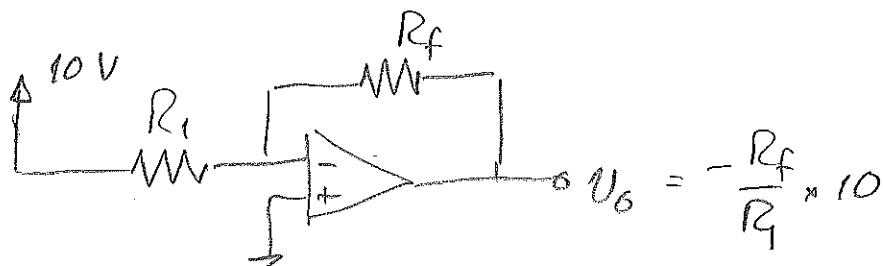- i) If we turn the pot all the way to the top, we will have (ignoring  $v_s$  input):



In this case, we need  $v_o = -4 \text{ V}$ ,  $\Rightarrow \frac{R_f}{R_1} = 0.4$

Room for extra work


#6

$$\text{choosing } R_f = 10 \text{ k}\Omega \Rightarrow R_1 = 25 \text{ k}\Omega$$

+4 To get an ac component of  $-2.5 \text{ V}$  (amplitude), we will need

$$R_2 = 4.1 \text{ k}\Omega$$

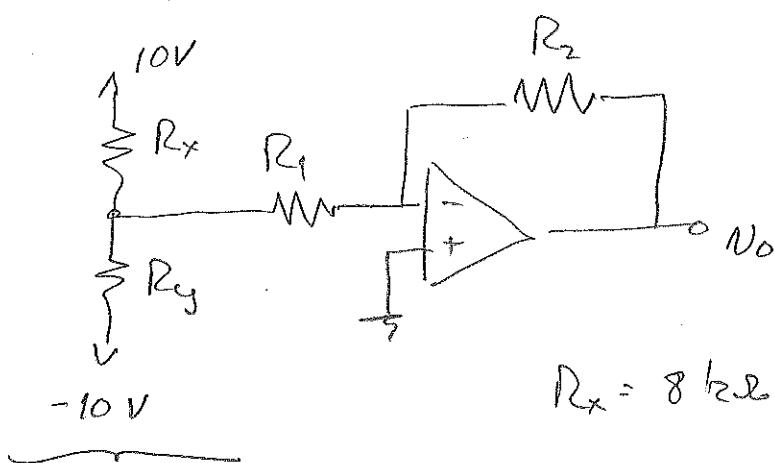ii At 4 turns, which is  $0.4 \times 20 \text{ k}\Omega = 8 \text{ k}\Omega$ , we have:



We again ignore  $V_s$  and focus on the dc component.


$$R_x = 8 \text{ k}\Omega \quad R_y = 12 \text{ k}\Omega$$

Taking a Thevenin equivalent, we have (dc component)

+10

$$R_{th} = 8 \text{ k}\Omega \parallel 12 \text{ k}\Omega = 4.8 \text{ k}\Omega \quad V_{Th} = 20 \cdot \frac{12}{20} - 10 = 2 \text{ V.}$$


+5

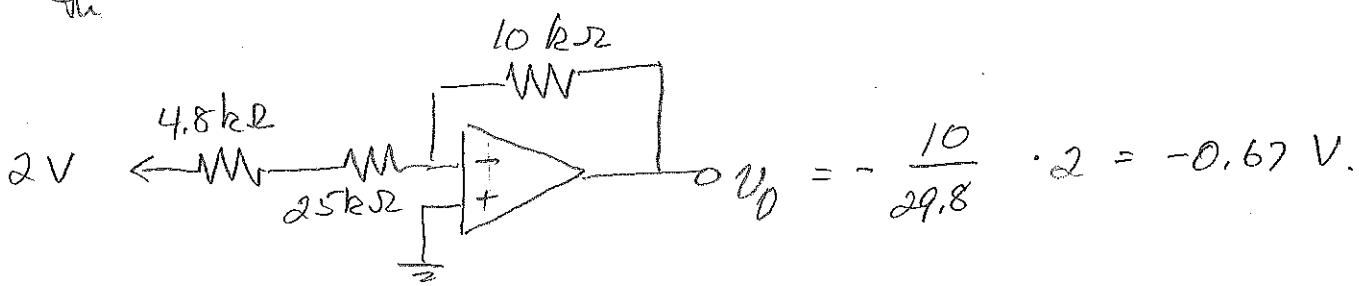

$$\therefore V_o = -0.67 - 2.5 \sin(\omega t)$$

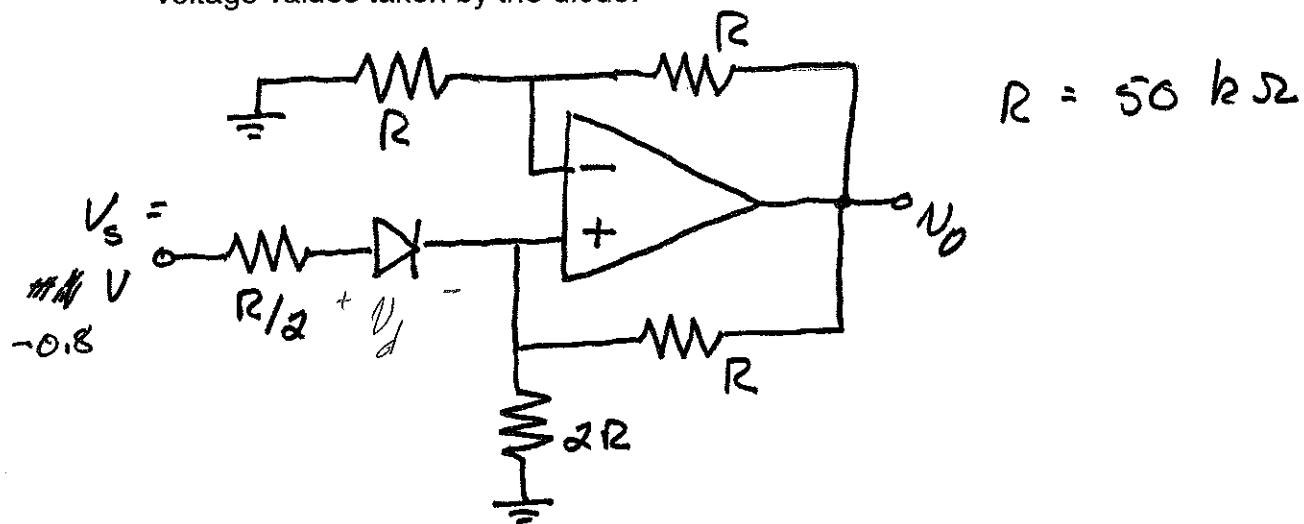4. (30 points) For the circuit below, do the following.

- Find the Thevenin equivalent circuit with respect to the terminals of the diode.
- The diode  $i_d - v_d$  characteristics are shown in the graph on the next page. On this graph, plot the load line for the circuit.
- Based on your plot, estimate all possible operating points, i.e., the current and voltage values taken by the diode.




This looks like the negative impedance converter but it's not identical. Let's do the analysis:

$$i_T' = \frac{V_+}{2R} + \frac{V_+ - V_o}{R}$$

$$V_o = V_+ \left(1 + \frac{R}{R}\right) = 2V_+$$

$$\Rightarrow i_T' = -\frac{V_+}{2R}$$

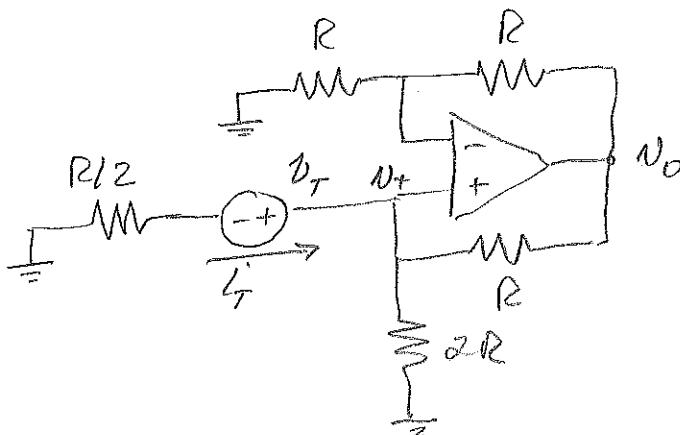


$$\text{KVL: } V_+ + \frac{R}{2} i_T' - V_T = 0$$

$$V_+ = V_T - \frac{R}{2} i_T'$$


With diode removed,  
 $V_T = -0.8 V. = V_{o0} = V_{Th}$

$$\Rightarrow i_T' = -\frac{V_T}{2R} + \frac{1}{4} i_T'$$
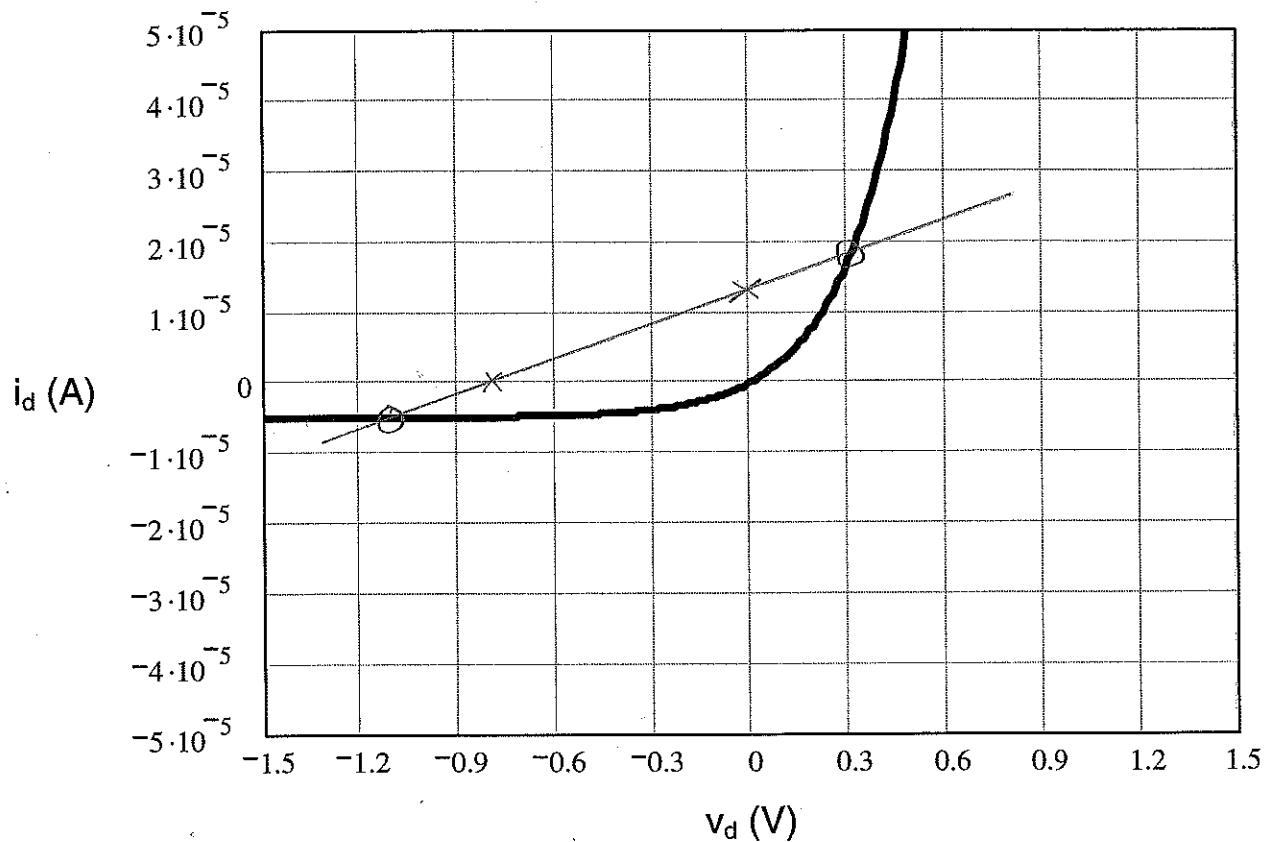
$$\underline{\underline{\frac{V_T}{i_T'} = -\frac{3}{2} R = R_{Th}}}.$$



1.9 So we have (+4)

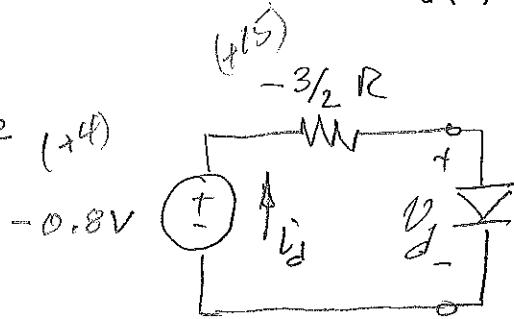

$$0.8 - i_d \cdot \frac{3}{2} R + v_d = 0$$

$$i_d = \frac{v_d + 0.8}{\frac{3}{2} R} = \frac{2}{3R} v_d + \frac{1.6}{3R}$$

1.8 So this is a straight line w/ slope =  $\frac{2}{3R}$  (+4)

For  $i_d = 0$ ,  $v_d = -0.8V$ ; For  $v_d = 0$ ,  $i_d = \frac{2}{3R} = 13.3 \mu A$ . These points are plotted above. The load line implies two possible operating points:

1.9  $i_d \approx -5 \mu A$ ,  $v_d \approx -1.1 V$ ;  $i_d \approx 11.9 \mu A$ ,  $v_d \approx 0.3 V$ .