

Name: Solutions! (please print)

Signature: _____

ECE 3355
Mid-Term Exam
July 5, 2017

- You may have one 8 ½ x 11 in. “crib” sheet, written on both sides, during the quiz. You may have any calculator you choose, but no computers.
- Show all work necessary to complete the problem on these pages. A solution without the work shown will receive no credit.
- Show units in intermediate and final results, and in figures.
- If your work is sloppy or difficult to follow, points will be subtracted.
- You have 90 minutes to work on the exam.

This exam has 10 pages, including the cover sheet. Raise your hand if you are missing a page.

1 _____ /25

2 _____ /25


3 _____ /30

4 _____ /20

Total _____ /100

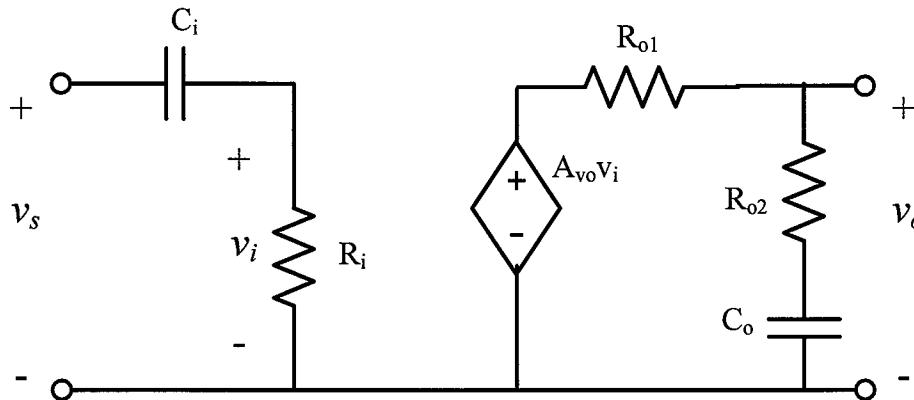1. (25 points) The amplifier circuit model below has a magnitude Bode plot whose straight-line approximation is shown on the next page. The Bode plot is for the transfer function $T(\omega) = V_o/V_s$.

- Find values for the circuit components that will produce the Bode plot shown.
- Find the transfer function for the circuit, and evaluate it at one frequency (your choice) to show that it agrees with the Bode plot.



$$V_o = A_{vo} V_i \frac{R_{o2} + \frac{1}{j\omega C_o}}{R_{o1} + R_{o2} + \frac{1}{j\omega C_o}}$$

$$V_i = V_s \frac{j\omega C_i R_i}{1 + j\omega C_i R_i}$$

$$T(\omega) = \frac{V_o}{V_s} = A_{vo} \frac{j\omega C_i R_i}{1 + j\omega C_i R_i} \frac{1 + j\omega C_o (R_{o1} + R_{o2})}{1 + j\omega C_o (R_{o1} + R_{o2})}$$

Bode plot has 20 dB/dec slopes with ...

zeros @ $0, 5000 \text{ rad/s}$

poles @ $200, 100000 \text{ rad/s}$


We set $\frac{1}{C_o R_{o2}} = 5000 \text{ rad/s}$ $\frac{1}{C_i R_i} = 200 \text{ rad/s}$

$\frac{1}{C_o (R_{o1} + R_{o2})} = 100000 \text{ rad/s}$

Uh-oh... we have a problem here ...

NS
10.5

$|T(\omega)|$ dB

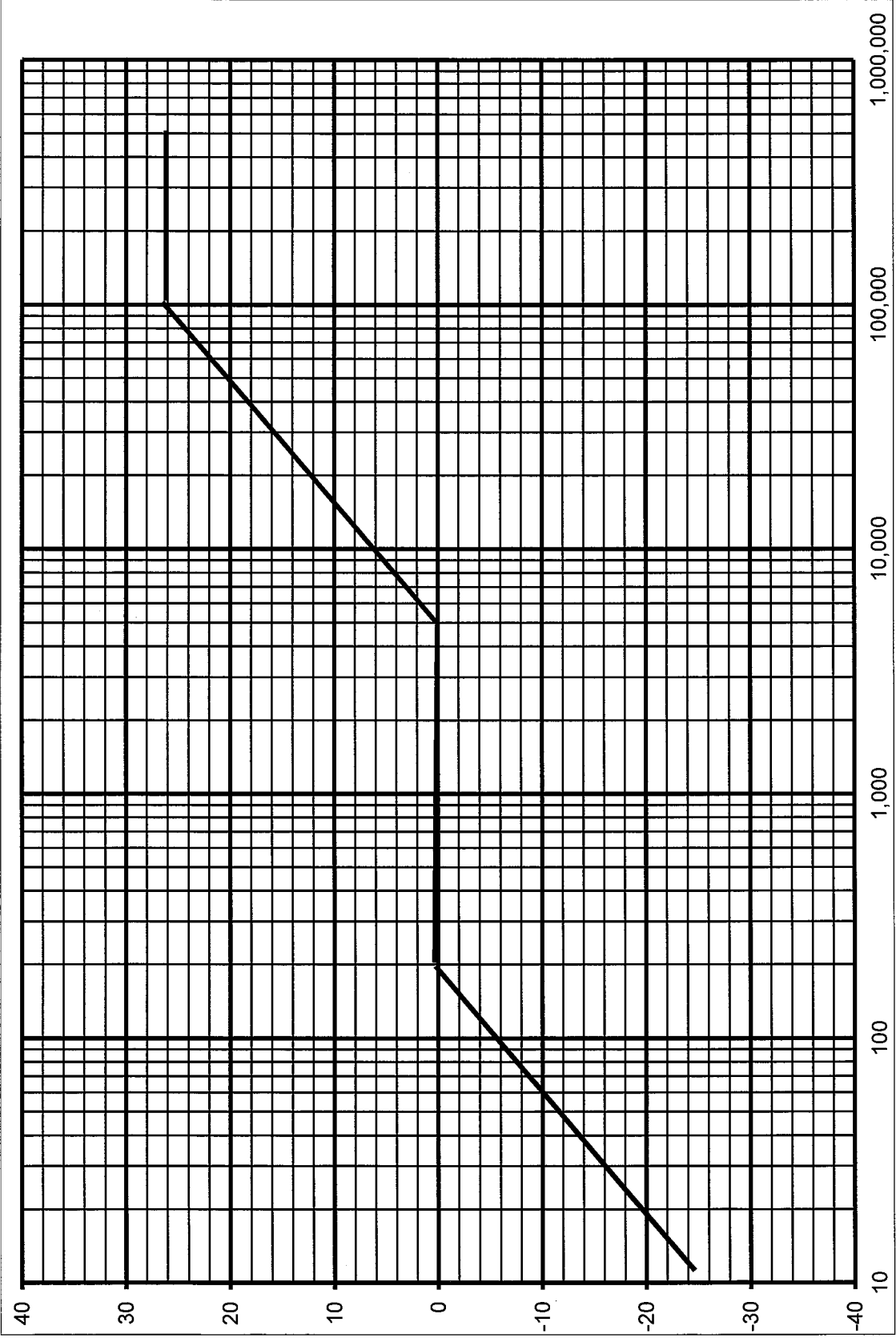

ω (rad/s)

Room for Extra Work

The zero at 5000 rad/s along with the pole at 100000 rad/s means that $R_{o1} + R_{o2} < R_{o2} \Rightarrow R_{o1}$ is negative. While this is technically possible, it's not in the spirit of this type of problem. The resolution is to change the Bode plot to show a pole at 5000 rad/s and a zero at 100000 rad/s . We will not do that here, but instead go ahead with it as is.

Choose $C_o = 0.1 \mu\text{F} \Rightarrow R_{o2} = \frac{1}{10^{-7}(5000)} = 2 \text{ k}\Omega$

a) Then $\frac{1}{C_o(R_{o1} + R_{o2})} = 100000 \text{ rad/s} \Rightarrow R_{o1} + R_{o2} = 100 \Omega$
 $\Rightarrow R_{o1} = -1900 \Omega$

Choose $C_i = 0.1 \mu\text{F} \Rightarrow R_{i1} = 50 \text{ k}\Omega$

PS!

b) We note that as $\omega \rightarrow \infty$, $T(\omega) \rightarrow A_{vo} \frac{R_{o2}}{R_{o1} + R_{o2}}$

$T(\omega) \rightarrow A_{vo} \frac{2000}{100} = 26 \text{ dB} = 19.95 \text{ V/V}$

$\therefore A_{vo} = 19.95 \frac{100}{2000} \approx 1.0$

$T(\omega = 1000 \text{ rad/s}) \approx 0 \text{ dB} \quad \checkmark$

Room for Extra Work

There is another possibility here, which is to reassign the poles:

$$\frac{1}{C_0(R_{01} + R_{02})} = 200 \frac{\text{rad}}{\text{s}} \Rightarrow R_{01} + R_{02} = 50 \text{ k}\Omega$$

$$\underline{R_{02} = 2 \text{ k}\Omega} \Rightarrow \underline{R_{01} = 48 \text{ k}\Omega}$$

$$\frac{1}{C_i R_i} = 500 \frac{\text{rad}}{\text{s}} \Rightarrow \underline{R_i = 20 \text{ k}\Omega}$$

We can keep $C_i = C_0 = 0.1 \text{ }\mu\text{F}$.

$$\text{Now } T_{(w \rightarrow \infty)} = A_{v0} \frac{R_{02}}{R_{01} + R_{02}} = A_{v0} \frac{2000}{50000} = 19.95 \%$$

$$\Rightarrow \underline{A_{v0} = 498.8}$$

2. (25 points) On the graph paper given on the next page, plot the phase Bode plot for the circuit given in Problem 1


For $\omega \rightarrow \infty$, $T(j\omega) \rightarrow j\omega C_1 R_2 \Rightarrow \angle T(j\omega) \rightarrow 90^\circ$.

We have indicated poles and zeroes, and $10x$ and $0.1x$ these values on the graph.

$$Z_1 = 5000 \text{ rad/s} \quad P_1 = 200 \text{ rad/s} \quad P_2 = 100000 \text{ rad/s}$$


For $\omega \rightarrow \infty$ $\angle T(j\omega) \rightarrow 0^\circ$ so this looks ok!

$\angle T(\omega)$ [deg]

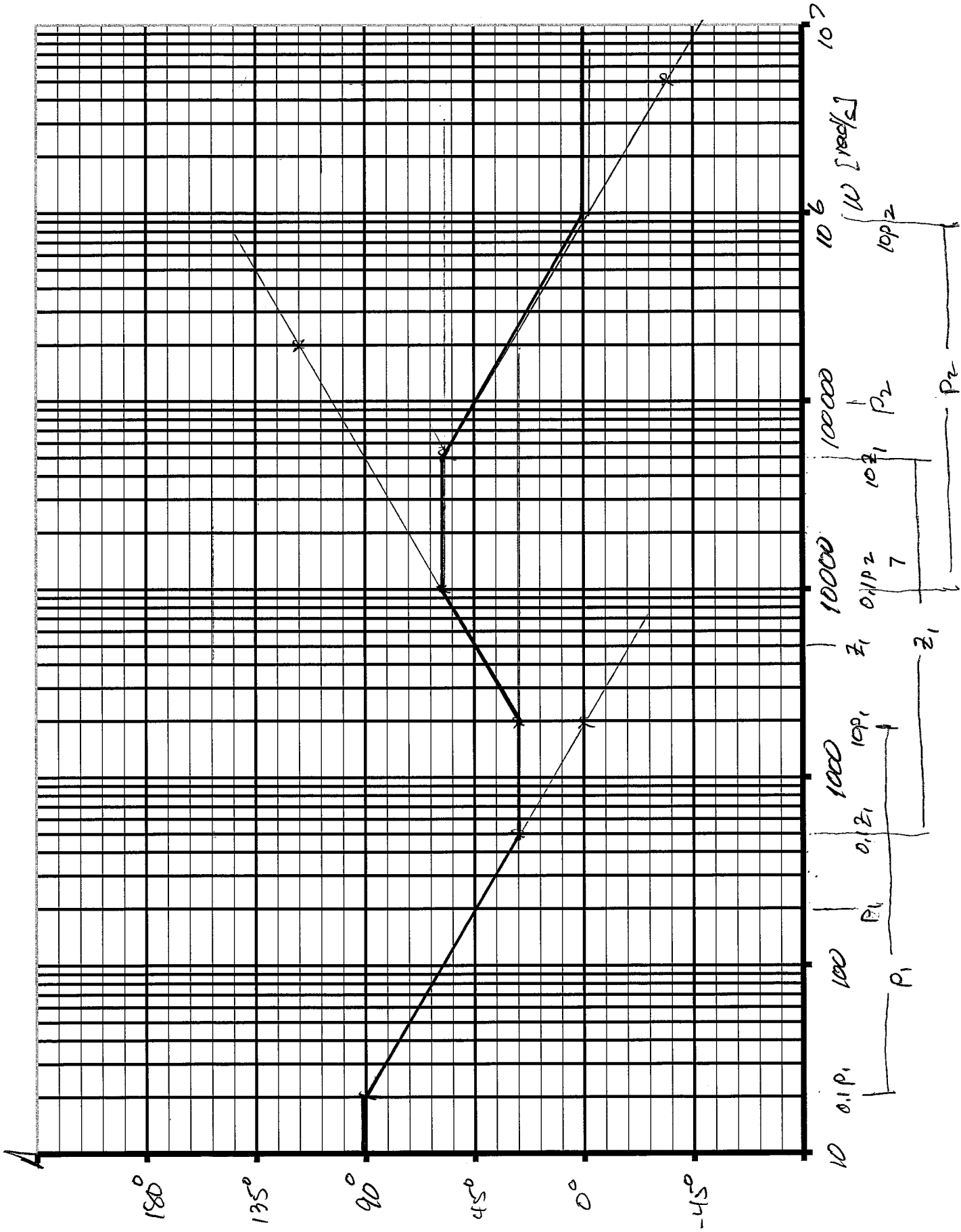

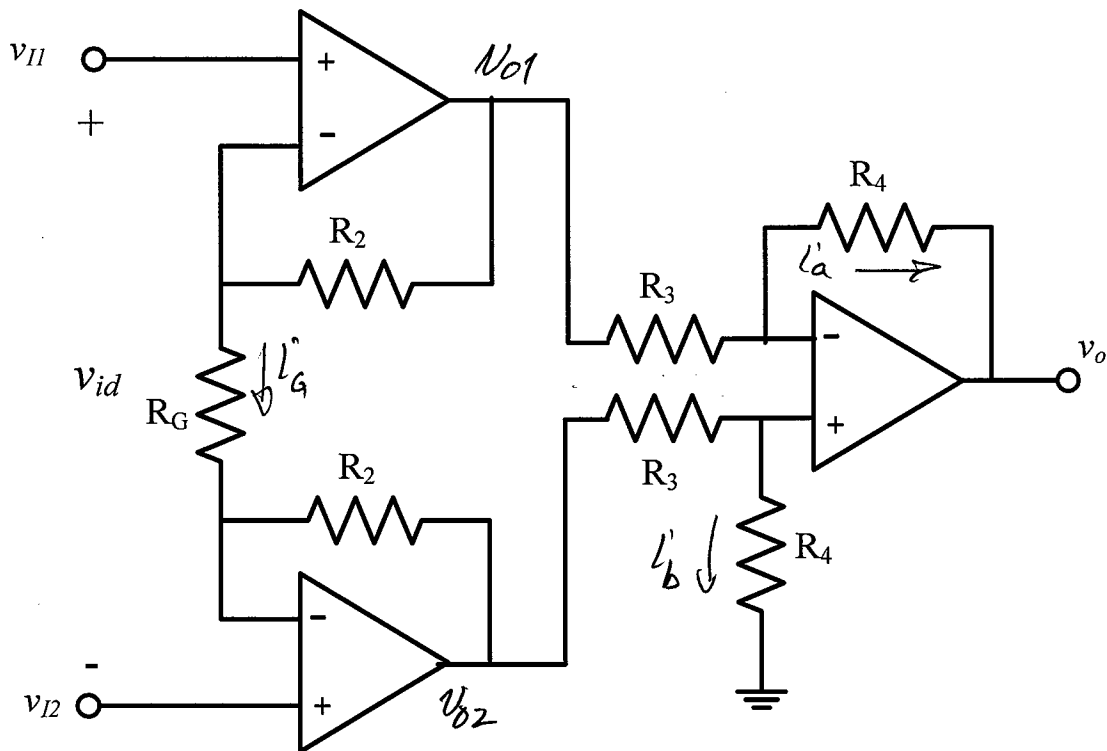3. (30 points) The circuit below is a differential amplifier.

- Find the output voltage v_o in terms of the resistances and the differential voltage $v_{id} = v_{I1} - v_{I2}$.
- By replacing one of the resistors in this circuit with a 10 k Ω potentiometer in series with a fixed resistor, we can make the gain v_o/v_{id} variable over the range 2 to 100. Make this replacement and choose resistance values to realize gain over the indicated range.



a)

All op amps have negative feedback, so...

$$v_{o1} - v_{I1} - i'_G R_2 = 0 \quad \Rightarrow \quad v_{o1} = v_{I1} + i'_G R_2$$

$$v_{o2} - v_{I2} + i'_G R_2 = 0 \quad \Rightarrow \quad v_{o2} = v_{I2} - i'_G R_2$$

$$i'_G = \frac{v_{I1} - v_{I2}}{R_G} = \frac{v_{id}}{R_G}$$

$$\begin{aligned} v_{o1} - v_{o2} &= v_{I1} - v_{I2} + 2i'_G R_2 \\ &= v_{id} + 2 \frac{v_{id}}{R_G} R_2 \end{aligned}$$

Room for Extra Work

$$i'_a = \frac{V_{o1} - V_o}{R_3 + R_4} \quad i'_b = \frac{V_{o2}}{R_3 + R_4}$$

KVL $V_o - i'_b R_4 + i'_a R_4 = 0$

$$V_o = V_{o2} \frac{R_4}{R_3 + R_4} - (V_{o1} - V_o) \frac{R_4}{R_3 + R_4}$$

$$V_o \left(1 - \frac{R_4}{R_3 + R_4}\right) = (V_{o2} - V_{o1}) \frac{R_4}{R_3 + R_4}$$

$$V_o \left(\frac{R_4}{R_3 + R_4} - 1\right) = V_{id} \left(1 + 2 \frac{R_2}{R_G}\right) \frac{R_4}{R_3 + R_4}$$
$$= \frac{R_3}{R_3 + R_4}$$

$$\Rightarrow \left[\frac{V_o}{V_{id}} = \left(1 + 2 \frac{R_2}{R_G}\right) \frac{R_4}{R_3} \right]$$

b) We want to replace R_G with 10 k Ω variable + R_{fixed} .
Set $R_4 = R_3$ and R_G to its lowest value: R_{fixed}

$$\frac{V_o}{V_{id}} = 100 = \left(1 + 2 \frac{R_2}{R_{fixed}}\right) \cdot 1$$

$$\therefore \frac{R_2}{R_{fixed}} = \frac{99}{2}$$

\checkmark
p 9'

Room for Extra Work

Now set R_s to it's highest value: $10k\Omega + R_{\text{fixed}}$.

$$\frac{V_o}{V_{id}} = 2 = \left(1 + 2 \frac{R_2}{10k + R_{\text{fixed}}}\right) \cdot 1$$

$$\therefore \frac{R_2}{10000 + R_{\text{fixed}}} = \frac{1}{2}$$


Solving gives

$$\begin{aligned} R_{\text{fixed}} &= 1.02 k\Omega \\ R_2 &= 50.5 k\Omega \end{aligned}$$

4. (20 points) Using any components you choose, design a high-pass filter with the following specifications.

- i) breakpoint at $\omega_0 = 200$ rad/s
- ii) gain at high frequency ($\omega \gg \omega_0$) of 20 dB.


There is more than one possibility...

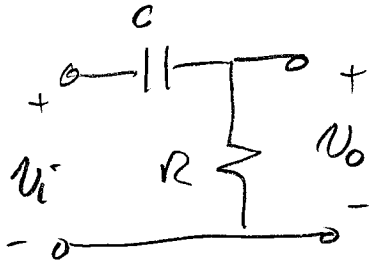

$$T(\omega) = \frac{j\omega CR}{1 + j\omega CR}$$

This has the high-pass configuration with a breakpoint at $1/CR$.

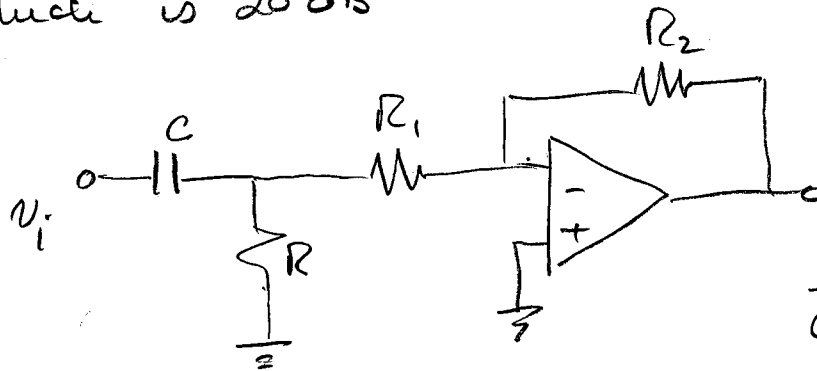
If we use this, we will need to amplify it by 10x, which is 20 dB :



$$R_2/R_1 = 10$$

$$\frac{1}{C(R_1/R_2)} = 200 \text{ rad/s}$$

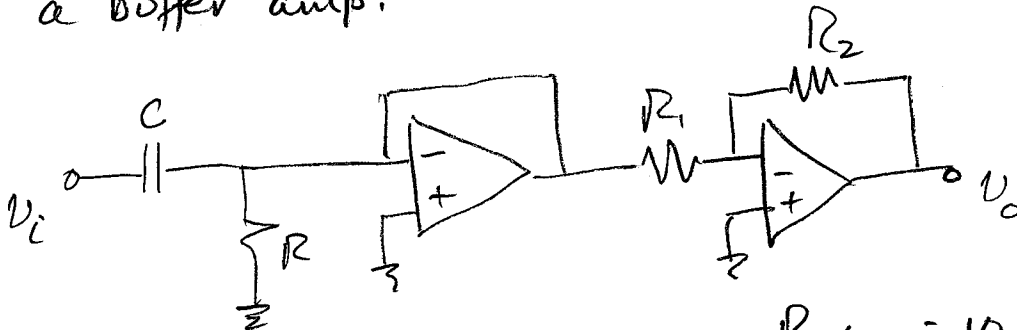If we want to isolate the filter first, we can use a buffer amp:




$$R_2/R_1 = 10$$

$$1/RC = 200 \text{ rad/s}$$

Room for Extra Work

We could also go this way:

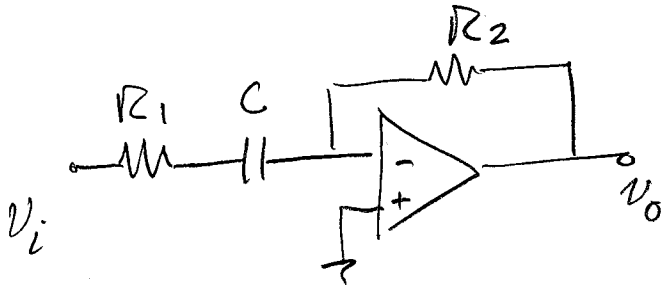

$$T(\omega) = - \frac{R_2}{R_1 + 1/j\omega C}$$
$$= - \frac{j\omega C R_2}{1 + j\omega C R_1}$$

For $\omega \rightarrow \infty$, $T(\omega) \rightarrow - \frac{R_2}{R_1}$,

so we choose $R_2/R_1 = 10$ and $1/CR_1 = 200 \text{ rad/s}$.