

P.S. This feedback amplifier circuit and the gain formula should remind you of an op amp connected in the noninverting configuration. We shall study feedback formally in Chapter 11.

✓ **7.125** For the common-emitter amplifier shown in Fig. P7.125, let $V_{CC} = 15\text{ V}$, $R_1 = 27\text{ k}\Omega$, $R_2 = 15\text{ k}\Omega$, $R_E = 2.4\text{ k}\Omega$, and $R_C = 3.9\text{ k}\Omega$. The transistor has $\beta = 100$. Calculate the dc bias current I_C . If the amplifier operates between a source for which $R_{sig} = 2\text{ k}\Omega$ and a load of $2\text{ k}\Omega$, replace the transistor with its hybrid- π model, and find the values of R_{in} , and the overall voltage gain v_o/v_{sig} .

D 7.126 Using the topology of Fig. P7.125, design an amplifier to operate between a $2\text{-k}\Omega$ source and a $2\text{-k}\Omega$ load with a gain v_o/v_{sig} of -40 V/V . The power supply available is 15 V . Use an emitter current of approximately 2 mA and a current of about one-tenth of that in the voltage divider that feeds the base, with the dc voltage at the base about one-third of the supply. The transistor available has $\beta = 100$. Use standard 5% resistors (see Appendix J).

 


Figure P7.125

D 7.127 A designer, having examined the situation described in Problem 7.125 and estimating the available gain to be approximately -36.3 V/V , wants to explore the possibility of improvement by reducing the loading

of the source by the amplifier input. As an experiment, the designer varies the resistance levels by a factor of approximately 3: R_1 to $82\text{ k}\Omega$, R_2 to $47\text{ k}\Omega$, R_E to $7.2\text{ k}\Omega$, and R_C to $12\text{ k}\Omega$ (standard values of 5% -tolerance resistors). With $V_{CC} = 15\text{ V}$, $R_{sig} = 2\text{ k}\Omega$, $R_L = 2\text{ k}\Omega$, and $\beta = 100$, what does the gain become? Comment.

D 7.128 The CE amplifier circuit of Fig. P7.128 is biased with a constant-current source I . It is required to design the circuit (i.e., find values for I , R_B , and R_C) to meet the following specifications:

- (a) $R_{in} \approx 10\text{ k}\Omega$.
- (b) The dc voltage drop across R_B is approximately 0.2 V .
- (c) The open-circuit voltage gain from base to collector is the maximum possible, consistent with the requirement that the collector voltage never fall by more than approximately 0.4 V below the base voltage with the signal between base and emitter being as high as 5 mV .

Assume that v_{sig} is a sinusoidal source, the available supply $V_{CC} = 5\text{ V}$, and the transistor has $\beta = 100$. Use standard 5% resistance values, and specify the value of I to one significant digit. What base-to-collector open-circuit voltage gain does your design provide? If $R_{sig} = R_L = 20\text{ k}\Omega$, what is the overall voltage gain?

 


Figure P7.128

7.131 In the circuit of Fig. P7.131, the BJT is biased with a constant-current source, and v_{sig} is a small sine-wave signal. Find R_{in} and the gain v_o/v_{sig} . Assume $\beta = 100$. If the amplitude of the signal v_{be} is to be limited to 5 mV, what is the largest signal at the input? What is the corresponding signal at the output?

 


Figure P7.131

*7.132 The BJT in the circuit of Fig. P7.132 has $\beta = 100$.

- (a) Find the dc collector current and the dc voltage at the collector.
- (b) Replacing the transistor by its T model, draw the small-signal equivalent circuit of the amplifier. Analyze the resulting circuit to determine the voltage gain v_o/v_i .

 


Figure P7.132

7.133 For the circuit in Fig. P7.133, find the input resistance R_{in} and the voltage gain v_o/v_{sig} . Assume that the source provides a small signal v_{sig} and that $\beta = 100$.

 


Figure P7.133

7.134 For the emitter-follower circuit shown in Fig. P7.134, the BJT used is specified to have β values in the range of 50 to 200 (a distressing situation for the circuit designer).

 


Figure P7.134

MSM = Multisim/PSpice; * = difficult problem; ** = more difficult; *** = very challenging; D = design problem