

## BJT DC ANALYSIS

To make use of the BJT we need to provide dc biasing. For example, to use it as an amplifier, we need to be sure it is operating in the linear (forward active) region.

To determine that dc biasing has been done correctly, we do a dc analysis of the circuit. This is done by:

- deactivating ac sources

ac voltage sources  $\rightarrow$  short

ac current sources  $\rightarrow$  open

- replacing reactive elements with dc equivalents

C  $\rightarrow$  open



L  $\rightarrow$  short

- guess & test: we replace the BJT with a model appropriate for the operating region we think the device is in, and test to see if our assumptions are correct.

The appropriate models for this last step are summarized in the figures from Hambley, 2 ed (Fig 4.19). We repeat them here for convenience.

(From Hambley, 2ed, Fig 4.19)
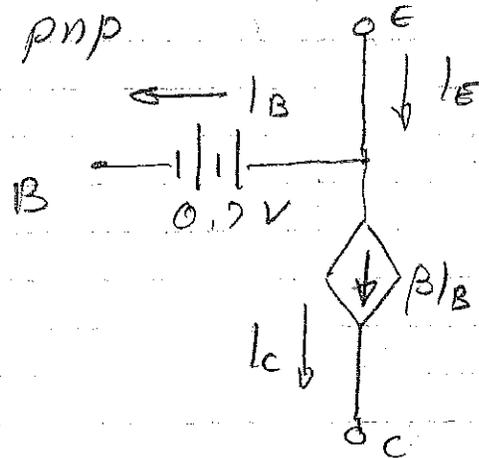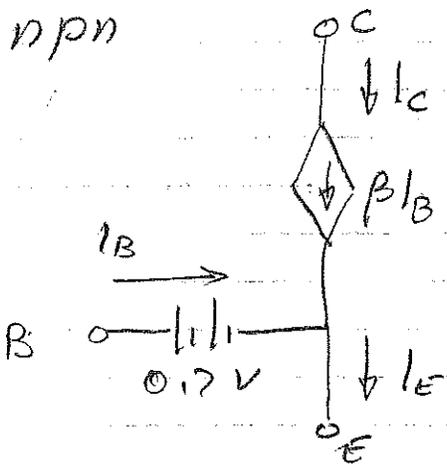
## ACTIVE REGION (FORWARD ACTIVE OR LINEAR)



$$I_B > 0$$

$$V_{CE} > 0.2 \text{ V}$$

$$I_B > 0$$



$$V_{CE} < -0.2 \text{ V}$$

TEST  
FOR

NOTE: We are assuming here a B-E diode threshold voltage of  $0.7 \text{ V}$ . This value depends on the BJT and in another case may take a different value.

The condition on  $V_{CE}$  is based on the assumed saturation voltage, which here is  $\pm 0.2 \text{ V}$ . This parameter is also dependent on the BJT. It takes whatever value is specified for  $V_{CE \text{ SAT}}$ .

## SATURATION REGION

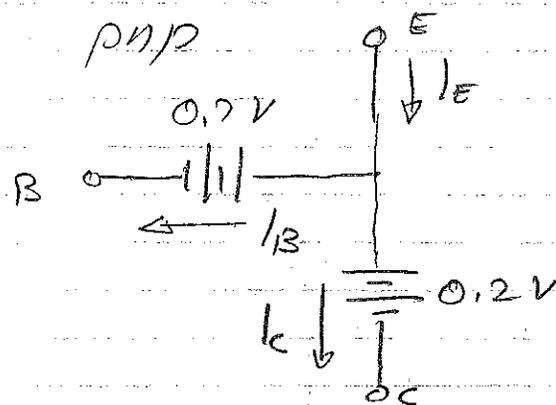
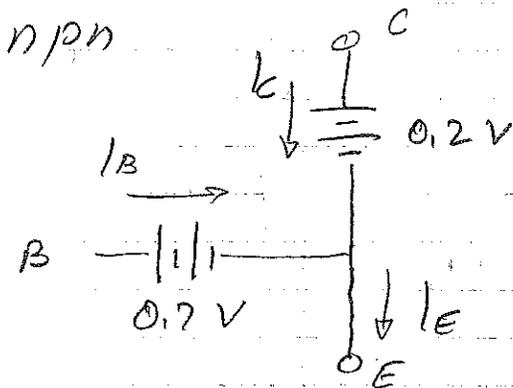


TEST }  $I_B > 0$   
 FOR }  $\beta I_B > I_C > 0$

$I_B > 0$   
 $\beta I_B > I_C > 0$

See previous comments concerning the BE threshold voltage and  $V_{CE\text{SAT}}$ . Note also the condition that for saturation, the  $I_C/I_B$  ratio is not equal to  $\beta$ .


## CUTOFF

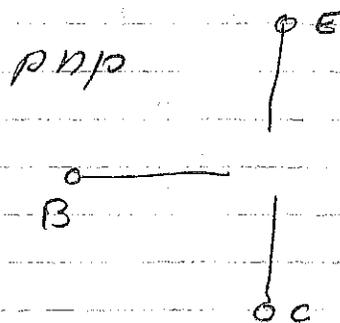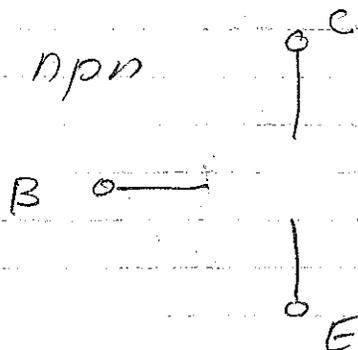

TEST }  $V_{BE} < 0.5V$   
 FOR }  $V_{BC} < 0.5V$

$V_{BE} > -0.5V$   
 $V_{BC} > -0.5V$


# EXAMPLE

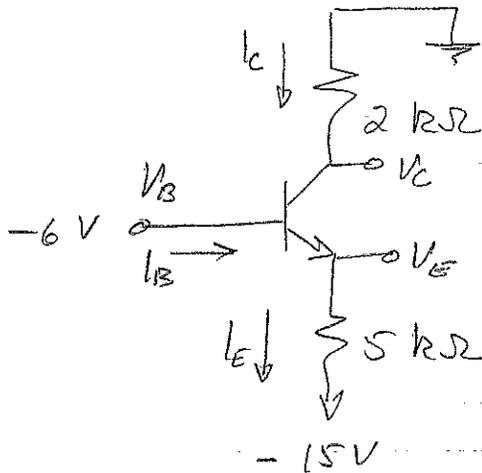

$$\beta = 100$$

$$V_{CE(SAT)} = 0.2V$$

ASSUME ACTIVE MODE

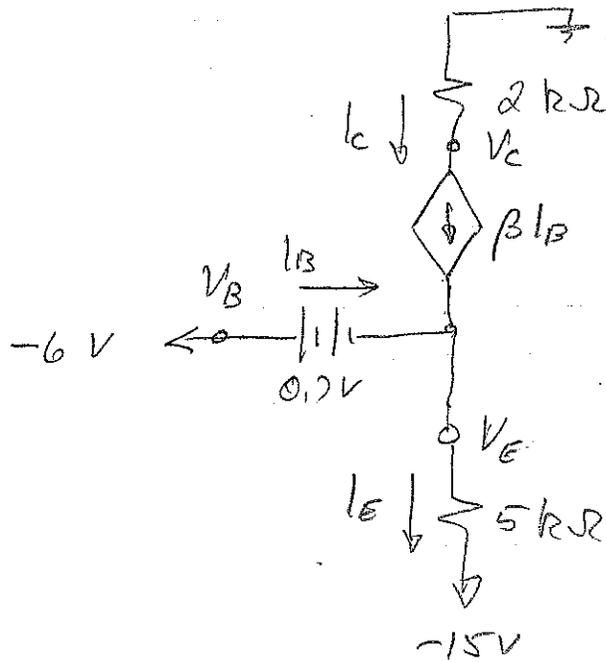

$$I_E = \frac{-6.7 - (-15)}{5k} = 1.66 \text{ mA}$$

$$I_E = I_B + \beta I_B \Rightarrow I_B = \frac{I_E}{\beta + 1} = 16.4 \mu\text{A}$$

$$I_C = \beta I_B = 1.64 \text{ mA}$$

$$V_C = -2000 I_C = -3.29 \text{ V}$$

$$V_E = -6.7 \text{ V} \quad V_B = -6 \text{ V} \quad (\text{given})$$

$$\text{TEST: } I_B > 0 \quad \checkmark$$

$$V_{CE} = V_C - V_E = -3.29 - (-6.7) = 3.41 \text{ V}$$

Note that  $V_{CB}$  is consistent with electron flow from base to collector, as must be the case for active operation.


$$I_c = \beta I_B = 1.64 \text{ mA}$$

$$V_c = 2000 I_c = 3.29 \text{ V}$$

$$V_E = 6.7 \text{ V}$$

$$V_{CE} = -3.41 \text{ V} < -0.2 \text{ V} \quad \checkmark$$


EXAMPLE

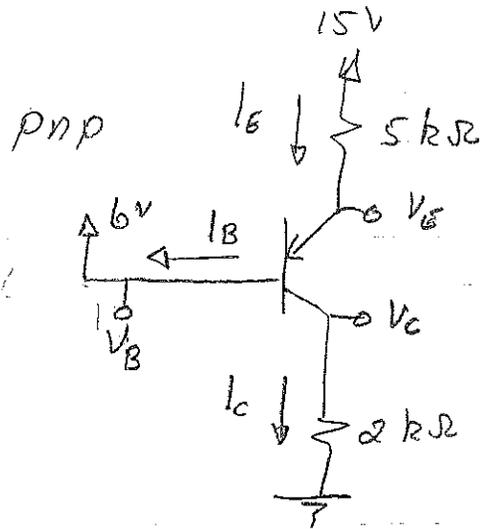

$$\beta = 100$$

$$V_{CESAT} = -0.3V$$

Assume ACTIVE mode

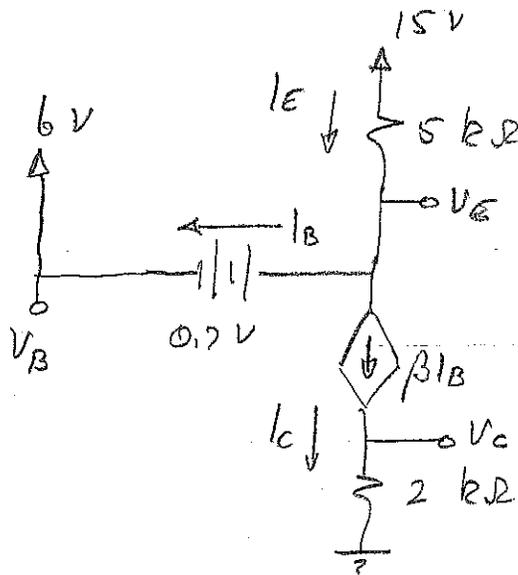


$$-15 + 5000 I_E + 0.7 + 6 = 0$$

$$I_E = \frac{15 - 6.7}{5k} = 1.66 \text{ mA}$$

$$I_B = \frac{I_E}{\beta + 1} = 16.4 \text{ } \mu\text{A} \quad \checkmark$$

28


# EXAMPLE

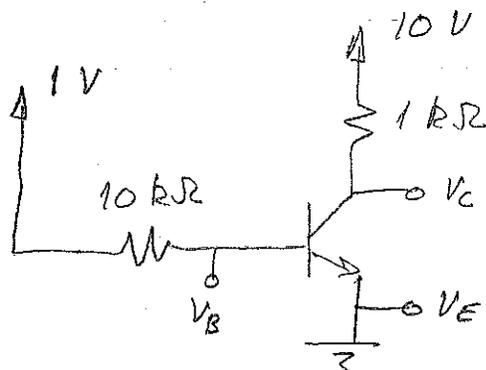

$$\beta = 50$$

$$V_{CE\text{ SAT}} = 0.2\text{ V}$$

Assume ACTIVE mode.

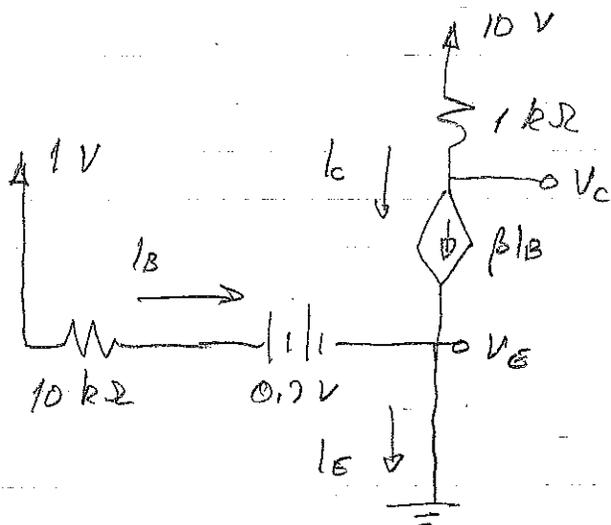

$$-1 + 10000 I_B + 0.7 = 0$$

$$I_B = \frac{1 - 0.7}{10k} = 30\ \mu\text{A}$$

$$I_C = \beta I_B = 1.5\ \text{mA}$$


$$I_E = (\beta + 1) I_B = 1.53\ \text{mA}$$

$$V_C = 10 - 1000 I_C = 8,5 V > 0,2 V \quad \checkmark$$

$$V_B = 1 - 10k I_B = 0,7 V$$

$$V_E = 0$$

Assume SATURATION

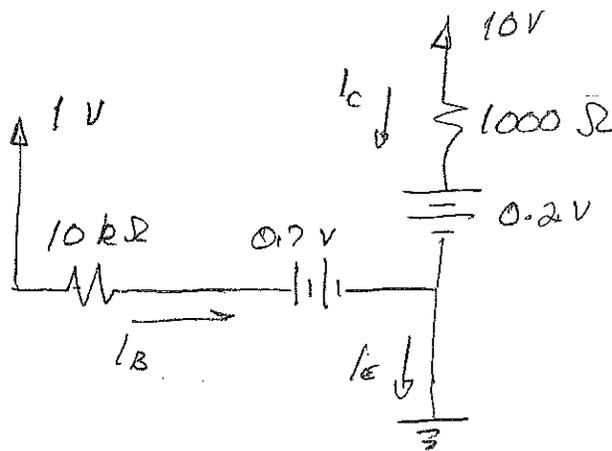

$$-1 + 10000 I_B + 0,7 = 0$$

$$I_B = 30 \mu A > 0 \quad \checkmark$$


$$I_C = \frac{10 - 0,2}{1000} = 9,8 \text{ mA}$$

$$I_E = I_C + I_B \approx 9,8 \text{ mA}$$

We need:  $\beta I_B > I_C = 50 I_B = 1,5 \text{ mA} > 9,8 \text{ mA} \quad \text{?} \quad \times$

So test for current magnitudes fails and saturation is wrong.


# EXAMPLE

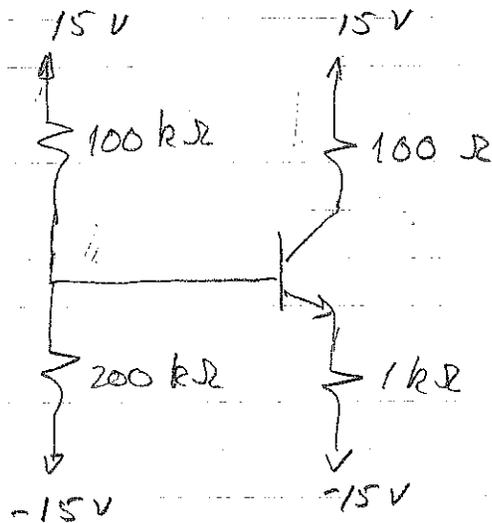

$$\beta = 100$$

$$V_{CE\ SAT} = 0.3\text{ V}$$

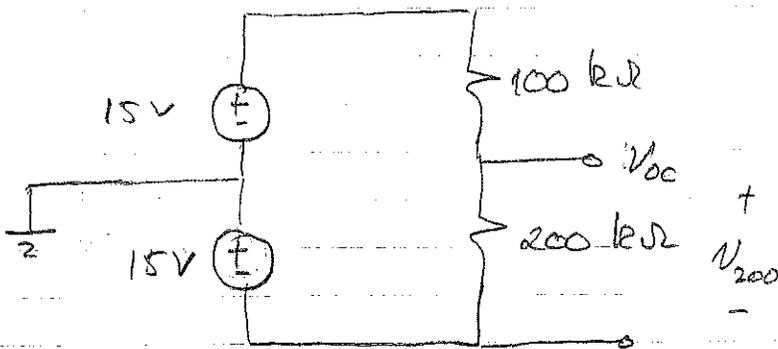Replace base circuit with Thevenin; re-draw circuit first to see how this works.




$$V_{200} = (30\text{ V}) \cdot \frac{200\text{ k}}{200\text{ k} + 100\text{ k}}$$

$$= 20\text{ V}$$

$$V_{oc} = V_{200} - 15 = 5\text{ V}$$

$$R_{eq} = 200\text{ k} \parallel 100\text{ k} = 66.7\text{ k}\Omega$$

Now assume ACTIVE mode...

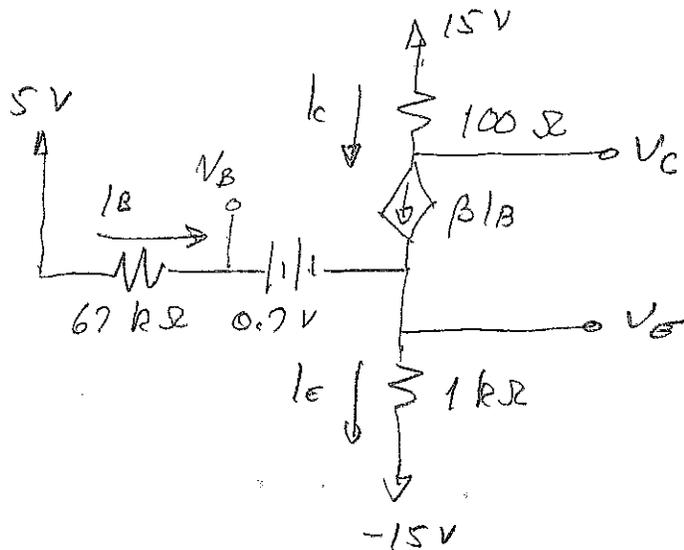

$$-5 + 67000 I_B + 0.7 + 1000 I_E - 15 = 0$$

$$I_E = (\beta + 1) I_B$$

→

$$67000 I_B + 1000 (101) I_B = 19.3$$

$$I_B = 0.115 \text{ mA} \quad \checkmark$$

$$I_E = 11.6 \text{ mA}$$

$$I_C = \beta I_B = 11.5 \text{ mA}$$


$$V_C = 15 - 100 I_C = 13.85 \text{ V}$$

$$V_E = 1000 I_E - 15 = -3.40 \text{ V}$$

$$V_{CE} = 17.25 \text{ V} \quad \checkmark$$

$> 0.3 \text{ V}$

Previous example assuming saturation:

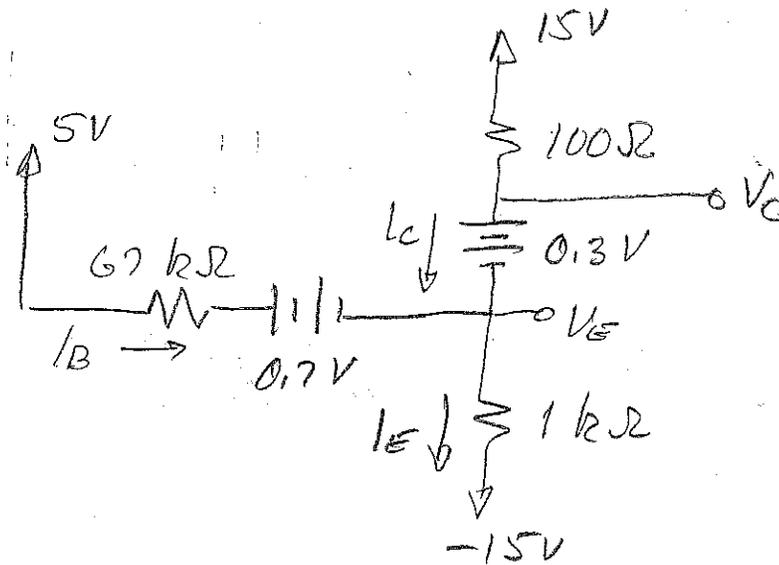

(2) A KVL around the base-emitter loop gives:

$$-5 + 67000 I_B + 0.7 \text{ V} + 1000 I_E - 15 = 0$$

Because we are in saturation,  $I_E \neq (\beta + 1) I_B$ .  
So to solve this we need additional equations:

$$I_E = \frac{V_E - (-15)}{1000}$$

$$V_E = V_C - 0.3$$

$$V_C = 15 - 1000 I_C$$

$$I_C = I_E - I_B$$

This is a bit messy. A better alternative is to use a KCL at  $V_E$  (node-voltage method):


$$0 = \frac{V_E + 15}{1000} + \frac{V_E - 5 - (-0.7)}{67000} + \frac{V_E - 15 - (-0.3)}{100}$$

The other terminal currents and voltages follow easily. Either way, the results here are:

$$V_E = 11.99 \text{ V}$$

$$I_B = -0.115 \text{ mA} \quad ! \quad \text{oops - wrong assumption}$$

# Example

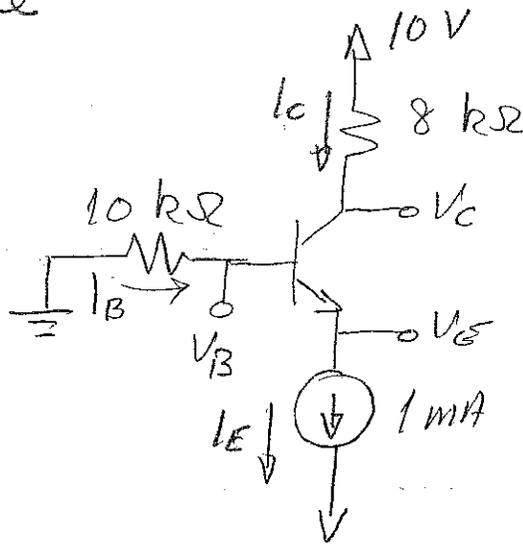

$$\beta = 100$$


$$V_{CESAT} = 0.3V$$

FIND  $V_B, V_C, V_E$

$I_C, I_B, I_E$

Biasing here is accomplished using both a voltage source and a current source.

Guess LINEAR region

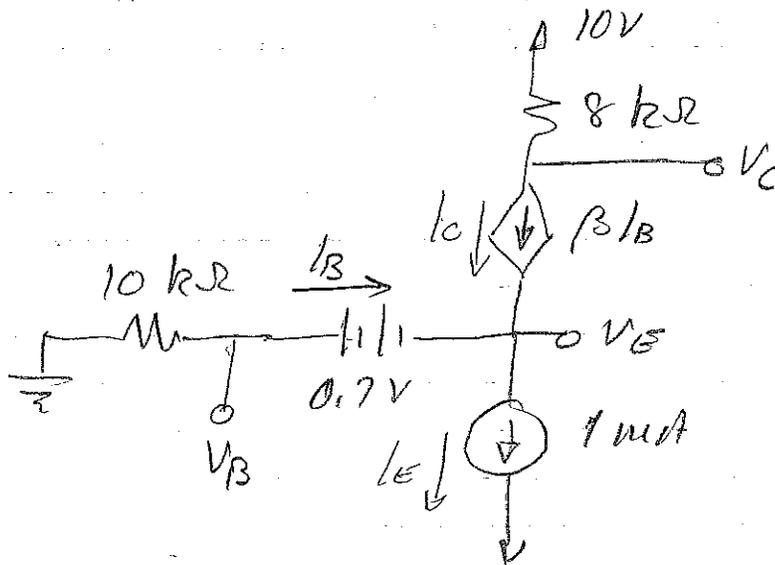

$$I_C = \beta I_B = \frac{\beta}{1+\beta} I_E$$

$$I_E = 1 \text{ mA} \Rightarrow I_C = 0.99 \text{ mA}$$

$$\therefore I_B = I_E - I_C = 0.01 \text{ mA} \quad \checkmark$$

$$V_B = -10000 I_B = -0.1 \text{ V}$$


$$V_E = V_B - 0.7 = -0.8 \text{ V}$$

$$V_C = 10 - 8000 I_C = 2.1 \text{ V}$$

$$V_{CE} = V_C - V_E = 2.1 - (-0.8) = 2.9 \text{ V} \quad \checkmark$$

So, this is the LINEAR region.

# EXAMPLE

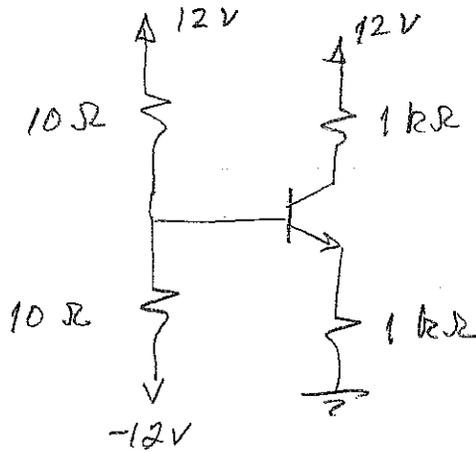


$$\beta = 100$$

$$V_{CE\text{ SAT}} = 0.3\text{ V}$$

Looking at base bias circuit, we note that Thevenin equivalent voltage is 0, and the emitter is grounded. Hmmm...

Assume CUT-OFF

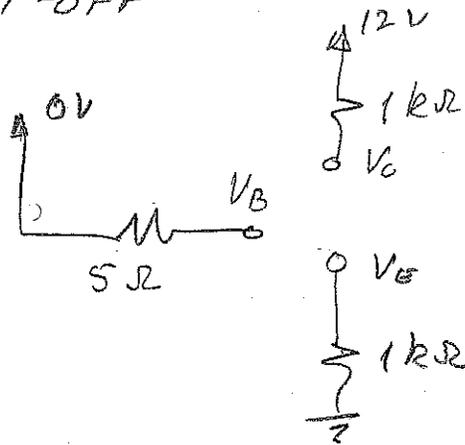


$$V_B = 0$$

$$V_C = 12\text{ V}$$

$$V_E = 0$$

- so BE junction is OFF and CB junction is reverse biased  $\Rightarrow$  CUTOFF is correct.

# Example

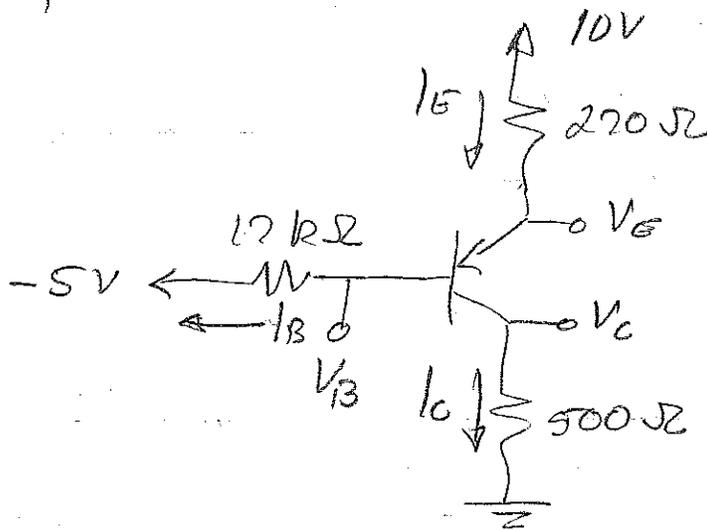


$$\beta = 80$$

$$V_{CESAT} = 0.2V$$

FIND  $V_B, V_E, V_C$

$I_B, I_E, I_C$

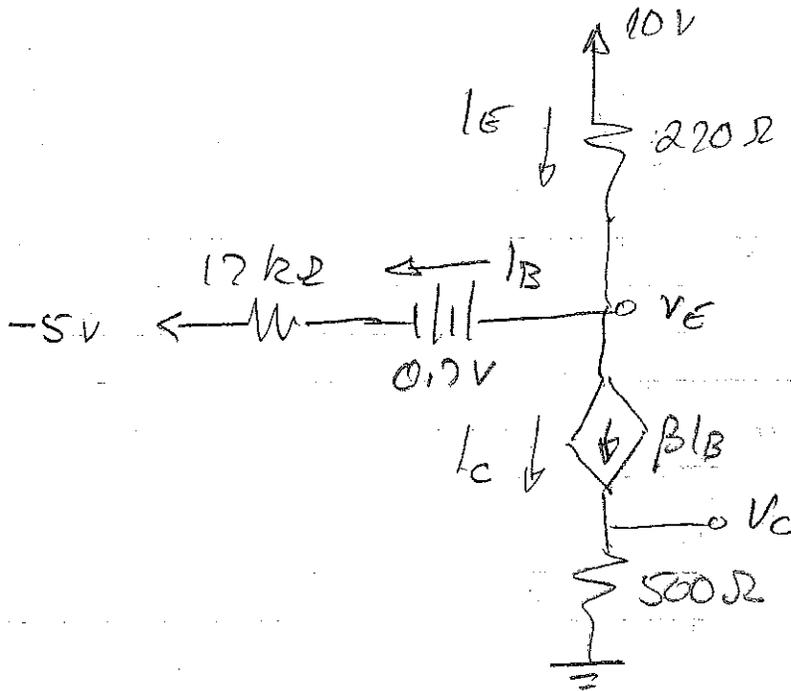Clearly the EB junction is ON. Let's guess LINEAR.



KVL:  $-10 + 220 I_E + 0.2 + 17000 I_B - 5 = 0$

$$I_E = (\beta + 1) I_B$$


$$-10 + 270(81)I_B + 0.2 + 17000I_B - 5 = 0$$

$$I_B = \frac{10 + 5 - 0.2}{17000 + 270(81)} = 0.368 \text{ mA} \quad \checkmark$$

$$\begin{aligned} V_{CE} &= V_C - V_E = 500I_C - (10 - 270I_B) \\ &= 500(\beta I_B) - (10 - 270(\beta + 1)I_B) \\ &= 16.2 - 10 + 8.83 \\ &= 12.8 \text{ V} \quad \times \end{aligned}$$

$V_{CE} < -0.2 \text{ V}$  for LINEAR region, which is not satisfied here.

Try SATURATION

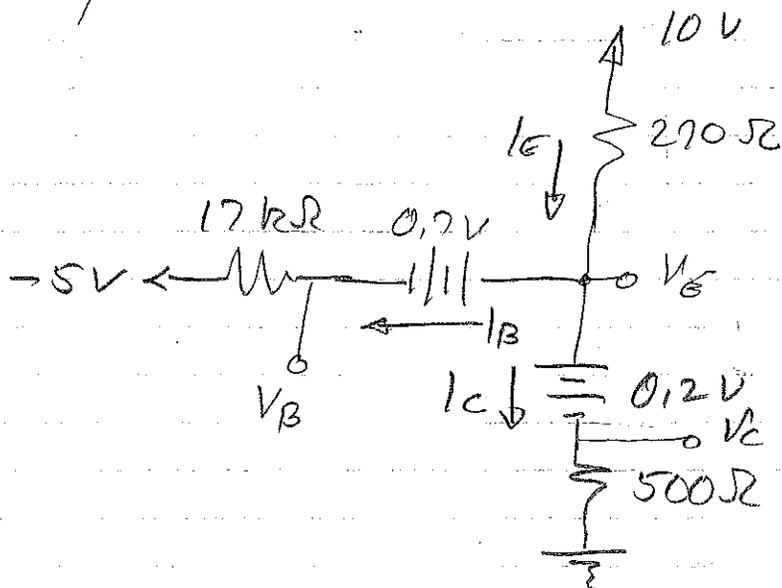

Node voltage equation for  $V_E$ :

$$\frac{V_E - 0.2}{500} + \frac{V_E - 10}{270} + \frac{V_E + 5 - 0.7}{17000} = 0$$

This is messy but solvable:  $\underline{V_E} = 6.45 \text{ V}$

So  $\underline{V_C} = V_E - 0.2 = 6.25 \text{ V}$ ;  $\underline{V_B} = V_E - 0.7 = 5.75 \text{ V}$

[ We could guess that the last term is negligible because the base resistance (17k $\Omega$ ) is large. If we do that, we have

$$\frac{V_E - 0.2}{500} + \frac{V_E - 10}{270} = 0$$

$$\Rightarrow V_E = 6.56 \text{ V}$$

This is pretty close to our previous result and will not change the operating region. ]

Now

$$\underline{I_B} = \frac{V_E + 5 - 0.7}{17000} = 0.632 \text{ mA} \checkmark$$

$$\underline{I_C} = \frac{V_E - 0.2}{500} = 12.5 \text{ mA}$$

$$\beta I_B = 50.6 \text{ mA} > I_C \checkmark$$

$$\underline{I_E} = I_B + I_C = 13.13 \text{ mA}$$