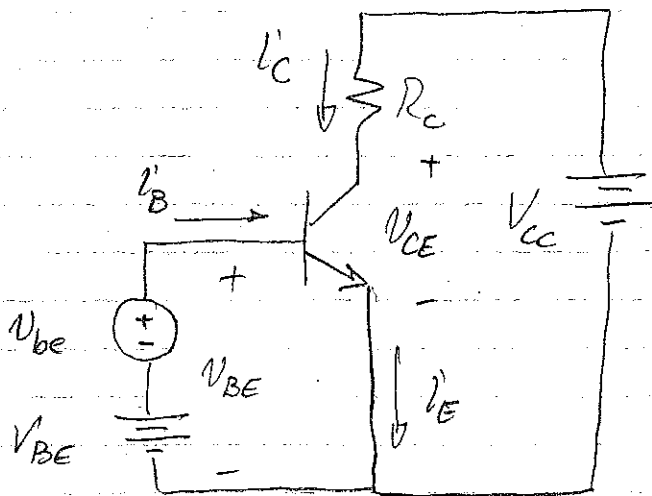


THE BJT AS AN AMPLIFIER

IDEA: If we bias the BJT into the linear (forward-active) region, we can superimpose an ac signal at the input and obtain an amplified version at the output.

NOTE: For most amplifier applications, we want the output to be simply a multiple of the input, that is, we want linear response. If the BJT is not properly biased or the signal is too large, we will get non-linear behavior; that is, the output will be a distorted copy of the input.

CONCEPTUAL ANALYSIS:



DC CONDITIONS:

$$I_C = I_S e^{V_{BE}/V_T} \quad (V_{BE} \gg V_T)$$

$$I_E = I_C / \alpha$$

$$I_B = I_C / \beta$$

$$V_C = V_{CC} - I_C R_C$$

Now consider current components when a signal is present:

$$V_{BE} = V_{be} + V_{BE}$$

COLLECTOR CURRENT

$$i_c = I_s e^{V_{BE}/V_T} e^{V_{be}/V_T}$$
$$= I_c e^{V_{be}/V_T}$$

For $V_{be} \ll V_T$ (say ≈ 10 mV),

$$i_c \approx I_c (1 + V_{be}/V_T)$$
$$= I_c + \frac{I_c}{V_T} V_{be}$$

So the ac component is

$$i_c = \frac{I_c}{V_T} V_{be} \equiv g_m V_{be}$$

The TRANSCONDUCTANCE is $g_m \equiv \frac{I_c}{V_T}$

INPUT RESISTANCE AT THE BASE

We also have

$$I_B = \frac{I_C}{\beta} = \frac{I_E}{\beta} + \frac{I_C}{\beta V_T} V_{BE}$$

and the ac component is

$$i_b = \frac{g_m}{\beta} v_{be}$$

We define

$$\Gamma_{\pi} \equiv \frac{v_{be}}{i_b} = \beta / g_m$$

which is the small-signal input resistance, looking into the base.

We can also write $\Gamma_{\pi} = \frac{V_T}{I_B}$ since

$$\frac{\beta}{g_m} = \frac{I_C / I_B}{I_C / V_T} = \frac{V_T}{I_B}$$

INPUT RESISTANCE AT THE EMITTER

$$r'_E = \frac{i_c}{\alpha} = \frac{i_c}{\alpha} + \frac{i_c}{\alpha}$$

The ac component is

$$\begin{aligned} i_c &= \frac{i_c}{\alpha} = \frac{i_c}{\alpha V_T} U_{be} \\ &= \frac{I_E}{V_T} U_{be} \end{aligned}$$

We define the small signal resistance between base and emitter, looking into the emitter, as

$$r_e \equiv \frac{V_T}{I_E} = \frac{\alpha}{g_m} \approx \frac{1}{g_m}$$

We can also show that

$$r_{\pi} = (\beta + 1)r_e$$

VOLTAGE GAIN

If we take as output the voltage v_{ce} , then

$$v_{ce} = v_{cc} - i_c R_c$$

ac component is

$$v_{ce} = -i_c R_c = -g_m U_{be} R_c$$


So

$$A_v \equiv \frac{v_{ce}}{U_{be}} = -g_m R_c$$

SMALL SIGNAL EQUIVALENT CIRCUIT MODELS

We can use these calculations to construct equivalent circuits that describe the BJT's response to ac circuits.

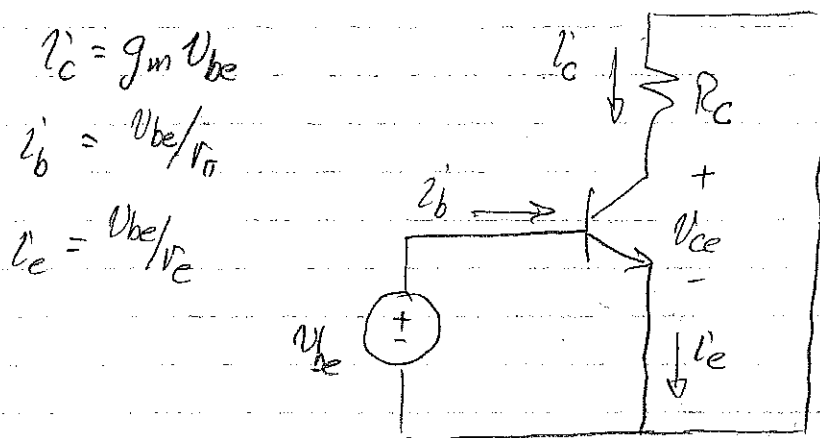AC-CIRCUIT: The "ac-portion" of the circuit shown above is



NOTE: DC sources were removed (de-activated).
In other words,


$$V_{DC} \rightarrow 0 \quad (\text{short circuit})$$

$$I_{DC} \rightarrow \infty \quad (\text{open circuit})$$

We can draw an equivalent circuit to replace the BJT as follows.

(The equivalent circuit applies to the BJT only.
It does not include external components like v_{be} , R_c , etc.)


HYBRID - PI MODEL

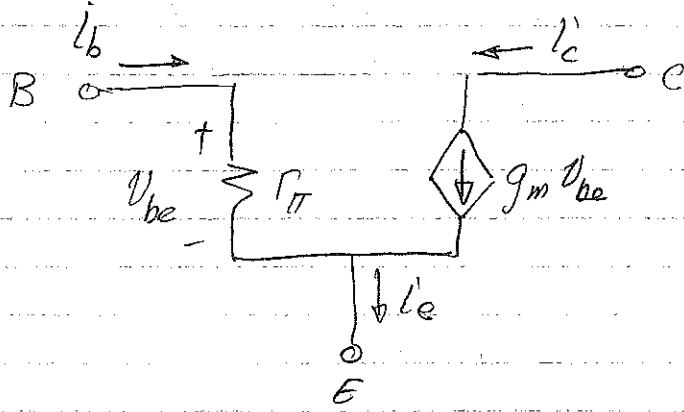

$$g_m = I_c / V_T$$

$$r_{\pi} = \beta / g_m$$

Alternatively...

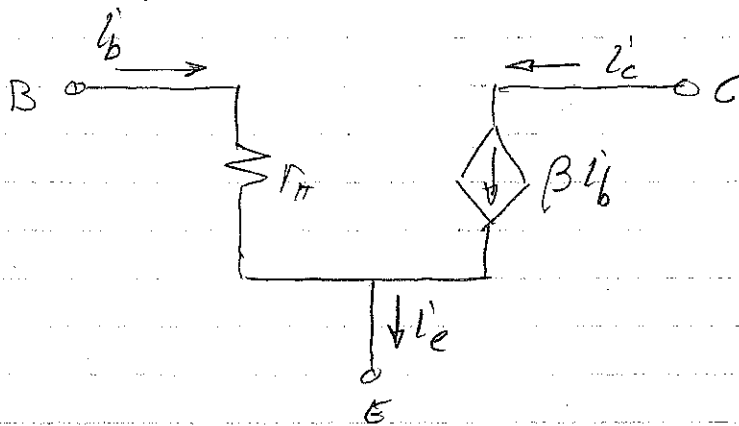

NOTES:

- Although r_e is not included, the model correctly predicts i_e :

$$i_e = \frac{v_{be}}{r_{\pi}} + g_m v_{be} = \frac{v_{be}}{r_{\pi}} (1 + g_m r_{\pi})$$

$$= \frac{v_{be}}{r_{\pi}} (1 + \beta) = v_{be} / \left(\frac{r_{\pi}}{1 + \beta} \right)$$


$$= v_{be} / r_e$$

- The parameters g_m , r_{π} depend on the biasing conditions through I_C . So if biasing conditions change, they have to be re-calculated.

- The models apply to npn and pnp BJTs without any modifications.

T MODEL

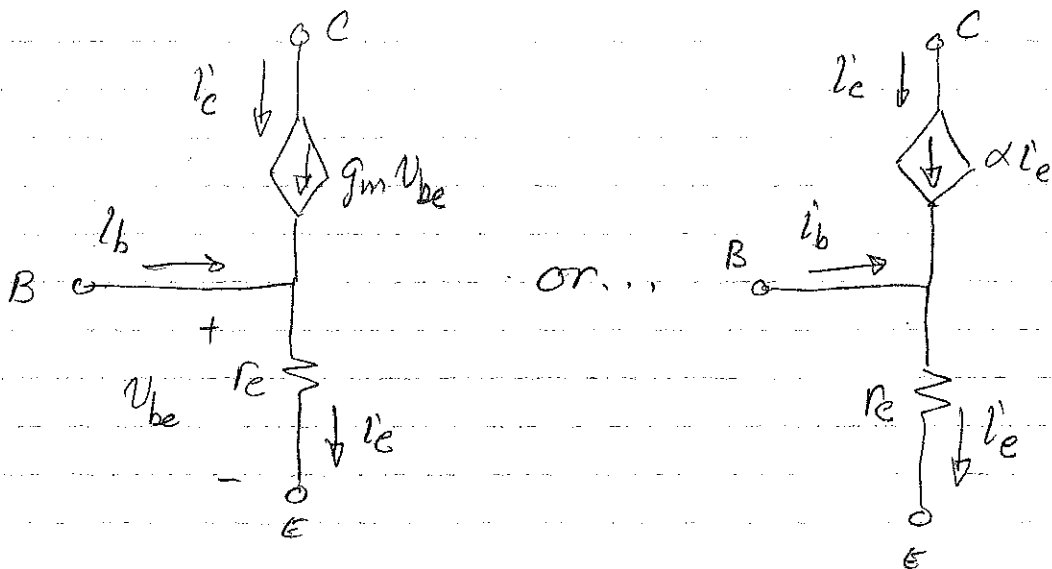Sometimes it is convenient to use a model that contains r_e explicitly.



Although r_{π} is not included, the model correctly predicts I_b . We can show that

$$I_b = \frac{V_{be}}{r_e} - g_m V_{be}$$

$$= \frac{V_{be}}{r_{\pi}}$$

SMALL SIGNAL MODELING

We now have the following prescription:

Given a BJT amplifier circuit...

1. Find the dc operating point and I_C in particular.

(We assume the BJT is in the linear mode.)


2. Calculate the small signal parameters r_{π} , g_m , r_e .

3. De-activate dc sources.

4. Replace the BJT with the Hybrid- π or T-Model.

5. Perform the ac analysis: voltage gain, input impedance, ...

EXAMPLE (From Shattuck's notes)

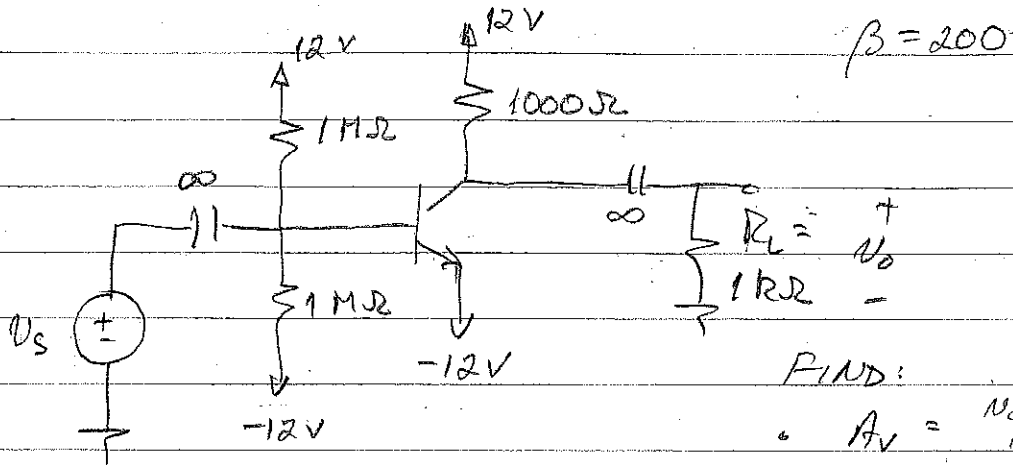

FIND:


- $A_v = v_o/v_s$
- Input/output

DC Analysis

Impedances

- Thevenin equivalent at base
- C → open circuit
- ac source v_s goes away (not relevant for dc)

Assume active region

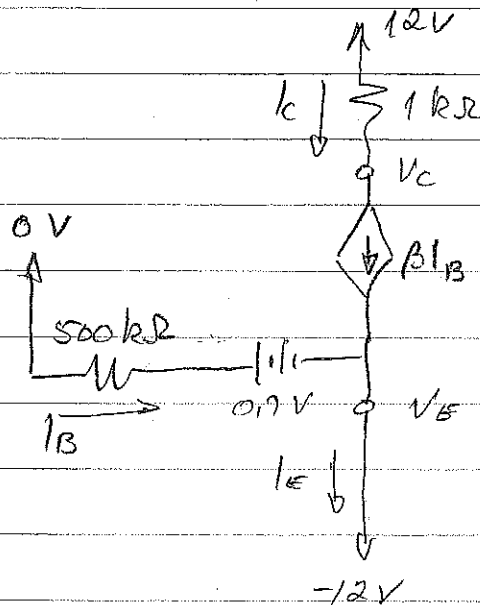

$$I_B = \frac{12 - 0.7}{500k} = 22.6 \mu A$$


$$I_C = \beta I_B = 4.52 \text{ mA}$$

$$V_C = 12 - 1000 I_C = 2.48 \text{ V}$$

So ACTIVE region is correct.

AC Analysis

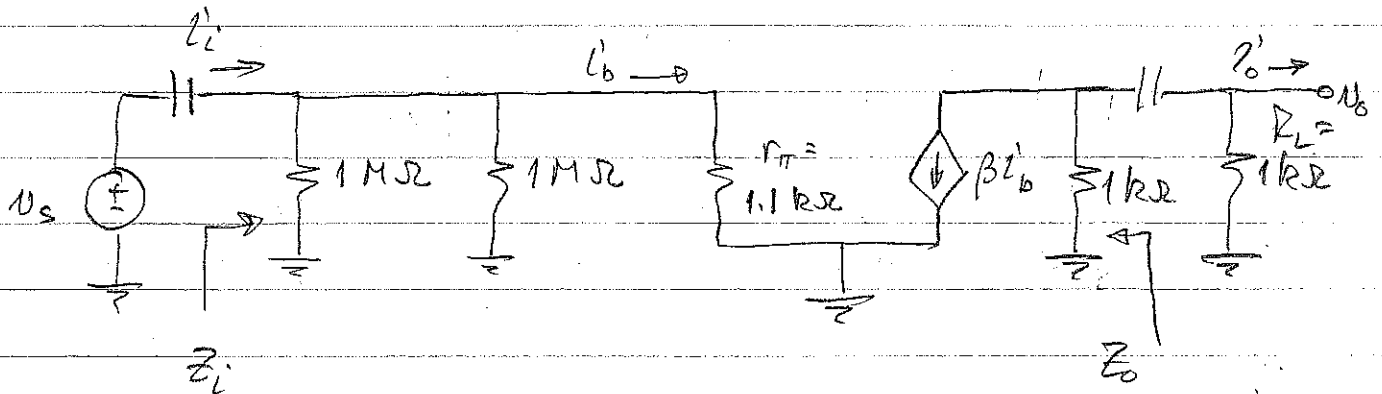- $C \rightarrow$ short circuit ($1/j\omega C \rightarrow 0$ since $C \rightarrow \infty$)
- dc sources \rightarrow short



$$r_{\pi} = \frac{V_T}{I_B} = \frac{25 \text{ mV}}{22.6 \mu\text{A}} = 1.1 \text{ k}\Omega$$

Analysis: $i_b = \frac{v_s}{r_{\pi}}$

$$v_o = -\beta i_b \cdot (1 \text{ k}\Omega \parallel 1 \text{ k}\Omega)$$

$$= -\frac{200 v_s}{r_{\pi}} \cdot 500$$


$$A_v = \frac{v_o}{v_s} = -200(500)/r_{\pi} = -91$$

$$Z_i = \left(\frac{1}{1 \text{ M}} + \frac{1}{1 \text{ M}} + \frac{1}{r_{\pi}} \right)^{-1} \approx r_{\pi} = 1.1 \text{ k}\Omega$$

$$Z_o = 1 \text{ k}\Omega$$

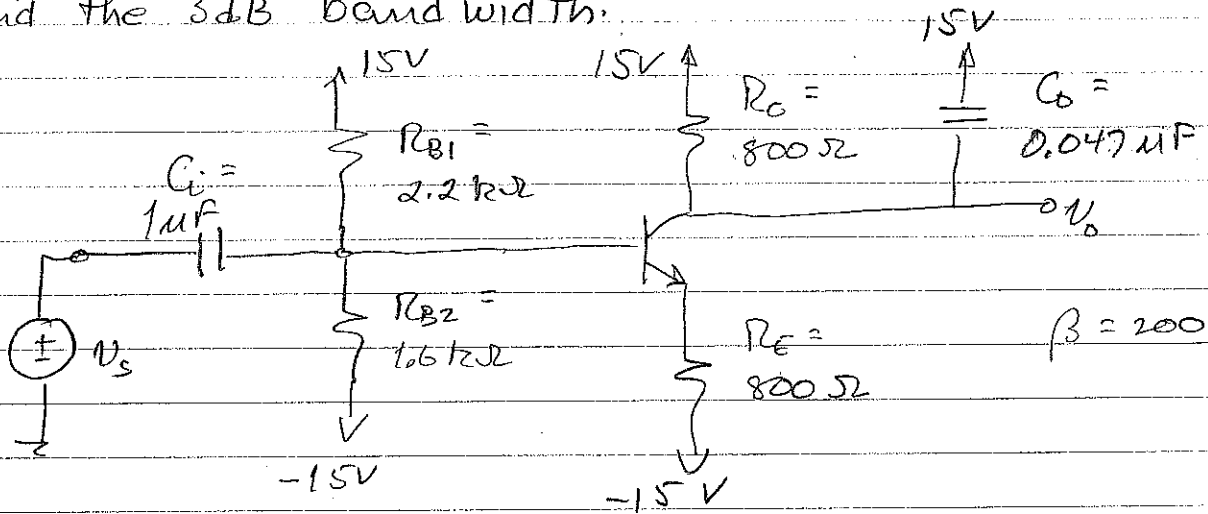EXAMPLE: Common Emitter Amplifier


Find $T_{i\omega} = \frac{V_o}{V_s}$. Find the gain in the pass band
 Find the 3dB bandwidth.



This is a small-signal analysis problem, but we need a dc analysis to find the necessary ac model parameters. We should also check to be sure we are biased in the linear region.

DC: Capacitors \rightarrow open.

Thevenizing the base, we have:

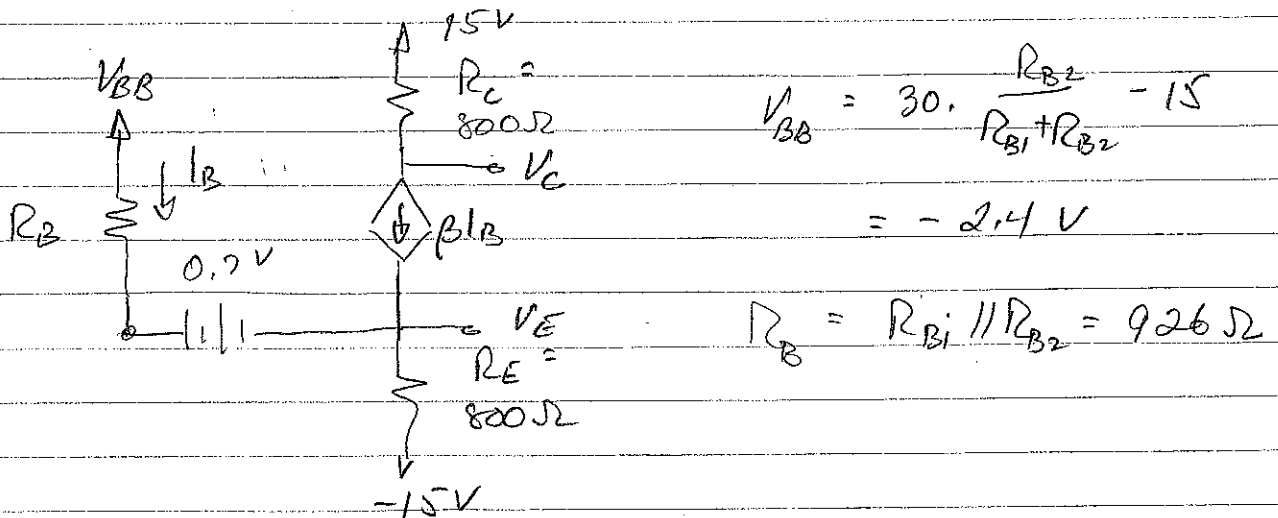

$$\text{KVL: } -V_{BB}'' + R_B I_B + 0.7 + (\beta + 1) R_E - 15 = 0$$

$$\Rightarrow +2.4 + 926 I_B + 0.7 + 201(800) = 15$$

$$I_B = 73.6 \mu\text{A} \quad \checkmark$$

$$V_{CE} = 15 - \beta I_B \cdot R_C - ((\beta + 1) I_B R_E - 15)$$

$$= 15 - 200(73.6 \times 10^{-6})(800)$$

$$- [201(73.6 \times 10^{-6})(800) - 15]$$


$$= 3.23 - (-3.17) = 6.40 \text{ V} \quad \checkmark$$

So we are in fact in the linear region. We can now find

$$r_{\pi} = \frac{V_T}{I_B} = \frac{25 \times 10^{-3}}{73.6 \times 10^{-6}} = 340 \Omega$$


AC MODEL

DC voltage sources \rightarrow short

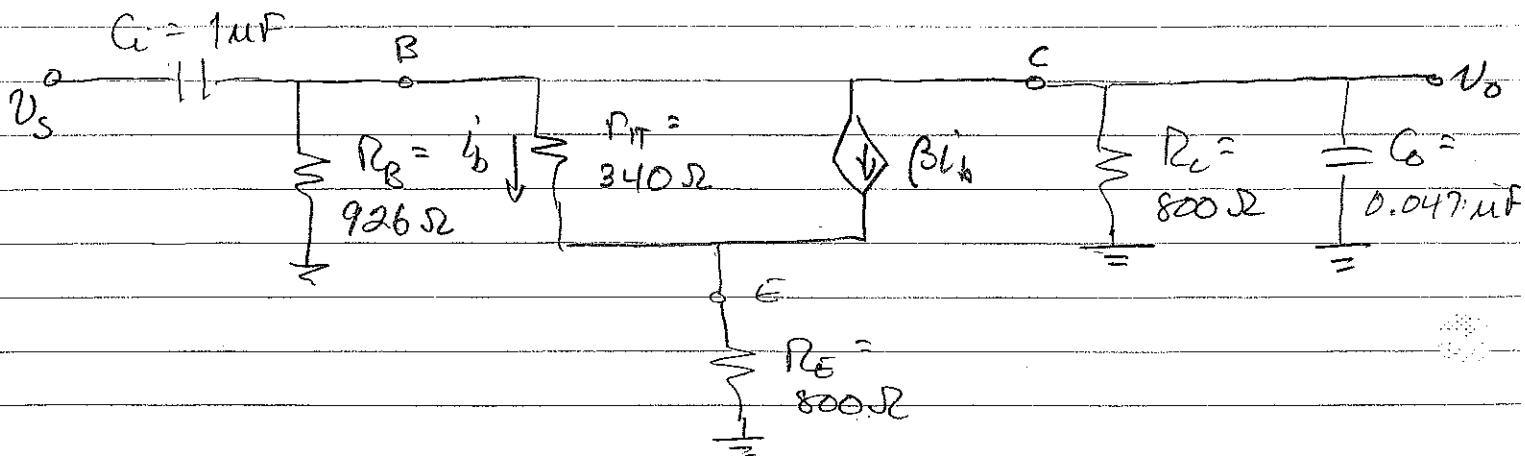

Miller's Dual is an option here. Let's do that:
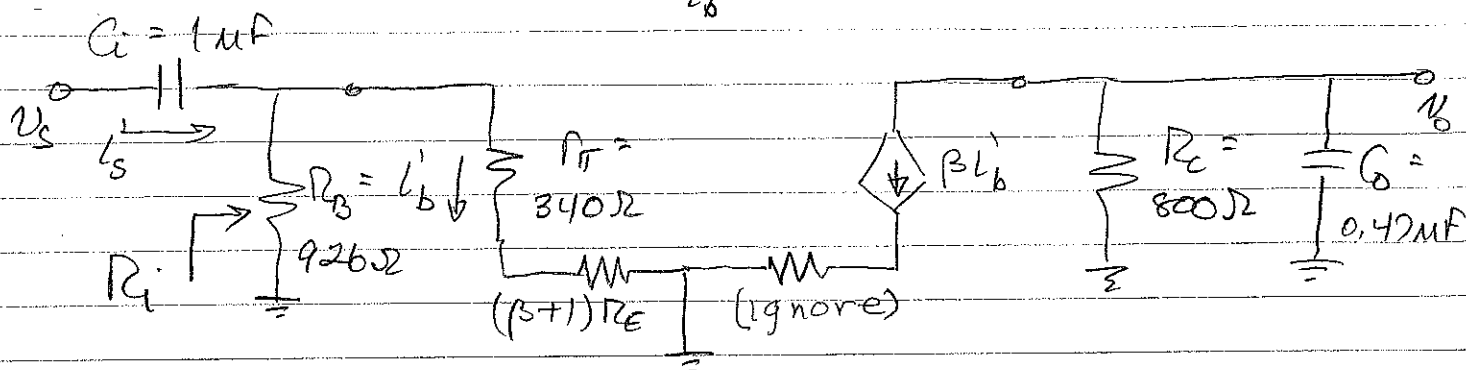
$$\text{Current ratio } I \equiv \frac{\beta I_b}{I_b} = \beta$$



Let's simplify the input a bit. The resistance R_i is

$$R_i = R_B \parallel (r_{\pi} + (\beta+1)R_E)$$

But $r_{\pi} \ll (\beta+1)R_E$ and $R_B \ll (\beta+1)R_E$ so

$$R_i \approx R_B \parallel (\beta+1)R_E \approx R_B.$$

Actual numbers =

$$R_i = 926 \parallel (340 + 201 \times 800) = 920.7 \Omega$$

so we are not far off if we say $R_i \approx R_B$.

This simplification will help us find I_b so...

Analysis...

$$\bar{V}_o = -\beta \bar{I}_b (R_c \parallel \frac{1}{j\omega C_c}) = -\beta \bar{I}_b \frac{R_c}{1+j\omega C_c R_c}$$

$$\bar{I}_s = \frac{\bar{V}_s}{\frac{1}{j\omega C_c} + R_i} = \frac{j\omega C_c \bar{V}_s}{1+j\omega C_c R_i}$$

But from above we have $R_i \approx R_B$ so

$$\bar{I}_s = \frac{j\omega C_c \bar{V}_s}{1+j\omega C_c R_B}$$

$$\bar{I}_b = \bar{I}_s \cdot \frac{R_B}{R_B + r_\pi + (\beta+1)R_E} \approx \bar{I}_s \cdot \frac{R_B}{R_B + (\beta+1)R_E}$$

$$\text{So } T(\omega) = \frac{\bar{V}_o}{\bar{V}_s} = -\beta \frac{R_c}{1+j\omega C_c R_c} \cdot \frac{j\omega C_c}{1+j\omega C_c R_B} \cdot \frac{R_B}{R_B + (\beta+1)R_E}$$


FREQUENCY ANALYSIS.

We have a zero at 0 and poles at

$$P_1 = \frac{1}{C_c R_c} = 26600 \text{ rad/s}$$

$$P_2 = \frac{1}{C_c R_B} = 1086 \text{ rad/s} \quad (I \text{ used } R_B = 921 \Omega)$$

So we have a pass-band response:

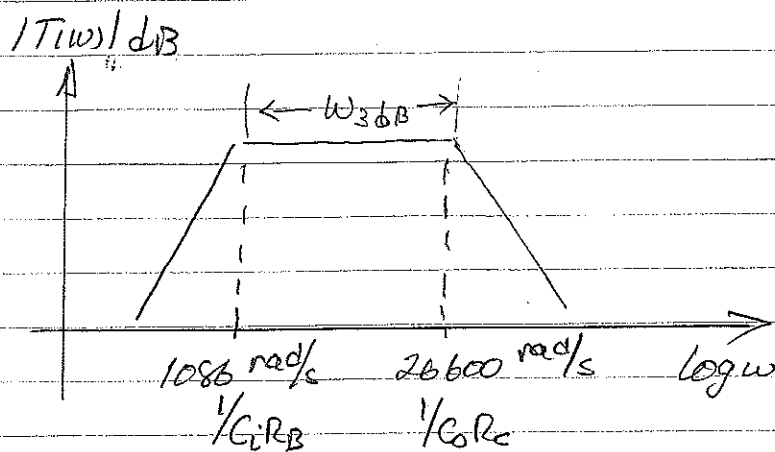

We can define the pass band as the roughly flat region between poles, i.e.

$$W_{3dB} = 26,600 - 1086 \approx 25,500 \text{ rad/s}$$

This is the 3 dB BANDWIDTH.

We can also find the GAIN IN THE PASSBAND. This is the gain in the region where $|T(j\omega)|$ is approximately constant.

The brute-force way to do this is to substitute a value of ω in the pass band region into $T(j\omega)$ and calculate the gain. We choose $\omega_0 = 10,000 \text{ rad/s}$ and find

$$T(j\omega_0) = -200 \frac{800}{1 + j(10^4)(4.7 \times 10^{-8})(800)} \cdot \frac{j10^4(10^{-6})}{1 + j10^4(10^{-6})(921)}$$

$$\times \frac{921}{921 \times (201)(800)}$$

$$= 0.92 \angle 165^\circ \text{ V}$$

$$|T(j\omega_0)|_{dB} \approx 0 \text{ dB}$$

There is a simpler way: Note that in the pass band, $T(\omega)$ is not a function of ω (otherwise it wouldn't be flat!). That means terms containing $j\omega$ are not having an effect. Why?

Look at the terms with $j\omega$ and evaluate at ω_0 :

$$\frac{R_c}{1 + j\omega C_0 R_c} = \frac{800}{1 + j10^4(4.2 \times 10^{-9})(800)}$$

$$= \frac{800}{1 + j(0.38)} \approx \frac{800}{1 + j0}$$

$$\frac{j\omega_0 C_i}{1 + j\omega_0 C_i R_B} = \frac{j(10^4)(10^{-6})}{1 + j10^4(10^{-6})(921)} = \frac{j(0.01)}{1 + j9.21} \approx \frac{j(0.01)}{j9.21}$$

More generally

$$\omega_0 \ll \frac{1}{C_0 R_c} \quad \text{and} \quad \omega_0 \gg \frac{1}{C_i R_B}$$

— This is evident from the Bode plot, so...

$$C_0 \ll \frac{1}{\omega_0 R_c} \quad \text{and} \quad C_i \gg \frac{1}{\omega_0 R_B}$$


For C_0 small, Z_{C_0} large, i.e., C_0 is an open ckt.

For C_i large, Z_{C_i} small, i.e., C_i is a short ckt.

Q. We can generalize this: In the passband, capacitors are either short or open (approximately), which is why $T(w)$ is not a function of frequency.

But which is which? In our example, C_i must be a short because if it were open, there would be no source. C_o must be open because if it were a short, V_o would be 0.

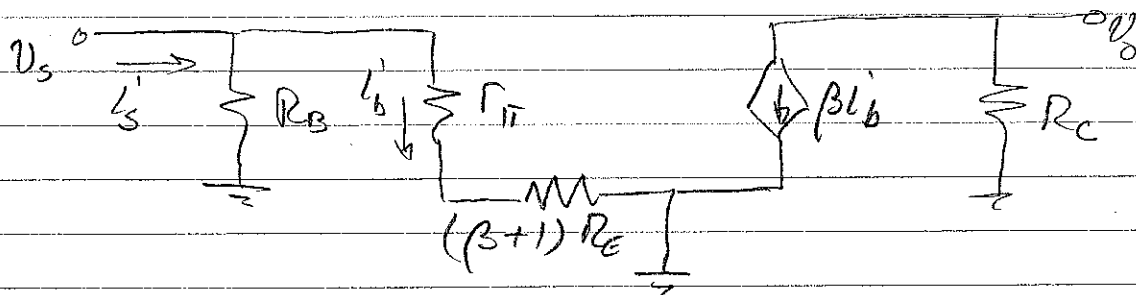We now re-do our ac analysis with
 $C_i \rightarrow$ short $C_o \rightarrow$ open



$$V_o = -\beta i_b' R_C$$

$$i_s' \approx \frac{V_s}{R_B}$$

$$i_b' = i_s' \frac{R_B}{R_B + (\beta+1)R_E}$$

$$\Rightarrow \frac{V_o}{V_s} = -\beta \frac{R_C}{R_B} \frac{R_B}{R_B + (\beta+1)R_E} = -\beta \frac{R_C}{R_B + (\beta+1)R_E}$$

$$\frac{V_o}{V_s} = -200 \frac{800}{800 + 201(800)}$$

$$= -0.99 \text{ V/V}$$

This is close to the value we got from plugging ω_0 into $T(\omega)$,

we could also have done this from the transfer function:

$$T(\omega) = \frac{-\beta R_c}{1 + j\omega C_o R_c} \cdot \frac{j\omega C_i}{1 + j\omega C_i R_B} \cdot \frac{R_B}{R_B + (\beta + 1)R_E}$$

$$\text{But } \omega_0 \ll \frac{1}{C_o R_c} \Rightarrow 1 + j\omega C_o R_c \approx 1$$

$$\omega_0 \gg \frac{1}{C_i R_B} \Rightarrow 1 + j\omega C_i R_B \approx j\omega C_i R_B$$

Then


$$\begin{aligned} T(\omega) &\approx \frac{-\beta R_c}{1} \cdot \frac{j\omega C_i}{j\omega C_i R_B} \cdot \frac{R_B}{R_B + (\beta + 1)R_E} \\ &= \frac{-\beta R_c}{R_B + (\beta + 1)R_E} \end{aligned}$$

... as we got before!

LOAD LINE ANALYSIS


We will do a load-line analysis on a simple BJT to see how this all fits together. We will use a plot of i_C vs. V_{CE} from Sedra & Smith 5ed. to record the results.

THE CIRCUIT

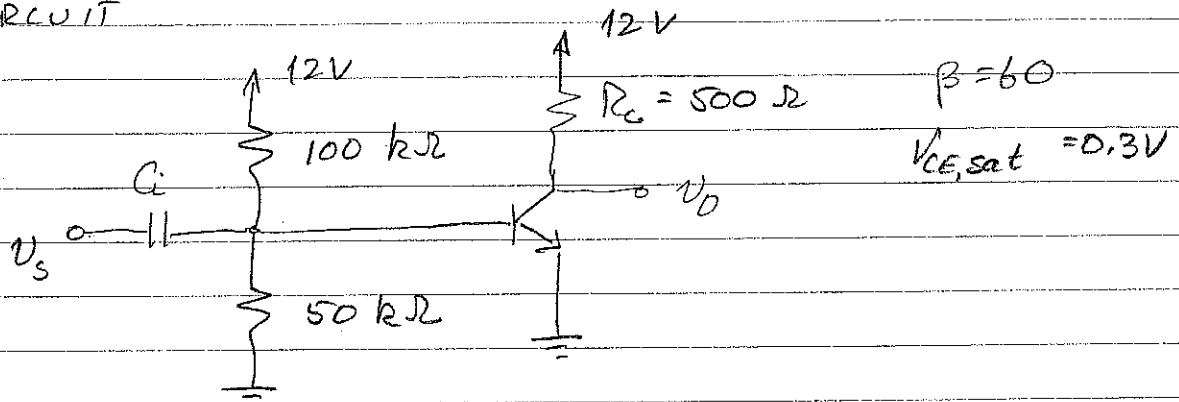

DC ANALYSIS

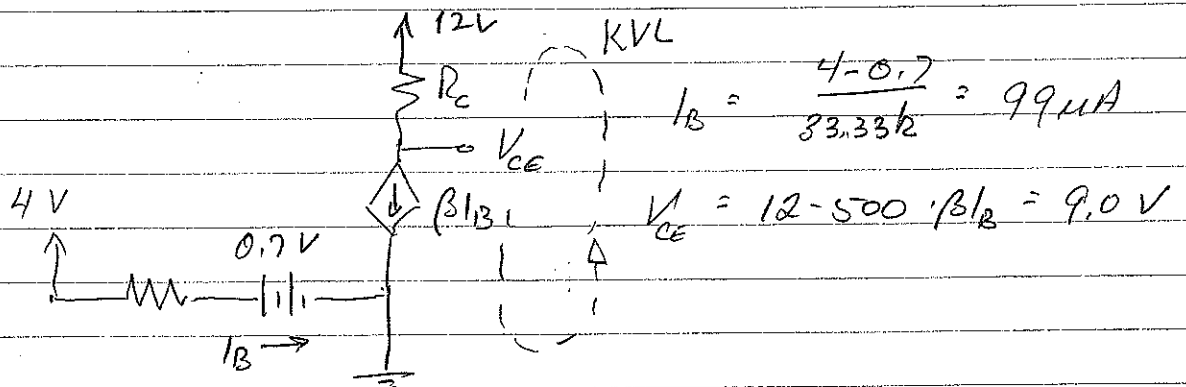Thevenizing the base, we have (C \rightarrow open)



We can now go to the i_C - V_{CE} plot and locate our Q-point. It is at $I_B = 99 \mu A$ and $V_{CE} = 9.0V$.

Also, $I_C = \beta I_B = 8.94 mA$. We have also indicated this on the plot.

LOAD LINE

The load line is based on the KVL at the output - that is, an equation relating I_C to V_{CE} .

KVL (indicated as dashed line on dc circuit):


$$-12 + I_C \cdot R_C + V_{CE} = 0$$

$$\Rightarrow I_C = \frac{12 - V_{CE}}{R_C}$$

This is a straight line of slope $-1/R_C$, y-intercept $12/R_C$, and x-intercept $12V$. These intercepts are indicated on the plot

AC ANALYSIS

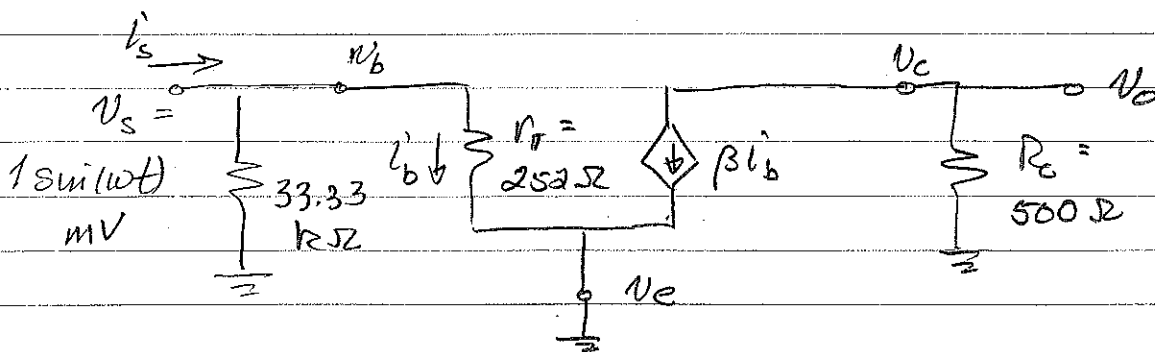We have $r_{\pi} = \frac{V_T}{I_B} = \frac{25 \times 10^{-3}}{99 \times 10^{-6}} = 252 \Omega$



We have assume large C_i so that for any ω we will consider, $C_i \rightarrow$ short.

We will take $v_s = 1 \sin(\omega t) \text{ mV}$

Now

$$i_b' = \frac{v_s}{R_B \parallel r_{\pi}} \cdot \frac{R_B}{R_B + r_{\pi}} \approx \frac{v_s}{r_{\pi}}$$

$i_s' \rightsquigarrow$

The approximation is based on the fact $R_B \gg r_{\pi}$.

At max/min $v_s = \pm 1 \text{ mV}$, we have

$$i_b' = \pm \frac{0.001}{r_{\pi}} = \pm 3.97 \mu\text{A} \approx \pm 4 \mu\text{A}$$

So the total signal i_B' is

$$\begin{aligned} i_B' &= i_b' + I_B = \pm 4 \mu\text{A} + 99 \mu\text{A} \\ &= 103 \mu\text{A}, 95 \mu\text{A} \end{aligned}$$

Also $i_c' = \beta i_b' = 240 \mu\text{A} = 0.240 \text{ mA}$

$$\begin{aligned} \Rightarrow i_c' &= \pm 0.240 + 5.94 \text{ mA} \\ &= 6.18 \text{ mA}, 5.70 \text{ mA} \end{aligned}$$


$$v_{ce} = \beta i_b' \cdot 500 = 0.12 \text{ V}$$

$$\begin{aligned} \Rightarrow v_{ce} &= \pm 0.12 + 9 \text{ V} \\ &= 9.12 \text{ V}, 8.88 \text{ V} \end{aligned}$$


These points are also indicated on the plot.

This analysis is valid for any BJT operating \curvearrowright

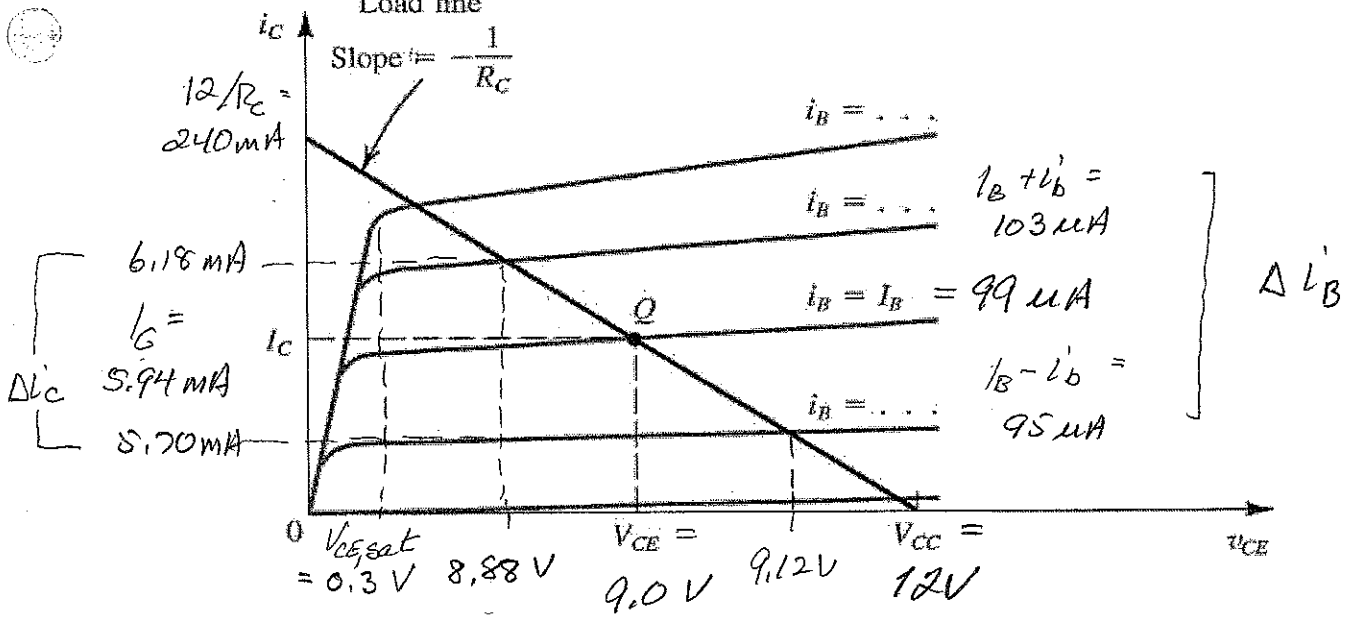in linear mode as an amplifier. We also note that our signal causes V_{CE} to move closer to 12V (which would be cut-off) and to 0.3V (which would be saturation). So if V_s is too large, or β is too large, the signal will drive the BJT out of the linear region, in which case we will get distortion.



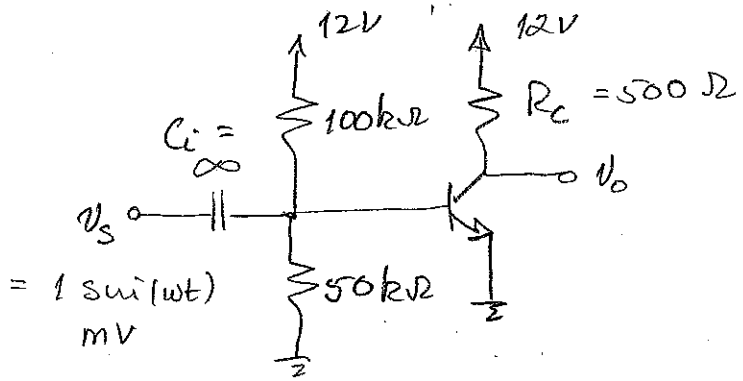
$$\frac{\Delta i'_C}{\Delta i'_B} = \frac{0.240}{0.004} = 60$$



EXAMPLE

FIND the gain in the passband.

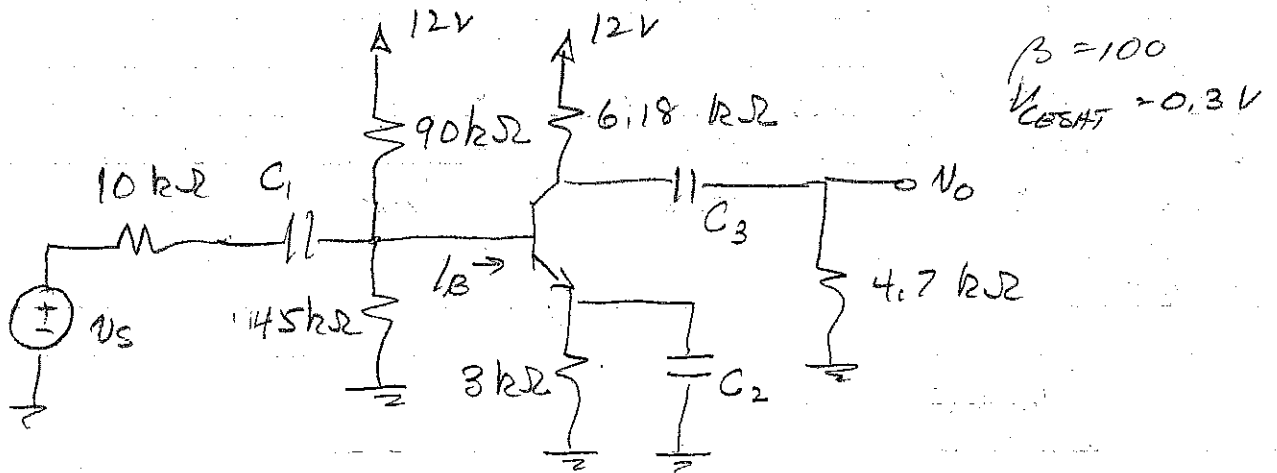

DC ANALYSIS

$C \rightarrow$ OPEN CKT

$$V_{BB} = 12 \cdot \frac{45}{45+90} = 4V$$

$$R_B = 90k \parallel 45k = 30k\Omega$$

$$\therefore I_B = \frac{4-0.3}{30k\Omega + (101)3k\Omega} = 0.01 \mu A$$

$$\Rightarrow I_C = 1 \mu A$$

$$g_m = I_C / V_T = 40 \text{ mS}$$


$$r_{\pi} = \beta V_T / I_C = 2.5 k\Omega$$

AC ANALYSIS

In the pass band, $C_1 \rightarrow \text{SHORT}$ (otherwise the input is cut off), $C_2 \rightarrow \text{SHORT}$, $C_3 \rightarrow \text{SHORT}$ (otherwise the output is cut off).

It's not terribly obvious that C_2 should be SHORT, but this is usually the case in the pass band. Typically C_2 is large, so $1/\omega C_2 \rightarrow 0$.

MODEL

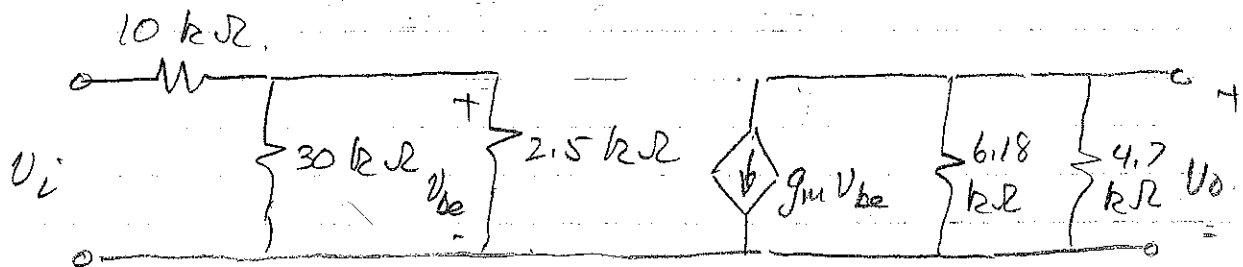


$$\frac{V_{be}}{V_i} = \frac{2.5k \parallel 30k}{2.5k \parallel 30k + 10k} = 0.187$$

$$\frac{V_o}{V_{be}} = -g_m \cdot 4.7k \parallel 6.18k$$

$$\therefore \frac{V_o}{V_i} = -0.187 \cdot 40 \times 10^{-3} \cdot 4.7k \parallel 6.18k = -20 \text{ V/V}$$

EXAMPLE

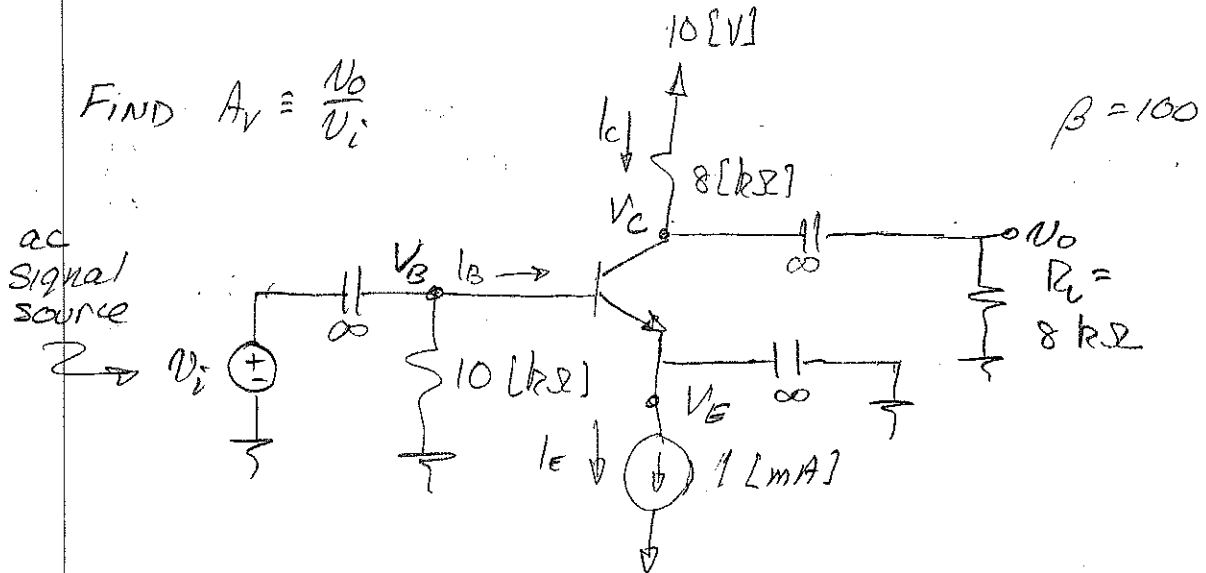

DC ANALYSIS: ASSUME LINEAR

a) $I_E = 1 \text{ [mA]} ; I_C = \frac{\beta}{1+\beta} I_E = 0.99 \text{ [mA]}$

$$I_B = I_E - I_C = 0.01 \text{ [mA]}$$

$$\therefore V_B = -I_B (10 \text{ k}) = -0.1 \text{ [V]}$$


$$V_E = V_B - 0.7 \text{ [V]} = -0.8 \text{ [V]}$$

$$V_C = 10 - I_C (8 \text{ k}) = 2.1 \text{ [V]}$$

b) $g_m = \frac{-I_C}{V_T} = \frac{0.99}{25} = 39.6 \text{ [mA/V]}$

$$r_{\pi} = \frac{\beta}{g_m} = 2.5 \text{ [k}\Omega\text{]}$$

c)

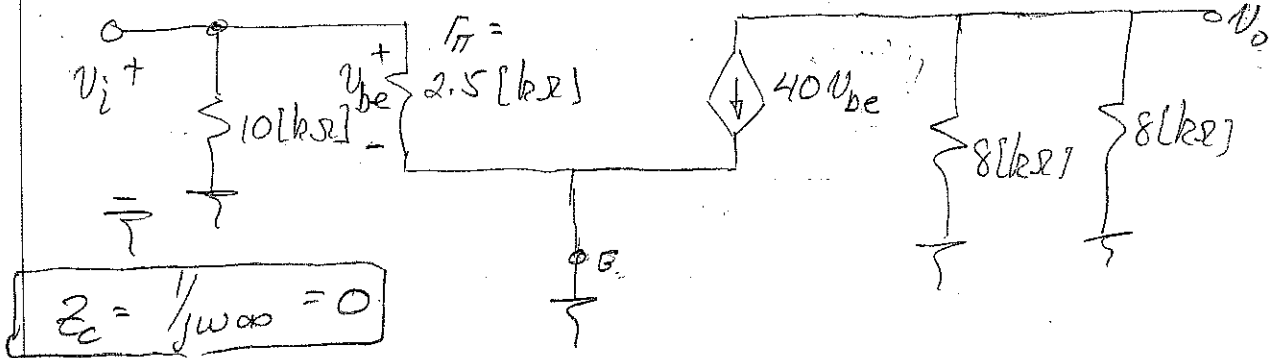

NOTE: To an ac signal, +10V looks like ground; 1 mA looks like $R = \infty$.

We say +10V = SIGNAL GROUND
1 mA = SIGNAL OPEN CRT

Then

$$v_o = -40 \left[\frac{\text{mA}}{\text{V}} \right] \times 4 \text{ [k}\Omega\text{]} v_{be}$$


$$= -160 \text{ [V/V]} v_{be}$$

$$v_{be} = v_i \quad \text{so}$$

$$\frac{v_o}{v_i} = A_v = -160 \text{ [V/V]}$$

We can also find input and output impedances.
 In general, there may be capacitance in the circuit,
 in which case this is a phasor analysis problem.
 For the example above, $C \rightarrow \infty \Rightarrow Z_C \rightarrow 0$, so
 this remains a resistive circuit only.

Redraw, defining impedances:

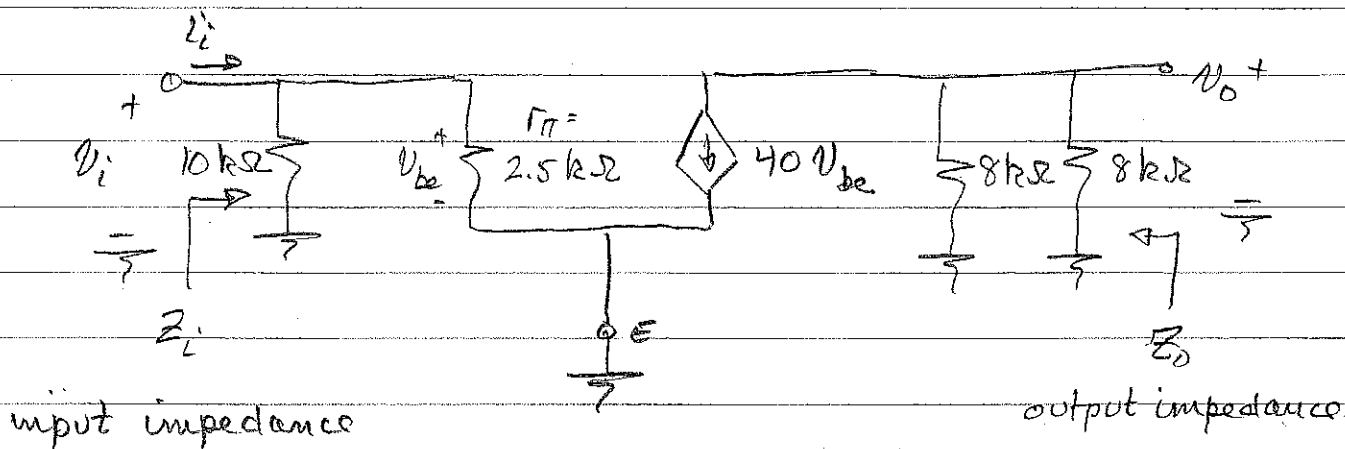

Q. How do we find Z_i , Z_o ?


A. Test-source method.

$$Z_i = \frac{V_i}{I_i} \rightarrow \frac{V_i}{I_i} \quad (\text{resistors-only})$$

$$Z_i = \frac{V_i}{10\text{k}} + \frac{V_{be}}{2.5\text{k}}, \quad V_{be} = V_i$$

$$\Rightarrow Z_i = \frac{V_i}{I_i} = \left(\frac{1}{10\text{k}} + \frac{1}{2.5\text{k}} \right)^{-1} = 2\text{k}\Omega$$

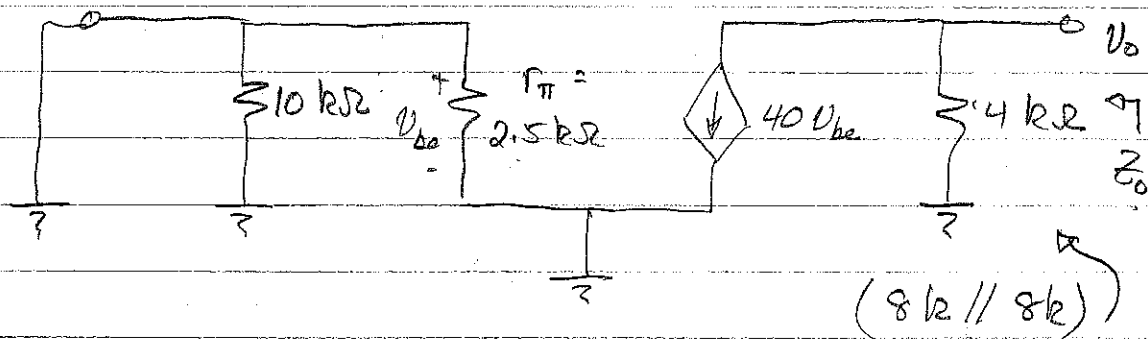Output Impedance is usually taken with the source connected. In using a test source, however, we short-circuit the independent sources. So...




$$\text{Now } V_{be} = 0 \Rightarrow 40 V_{be} = 0 \Rightarrow \underline{\underline{Z_o = 4\text{ k}\Omega}}$$

EARLY EFFECT


OBSERVATION: In the linear region, $I_C - V_{CE}$ curves are not flat, but tilt upwards slightly. In other words, I_C is not completely independent of V_{CE} but increases slightly.

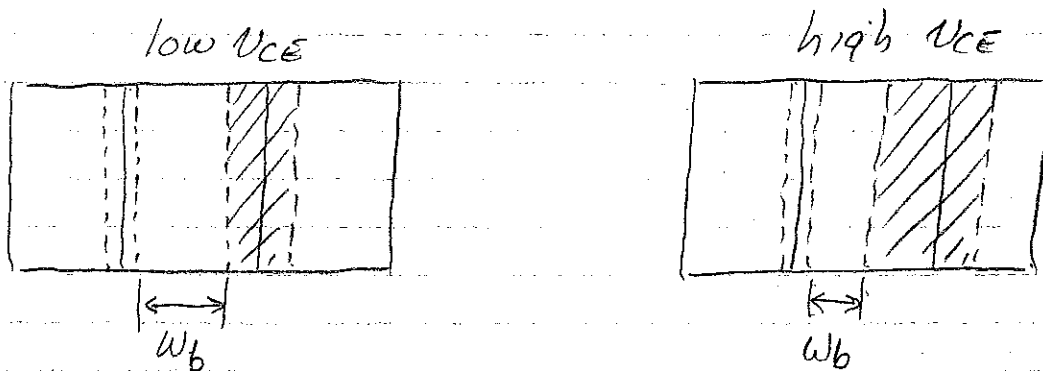REASON: As CB junction becomes increasingly reverse-biased, the "depletion region" in the CB junction increases and the base width is reduced. Smaller base \Rightarrow higher β , so I_C increases.



$w_b \equiv$ base width

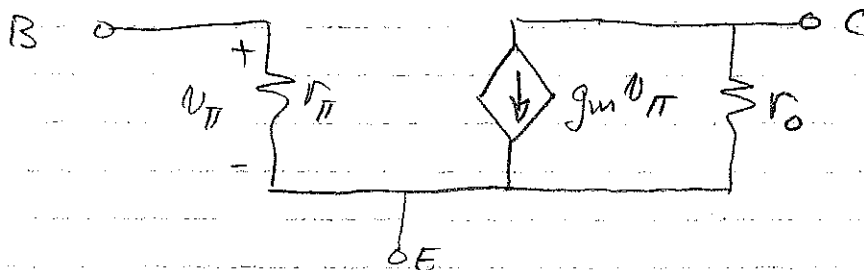MODELING we can account for this in our small-signal model by adding an output resistance r_o :



$$r_o = \frac{|V_A|}{I_C}$$