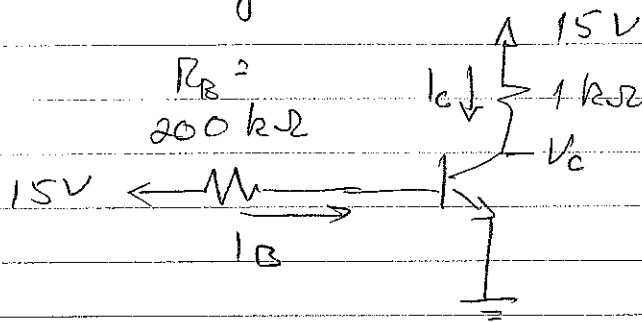


BIASING: VARIATION IN β

We need to account for potentially very large changes in β from one device to the next.
Here's why:



GIVEN: β varies between 100 & 300.

Suppose we have designed for forward active mode with $\beta = 100$. We have

$$I_B = \frac{15 - 0.7}{200000} = 71.5 \mu\text{A}$$

$$V_{CE} = V_C = 15 - 1000 \beta I_B = 7.85 \text{ V} \quad \checkmark$$

Now suppose $\beta = 300$:

$$I_B = \frac{15 - 0.7}{200000} = 71.5 \mu\text{A}$$

$$V_{CE} = V_C = 15 - 1000 \beta I_B = -6.45 \text{ V} \quad ?!$$

So we are no longer in active mode.

The problem here is that I_B is fixed by R_B and V_{BB} . We need to re-think this design.



BIASING FOR DISCRETE CIRCUIT DESIGN


ISSUES:

- β varies dramatically among different discrete BJTs
- Change in temperature affects device operation
- Q-point must allow sufficient "room" for output voltage swing.

We need to consider these issues in designing bias circuits, especially the variation in β .

SINGLE POWER SUPPLY

Four-Resistor Bias circuit:

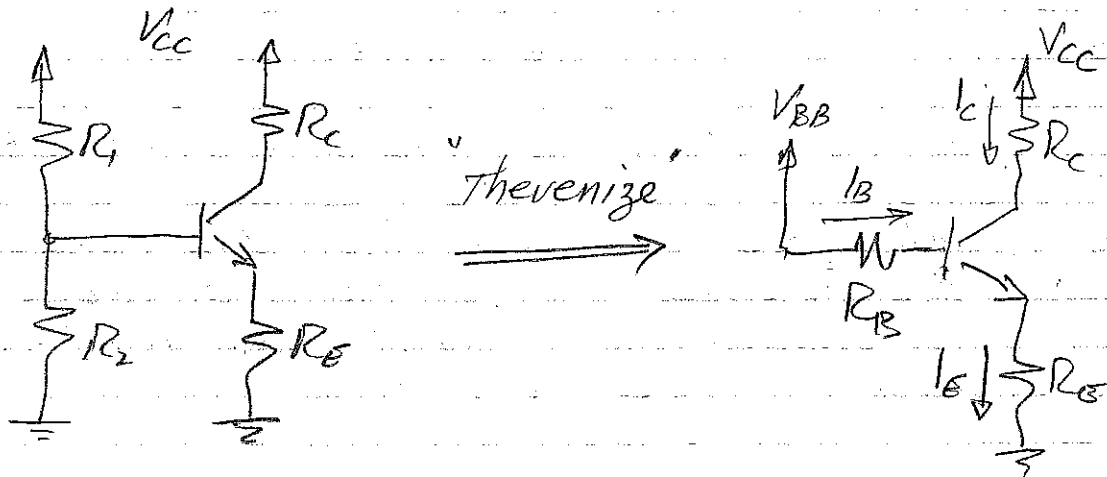

$$R_B = R_1 \parallel R_2 \quad V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2}$$

Now we have

$$-V_{BB} + R_B I_B + 0.7 + I_E R_E = 0$$

$$I_E = (\beta + 1) I_B$$

$$\Rightarrow I_B = \frac{V_{BB} - 0.7}{R_B + (\beta + 1) R_E}$$

Some numbers:

$$R_1 = 10 \text{ k}\Omega, R_2 = 5 \text{ k}\Omega \Rightarrow R_B = 3.33 \text{ k}\Omega$$

$$V_{CC} = 15 \text{ V} \Rightarrow V_{BB} = 5 \text{ V}$$

$$R_C = R_E = 1000 \Omega$$

$$\text{Then for } \beta = 100, I_B = 41.2 \mu\text{A}, I_C = 4.12 \text{ mA}$$

$$\beta = 300, I_B = 14.1 \mu\text{A}, I_C = 4.24 \text{ mA}$$

So I_C changes by only 3%. The reason is that an increase in β causes a decrease in I_B , so a change in β is compensated by a change in base current.

Note: we do not mean to imply here that β for a particular BJT can change. What we mean is that different BJTs can have very different β , even though they are nominally the same device.

Another way to look at the circuit is this:

$$-V_{BB} + I_B R_B + 0.7 + I_E R_E = 0$$

$$I_B = \frac{I_E}{\beta + 1}$$

$$\Rightarrow I_E = \frac{V_{BB} - 0.7}{R_E + R_B / (\beta + 1)}$$


Now I_E will be relatively insensitive to β if

$$R_E \gg R_B / (\beta + 1)$$

Also, we want $V_{BB} \gg 0.7 \text{ V}$

These conditions will ensure "stability".

DOUBLE POWER SUPPLY

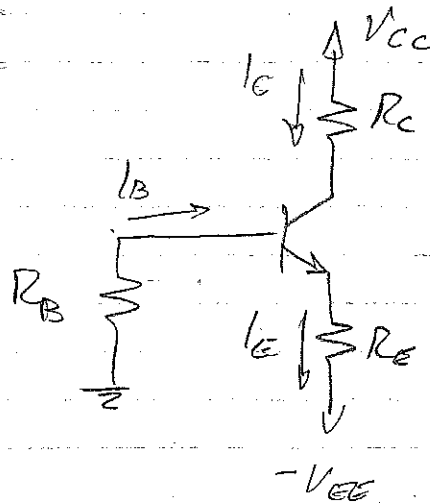


We have an equation similar to the previous one:

$$I_E = \frac{V_{EE} - 0.7}{R_E + R_B/(\beta+1)}$$

so the same stability conditions hold.

... and a couple of others...

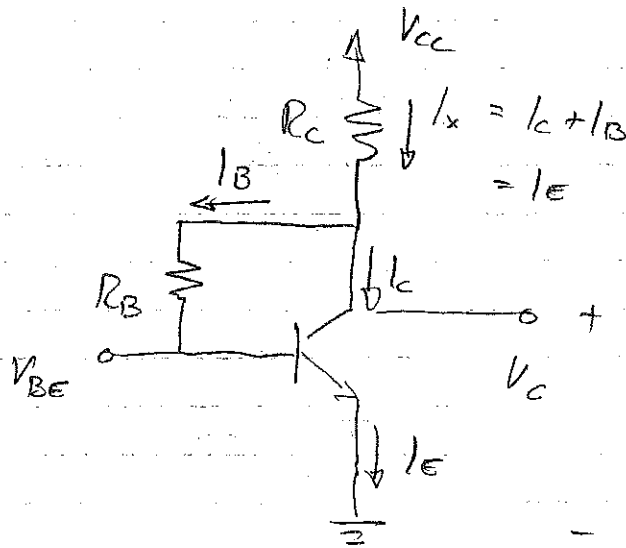

Here,

$$I_E = \frac{V_{CC} - V_{BE}}{R_C + R_B / (\beta + 1)}$$


so now we want $R_C \gg R_B / (\beta + 1)$

Collector voltage "swing" is

$$V_{CB} = I_B R_B = \frac{I_E R_B}{(\beta + 1)}$$

so R_B determines this.


... current-source biasing...

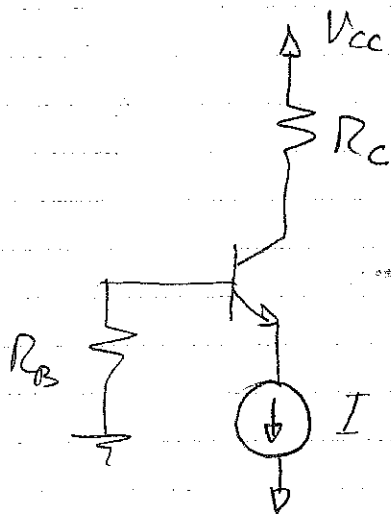

Here, I_c does not depend on β or R_B .

But where do we get the current source??

Try this...

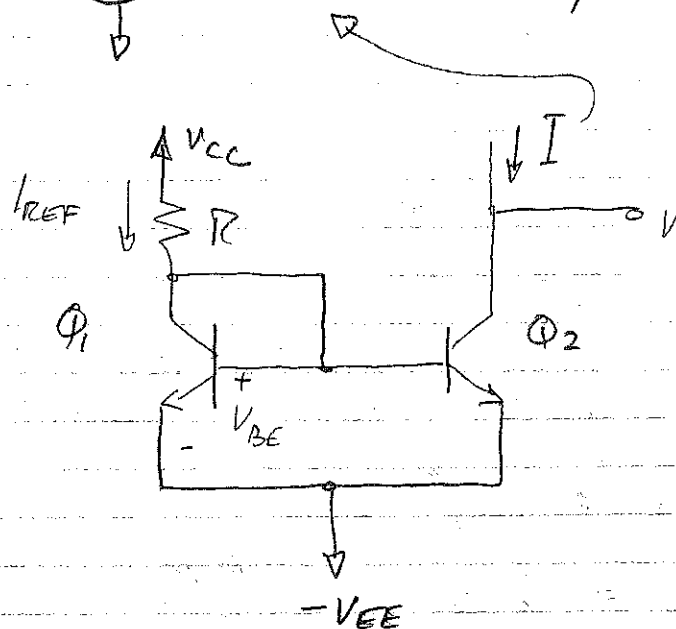

If I_B is negligible for Q_1, Q_2 , we have

$$I_{REF} \approx \frac{1}{R} (V_{CC} + V_{EE} - V_{BE})$$

If $V_{BE Q1} = V_{BE Q2}$ (matched BJTs), we must have


$$I = I_{REF}$$

This is a CURRENT MIRROR.

BJT AMPLIFIER CONFIGURATIONS.

On the following pages, we summarize the basic characteristics of single-stage BJT amps. First, we show simple diagrams indicating input/output parameters and gains. More complete analysis follows.


COMMON BASE

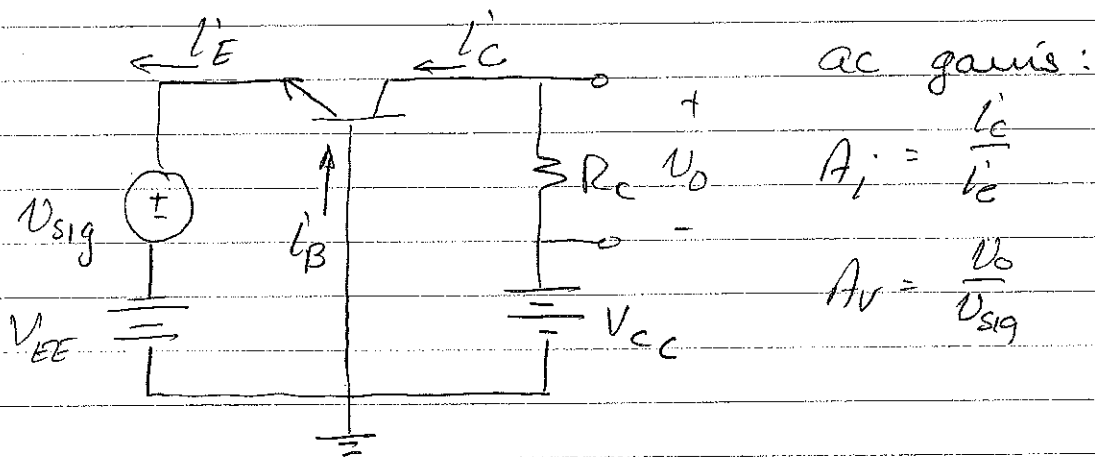

Since $i_c \approx i_e$, $A_i \approx 1$.

Since $i_c R_c$ can be large, $A_v > 1$


COMMON EMITTER

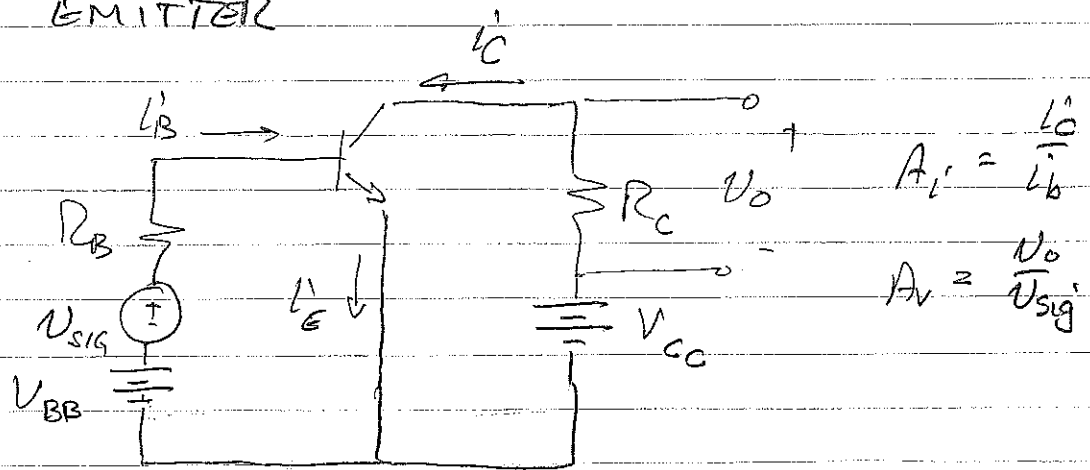

$$I_C > I_B \Rightarrow A_i > 1$$

Since $I_C R_C$ can be large, $A_v > 1$.

COMMON COLLECTOR

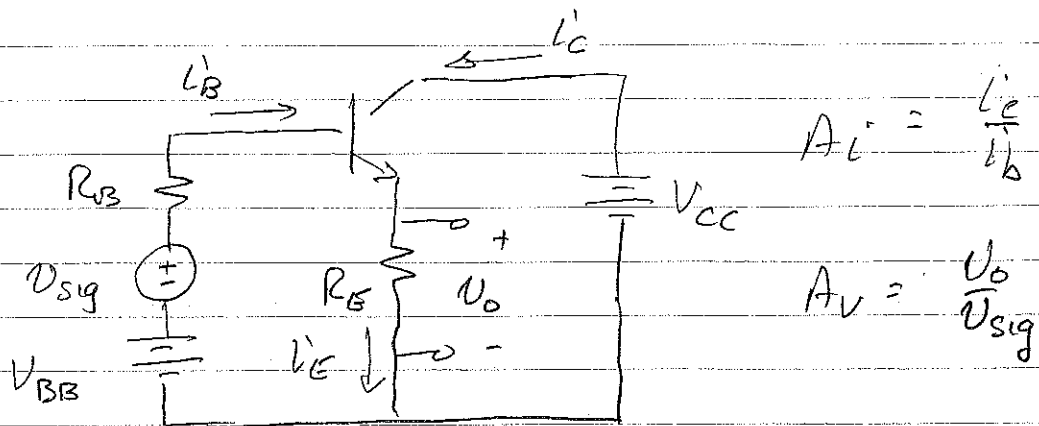

$V_B \approx V_E$ except for B-E voltage drop, so


$$A_v \approx 1.$$

Since $I_E > I_B$, $A_i > 1$.

SINGLE STAGE BJT AMPLIFIER CONFIGURATIONS


Following Sedra & Smith Section 5.7, we review basic properties of single stage BJT amplifiers. Here we only summarize; Sedra & Smith provide more detail.

COMMON EMITTER (FIG 5.60)

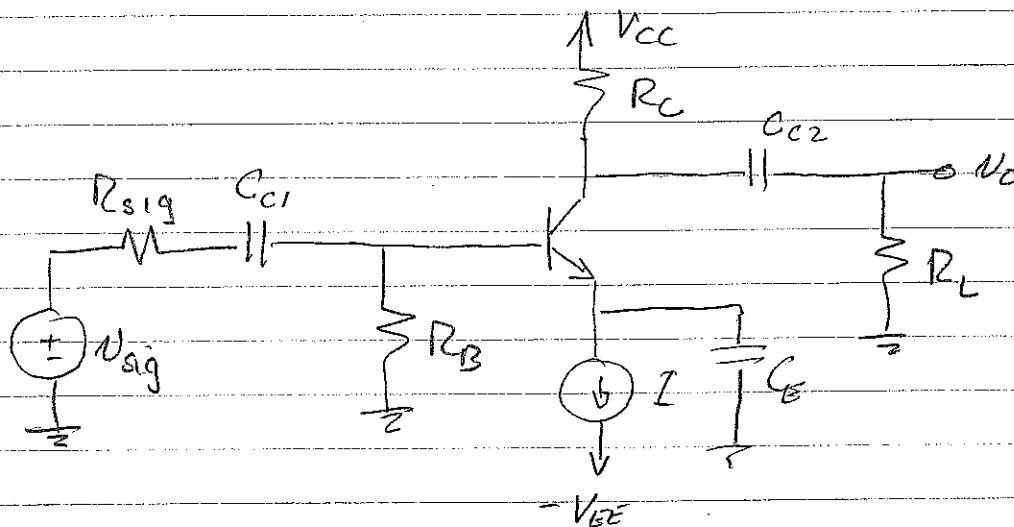

The current source biasing is a convenience, and simplifies the ac analysis.

AC ANALYSIS

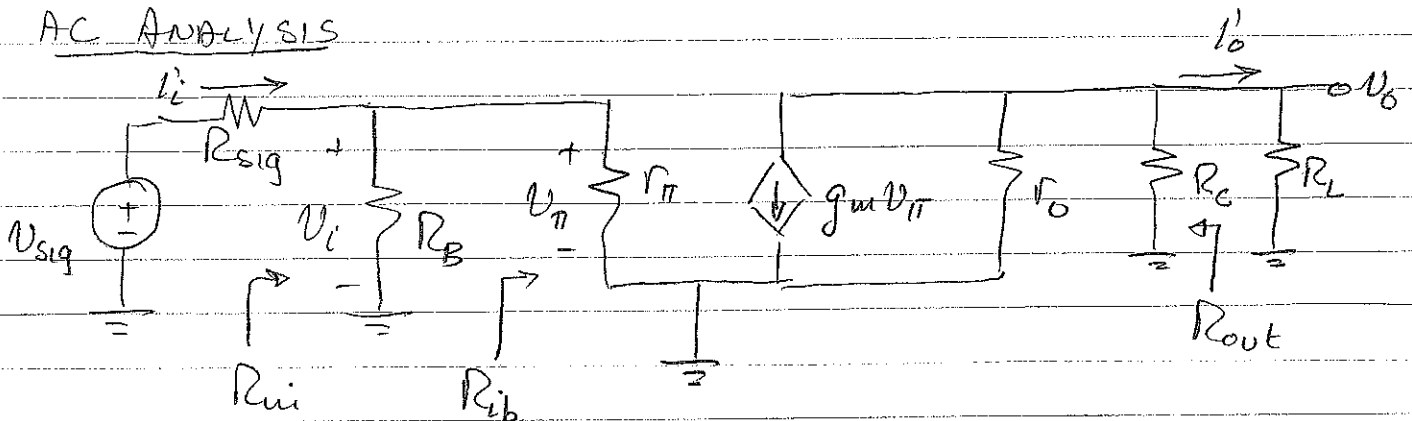

A more complete analysis of the CE amplifier circuit is found in the text. Here we summarize important aspects.

Common-Emitter Analysis

- Input resistance $R_{ib} = r_{\pi}$ (moderately large)
- $A_v \equiv v_o/v_i = -g_m (r_o \parallel R_c \parallel R_L)$
- $G_v \equiv v_o/v_{sig}$ If R_B is large, then
$$G_v = v_o/v_{sig} = -\beta(R_c \parallel R_L \parallel r_o)/(r_{\pi} + R_{sig})$$

Note that $\beta = g_m r_{\pi}$. So for $R_{sig} \gg r_{\pi}$, G_v is β -dependent. But for $R_{sig} \ll r_{\pi}$,

$$G_v \approx -g_m (R_c \parallel r_o \parallel R_L)$$


- $A_{is} \equiv \frac{v_{os}}{i_i} = -g_m R_{in} \approx -\beta$ (short-circuit gain)

with $R_{in} = R_B \parallel r_{\pi}$. For $R_B \gg r_{\pi}$, $A_{is} = -g_m r_{\pi} = -\beta$.


- output resistance $R_{out} = R_c \parallel r_o$

So the CE has large voltage and current gain, moderate R_i and large R_o (which is a bad thing for a voltage amp).

COMMON EMITTER WITH R_E (FIG. S.61)

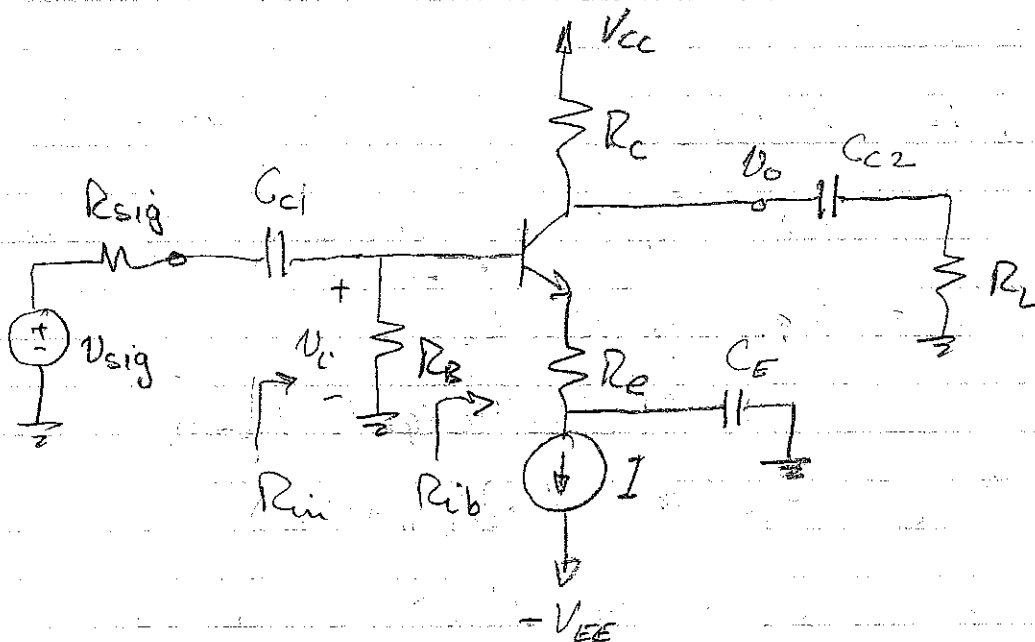

We use a T-Model here:

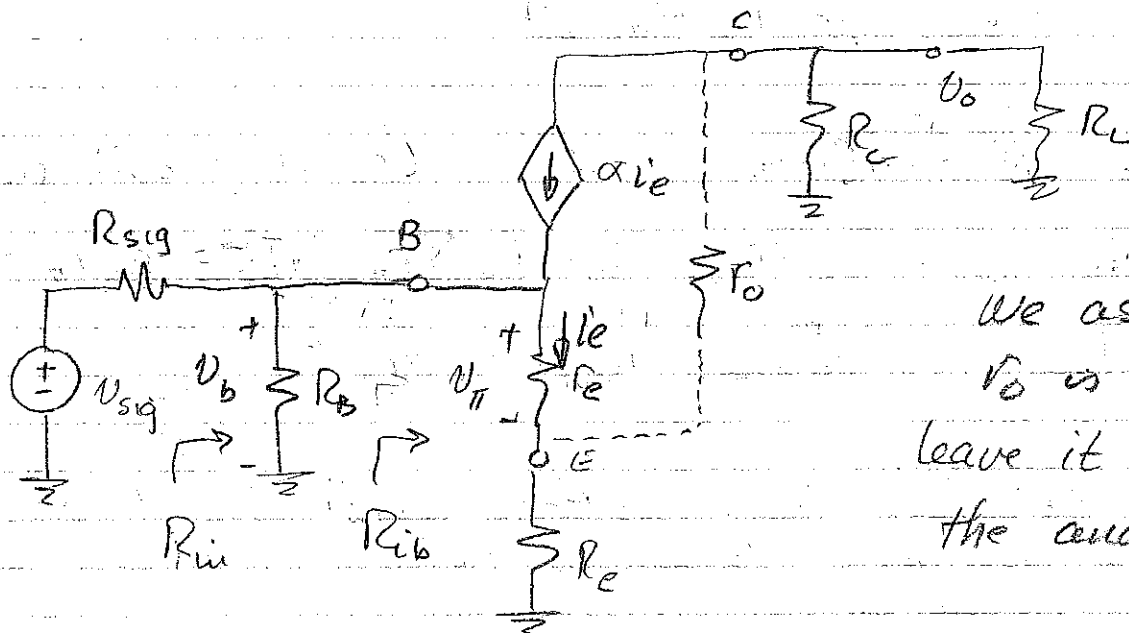

We assume r_o is large and leave it out of the analysis.

Analysis:

• Input resistance $R_{ib} = (\beta + 1)(r_e + R_e)$

Multiplication by $(\beta + 1)$: "resistance reflection rule".
This represents a large increase in R_i .


• Voltage gain

$$G_v \equiv \frac{V_o}{V_{sig}} = \frac{-\alpha I_e R_c / R_e}{\frac{I_e}{\beta + 1} R_s + I_e (r_e + R_e)} = \frac{-\beta R_c / R_e}{R_s + (\beta + 1)(r_e + R_e)}$$

Partial gain "base to collector":

$$\frac{V_o}{V_b} = \frac{-\alpha R_c}{r_e + R_e} \approx \frac{-R_c}{r_e + R_e} \quad (\text{if } R_c \rightarrow \infty)$$

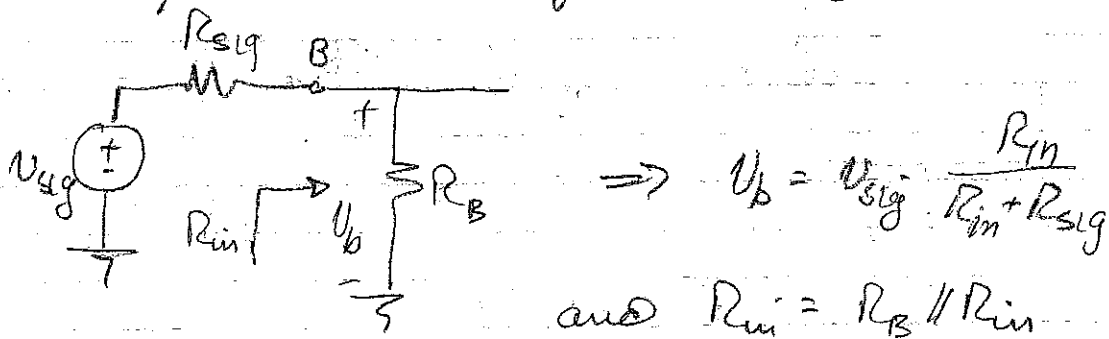Here's a trick: if we have R_{in} we can use it in a voltage divider to find V_b/V_s :



• Increased signal amplitude will not cause saturation:

$$\frac{V_{\pi}}{V_b} = \frac{r_e}{r_e + R_e} \approx \frac{1}{1 + g_m R_e}$$



so the base voltage, which was V_{π} in the

CE with no R_e , is now $v_{out} (1 + g_m R_e)$, which is considerably larger.


- output resistance $R_{out} = R_c$
- current gain $A_i = \frac{i_o}{i_b} = -\beta$

Summary: Voltage gain has been reduced, but is less sensitive to variations in β . However, reduced voltage gain has been traded for increased R_{ib} , increased input signal, and better hi f performance (later).

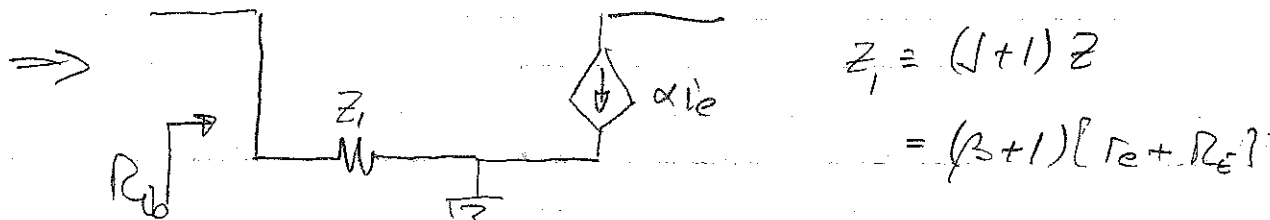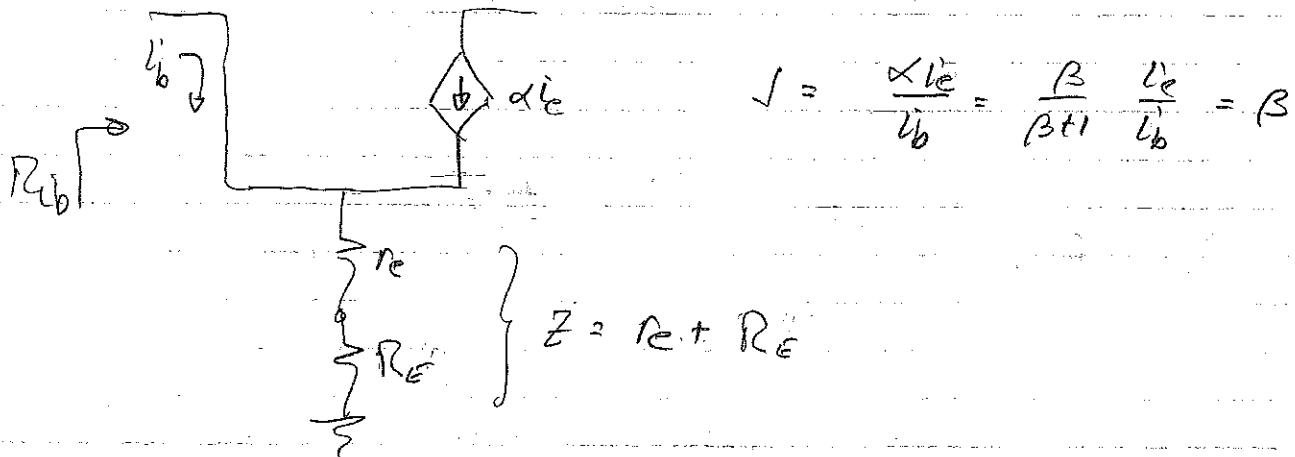
NOTE: The "resistance reflection rule" is nothing more than application of Miller's theorem:



COMMON BASE (FIG. 5.62)

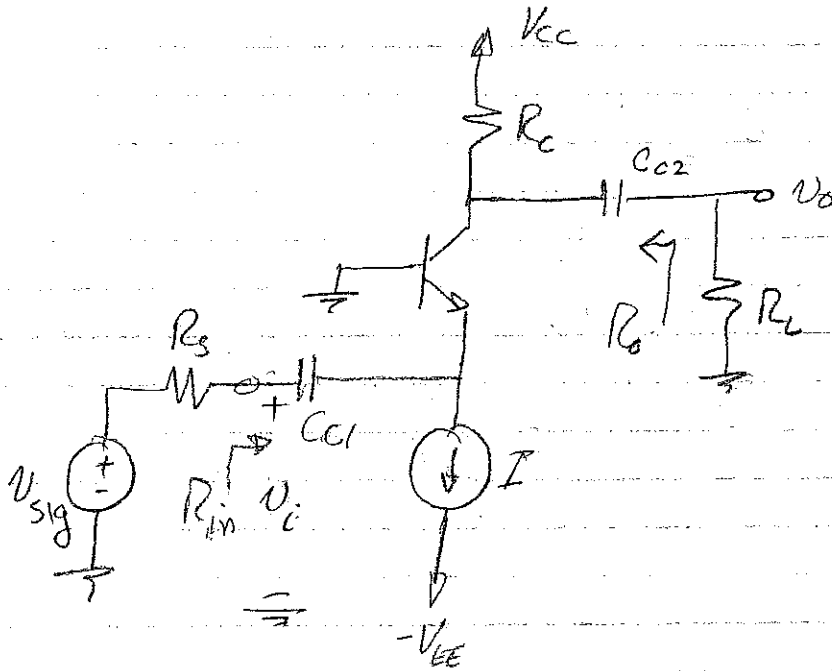

T-Model

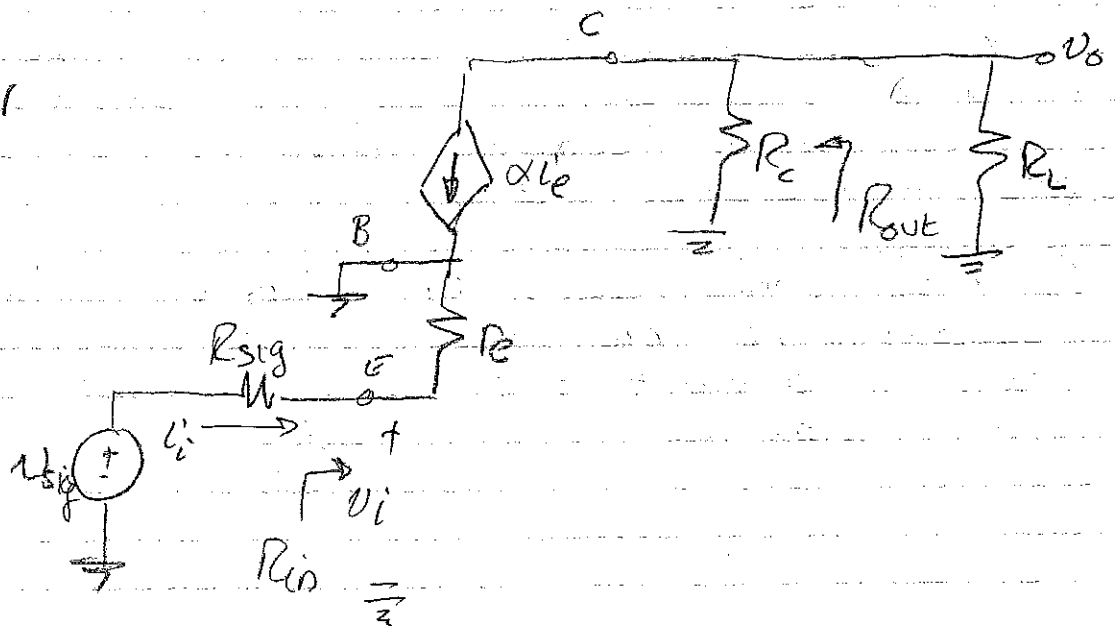

• Input resistance $R_{in} = r_e$

• Voltage gain is non-inverting.

$$A_v = \frac{V_o}{V_{sig}} = \frac{\alpha R_c}{R_{sig} + r_e}$$

Now, r_e is small, so A_v depends critically on R_{sig} .



• Current gain is small: $A_{is} = \frac{I_o}{I_i} = \alpha$

• Output impedance is $R_{out} = R_c$ (large)

So this is not a good voltage amp because R_i is small. However, it is a good unity-gain current amp because R_{out} is large. Also has good f response (later).

Current Buffer: The CB amp accepts a current at low input resistance and delivers almost the same output current to a high resistance load.

COMMON COLLECTOR (FIG. 5.63)

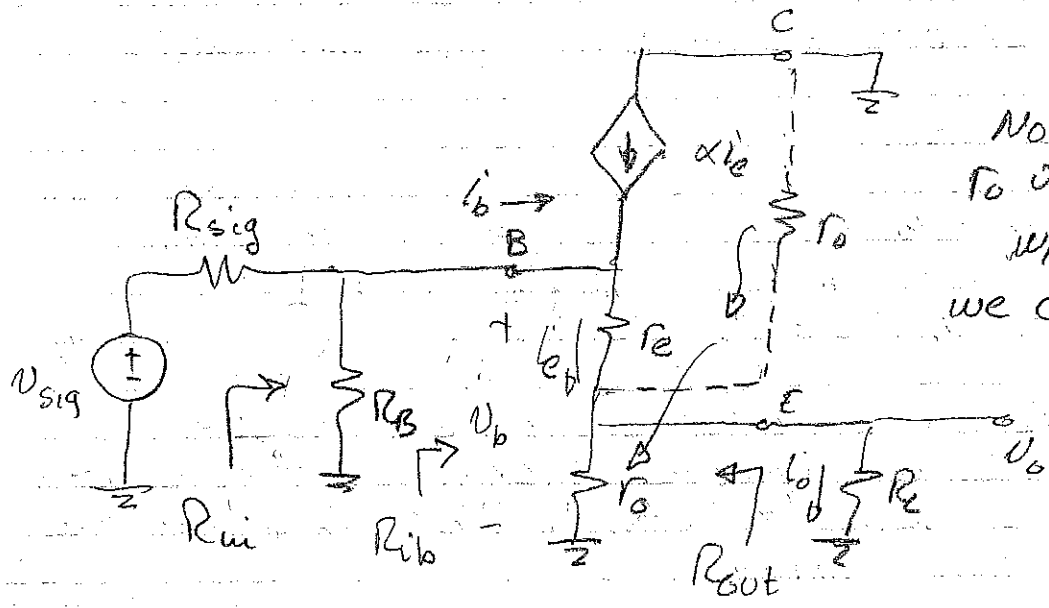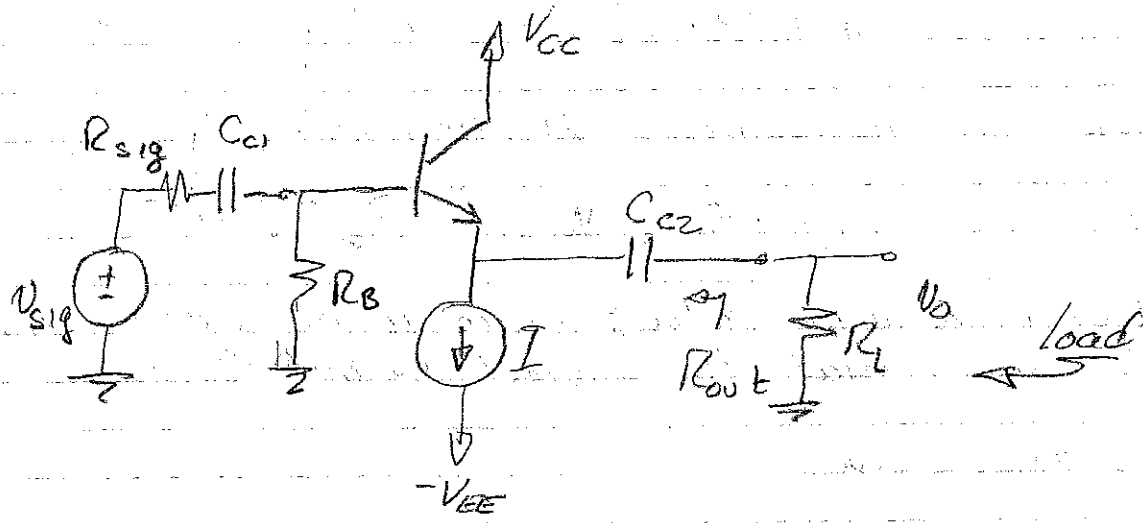

Note that r_o is in parallel w/ R_L , so we can move it.

This looks like the CE amplifier with $R_C = 0$ and $R_e \rightarrow r_o \parallel R_L$

so we can take some results from that case.

• Input resistance

$$R_{ib} = (\beta + 1) [r_e + r_o \parallel R_L]$$

$$\frac{V_o}{V_s} = \frac{V_b}{V_b} \frac{V_b}{V_s}$$

$$\frac{V_b}{V_s} = \frac{(\beta + 1)(r_e + r_o \parallel R_L)}{R_s + (\beta + 1)(r_e + r_o \parallel R_L)}$$

from the resistance reflection rule, $\frac{V_o}{V_b} = \frac{r_o \parallel R_L}{r_e + r_o \parallel R_L}$

If $r_e \ll R_L \ll r_o$, then $R_{ib} \approx (\beta + 1)R_L$

This is a large value; since it depends on R_L , it means that the signal is not "loaded" down.

• Voltage gain

$$G_v \equiv \frac{V_o}{V_{sig}} = \frac{(\beta + 1)(r_o \parallel R_L)}{R_{sig} + (\beta + 1)[r_e + r_o \parallel R_L]} = \frac{(r_o \parallel R_L)}{\frac{R_{sig}}{\beta + 1} + r_e + (r_o \parallel R_L)}$$

This is less than 1.

• Output resistance

↙ inverse resistance reflection

$$R_{out} = r_o \parallel \left[r_e + \frac{R_{sig}}{\beta + 1} \right]$$

This is r_o in parallel with r_e plus the source resistance reflected back into the emitter (inverse resistance-reflection). Note r_e , $R_s/(\beta + 1)$ are small, so R_o is small.

• Current gain

$$i_b = (1 - \alpha) i_e = \frac{i_e}{\beta + 1}$$

$$A_i \equiv \frac{i_o}{i_b} = (\beta + 1) \frac{r_o}{r_o + R_L}$$

So we have high R_i , low R_o , $A_v \approx 1$ and large current gain. We can connect a high resistance source to a low resistance load.

Emitter "follows" input at base → EMITTER FOLLOWER