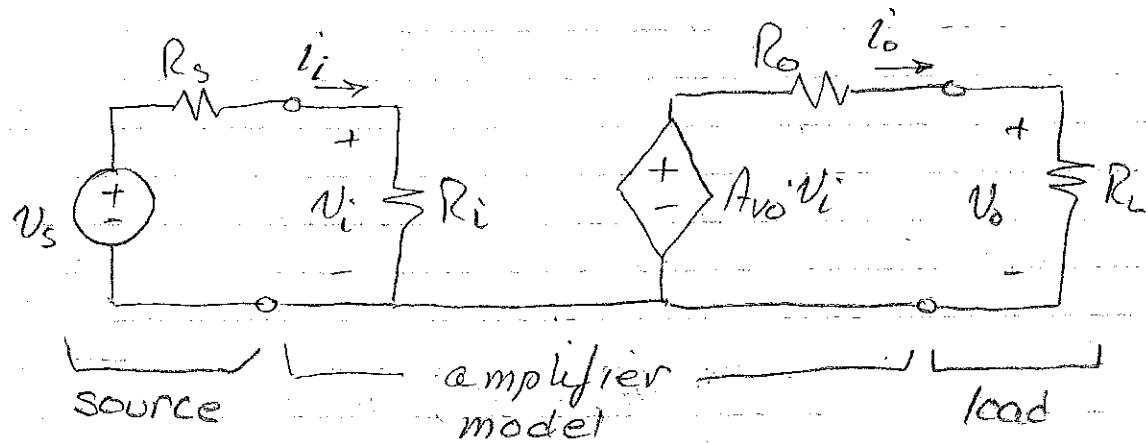


AMPLIFIER CIRCUIT MODELS

VOLTAGE AMPLIFIER

We can construct a circuit model for a voltage amplifier as follows. We have attached a Thevenin equivalent to represent the signal source (a transducer) as well as a resistance to represent a load.



The source is V_s but the voltage input to the amplifier is V_i :

$$V_i = V_s \frac{R_i}{R_i + R_s}$$

So we can define two voltage gains. To be clear, we'll give them different names:

$$A_{VS} = \frac{V_o}{V_s} \quad A_{Vi} = \frac{V_o}{V_i}$$

Analysis:

$$V_o = A_{vo} V_i \frac{R_L}{R_L + R_o}$$

$$\therefore A_{vi} = \frac{V_o}{V_i} = A_{vo} \frac{R_L}{R_L + R_o}$$

Also,

$$A_{vs} = \frac{V_o}{V_s} = A_{vo} \frac{R_L - R_i}{R_L + R_o R_i + R_s}$$

Now if $R_L = \infty$, i.e. the output is open-circuit, the gain $A_{vi} = A_{vo}$. So we call A_{vo} the OPEN-CIRCUIT VOLTAGE GAIN.

Looking at A_{vs} , we see that if we have

$$R_i \gg R_s \text{ and } R_o \ll R_L \Rightarrow A_{vs} \approx A_{vo}$$



If these conditions on R_i and R_o hold, then the amplifier is close to an "ideal" amplifier in the sense that

$$V_i \approx V_s \quad V_o \approx A_{vo} V_i,$$

that is, there is no loss of signal across R_s or R_o .

Bottom line: We want a voltage amplifier to have a high input impedance and a low output impedance. We will define these impedances more carefully later.

EXAMPLE

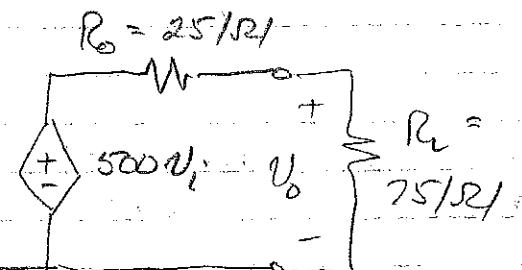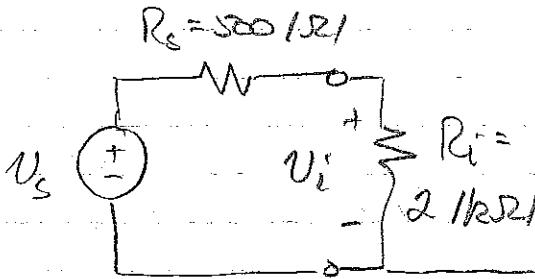

GIVEN: $U_s = 20\sqrt{2} \cos(\omega t + \phi) \text{ mV}$

FIND: A_{us}, A_{vi}, A_i, A_p

ANALYSIS:

$$V_o = 500 V_i \cdot \frac{R_L}{R_L + R_o} = 375 V_i$$

$$V_i = U_s \cdot \frac{R_i}{R_i + R_s} = 0.8 U_s$$

$$\text{so } A_{us} = \frac{V_o}{U_s} = 500 \cdot \frac{R_L}{R_L + R_o} \cdot \frac{R_i}{R_i + R_s} = 300 \text{ dB/V}$$

$$A_{vi} = \frac{V_o}{V_i} = 500 \cdot \frac{R_L}{R_L + R_o} = 375 \text{ dB/V}$$

$$A_i = \frac{V_o/R_L}{V_i/R_i} = A_{vi} \cdot \frac{R_i}{R_L} = 10^4 \text{ dB/VA}$$

$$A_p = A_{vi} A_i = 3.75 \times 10^6 \text{ dB/W}$$

dB?

$$A_{us} = 300 \text{ mV} = 49.5 \text{ dB}$$

$$A_{vi} = 375 \text{ mV} = 51.5 \text{ dB}$$

$$A_i = 10^4 \text{ VA} = 80.0 \text{ dB}$$

$$A_p = 3.75 \times 10^6 \text{ W} = 65.7 \text{ dB}$$

CASCADED AMPLIFIERS

SEDR A Ex 1.3

We can show that for two cascaded amplifiers, with gains A_{v1} and A_{v2} ,

$$A_v = A_{v1} \cdot A_{v2}$$

so the voltage gains multiply.

This example is from Hambley, 2nd ed.


Given: Amplifier 1: $A_{v1} = 10$ $R_i = 1\text{ k}\Omega$ $R_o = 100\text{ }\Omega$

Amplifier 2: $A_{v2} = 20$ $R_i = 2\text{ k}\Omega$ $R_o = 200\text{ }\Omega$

Amplifier 3: $A_{v3} = 30$ $R_i = 3\text{ k}\Omega$ $R_o = 300\text{ }\Omega$

Find: Parameters of "simplified" model, if amps are cascaded in the order 1, 2, 3.

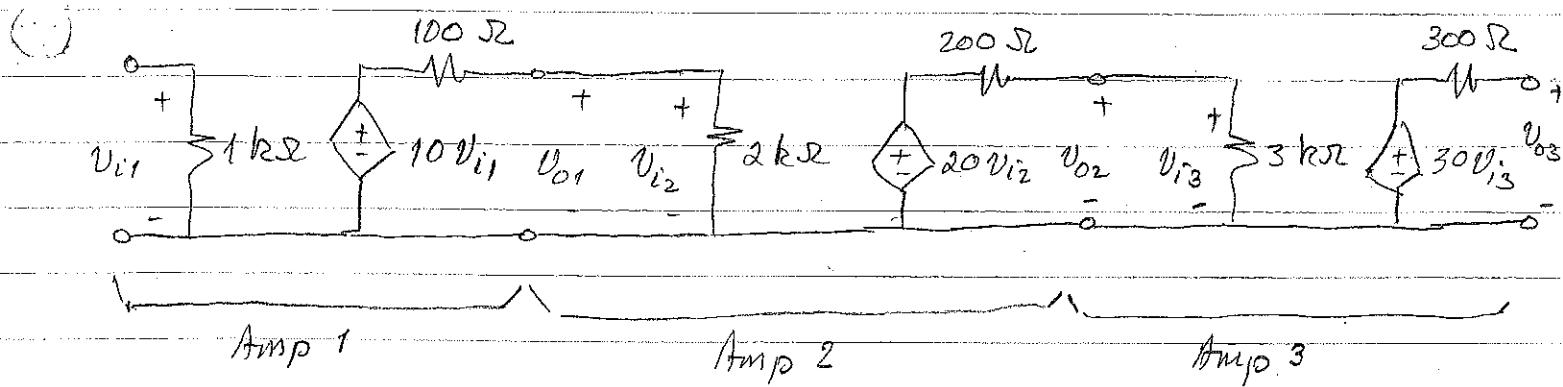Solution: The best approach here is to draw the cascaded amplifiers and see what's going on.



Analysis:

$$v_{o1} = v_{i2} = 10 v_{ii} \cdot \frac{2000}{2100}$$

$$v_{o2} = v_{i3} = 20 v_{i2} \cdot \frac{3000}{3200}$$


$$v_{o3} = 30 v_{i3}$$

$$\text{But then } v_{o3} = 30 \cdot 20 \cdot 10 v_{ii} \cdot \frac{3000}{3200} \cdot \frac{2000}{2100}$$

Or:

$$\frac{V_{o3}}{V_{i1}} = 5357.$$

So the overall effect is

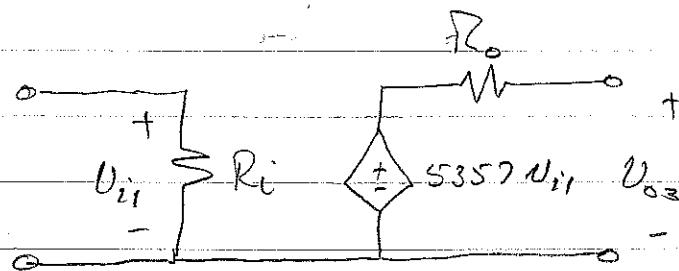

What about R_i , R_o ?


We will learn to calculate input/output impedance rigorously, but for now it should be clear that

$$R_i = 1 \text{ k}\Omega$$

$$R_o = 300 \text{ }\Omega$$

Analysis of Current Amplifier Model

Let's assume a current source as input:

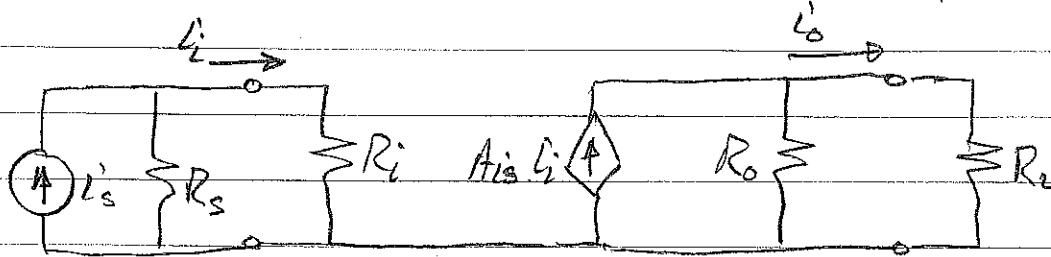

Then:

$$i_i = i_s \cdot \frac{R_s}{R_s + R_i}$$


$$i_o = A_i s \cdot i_i \cdot \frac{R_o}{R_o + R_L}$$

$$\Rightarrow \frac{i_o}{i_s} = A_i s \left(\frac{R_o}{R_o + R_L} \right) \left(\frac{R_s}{R_s + R_i} \right)$$

Re-write as $\frac{i_o}{i_s} = A_i s \cdot \frac{1}{1 + R_i/R_s} \cdot \frac{1}{1 + R_L/R_o}$

So i_o approaches $A_i s i_s$ if $R_o \gg R_L$ and $R_i \ll R_s$. These conditions for "ideality" are opposite those for the voltage amplifier.

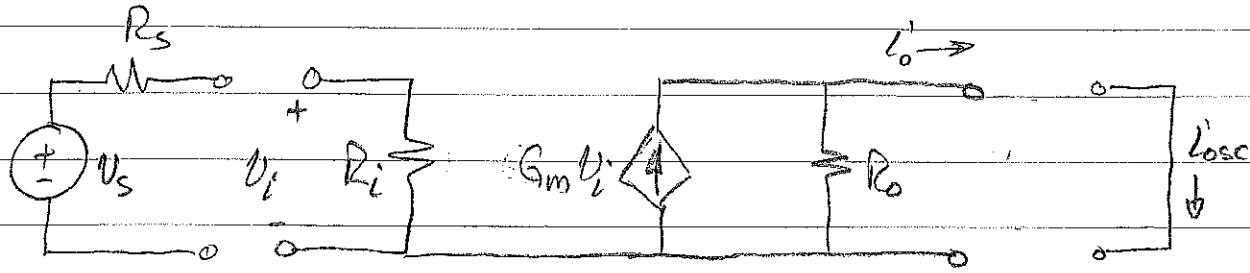
TRANSCONDUCTANCE AMPLIFIER is modeled using a voltage controlled current source:



Here, $I_o = G_m V_i$, hence we have

$$G_m = \frac{I_o}{V_i} \quad \text{UNITS: S (Siemens)}$$

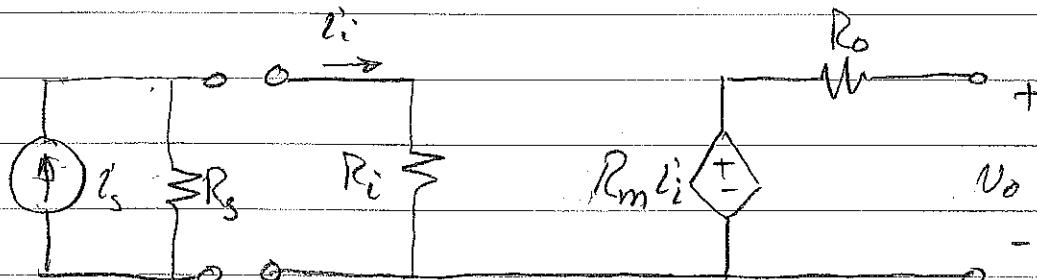
TRANSRESISTANCE AMPLIFIER is modeled using a current-controlled voltage source:




$$V_o = R_m I_i \Rightarrow R_m = \frac{V_o}{I_i}$$

UNITS: S2 (Ohms)

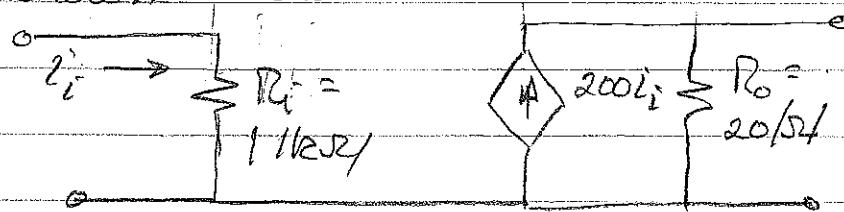EXAMPLE: Find the parameters of a voltage amplifier that has the same l_{osc} as the current amplifier shown below



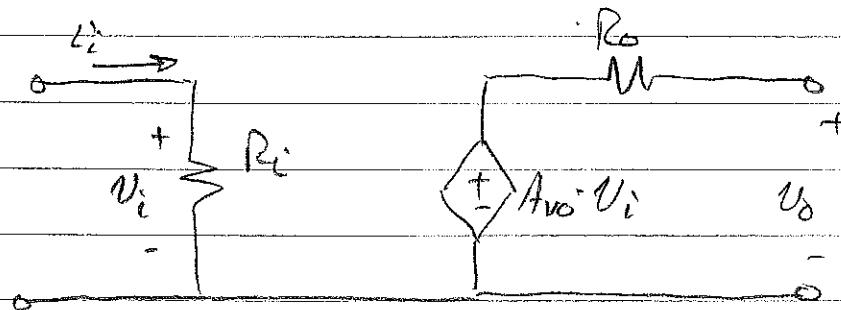Let's first draw what we are looking for:



$$l_{osc} = 200 i_i = 200 \frac{v_i}{R_i}$$

$$\text{But we also have } l_{osc} = \frac{Avo \cdot v_i}{R_o}$$

$$\text{So } \frac{Avo v_i}{R_o} = 200 \frac{v_i}{R_i} \Rightarrow Avo = 200 \frac{R_o}{R_i} = 4$$


Also, R_i and R_o stay the same so...

$$Avo = 4 \quad R_i = 1000 \Omega, \quad R_o = 20 \Omega$$

OTHER AMPLIFIER TYPES

We can model the amplification process in several different ways.

CURRENT AMPLIFIER

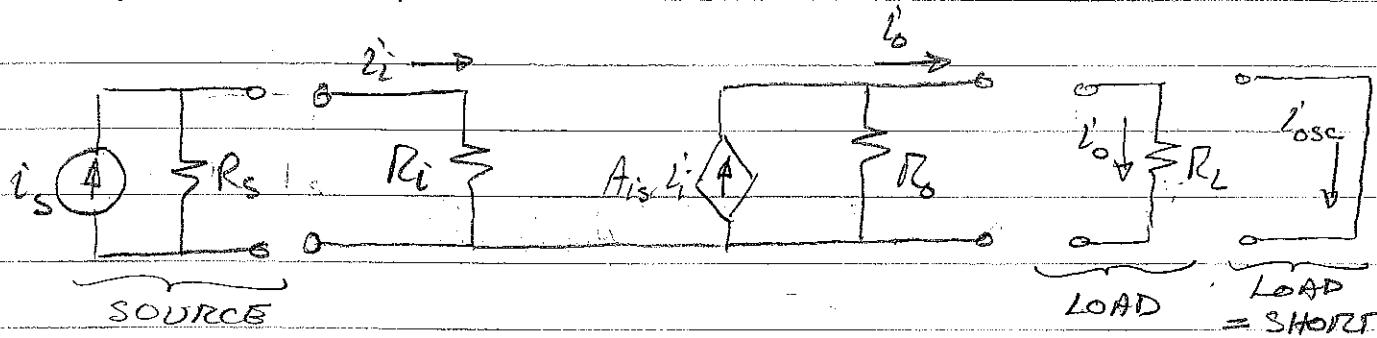

For the current amplifier we use a current-controlled current source:

- controlling current = input current i_i
- gain is specified by short-circuit output current A_{iS}


So if the output \rightarrow short, $i_o = i_{osc}$ and $A_i = A_{iS}$.

$$\text{Thus, } A_{iS} \equiv \frac{i_{osc}}{i_i}$$

so A_{iS} is the SHORT CIRCUIT CURRENT GAIN

Source Transformation Viewpoint

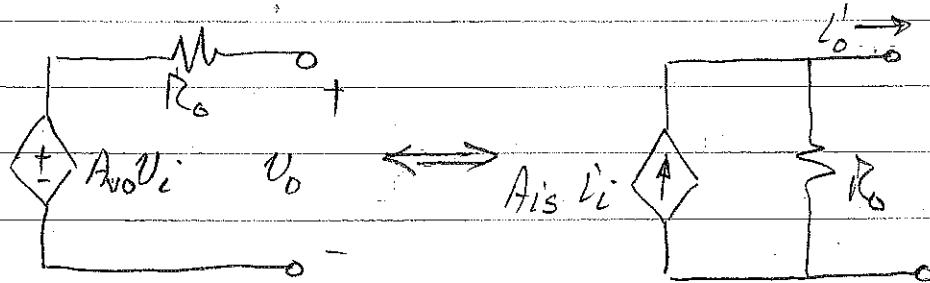We can obtain a current amplifier model from a voltage amplifier model (or vice-versa) using source transformation:



$$So \quad R_o \longleftrightarrow R_o$$

$$\frac{A_{vo}V_i}{R_o} = I_{osc} = A_{Is}I_i$$

$$\text{But } I_i = V_i/R_i, \text{ so } A_{Is} = \underline{\underline{A_{vo} \frac{R_i}{R_o}}}$$

INPUT/OUTPUT RESISTANCE

Definitions:

Input Resistance is the Thvenin equivalent resistance seen at the input terminals of the amp, with a load connected at the output.

Output Resistance is the Thvenin equivalent resistance seen at the output terminals of the amp, with a source connected at the input.

For IDEAL amplifier models, Table 1.1 gives values of R_i , R_o .

Amplifier Type	R_i	R_o	Gain
voltage	∞	0	A_{vo}
current	0	∞	A_{ic}
transconductance	∞	∞	G_{me}
transresistance	0	0	R_{me}