
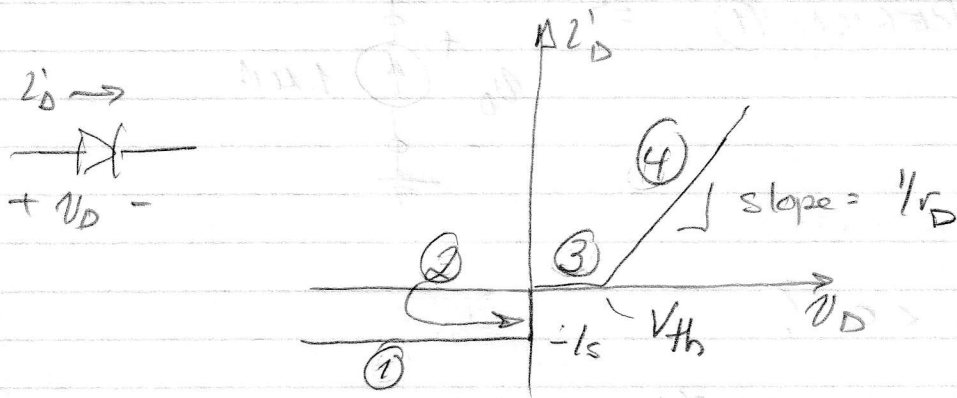


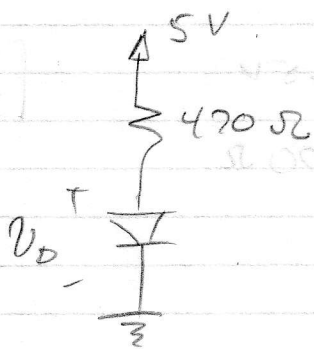Examples: Full piece-wise linear model:-

$$I_s = 10^{-6} \text{ A} \quad r_D = 50 \text{ } \Omega \quad V_{th} = 0.7 \text{ V}$$




The following examples cover all four regions labelled on the plot.




GUESS:

REGION ④ \Rightarrow

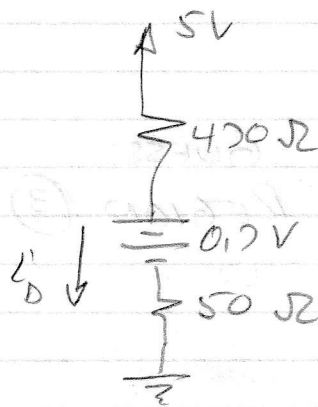


TEST: $I_D' \geq 0$?
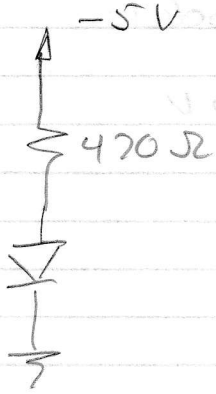
$$I_D' = \frac{5 - 0.7}{520} = 8.3 \text{ mA} \quad \checkmark \quad \text{OK.}$$




GUESS:
REGION (1) \Rightarrow

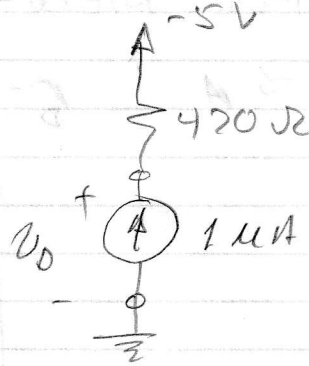


TEST: $V_D < 0$?

$$\text{KVL: } 5 - 470(10^{-6}) + V_D = 0$$
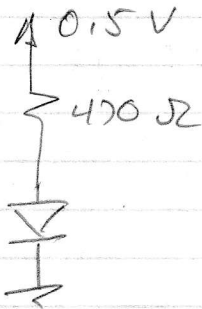
$$V_D \approx -5 \text{ V} \quad \checkmark \quad \text{OK}$$




GUESS:
REGION (3) \Rightarrow

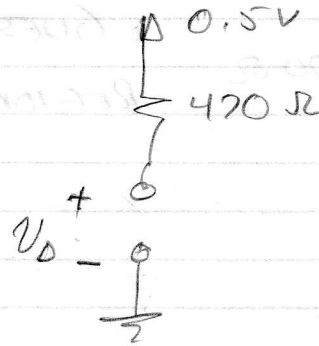


The power supply (0.5V) is positive but not sufficient to turn the device on, so we guess region (3).

TEST: $0 \leq V_D \leq 0.7 \text{ V}$?
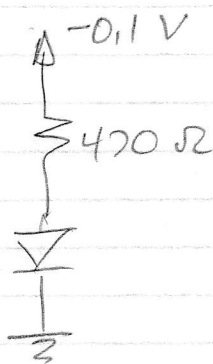
$$V_D = 0.5 \text{ V} \quad \checkmark \quad \text{OK.}$$



GUESS:
REGION ①

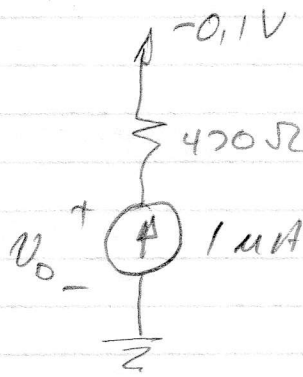


TEST: $V_D \leq 0$?


$$+0.1 - 470(10^{-6}) + V_D = 0$$

$$V_D \approx -0.1 \text{ V} \quad \checkmark \quad \text{OK}$$

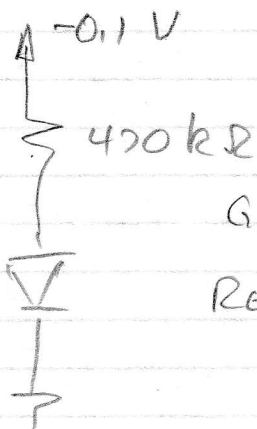If the resistor is large, we might find the diode in region 2:




GUESS:
REGION ②

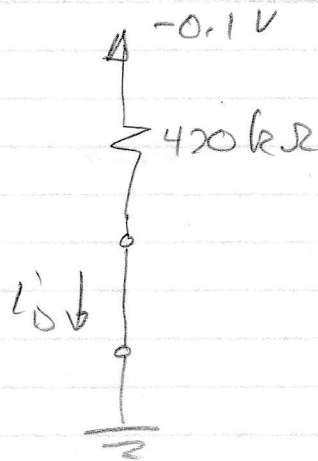

TEST: $0 \geq I_D \geq -1.0 \times 10^{-6} \text{ A}$?

$$I_D = \frac{-0.1}{470 \text{ k}} = -0.213 \text{ mA} \quad \checkmark \quad \text{OK.}$$

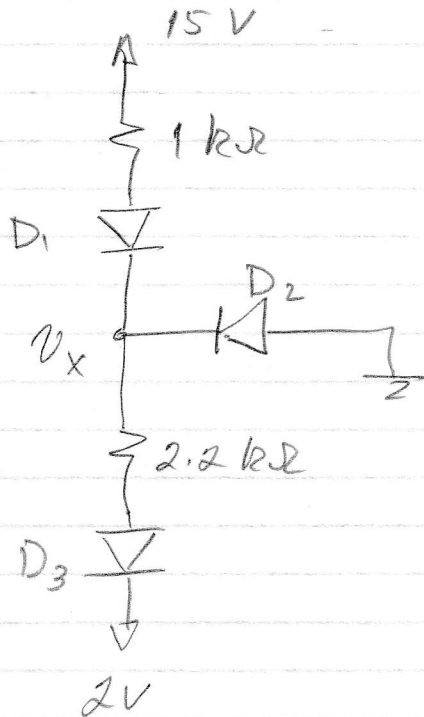Example: $I_s = 100 \mu A$ $r = 50 \Omega$ $V_{th} = 0.7 V$



It would appear that $D_1 \rightarrow ON$

If V_x is more than 2.7V, D_3 will be ON, and D_2 will be OFF.

Let's try that...

$$0 = \frac{V_x - 15 + 0.7}{1050} + \frac{V_x - 2 - 0.7}{2250} + 10^{-4}$$


$$\Rightarrow V_x = 10.54 V$$

$$I_{D1}' = \frac{15 - V_x - 0.7}{1050} = 3.58 \text{ mA} \quad \checkmark$$

$$I_{D2}' = \frac{V_x - 2 - 0.7}{2250} = 3.48 \text{ mA} \quad \checkmark$$

$$-V_{D3} = 2250 I_{D2}' + 0.7$$

$$V_{D3} = -8.53 V \quad \checkmark$$

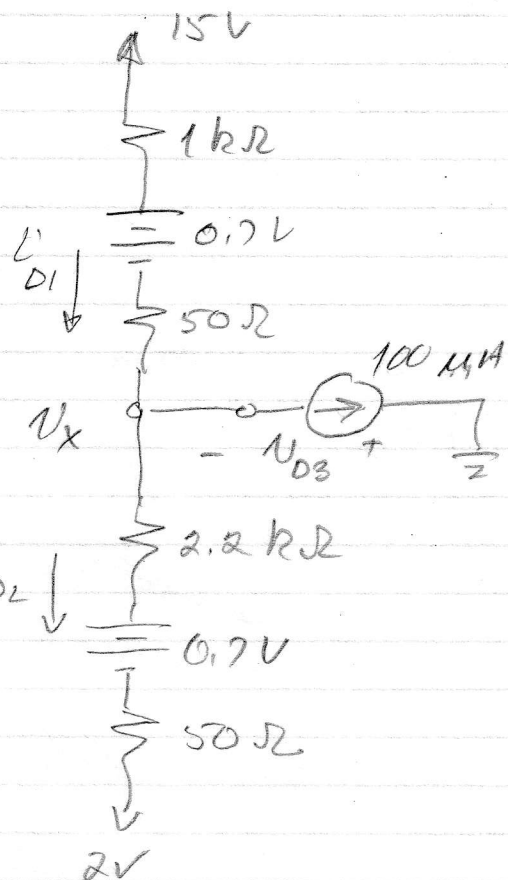


GOOD ASSUMPTION!

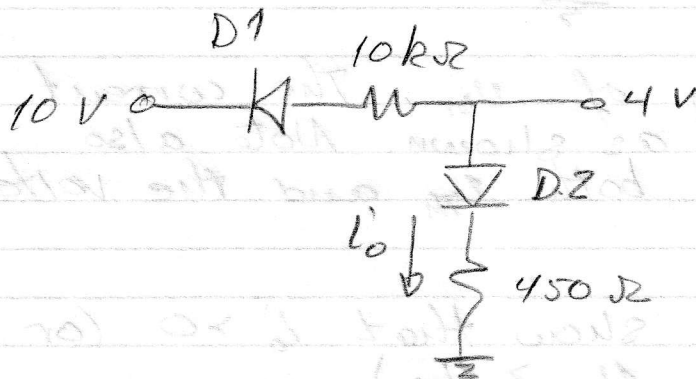Example using Piece-wise Linear model (based on Quiz 3 Spring 2000)

Use the linear piece-wised diode model with $V_{Th} = 0.6\text{ V}$, $r = 50\ \Omega$, and $I_S = 1\text{ mA}$ to I_0 in the circuit below.


For each of the diodes, be sure to prove that the diode is operating in the state you assume.



Because of the +4V source, we will guess that D2 is ON, and in the forward bias ($V_D > V_{Th}$) region.

Because the 10V source is in a position to put D1 in reverse bias, we will assume it is OFF, with $V_D < 0$.

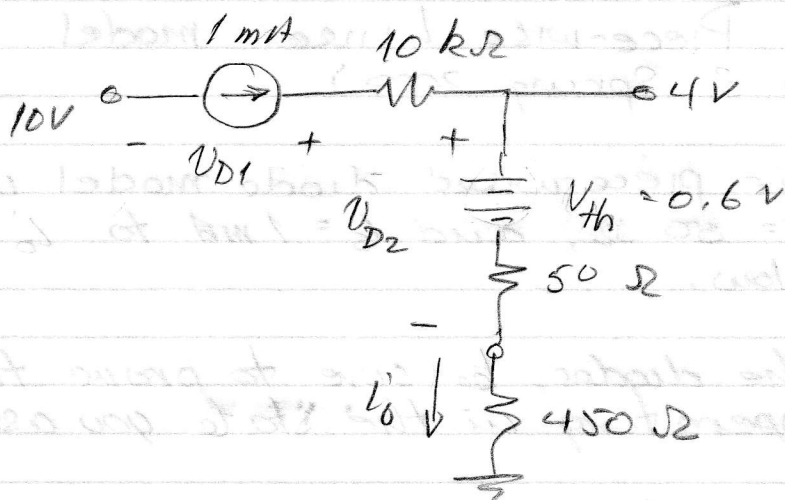Re-drawing with appropriate diode models, we have ...



NOTE the polarity of V_{D1} . The current source is positive as shown. Note also that V_{D2} includes both V_{th} and the voltage across r .

TEST we need to show that $I_o > 0$ (or equivalently that $V_{D2} > V_{th}$).

$$I_o = \frac{4 - 0.6}{500} = 6.8 \text{ mA} \quad \checkmark$$

So this is OK

TEST we need to show that V_{D1} is negative.

$$\text{KVL} \quad -10 - V_{D1} + 10^{-3}(10000) + 4 = 0$$

$$\therefore V_{D1} = -6 + 10 = +4 \text{ V} \quad \text{X}$$


No Good! This is a contradiction since $V_{D1} = 4 \text{ V}$ suggests forward bias. So we need another guess.

So now what? It seems clear that D_1 cannot be forward biased (because of the 10V source) so we have two possibilities:

$$i_{D_1}' = 0 \quad 0 \leq v_{D_1} \leq V_{th} \quad (\text{region 3})$$

$$\text{OR} \quad -I_s \leq i_{D_1}' \leq 0 \quad v_{D_1} = 0 \quad (\text{region 2})$$

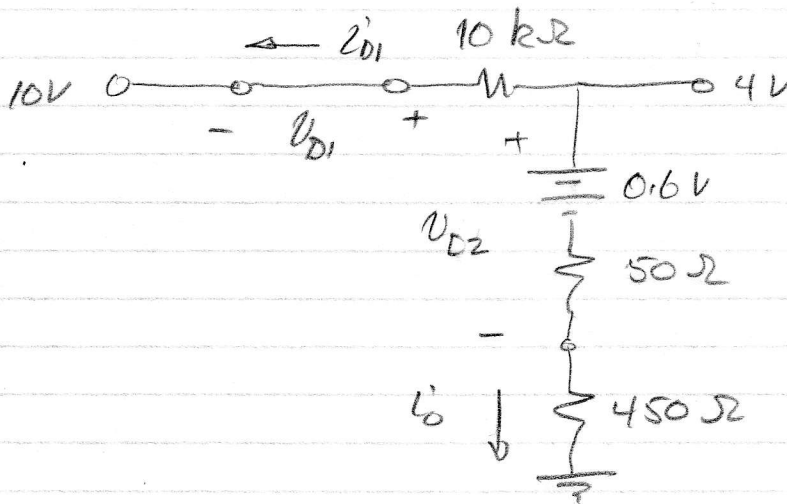Let's choose region 2 (it looks easier to test!):



Note that i_o has not changed, so we don't need to fuss with D_2 . Now

$$i_{D_1}' = \frac{4 - 10}{10k} = -0.6 \text{ mA}$$

So this is GOOD! we have

$$v_{D_1} = 0 \quad -1 \text{ mA} \leq i_{D_1}' \leq 0$$

which is region 2.