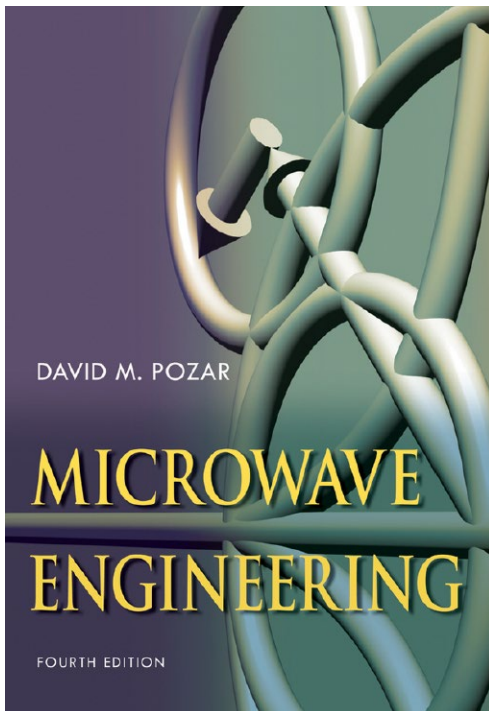


ECE 5317-6351

Microwave Engineering


Fall 2019

Prof. David R. Jackson
Dept. of ECE



Notes 16

Network Analysis

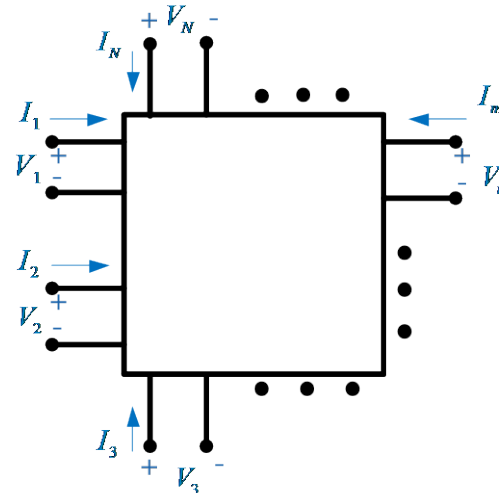


Multiport Networks

A general circuit can be represented by a multi-port network, where the “ports” are defined as access terminals at which we can define voltages and currents.


Note:
Equal and opposite currents are assumed on the two wires of a port.

Examples:

1) One-port network

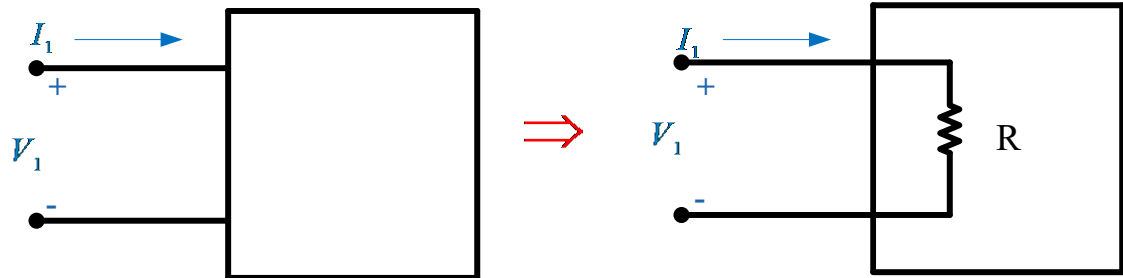


2) Two-port network

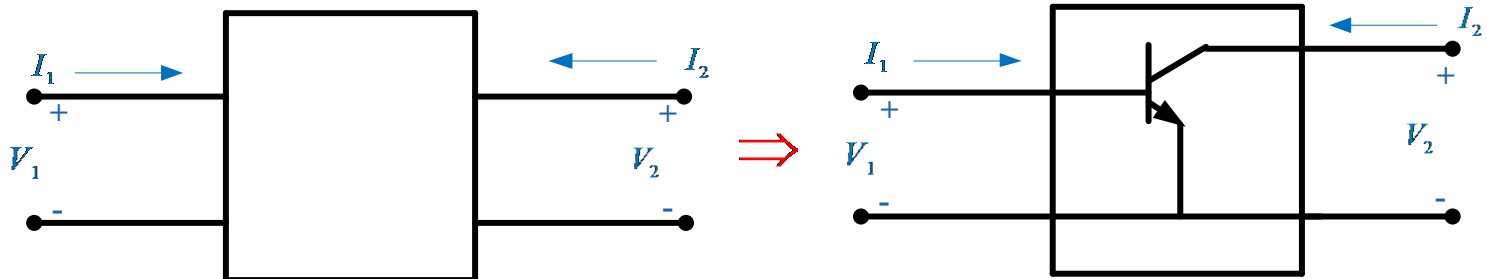

Multiport Networks (cont.)


3) N -port network

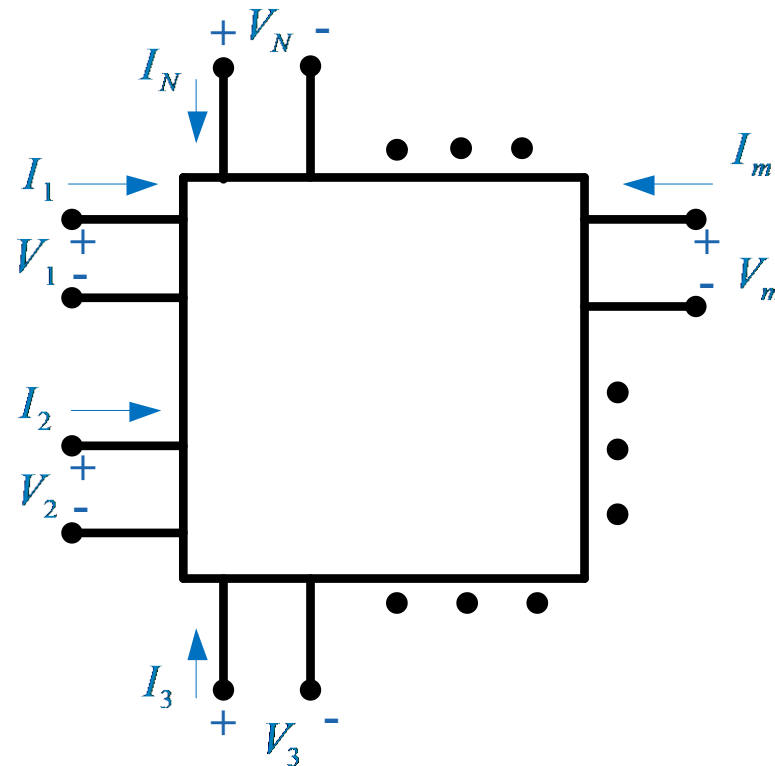

Note: Passive sign convention is used at the ports.

Multiport Networks (cont.)

N -port network

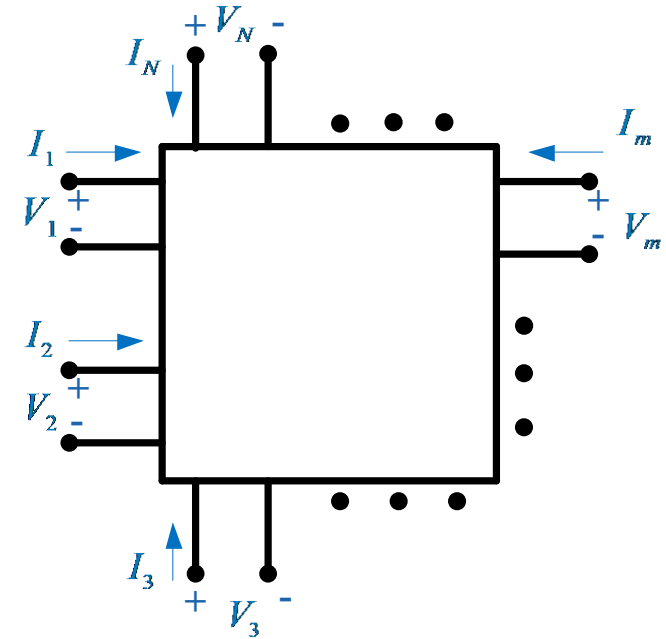


To represent multi-port networks we use:

- Z (impedance) parameters
 - Y (admittance) parameters
 - $ABCD$ parameters
- Not easily measurable at high frequency
- S (scattering) parameters
- Measurable at high frequency

Two-Port Networks

Consider a 2-port linear network:

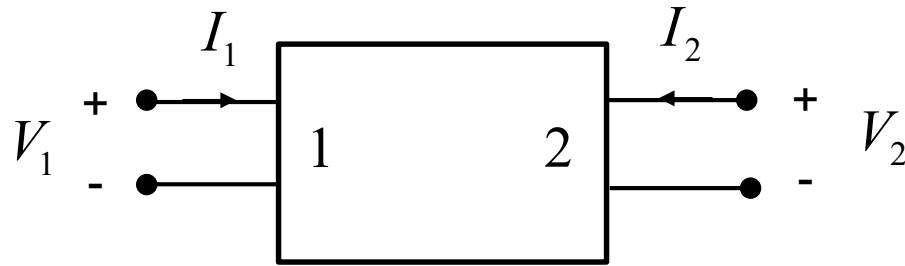

In terms of Z-parameters, we have (from superposition):

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Impedance (Z) matrix

Therefore

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \Rightarrow [V] = [Z][I]$$

Elements of Z-Matrix: Z-Parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Port 2 open circuited

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$


$$Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_k=0 \quad k \neq j}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

Port 1 open circuited

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$


$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

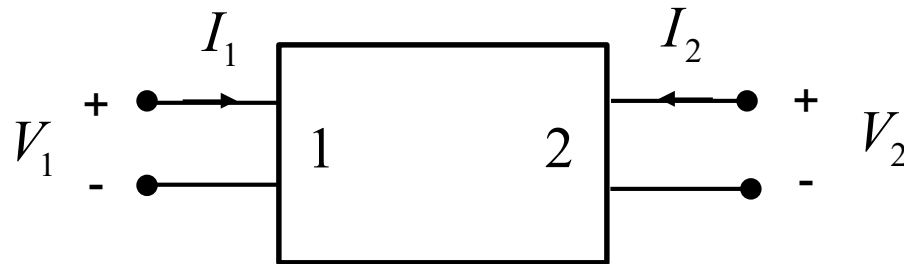

Z-Parameters (cont.)

N-port network

$$Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_k=0 \quad k \neq j}$$

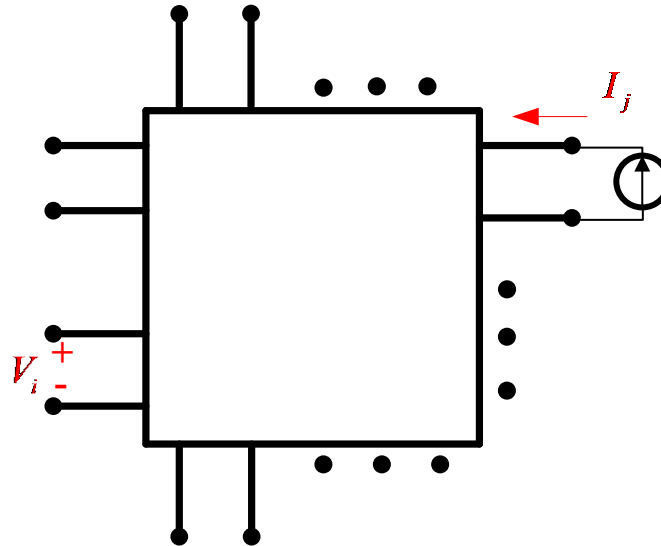



We inject a current into port *j* and measure the voltage (with an ideal voltmeter) at port *i*. All ports are open-circuited except *j*.

Summary of Z Parameters

Summary of Z Parameters


$$[V] = [Z][I]$$

$$Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_k=0 \quad k \neq j}$$

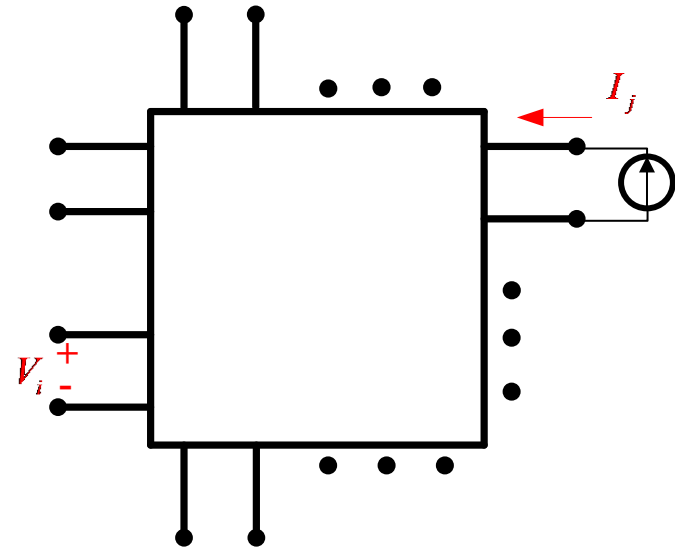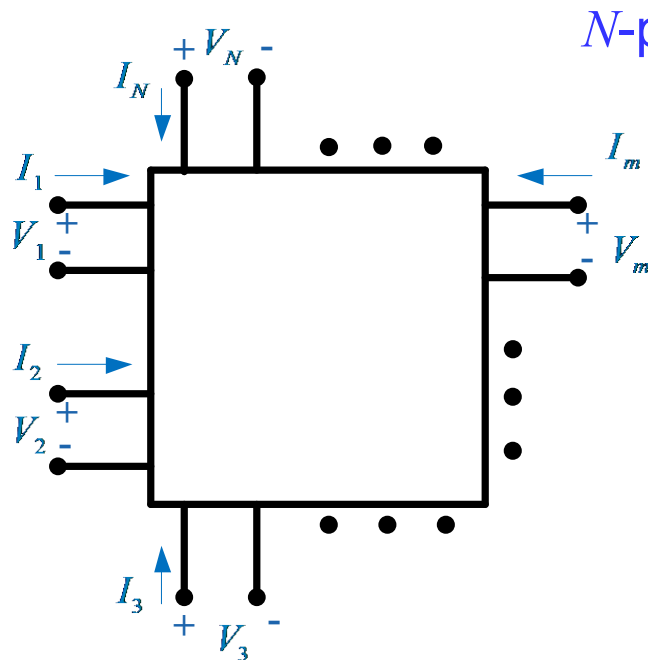

Admittance (Y) Parameters

Consider a 2-port linear network:

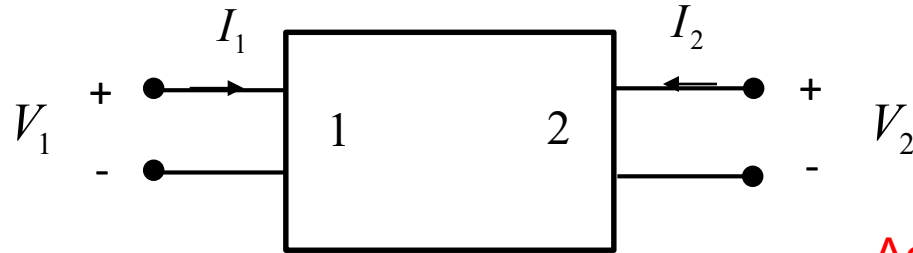

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Admittance matrix

or

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow [I] = [Y][V]$$


$$Y_{ij} = \frac{I_i}{V_j} \Big|_{V_k=0 \quad k \neq j}$$

Y-Parameters (cont.)

N-port network

$$[I] = [Y][V]$$

$$Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_k=0 \quad k \neq j}$$

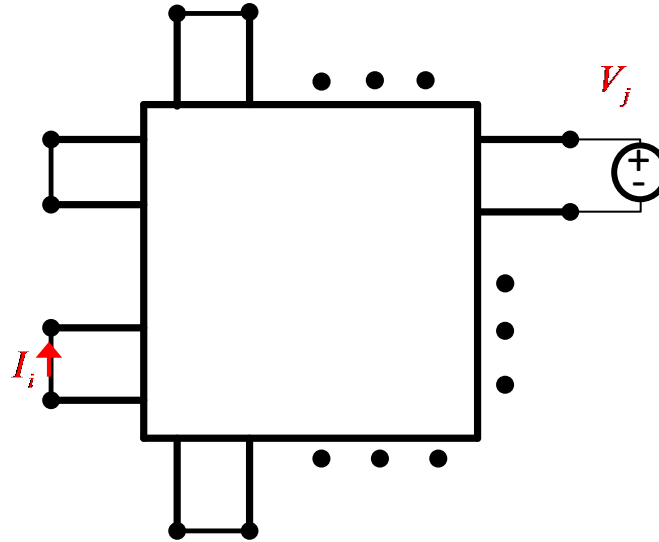

We apply a voltage across port j and measure the current (with an ideal current meter) at port i . All ports are short-circuited except j .



Summary of Y Parameters

Summary of Y Parameters

$$[I] = [Y][V]$$

$$Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_k=0 \quad k \neq j}$$

N -port network

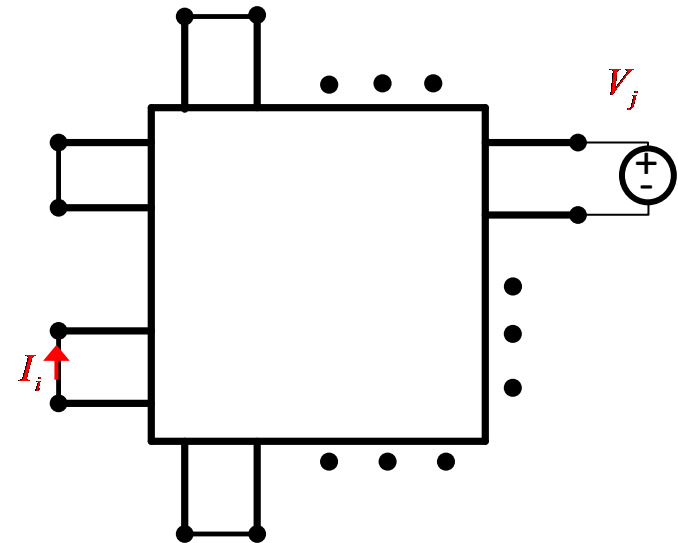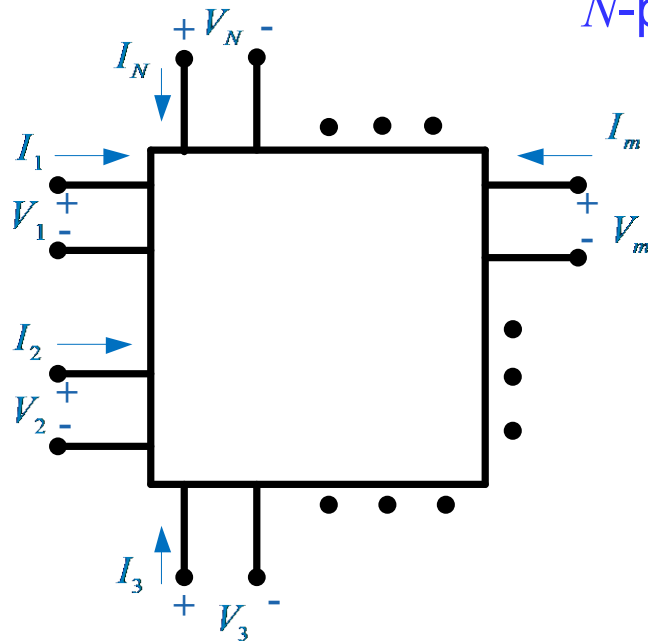

Relation Between Z and Y Parameters

Relation between $[Z]$ and $[Y]$ matrices:

$$[V] = [Z][I]$$

$$[I] = [Y][V]$$

Hence:

$$\begin{aligned} [V] &= [Z]([Y][V]) \\ &= ([Z][Y])[V] \end{aligned}$$

It follows that

$$[Z][Y] = [U] = \text{Identity Matrix}$$

Therefore $[Y] = [Z]^{-1}$

Reciprocal Networks

If a network does not contain non-reciprocal devices or materials* (i.e. ferrites, or active devices), then the network is “reciprocal”, which means that the Z and Y matrices are symmetric.

$$\Rightarrow Z_{ij} = Z_{ji} \quad (Y_{ij} = Y_{ji})$$

$\Rightarrow [Z]$ and $[Y]$ are symmetric matrices
(proof omitted)

Note:

The inverse of a symmetric matrix is symmetric.

* A reciprocal material is one that has symmetric permittivity and permeability matrices. A reciprocal device is one that is made from reciprocal materials.

Example of a nonreciprocal material: a biased ferrite
(This is very useful for making isolators and circulators.)

Reciprocal Materials

$$\underline{D} = \underline{\underline{\epsilon}} \cdot \underline{E} \quad \underline{B} = \underline{\underline{\mu}} \cdot \underline{H}$$

$$\begin{bmatrix} D_x \\ D_y \\ D_z \end{bmatrix} = \begin{bmatrix} \epsilon_{xx} & \epsilon_{xy} & \epsilon_{xz} \\ \epsilon_{yx} & \epsilon_{yy} & \epsilon_{yz} \\ \epsilon_{zx} & \epsilon_{zy} & \epsilon_{zz} \end{bmatrix} \begin{bmatrix} E_x \\ E_y \\ E_z \end{bmatrix} \quad \begin{bmatrix} B_x \\ B_y \\ B_z \end{bmatrix} = \begin{bmatrix} \mu_{xx} & \mu_{xy} & \mu_{xz} \\ \mu_{yx} & \mu_{yy} & \mu_{yz} \\ \mu_{zx} & \mu_{zy} & \mu_{zz} \end{bmatrix} \begin{bmatrix} H_x \\ H_y \\ H_z \end{bmatrix}$$

Reciprocal: $\epsilon_{ij} = \epsilon_{ji}, \mu_{ij} = \mu_{ji}$


Ferrite: $\underline{\underline{\mu}} = \mu_0 \begin{bmatrix} \alpha & j\gamma & 0 \\ -j\gamma & \alpha & 0 \\ 0 & 0 & 1 \end{bmatrix}$ $\underline{\underline{\mu}}$ is not symmetric!
(not a reciprocal material)

Reciprocal Networks (cont.)

We can show that the equivalent circuits for reciprocal 2-port networks are:


T-equivalent

“T network”

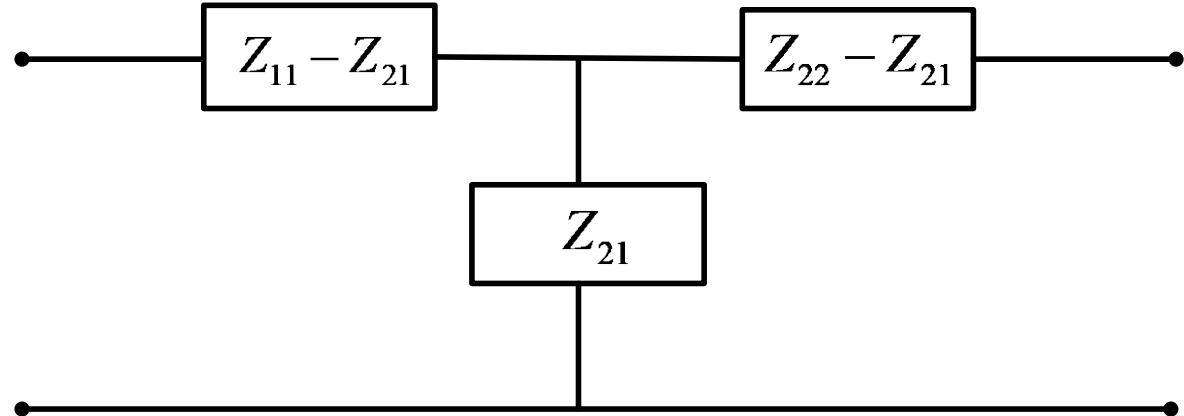

Pi-equivalent


“Π network”

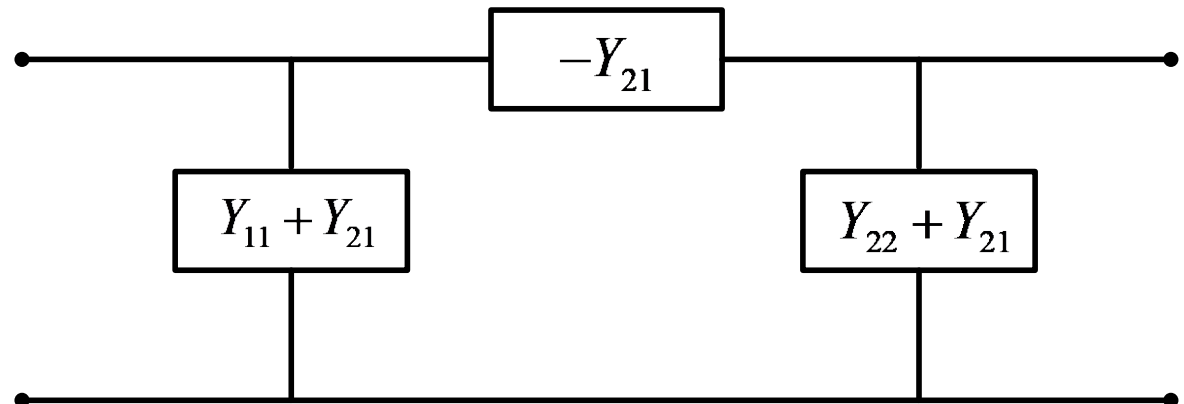

ABCD-Parameters

There are defined only for 2-port networks.
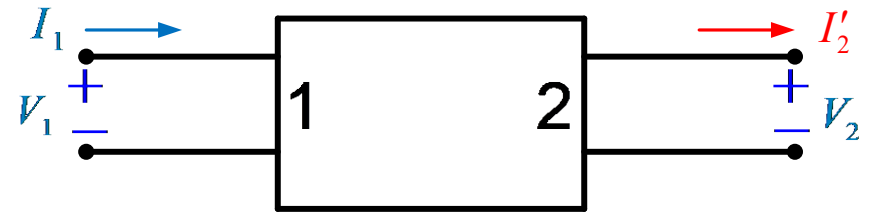
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I'_2 \end{bmatrix}$$



$$I'_2 = -I_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I'_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I'_2=0}$$


$$B = \left. \frac{V_1}{I'_2} \right|_{V_2=0}$$

$$D = \left. \frac{I_1}{I'_2} \right|_{V_2=0}$$

Cascaded Networks

Port 1

Port 2

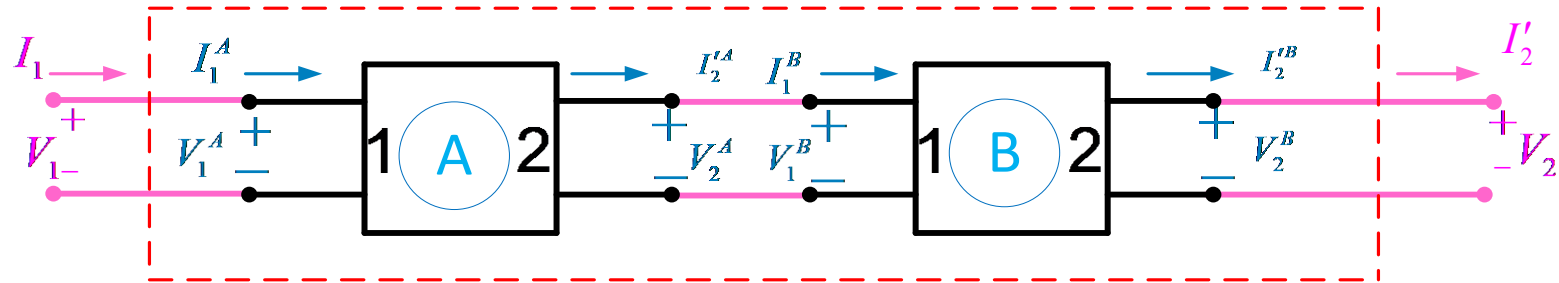

$$\begin{aligned} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} &= \begin{bmatrix} V_1^A \\ I_1^A \end{bmatrix} = [ABCD^A] \begin{bmatrix} V_2^A \\ I_2^A \end{bmatrix} \\ &= [ABCD^A] \begin{bmatrix} V_1^B \\ I_1^B \end{bmatrix} \\ &= [ABCD^A] [ABCD^B] \begin{bmatrix} V_2^B \\ I_2^B \end{bmatrix} \end{aligned}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = [ABCD^{AB}] \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

A nice property of the ABCD matrix is that it is easy to use with cascaded networks: you simply multiply the ABCD matrices together.


Scattering Parameters

- At high frequencies, Z , Y , and $ABCD$ parameters are difficult (if not impossible) to measure.
 - V and I are not always uniquely defined (e.g., microstrip, waveguides).
 - Even if defined, V and I are extremely difficult to measure (particularly I).
 - Required open and short-circuit conditions are often difficult to achieve.
- Scattering (S) parameters are often the best representation for multi-port networks at high frequency.

Note: We can always convert from S parameters to Z , Y , or $ABCD$ parameters.

Scattering Parameters (cont.)

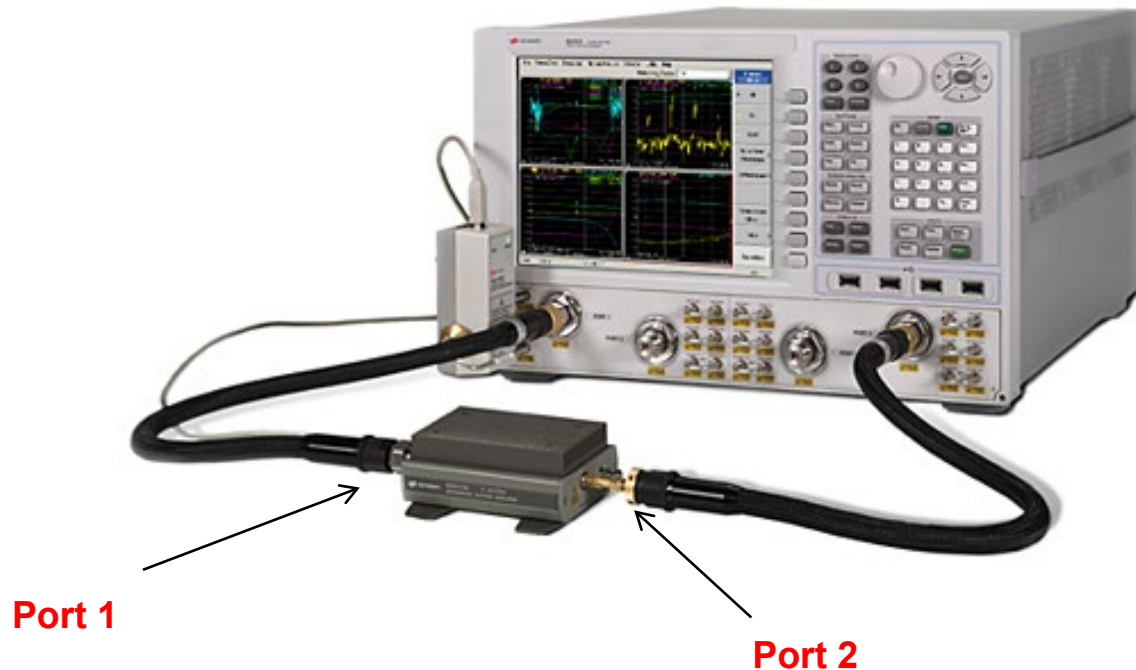
A Vector Network Analyzer (VNA) is usually used to measure S parameters.



Keysight (formerly Agilent) VNA shown performing a measurement.


Scattering Parameters (cont.)

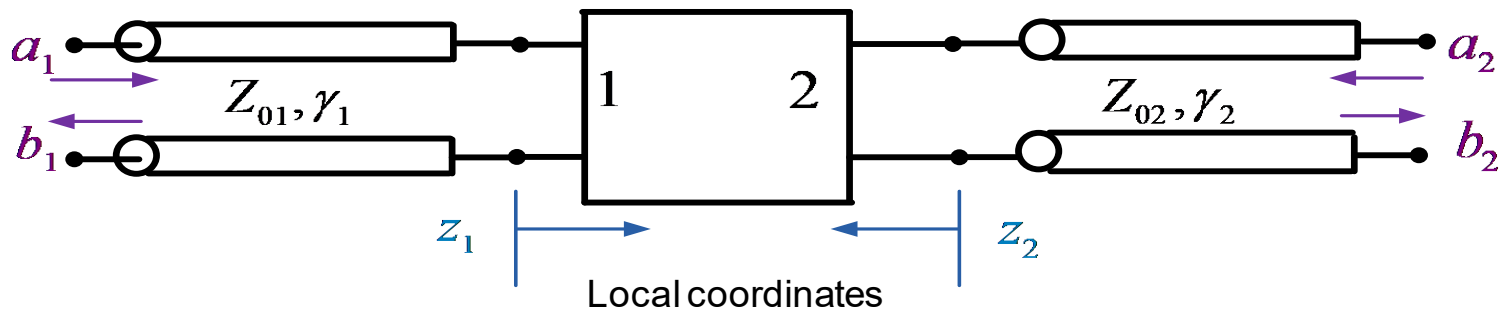For scattering parameters, we think in terms of incident and reflected waves on transmission lines connected to a device.



- The a coefficients represent incident waves.
- The b coefficients represent reflected waves.

Scattering Parameters (cont.)

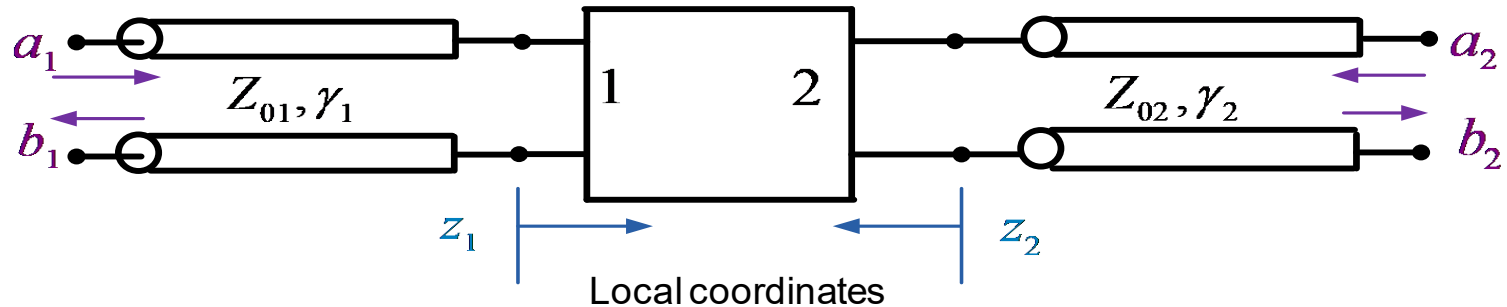

On each transmission line:

$$V_i(z_i) = V_{i0}^+ e^{-\gamma_i z_i} + V_{i0}^- e^{+\gamma_i z_i} = V_i^+(z_i) + V_i^-(z_i)$$

$$I_i(z_i) = \frac{V_i^+(z_i)}{Z_{0i}} - \frac{V_i^-(z_i)}{Z_{0i}} \quad i = 1, 2$$

We define normalized voltage wave functions:

Incoming wave function $\equiv a_i(z_i) \equiv V_i^+(z_i) / \sqrt{Z_{0i}}$

Outgoing wave function $\equiv b_i(z_i) \equiv V_i^-(z_i) / \sqrt{Z_{0i}}$


Scattering Parameters (cont.)

Why are the wave functions (a and b) defined as they are?

- ❖ The normalization makes power calculation easy (see next slide).
- ❖ The $[S]$ matrix is unitary (discussed later).

Scattering Parameters (cont.)

Power Calculations

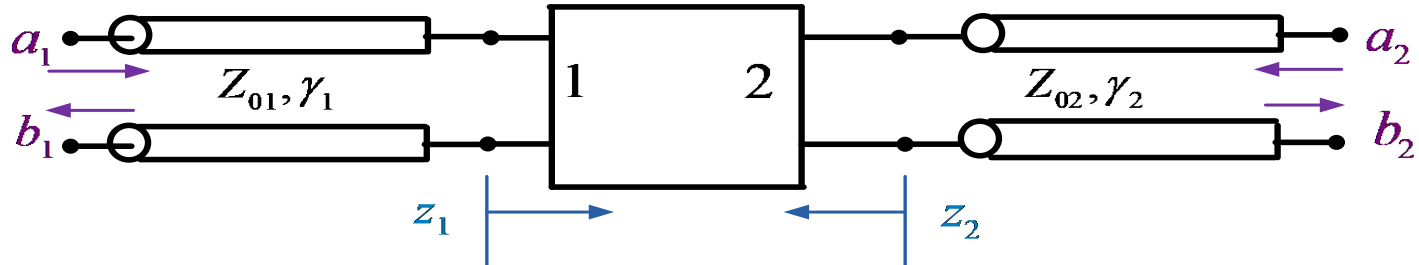

$i = 1, 2$

$$P_i^+(0) = \frac{1}{2} \operatorname{Re} \left[V_i^+(0) I_i^{+*}(0) \right] = \frac{1}{2} \frac{|V_i^+(0)|^2}{Z_{0i}} \quad (\text{assuming lossless lines, so } Z_0 \text{ is real})$$

Recall: $a_i(0) \equiv V_i^+(0) / \sqrt{Z_{0i}}$


$$\Rightarrow P_i^+(0) = \frac{1}{2} |a_i(0)|^2$$

Similarly,

$$P_i^-(0) = \frac{1}{2} \frac{|V_i^-(0)|^2}{Z_{0i}} = \frac{1}{2} |b_i(0)|^2$$

A One-Port Network
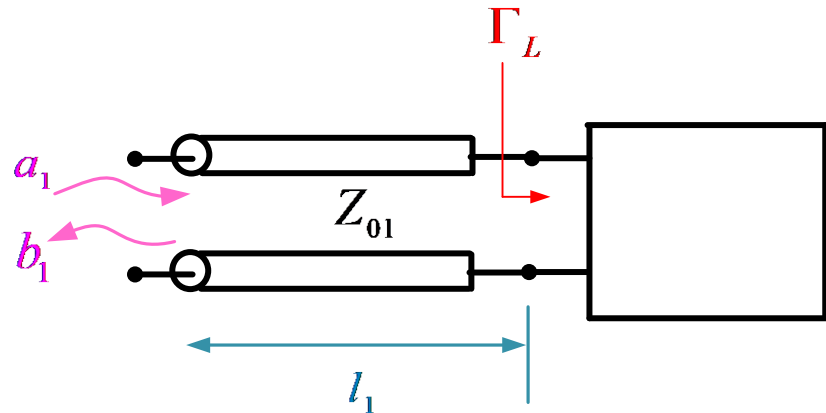
$$\begin{aligned}\Gamma_L &= \frac{V_1^-(0)}{V_1^+(0)} \\ &= \frac{V_1^-(0)/\sqrt{Z_{01}}}{V_1^+(0)/\sqrt{Z_{01}}} \\ &= \frac{b_1(0)}{a_1(0)}\end{aligned}$$



$$b_1(0) = S_{11}a_1(0)$$

Definition of S_{11} for a one-port

$$S_{11} = \Gamma_L$$


For a one-port network, S_{11} is the same as Γ_L .

Recall:

Incoming wave function $\equiv a_i(z_i) \equiv V_i^+(z_i)/\sqrt{Z_{0i}}$

Outgoing wave function $\equiv b_i(z_i) \equiv V_i^-(z_i)/\sqrt{Z_{0i}}$

A Two-Port Network

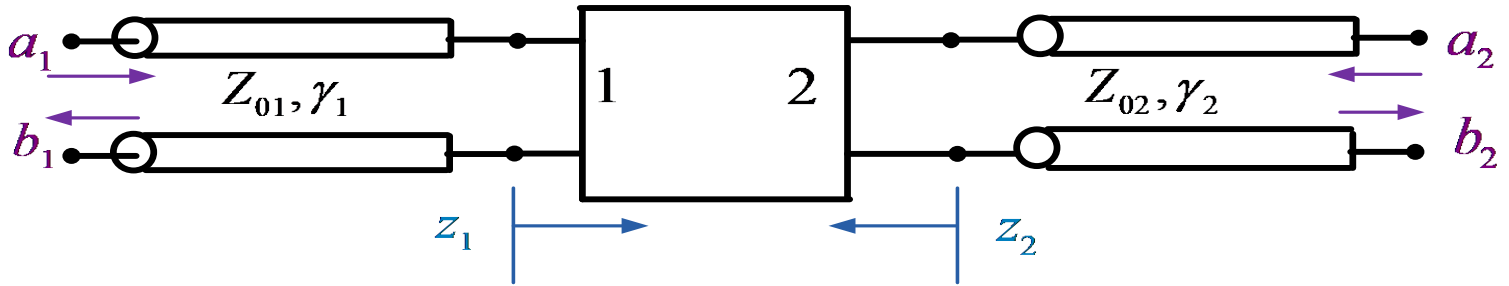

From linearity:

$$b_1(0) = S_{11}a_1(0) + S_{12}a_2(0)$$

$$b_2(0) = S_{21}a_1(0) + S_{22}a_2(0)$$

Scattering matrix

or

$$\begin{bmatrix} b_1(0) \\ b_2(0) \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1(0) \\ a_2(0) \end{bmatrix} \Rightarrow [b] = [S][a]$$





A Two-Port Network (cont.)

$$b_1(0) = S_{11}a_1(0) + S_{12}a_2(0)$$

$$b_2(0) = S_{21}a_1(0) + S_{22}a_2(0)$$

| | | |
|---|---------------------|---|
| $S_{11} = \left. \frac{b_1(0)}{a_1(0)} \right _{a_2=0}$ | ← Output is matched | ← input reflection coef. w/ output matched |
| $S_{12} = \left. \frac{b_1(0)}{a_2(0)} \right _{a_1=0}$ | ← Input is matched | ← reverse transmission coef. w/ input matched |
| $S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right _{a_2=0}$ | ← Output is matched | ← forward transmission coef. w/ output matched |
| $S_{22} = \left. \frac{b_2(0)}{a_2(0)} \right _{a_1=0}$ | ← Input is matched | ← output reflection coef. w/ input matched |

A Two-Port Network (cont.)

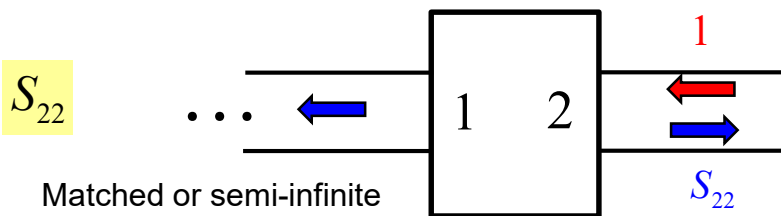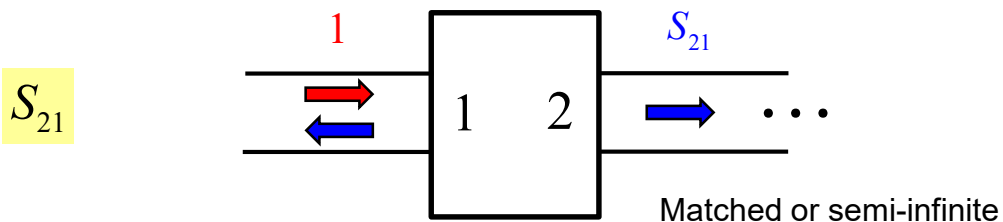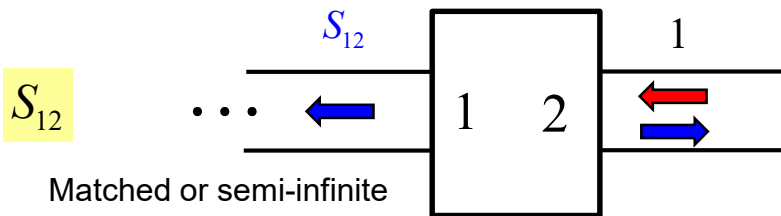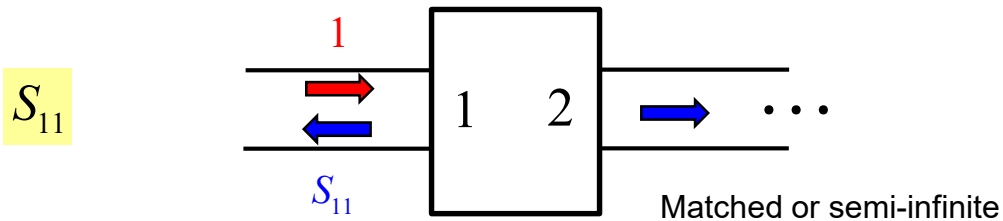

$$S_{11} = \left. \frac{b_1(0)}{a_1(0)} \right|_{a_2=0}$$


$$S_{12} = \left. \frac{b_1(0)}{a_2(0)} \right|_{a_1=0}$$

$$S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right|_{a_2=0}$$

$$S_{22} = \left. \frac{b_2(0)}{a_2(0)} \right|_{a_1=0}$$

Three-Port Network

Illustration of a three-port network

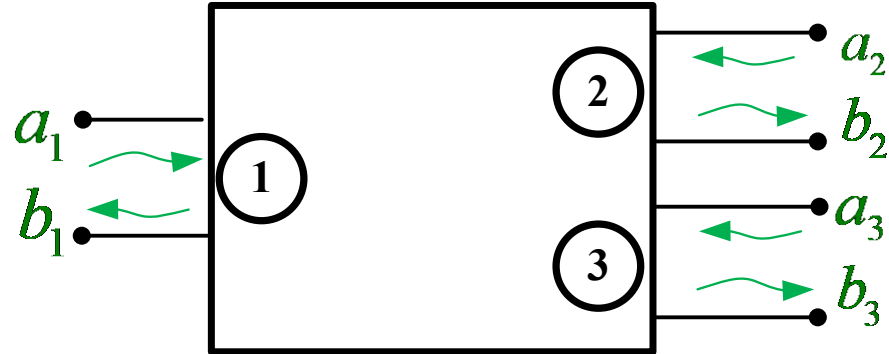

$$b_1(0) = S_{11}a_1(0) + S_{12}a_2(0) + S_{13}a_3(0)$$

$$b_2(0) = S_{21}a_1(0) + S_{22}a_2(0) + S_{23}a_3(0)$$


$$b_3(0) = S_{31}a_1(0) + S_{32}a_2(0) + S_{33}a_3(0)$$

To Illustrate:

$$b_2(0) = S_{21}a_1(0) + S_{22}a_2(0) + S_{23}a_3(0) \Rightarrow S_{21} = \frac{b_2(0)}{a_1(0)} \text{ when } a_2 = a_3 = 0$$

Three-Port Network (cont.)

Illustration of S_{21} :

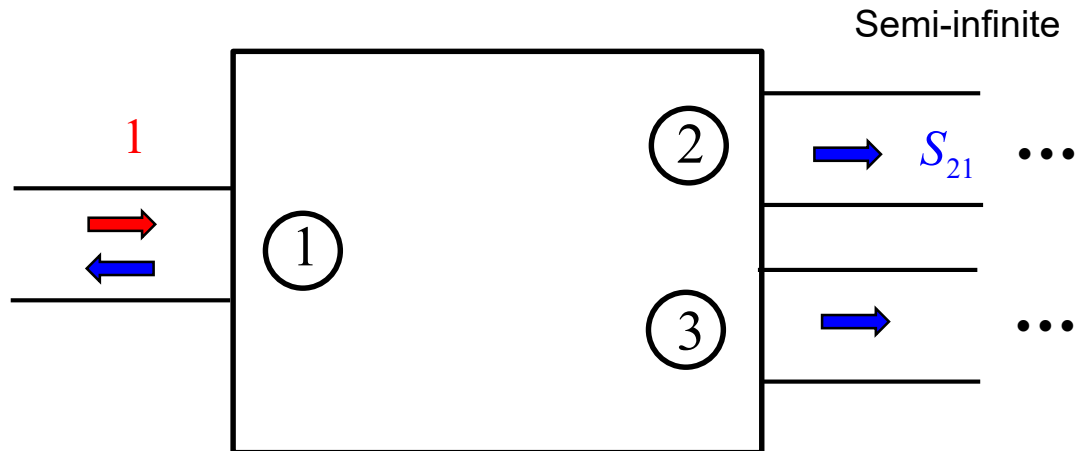


$$S_{21} = \frac{b_2(0)}{a_1(0)} \quad \text{when } a_2 = a_3 = 0$$

N-Port Network

For a general multiport network:

$$S_{ij} = \frac{b_i(0)}{a_j(0)} \Big|_{a_k=0, k \neq j}$$

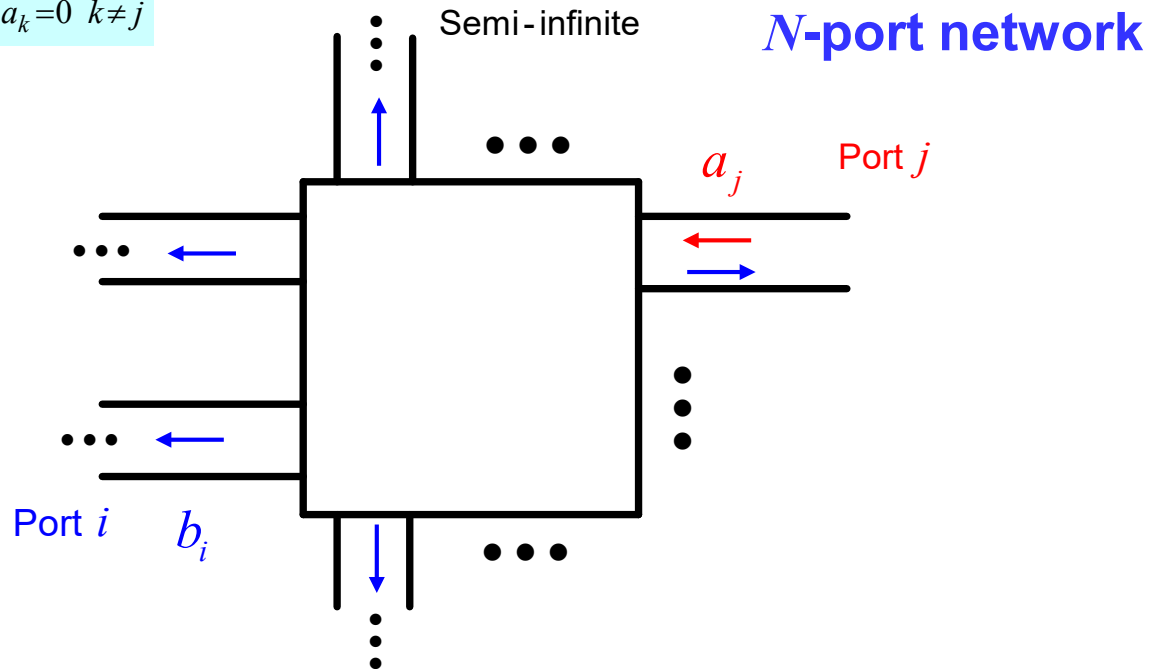All ports except port j are semi-infinite (or with matched load at ports) with no incident wave.




We send in an incident wave on port j and measure the outgoing wave on port i , when all lines except j are semi-infinite (or terminated in a matched load), and thus there is an incident wave only on port j .

Summary of S Parameters

Summary of S Parameters



$$[b] = [S][a]$$

$$S_{ij} = \left. \frac{b_i(0)}{a_j(0)} \right|_{a_k=0 \quad k \neq j}$$

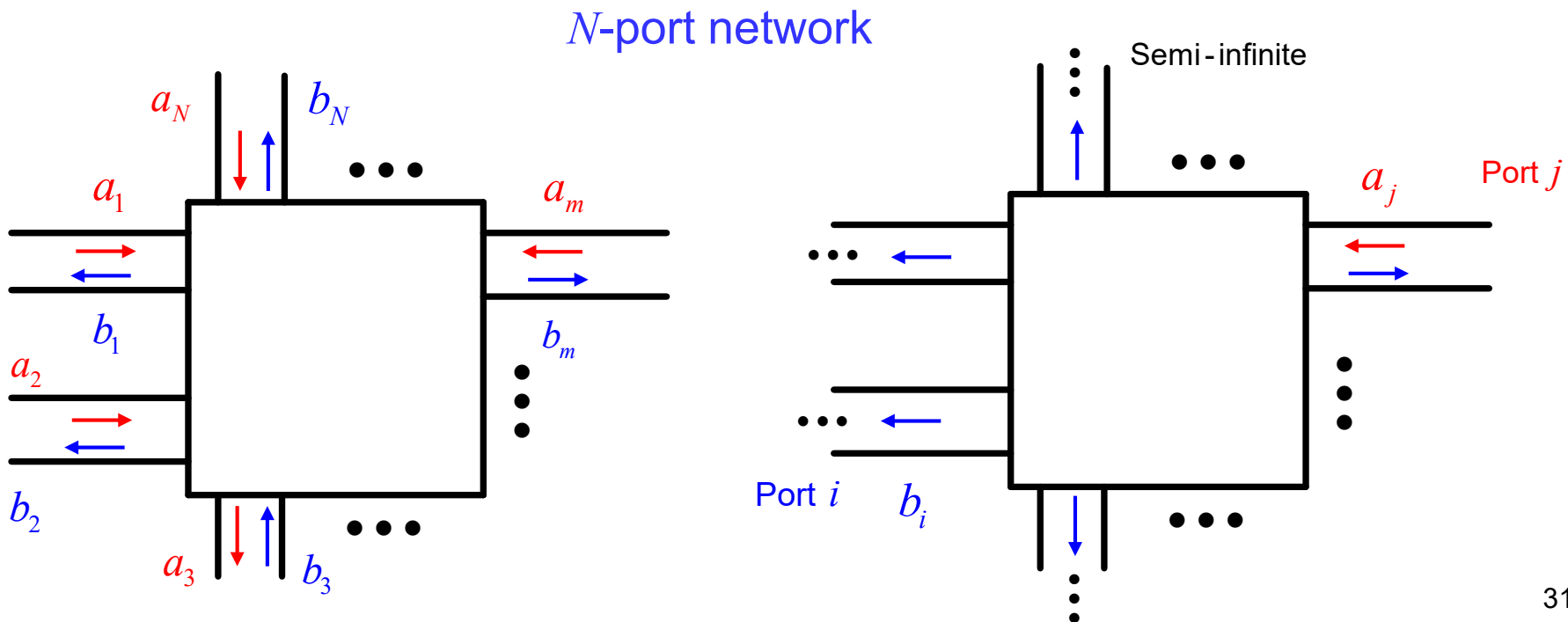


Scattering Parameters with Waveguides

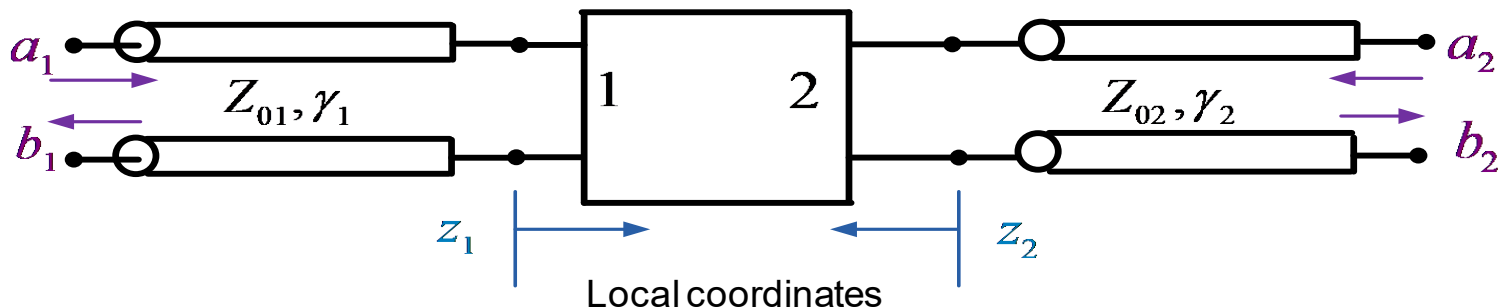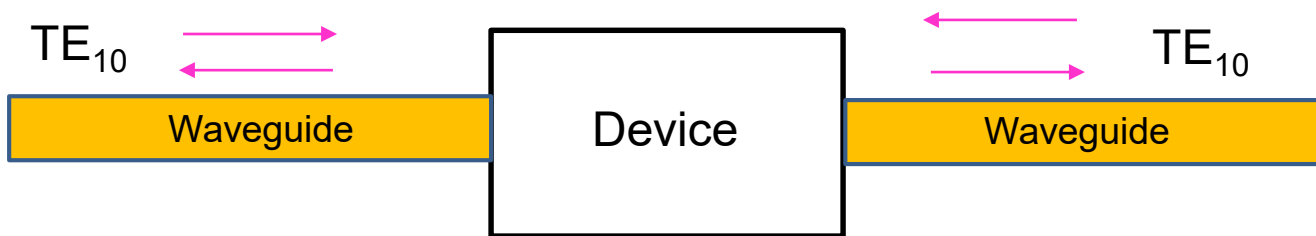A microwave system may have waveguides entering a device. In this case, the transmission lines are TEN models for the waveguides.



Shift in Reference Planes

(illustrated for a two-port)

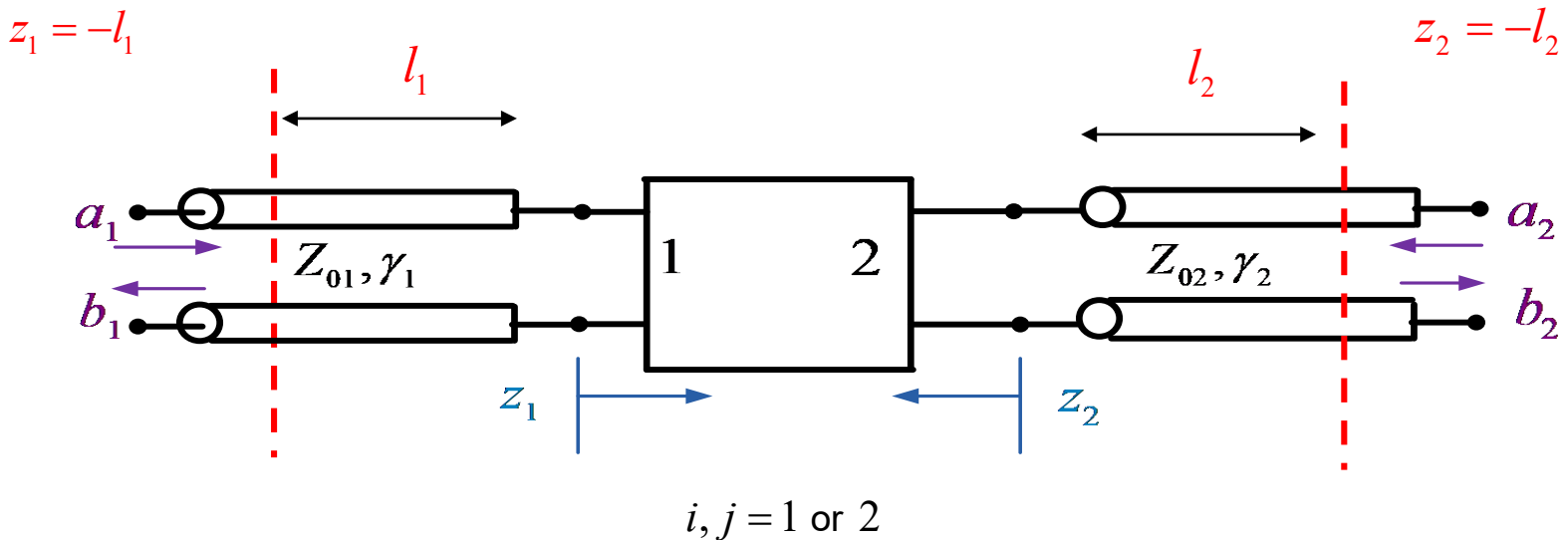

$$S'_{ij} = \left. \frac{b_i(z_i)}{a_j(z_j)} \right|_{a_k=0, k \neq j} \Rightarrow S'_{ij} = \left. \frac{b_i(0) e^{+\gamma_i z_i}}{a_j(0) e^{-\gamma_j z_j}} \right|_{a_k=0, k \neq j} \Rightarrow S'_{ij} = \left. \frac{b_i(0) e^{-\gamma_i l_i}}{a_j(0) e^{+\gamma_j l_j}} \right|_{a_k=0, k \neq j}$$

$$S'_{ij} = S_{ij} e^{-\gamma_i l_i} e^{-\gamma_j l_j}$$

Properties of the S Matrix

For reciprocal networks (networks containing only reciprocal materials), the S -matrix is symmetric:

$$S_{ij} = S_{ji} \quad i \neq j$$

$$\Rightarrow [S] = [S]^T$$

Example of a nonreciprocal material: a biased ferrite

Properties of the S Matrix (cont.)

❖ For lossless networks, the S -matrix is unitary[†].

$$\Rightarrow [S]^T [S]^* = [S]^* [S]^T = [U]$$

Identity matrix

Hence,

$$[S]^T = [S^*]^{-1} = [S]^{-1*}$$

$$\Rightarrow [S]^{T*} = [S]^{-1}$$

(a “unitary” matrix)

Alternate notation:

$$[S]^\dagger = [S]^H \equiv [S]^{T*}$$

$$\text{Therefore, } [S]^\dagger = [S]^{-1}$$

(“Hermetian conjugate” or “Hermetian transpose”)

Note :
If $[A][B] = [U]$
then $[B][A] = [U]$

[†]A proof is in the Pozar book.

Properties of the S Matrix (cont.)

Start with the first part of the unitary equation:

$$[S]^T [S]^* = [U]$$

N -port network

Take (i, j) element $\Rightarrow \sum_{k=1}^N S_{ik}^T S_{kj}^* = \sum_{k=1}^N S_{ki} S_{kj}^* = \delta_{ij}$

$$\delta_{ij} = \begin{cases} 1; & i = j \\ 0; & i \neq j \end{cases}$$

Properties of the S Matrix (cont.)

$$\sum_{k=1}^N S_{ki} S_{kj}^* = \delta_{ij}$$

Interpretation: The inner product of columns i and j is zero unless $i = j$.

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{23} & S_{33} \end{bmatrix}$$

\underline{S}_1 vector \underline{S}_3 vector

The rows also form orthogonal sets (this follows from starting with the second part of the unitary equation).

$$\underline{S}_i \cdot \underline{S}_j^* = \delta_{ij}$$

Physical interpretation: All of the power outgoing on the ports is equal to all of the power incident on the ports.

Comment on Normalization

Note: If all lines entering the network have the same characteristic impedance, then

$$S_{ij} = \frac{b_i(0)}{a_j(0)} = \frac{V_i^-(0)}{V_j^+(0)} \Big|_{V_k^+=0 \quad k \neq j}$$

In this case, there is no difference between normalized and unnormalized scattering parameters.

In general (different characteristic impedances):

$$S_{ij} \equiv \frac{V_i^-(0)}{V_j^+(0)} \Big|_{V_k^+=0 \quad k \neq j}$$

“unnormalized” scattering parameters

$$S_{ij} \equiv \frac{b_i(0)}{a_j(0)} \Big|_{a_k=0 \quad k \neq j}$$

“normalized” scattering parameters


Note:

The unitary property of the scattering matrix requires normalized parameters.
We use normalized parameters in these notes.

Note on Z_0

Important Note:

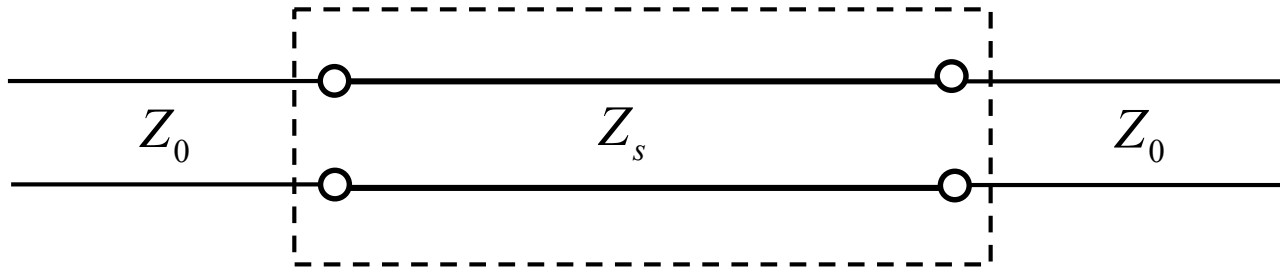The S parameters depend on Z_0 .
(The Z and Y parameters do not.)



Example: The device is a section of transmission line.

$$S_{11} = 0 \quad \text{when} \quad Z_0 = Z_s$$

$$S_{11} \neq 0 \quad \text{when} \quad Z_0 \neq Z_s \quad (\text{in general})$$


Scattering Parameters (cont.)

A general formula for converting from Z parameters to S parameters is:

$$[S] = \left(\frac{1}{Z_0} [Z] - [U] \right) \left([U] + \frac{1}{Z_0} [Z] \right)^{-1}$$

$$[Z] = Z_0 ([U] + [S]) \left(([U] - [S]) \right)^{-1}$$

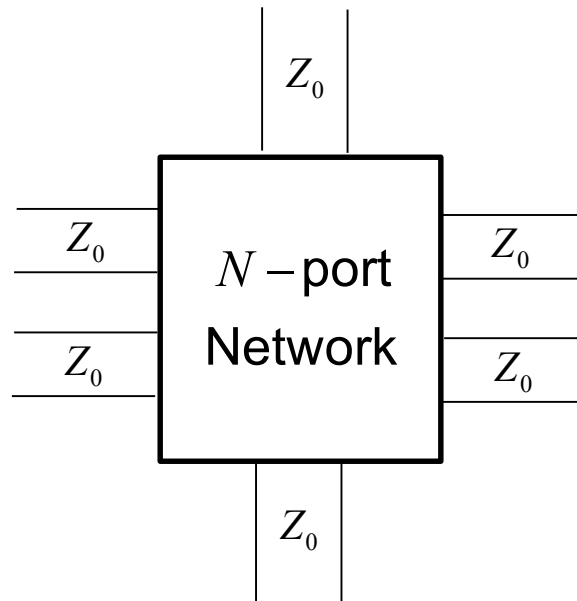
(This assumes all transmission lines are identical with characteristic impedance Z_0 .)



Note:
The derivation is in
the Pozar book.

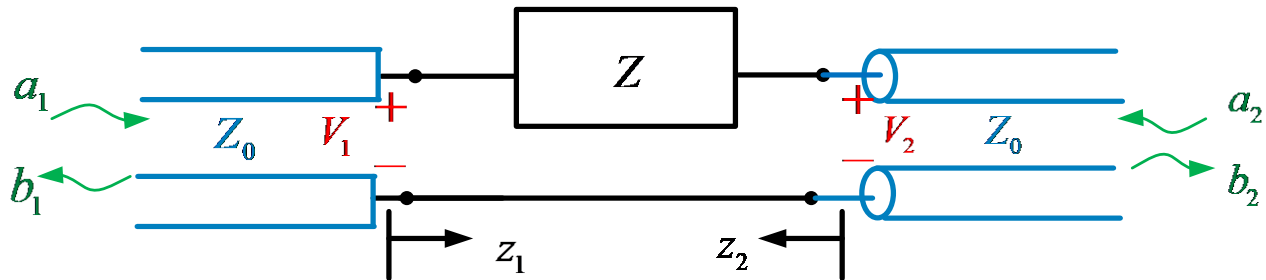
Example

Find the S parameters for a series impedance Z .



Note that two different coordinate systems are being used here!

Example (cont.)

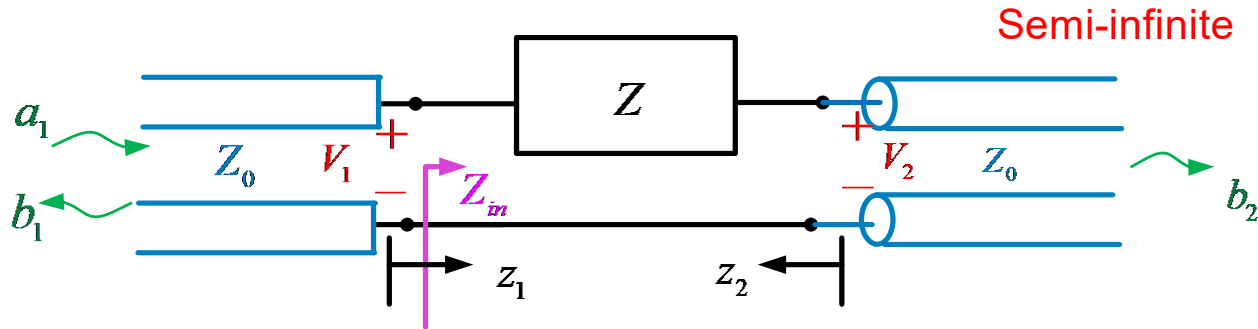

S_{11} Calculation:

$$S_{11} = \left. \frac{b_1(0)}{a_1(0)} \right|_{a_2=0} = \frac{V_1^-(0)}{V_1^+(0)} = \left. \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \right|_{a_2=0} = \frac{(Z + Z_0) - Z_0}{(Z + Z_0) + Z_0}$$


$$\Rightarrow S_{11} = \frac{Z}{Z + 2Z_0}$$

By symmetry:

$$S_{22} = S_{11}$$

Example (cont.)

S_{21} Calculation:

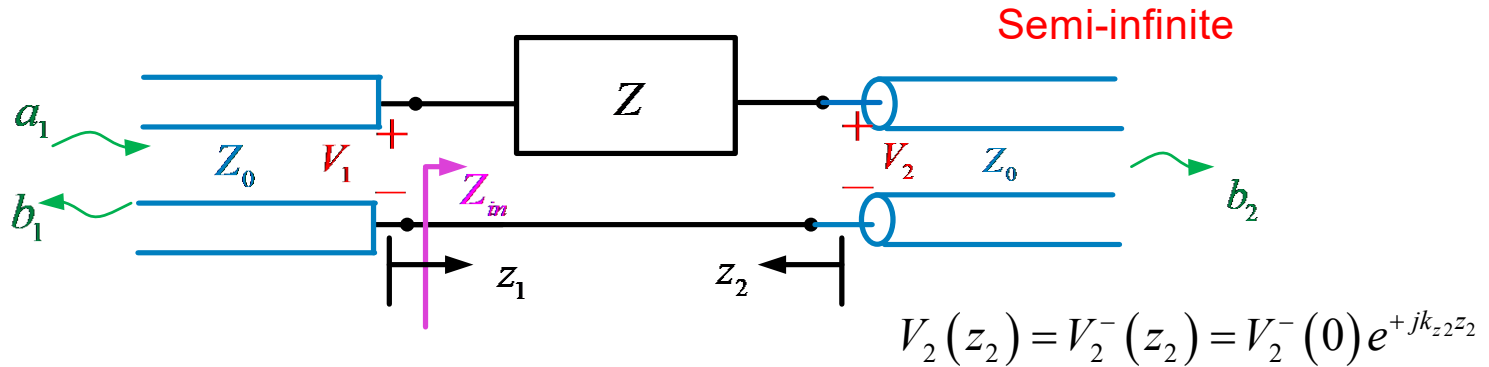

$$S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right|_{a_2=0}$$

$$= \left. \frac{V_2^-(0)}{V_1^+(0)} \right|_{a_2=0}$$


Voltage divider: $V_2^-(0) = V_2(0) = V_1(0) \left(\frac{Z_0}{Z + Z_0} \right)$

Input voltage: $V_1(0) = V_1^+(0)(1 + S_{11})$

From first equation: $V_2^-(0) = V_1^+(0)(1 + S_{11}) \left(\frac{Z_0}{Z + Z_0} \right)$

$\Rightarrow S_{21} = \frac{V_2^-(0)}{V_1^+(0)} = (1 + S_{11}) \left(\frac{Z_0}{Z + Z_0} \right)$

Example (cont.)

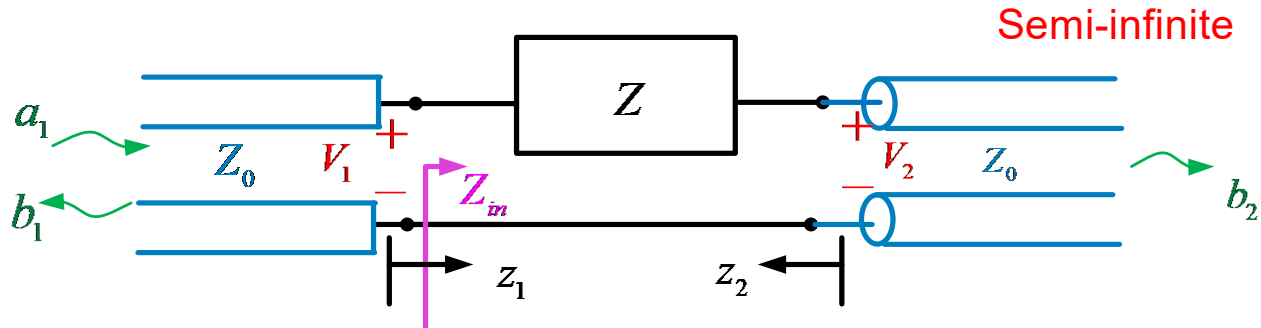

Hence

$$S_{21} = (1 + S_{11}) \left(\frac{Z_0}{Z + Z_0} \right) = \left(1 + \frac{Z}{Z + 2Z_0} \right) \left(\frac{Z_0}{Z + Z_0} \right) = \left(\frac{2Z + 2Z_0}{Z + 2Z_0} \right) \left(\frac{Z_0}{Z + Z_0} \right) = 2 \left(\frac{Z + Z_0}{Z + 2Z_0} \right) \left(\frac{Z_0}{Z + Z_0} \right)$$


We then have:

$$S_{21} = \frac{2Z_0}{Z + 2Z_0}$$

$$S_{12} = S_{21}$$

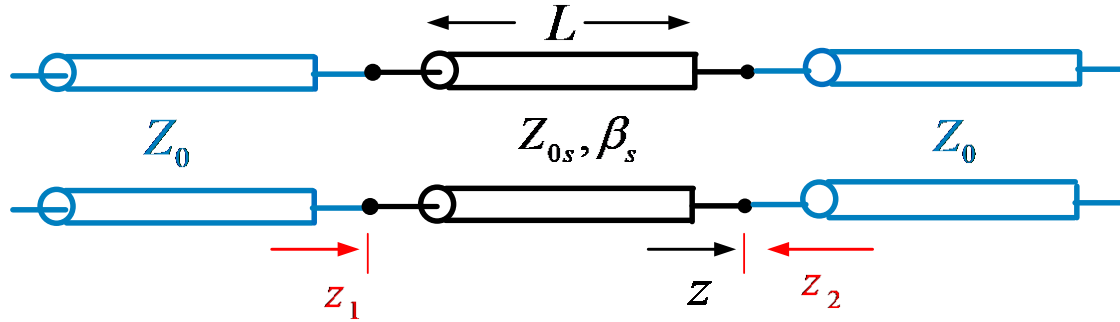Example

Find the S parameters for a length L of transmission line.




Note that three different coordinate systems are being used here!

(The subscript “ s ” denotes the middle section.)

Example (cont.)


S_{11} Calculation:

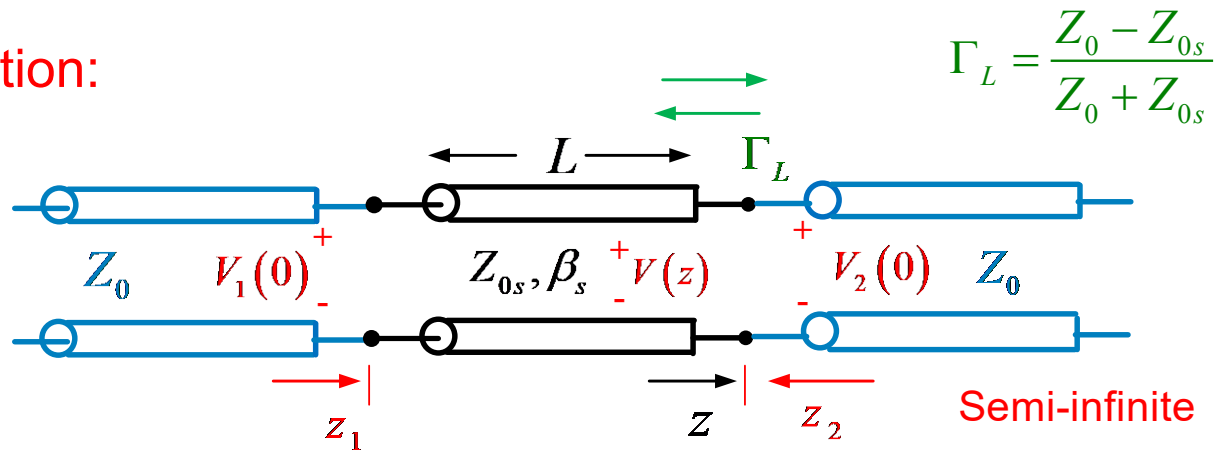

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \frac{Z_{in}|_{a_2=0} - Z_0}{Z_{in}|_{a_2=0} + Z_0} = S_{22} \text{ (by symmetry)}$$

$$Z_{in}|_{a_2=0} = Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} = Z_{0s} \frac{(1 + \Gamma_L e^{-j2\beta_s L})}{(1 - \Gamma_L e^{-j2\beta_s L})}$$

Example (cont.)

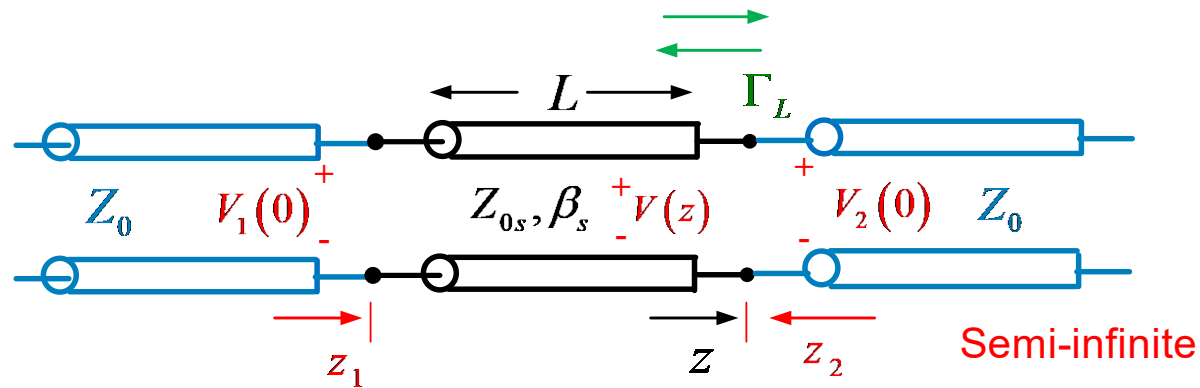


Hence

$$S_{11} = S_{22} = \frac{Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} - Z_0}{Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} + Z_0}$$

Note: If $Z_{0s} = Z_0 \Rightarrow Z_{in}|_{a_2=0} = Z_0 \Rightarrow S_{11} = S_{22} = 0$

Example (cont.)

S_{21} Calculation:

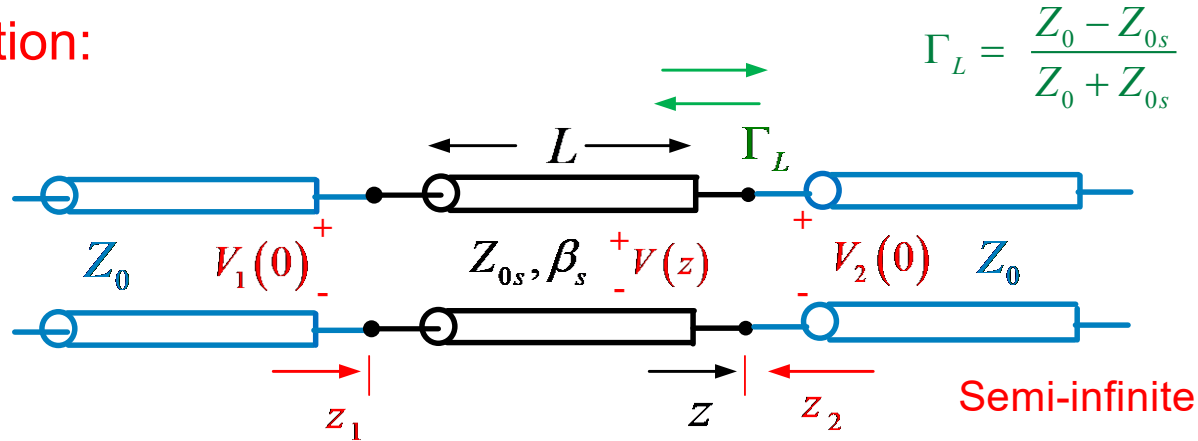

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} = \left. \frac{V_2^-(0)/\sqrt{Z_0}}{V_1^+(0)/\sqrt{Z_0}} \right|_{a_2=0} = \left. \frac{V_2^-(0)}{V_1^+(0)} \right|_{V_2^-=0}$$


Total voltage at port 1: $V_1(0) = V_1^+(0)(1 + S_{11})$

Hence, for the denominator of the S_{21} equation we have

$$V_1^+(0) = \frac{V_1(0)}{1 + S_{11}}$$

We now try to put the numerator of the S_{21} equation in terms of $V_1(0)$.

Example (cont.)

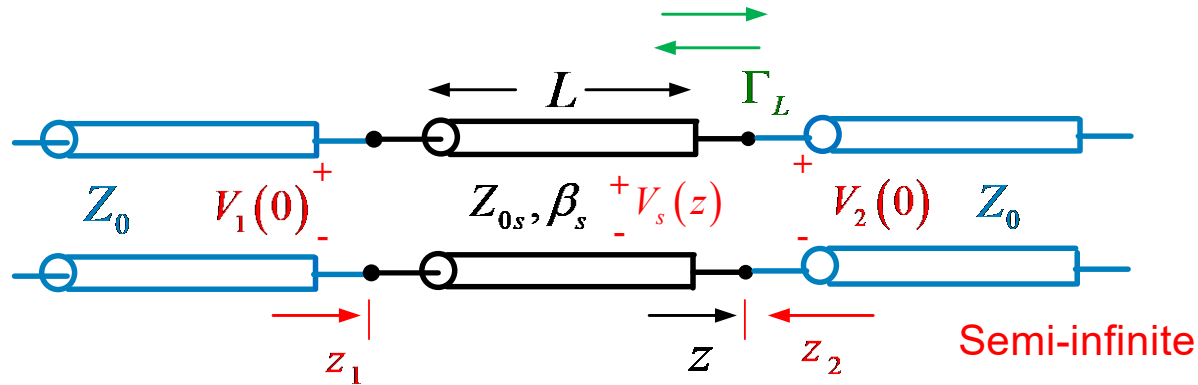

$$V_2^-(0) = V_2(0) = V_s(0) = V_s^+(0)(1 + \Gamma_L)$$

Next, we need to get $V_s^+(0)$ in terms of $V_1(0)$:

$$V_s(z) = V_s^+(0)e^{-j\beta_s z} (1 + \Gamma_L e^{+j2\beta_s z})$$


$$\Rightarrow V_1(0) = V_s(-L) = V_s^+(0)e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})$$

$$\Rightarrow V_s^+(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})}$$

Hence, from the top equation we have

$$V_2^-(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})} (1 + \Gamma_L)$$

Example (cont.)

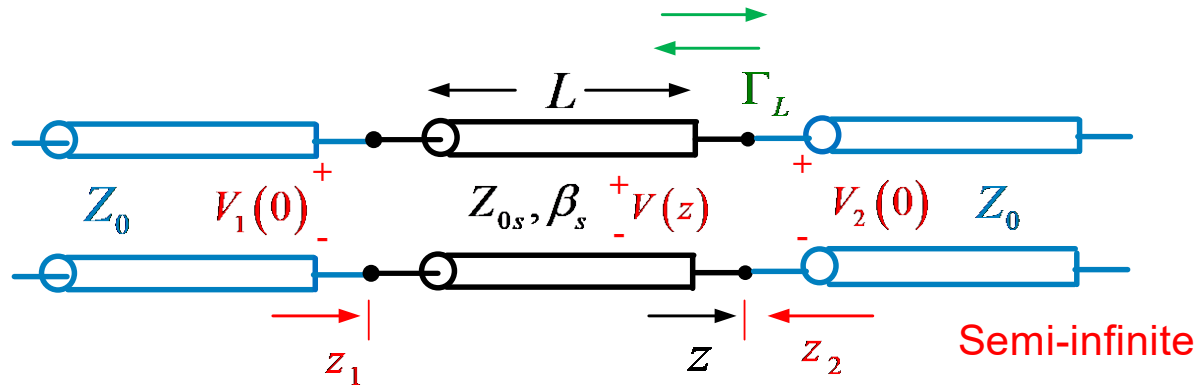

$$V_2^-(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})} (1 + \Gamma_L)$$

Therefore, we have

$$V_1^+(0) = \frac{V_1(0)}{1 + S_{11}}$$

$$S_{21} = \left. \frac{V_2^-(0)}{V_1^+(0)} \right|_{a_2=0} = \frac{(1 + S_{11})(1 + \Gamma_L) e^{-j\beta_s L}}{1 + \Gamma_L e^{-j2\beta_s L}}$$

so

$$S_{21} = \frac{(1 + S_{11})(1 + \Gamma_L) e^{-j\beta_s L}}{1 + \Gamma_L e^{-j2\beta_s L}} = S_{12} \text{ (the } S \text{ matrix is symmetric)}$$

Example (cont.)

Special cases:

a) $Z_{0s} = Z_0$

$$Z_{0s} = Z_0 \Rightarrow S_{11} = S_{22} = 0, \quad \Gamma_L = 0$$


$$S_{21} = S_{12} = e^{-j\beta_s L}$$

b) $L = \frac{\lambda_g}{2}$

$$L = \frac{\lambda_g}{2} \Rightarrow \beta_s L = \frac{2\pi}{\lambda_g} \frac{\lambda_g}{2} = \pi$$

$$\Rightarrow Z_{in}|_{a_2=0} = Z_0 \Rightarrow S_{11} = S_{22} = 0$$
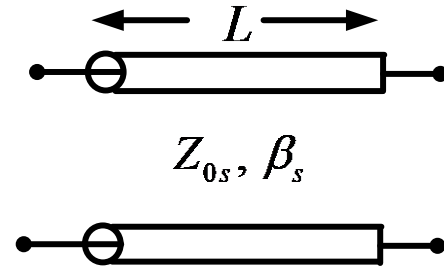
$$e^{-j\beta_s L} = -1, \quad e^{-j2\beta_s L} = +1 \Rightarrow S_{21} = -1$$



a) $[S] = \begin{bmatrix} 0 & e^{-j\beta_s L} \\ e^{-j\beta_s L} & 0 \end{bmatrix}$


b) $[S] = \begin{bmatrix} 0 & -1 \\ -1 & 0 \end{bmatrix}$

Example

Find the S parameters for a step-impedance discontinuity.

S_{11} Calculation:
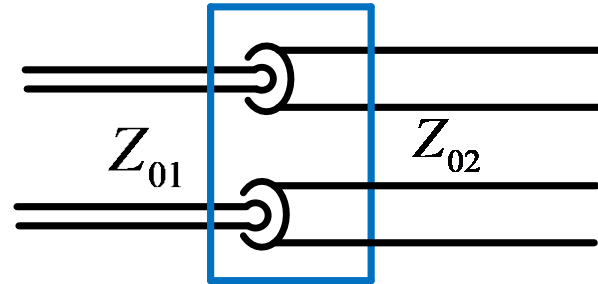
$$S_{11} = \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}}$$
$$S_{22} = \frac{Z_{01} - Z_{02}}{Z_{02} + Z_{01}} = -S_{11}$$




S_{21} Calculation:

$$S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right|_{a_2=0} = \left. \frac{\frac{V_2^-(0)}{\sqrt{Z_{02}}}}{\frac{V_1^+(0)}{\sqrt{Z_{01}}}} \right|_{a_2=0}$$

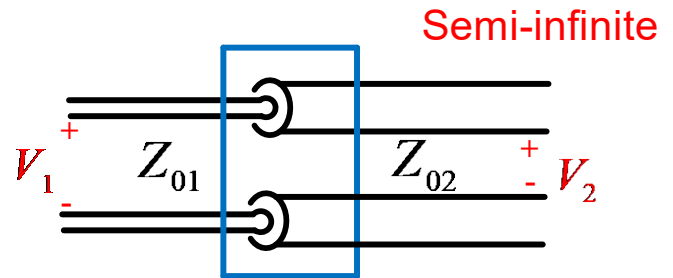Example (cont.)

Because of continuity of the voltage across the junction, we have:



$$V_2^-(0)\Big|_{a_2=0} = V_2(0)\Big|_{a_2=0} = V_1(0)\Big|_{a_2=0} = V_1^+(0)(1+S_{11})$$

$$S_{21} = \frac{V_2^-(0)}{\sqrt{Z_{02}}} \Big|_{a_2=0} = \frac{V_1^+(0)(1+S_{11})}{\sqrt{Z_{02}}} \Big|_{a_2=0} = \frac{V_1^+(0)}{\sqrt{Z_{01}}} \Big|_{a_2=0} \frac{1+S_{11}}{\sqrt{Z_{02}}} \frac{\sqrt{Z_{01}}}{\sqrt{Z_{01}}}$$

$$1+S_{11} = 1 + \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} = \frac{2Z_{02}}{Z_{02} + Z_{01}}$$

so


$$S_{21} = (1+S_{11}) \sqrt{\frac{Z_{01}}{Z_{02}}}$$

Hence

$$S_{21} = S_{12} = 2 \frac{\sqrt{Z_{01}Z_{02}}}{Z_{01} + Z_{02}}$$

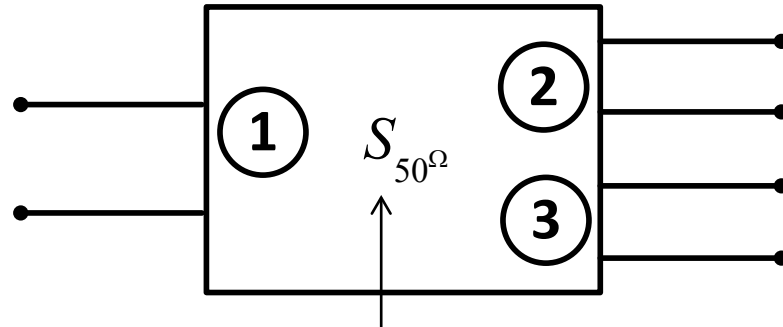Example

$$[S_{50\Omega}] = \begin{bmatrix} 0 & \frac{-j}{\sqrt{2}} & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 \\ \frac{-j}{\sqrt{2}} & 0 & 0 \end{bmatrix}$$



These are the S parameters assuming $50\ \Omega$ lines entering the device.

Not unitary \rightarrow **lossy**

(For example, column 2 dotted with the conjugate of column 3 is not zero.)


- 1) Find the input impedance looking into port 1 when ports 2 and 3 are terminated in $50\ [\Omega]$ loads.
- 2) Find the input impedance looking into port 1 when port 2 is terminated in a $75\ [\Omega]$ load and port 3 is terminated in a $50\ [\Omega]$ load.

Example (cont.)

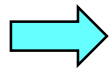1) Z_{in} if ports 2 and 3 are terminated in $50 [\Omega]$: $a_2 = a_3 = 0$


$$b_1 = S_{11}a_1 + S_{12}a_2 + S_{13}a_3$$

$$\Rightarrow \Gamma_{in1} = \frac{b_1}{a_1} = S_{11} = 0 \quad \Rightarrow \quad Z_{in1} = Z_{01}$$



$$Z_{in1} = 50 [\Omega]$$
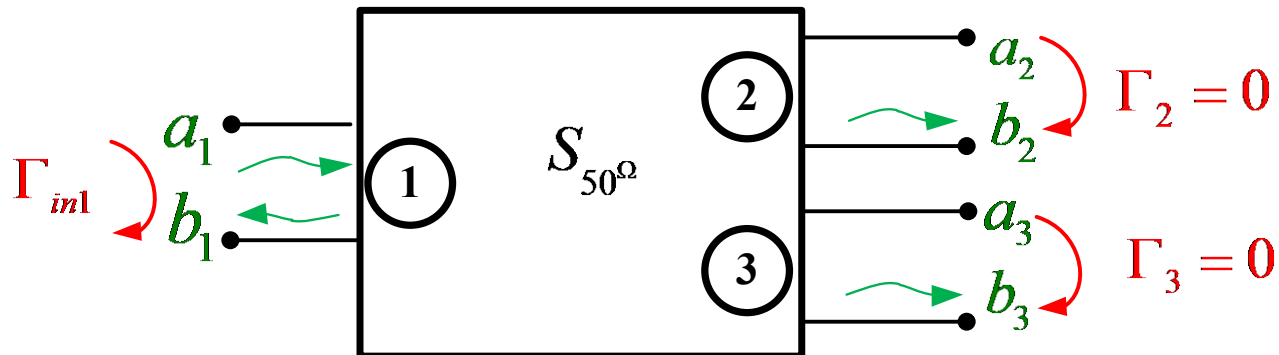
$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix} = \begin{bmatrix} 0 & \frac{-j}{\sqrt{2}} & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 \\ \frac{-j}{\sqrt{2}} & 0 & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \end{bmatrix}$$




Example (cont.)

2) Z_{in} if port 2 is terminated in $75 [\Omega]$ and port 3 in $50 [\Omega]$:

$$\Gamma_2 = \frac{a_2}{b_2} = \frac{75 - 50}{75 + 50} = \frac{1}{5}$$


$$\Gamma_3 = \frac{a_3}{b_3} = \frac{50 - 50}{50 + 50} = 0$$
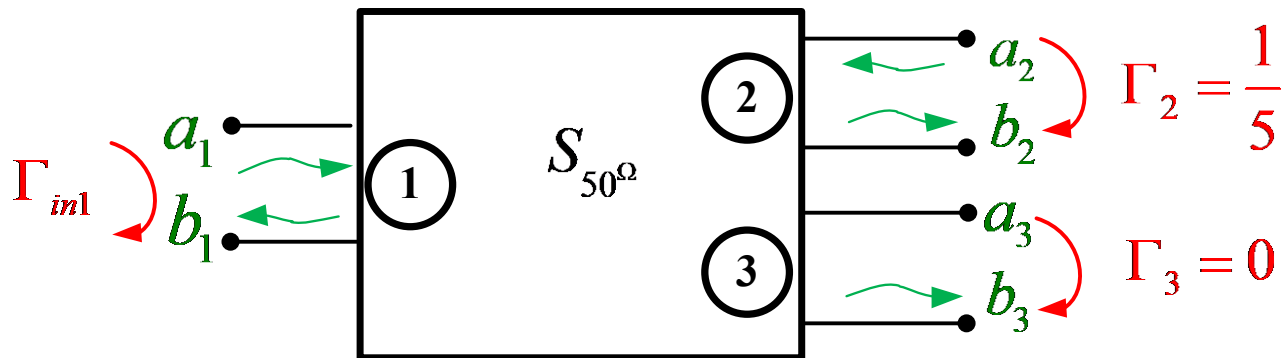
$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix} = \begin{bmatrix} 0 & \frac{-j}{\sqrt{2}} & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 \\ \frac{-j}{\sqrt{2}} & 0 & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \end{bmatrix}$$



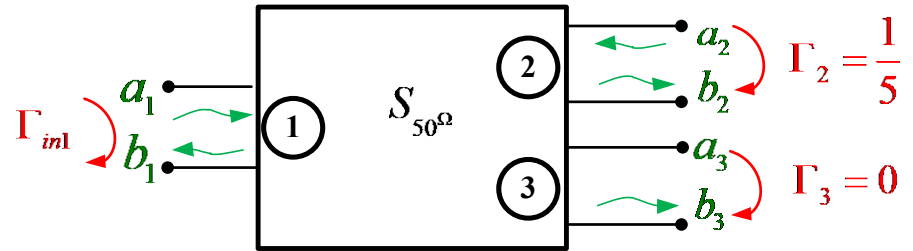Example (cont.)

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix} = \begin{bmatrix} 0 & \frac{-j}{\sqrt{2}} & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 \\ \frac{-j}{\sqrt{2}} & 0 & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \end{bmatrix}$$



$$\Rightarrow \Gamma_{in1} = \frac{b_1}{a_1} = \cancel{S_{11}} + S_{12} \frac{a_2}{a_1} + S_{13} \frac{a_3}{a_1}$$

$b_2 / a_1 = S_{21} + \cancel{S_{22}} \left(\frac{a_2}{a_1} \right) + \cancel{S_{23}} \left(\frac{a_3}{a_1} \right)$


$$= S_{12} \left(\frac{\Gamma_2 b_2}{a_1} \right) = S_{12} (\Gamma_2 S_{21}) = \left(\frac{-j}{\sqrt{2}} \right) \left(\frac{1}{5} \right) \left(\frac{-j}{\sqrt{2}} \right) = -\frac{1}{10}$$

$$a_2 = \Gamma_2 b_2$$

Hence $Z_{in1} = 50 \left(\frac{1 + \Gamma_{in1}}{1 - \Gamma_{in1}} \right) = 44.55 \text{ } [\Omega]$

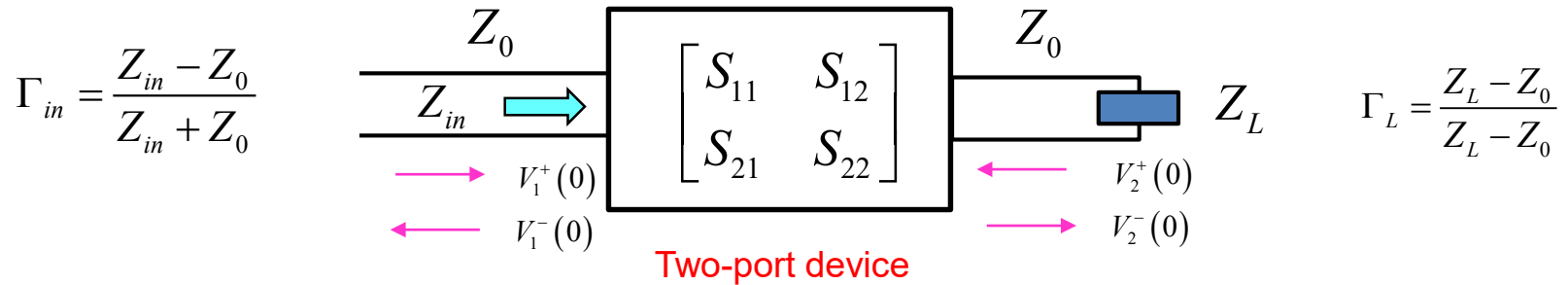Example

Find Γ_{in} for the general two-port system shown below.



$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$


Assume : $V_1^+(0) = 1V$

so $\Gamma_{in} = V_1^-(0) = S_{11}(1) + S_{12}V_2^+(0)$

We also have:

$$\left. \begin{aligned} V_2^+(0) &= \Gamma_L V_2^-(0) \\ V_2^-(0) &= S_{21}(1) + S_{22}V_2^+(0) \end{aligned} \right\} \begin{aligned} V_2^+(0) &= \Gamma_L (S_{21}(1) + S_{22}V_2^+(0)) \\ \downarrow \text{Solve for } V_2^+(0) \\ V_2^+(0) &= \frac{\Gamma_L S_{21}}{1 - S_{22}\Gamma_L} \end{aligned}$$

Example (cont.)

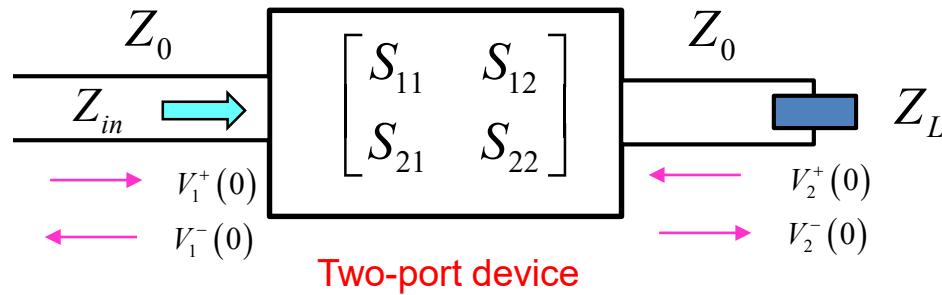

Hence


$$\begin{aligned}\Gamma_{in} &= S_{11} + S_{12}V_2^+(0) \\ &= S_{11} + S_{12}\left(\frac{\Gamma_L S_{21}}{1 - S_{22}\Gamma_L}\right)\end{aligned}$$

so

$$\Gamma_{in} = S_{11} + \left(\frac{\Gamma_L S_{12} S_{21}}{1 - S_{22} \Gamma_L}\right) \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Transfer (T) Matrix

For cascaded 2-port networks:

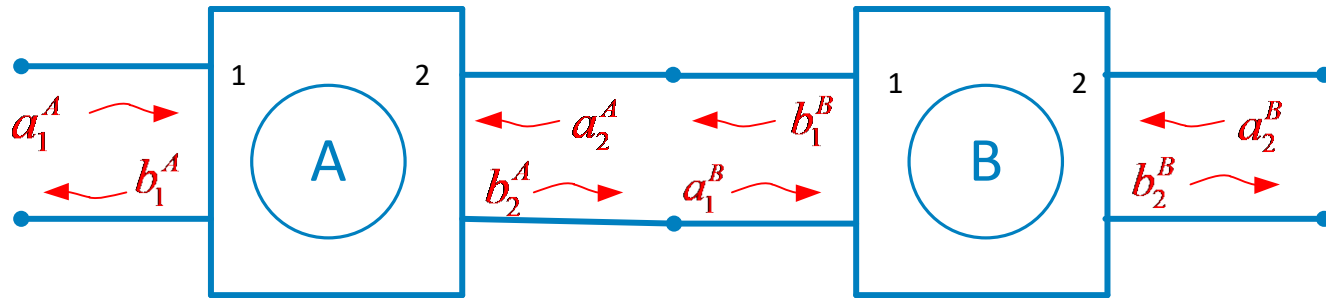

T Matrix:

$$\begin{bmatrix} a_1 \\ b_1 \end{bmatrix} = \begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} \begin{bmatrix} b_2 \\ a_2 \end{bmatrix}$$

$$= [T] \begin{bmatrix} b_2 \\ a_2 \end{bmatrix}$$

$$[T] = \begin{bmatrix} \frac{1}{S_{21}} & \frac{-S_{22}}{S_{21}} \\ \frac{S_{11}}{S_{21}} & S_{12} - \frac{S_{11}S_{22}}{S_{21}} \end{bmatrix}$$

$$[S] = \begin{bmatrix} \frac{-T_{21}}{T_{22}} & \frac{1}{T_{22}} \\ T_{11} - \frac{T_{12}^2}{T_{22}} & \frac{T_{12}}{T_{22}} \end{bmatrix}$$

(derivation omitted)

Transfer (T) Matrix (cont.)

Cascading property:

$$\begin{aligned} \begin{bmatrix} a_1^A \\ b_1^A \end{bmatrix} &= \begin{bmatrix} T^A \end{bmatrix} \begin{bmatrix} b_2^A \\ a_2^A \end{bmatrix} && \text{(definition of } T \text{ matrix)} \\ &= \begin{bmatrix} T^A \end{bmatrix} \begin{bmatrix} a_1^B \\ b_1^B \end{bmatrix} \\ &= \begin{bmatrix} T^A \end{bmatrix} \begin{bmatrix} T^B \end{bmatrix} \begin{bmatrix} b_2^B \\ a_2^B \end{bmatrix} \end{aligned}$$

so that

$$\begin{bmatrix} a_1^A \\ b_1^A \end{bmatrix} = \underbrace{\begin{bmatrix} T^A \end{bmatrix} \begin{bmatrix} T^B \end{bmatrix}}_{\begin{bmatrix} T^{AB} \end{bmatrix}} \begin{bmatrix} b_2^B \\ a_2^B \end{bmatrix}$$

Conclusion:

The T matrices can be multiplied together, just as for ABCD matrices.

Conversion Between Parameters (Two-Ports)

TABLE 4.2 Conversions Between Two-Port Network Parameters

| | <i>S</i> | <i>Z</i> | <i>Y</i> | <i>ABCD</i> |
|------------------------|---|--|--|--|
| <i>S</i> ₁₁ | <i>S</i> ₁₁ | $\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$ | $\frac{(Y_0 - Y_{11})(Y_0 + Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$ | $\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$ |
| <i>S</i> ₁₂ | <i>S</i> ₁₂ | $\frac{2Z_{12}Z_0}{\Delta Z}$ | $\frac{-2Y_{12}Y_0}{\Delta Y}$ | $\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$ |
| <i>S</i> ₂₁ | <i>S</i> ₂₁ | $\frac{2Z_{21}Z_0}{\Delta Z}$ | $\frac{-2Y_{21}Y_0}{\Delta Y}$ | $\frac{2}{A + B/Z_0 + CZ_0 + D}$ |
| <i>S</i> ₂₂ | <i>S</i> ₂₂ | $\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$ | $\frac{(Y_0 + Y_{11})(Y_0 - Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$ | $\frac{-A + B/Z_0 - CZ_0 + D}{A + B/Z_0 + CZ_0 + D}$ |
| <i>Z</i> ₁₁ | $Z_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$ | <i>Z</i> ₁₁ | $\frac{Y_{22}}{ Y }$ | $\frac{A}{C}$ |
| <i>Z</i> ₁₂ | $Z_0 \frac{2S_{12}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$ | <i>Z</i> ₁₂ | $\frac{-Y_{12}}{ Y }$ | $\frac{AD - BC}{C}$ |
| <i>Z</i> ₂₁ | $Z_0 \frac{2S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$ | <i>Z</i> ₂₁ | $\frac{-Y_{21}}{ Y }$ | $\frac{1}{C}$ |
| <i>Z</i> ₂₂ | $Z_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$ | <i>Z</i> ₂₂ | $\frac{Y_{11}}{ Y }$ | $\frac{D}{C}$ |
| <i>Y</i> ₁₁ | $Y_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$ | $\frac{Z_{22}}{ Z }$ | <i>Y</i> ₁₁ | $\frac{D}{B}$ |
| <i>Y</i> ₁₂ | $Y_0 \frac{-2S_{12}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$ | $\frac{-Z_{12}}{ Z }$ | <i>Y</i> ₁₂ | $\frac{BC - AD}{B}$ |
| <i>Y</i> ₂₁ | $Y_0 \frac{-2S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$ | $\frac{-Z_{21}}{ Z }$ | <i>Y</i> ₂₁ | $\frac{-1}{B}$ |
| <i>Y</i> ₂₂ | $Y_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$ | $\frac{Z_{11}}{ Z }$ | <i>Y</i> ₂₂ | $\frac{A}{B}$ |
| <i>A</i> | $\frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}}$ | $\frac{Z_{11}}{Z_{21}}$ | $\frac{-Y_{22}}{Y_{21}}$ | <i>A</i> |
| <i>B</i> | $Z_0 \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$ | $\frac{ Z }{Z_{21}}$ | $\frac{-1}{Y_{21}}$ | <i>B</i> |
| <i>C</i> | $\frac{1}{Z_0} \frac{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$ | $\frac{1}{Z_{21}}$ | $\frac{- Y }{Y_{21}}$ | <i>C</i> |
| <i>D</i> | $\frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{2S_{21}}$ | $\frac{Z_{22}}{Z_{21}}$ | $\frac{-Y_{11}}{Y_{21}}$ | <i>D</i> |


$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21}; \quad |Y| = Y_{11}Y_{22} - Y_{12}Y_{21}; \quad \Delta Y = (Y_{11} + Y_0)(Y_{22} + Y_0) - Y_{12}Y_{21}; \quad \Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}; \quad Y_0 = 1/Z_0.$

Example

Derive S_{ij} from the Z parameters for a 2 port network.


(The result is given inside row 1, column 2, of the previous table.)

S_{11} Calculation:

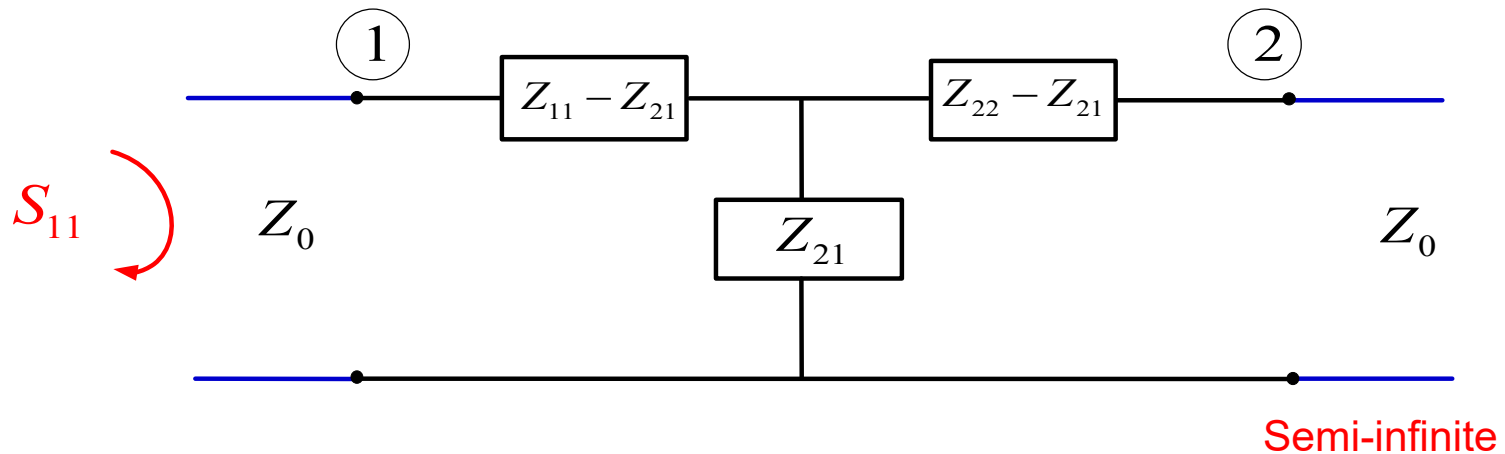


$$S_{11} = \Gamma_{in1} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}, \quad Z_{in} = (Z_{11} - Z_{21}) + ((Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0])$$

Example (cont.)

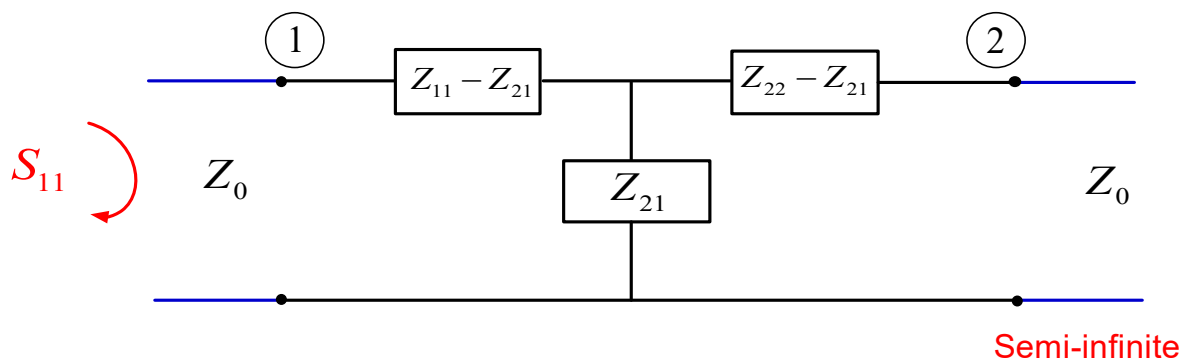

$$\begin{aligned}
 Z_{in} &= (Z_{11} - Z_{21}) + \left((Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0] \right) \\
 &= (Z_{11} - Z_{21}) + \frac{Z_{21} (Z_{22} - Z_{21} + Z_0)}{\cancel{Z_{21}} + ((\cancel{Z_{22}} - \cancel{Z_{21}}) + Z_0)} \\
 &= \frac{(Z_{11} - Z_{21})(Z_{22} + Z_0) + Z_{21}(Z_{22} - Z_{21} + Z_0)}{Z_{22} + Z_0} \\
 &= \frac{Z_{11}Z_{22} + Z_{11}Z_0 - \cancel{Z_{21}}Z_{22} - \cancel{Z_{21}}Z_0 + \cancel{Z_{21}}Z_{22} - Z_{21}^2 + \cancel{Z_{21}}Z_0}{Z_{22} + Z_0} \\
 &= \frac{Z_{11}Z_{22} + Z_{11}Z_0 - Z_{21}^2}{Z_{22} + Z_0}
 \end{aligned}$$

Example (cont.)

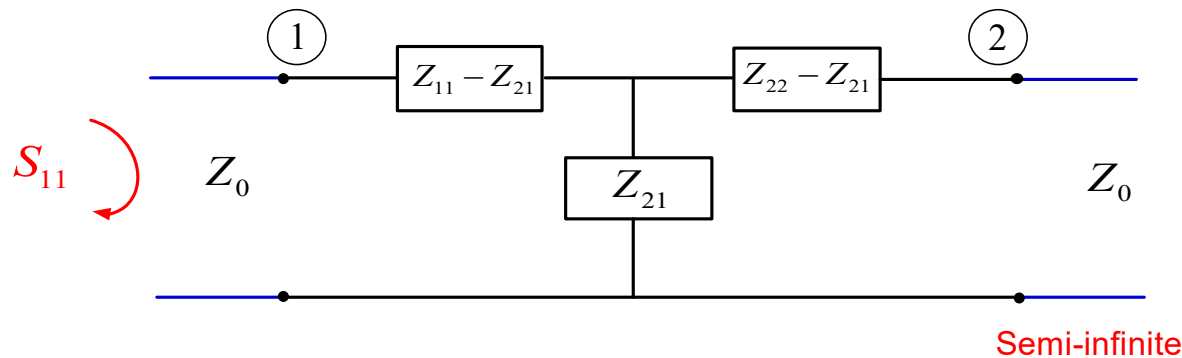

From the last slide:


$$Z_{in} = \frac{Z_{11}(Z_0 + Z_{22}) - Z_{21}^2}{Z_{22} + Z_0}$$

so

$$S_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_{in}(Z_0 + Z_{22}) - Z_0(Z_0 + Z_{22})}{Z_{in}(Z_0 + Z_{22}) + Z_0(Z_0 + Z_{22})} = \frac{(Z_{11}(Z_0 + Z_{22}) - Z_{21}^2) - Z_0(Z_0 + Z_{22})}{(Z_{11}(Z_0 + Z_{22}) - Z_{21}^2) + Z_0(Z_0 + Z_{22})}$$


We next simplify this.

Example (cont.)

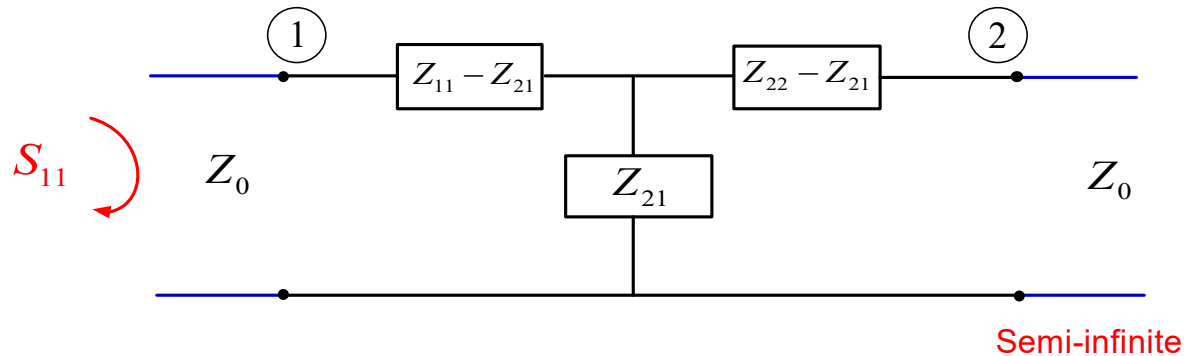

$$\begin{aligned}
 S_{11} &= \frac{Z_{11}(Z_0 + Z_{22}) - Z_{21}^2 - Z_0(Z_0 + Z_{22})}{Z_{11}(Z_0 + Z_{22}) - Z_{21}^2 + Z_0(Z_0 + Z_{22})} \\
 &= \frac{Z_{11}Z_0 + Z_{11}Z_{22} - Z_{21}^2 - Z_0^2 - Z_0Z_{22}}{Z_{11}Z_0 + Z_{11}Z_{22} - Z_{21}^2 + Z_0^2 + Z_0Z_{22}} \\
 &= \frac{(Z_0 + Z_{22})(Z_{11} - Z_0) - Z_{21}^2}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}
 \end{aligned}$$

Example (cont.)

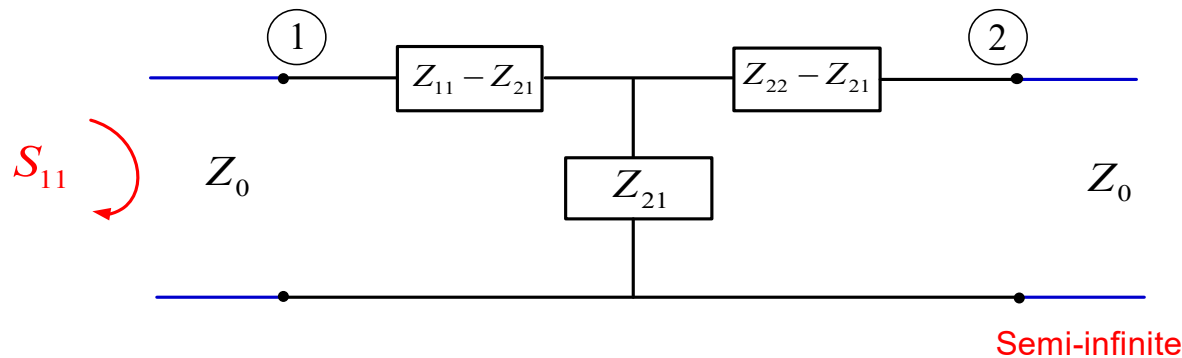

Hence

$$S_{11} = \frac{(Z_0 + Z_{22})(Z_{11} - Z_0) - Z_{21}^2}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}$$

To get S_{22} , simply let $Z_{11} \rightarrow Z_{22}$ in the previous result.
Hence, we have:

$$S_{22} = \frac{(Z_0 + Z_{11})(Z_{22} - Z_0) - Z_{21}^2}{(Z_0 + Z_{11})(Z_{22} + Z_0) - Z_{21}^2}$$


This agrees with the table.

This agrees with the table.

| Z |
|--|
| $\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$ |
| $\frac{2Z_{12}Z_0}{\Delta Z}$ |
| $\frac{2Z_{21}Z_0}{\Delta Z}$ |
| $\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$ |
| $\Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}$ |

Example (cont.)

S_{21} Calculation:

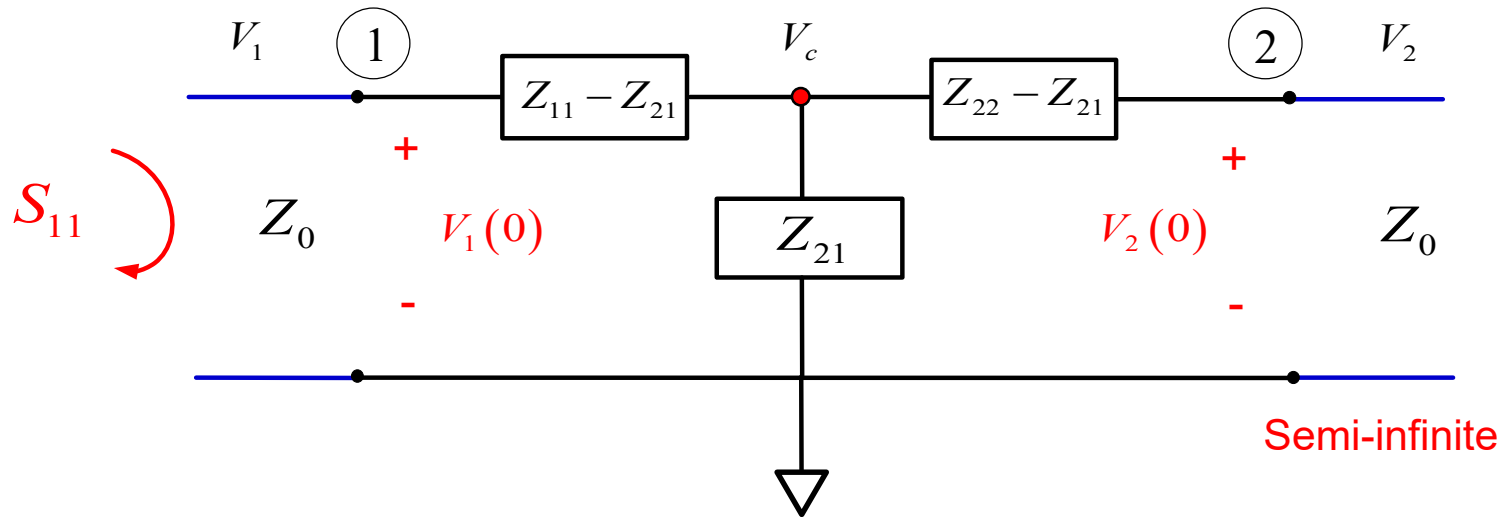

Assume $V_1^+(0) = 1$ [V]


$$V_1(0) = 1 + S_{11}$$

$$\Rightarrow S_{21} = V_2^-(0) = V_2(0)$$

Use voltage divider equation twice to get $V_2(0)$: $V_1(0) \rightarrow V_c \rightarrow V_2(0)$

Example (cont.)

$$V_1(0) = 1 + S_{11}$$

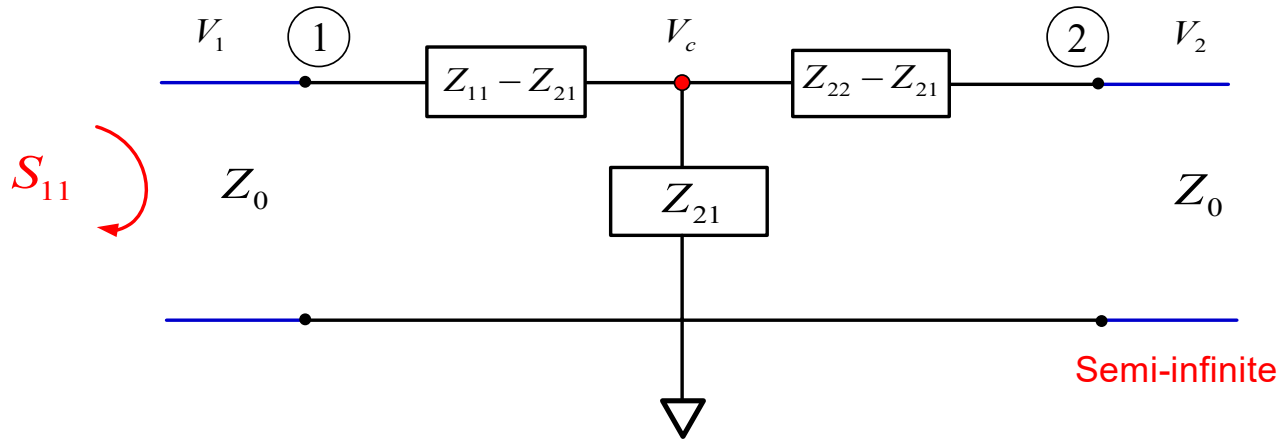


Use voltage divider equation twice:

$$V_c = V_1(0) \left(\frac{(Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]}{(Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]} \right)$$

$$V_2(0) = V_c \left(\frac{Z_0}{(Z_{22} - Z_{21}) + Z_0} \right)$$

Example (cont.)

$$V_1(0) = 1 + S_{11}$$

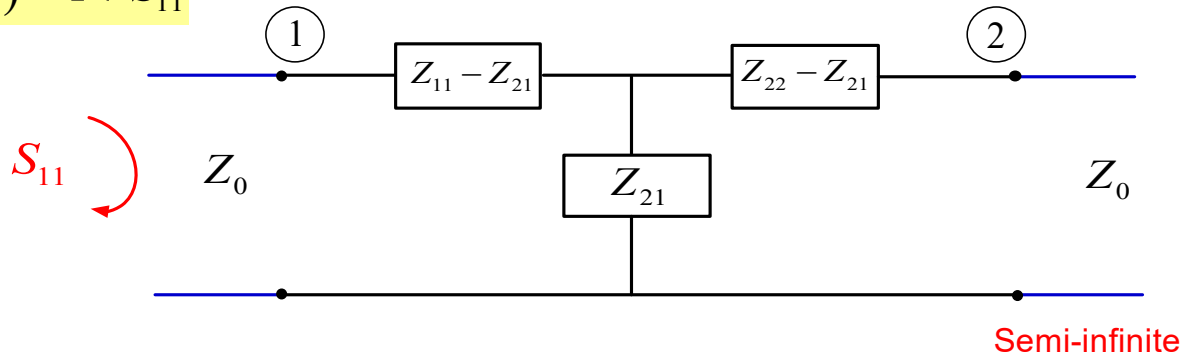

Hence

$$S_{21} = V_2(0) = (1 + S_{11}) \left(\frac{(Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]}{(Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]} \right) \left(\frac{Z_0}{(Z_{22} - Z_{21}) + Z_0} \right)$$

where

$$1 + S_{11} = 1 + \frac{(Z_0 + Z_{22})(Z_{11} - Z_0) - Z_{21}^2}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}$$

Example (cont.)

Our result:

$$S_{21} = (1 + S_{11}) \left(\frac{(Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]}{(Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]} \right) \left(\frac{Z_0}{(Z_{22} - Z_{21}) + Z_0} \right)$$

where

$$1 + S_{11} = 1 + \frac{(Z_0 + Z_{22})(Z_{11} - Z_0) - Z_{21}^2}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}$$

After simplifying, we should get the result in the table:

(You are welcome to check it!)

$$S_{21} = S_{21} = \frac{2Z_{12}Z_0}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}$$

This is the result in the table.

Example (cont.)

Different approach: Use the formula on slide 40:

$$[S] = \left(\frac{1}{Z_0} [Z] - [U] \right) \left([U] + \frac{1}{Z_0} [Z] \right)^{-1}$$

so

$$[S] = \left([\bar{Z}] - [U] \right) \left([U] + [\bar{Z}] \right)^{-1}$$

where

$$[\bar{Z}] \equiv \frac{1}{Z_0} [Z]$$

Hence, for a two-port, we have

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \left(\begin{bmatrix} \bar{Z}_{11} - 1 & \bar{Z}_{12} \\ \bar{Z}_{21} & \bar{Z}_{22} - 1 \end{bmatrix} \right) \left(\begin{bmatrix} \bar{Z}_{11} + 1 & \bar{Z}_{12} \\ \bar{Z}_{21} & \bar{Z}_{22} + 1 \end{bmatrix} \right)^{-1}$$

Example (cont.)

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \left(\begin{bmatrix} \bar{Z}_{11} - 1 & \bar{Z}_{12} \\ \bar{Z}_{21} & \bar{Z}_{22} - 1 \end{bmatrix} \right) \left(\begin{bmatrix} \bar{Z}_{11} + 1 & \bar{Z}_{12} \\ \bar{Z}_{21} & \bar{Z}_{22} + 1 \end{bmatrix} \right)^{-1}$$

Hence,

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \left(\begin{bmatrix} \bar{Z}_{11} - 1 & \bar{Z}_{12} \\ \bar{Z}_{21} & \bar{Z}_{22} - 1 \end{bmatrix} \right) \left(\begin{bmatrix} \bar{Z}_{22} + 1 & -\bar{Z}_{12} \\ -\bar{Z}_{21} & \bar{Z}_{11} + 1 \end{bmatrix} \frac{1}{\Delta} \right)$$

where


$$\Delta = \text{determinant} = (\bar{Z}_{11} + 1)(\bar{Z}_{22} + 1) - \bar{Z}_{21}\bar{Z}_{12}$$

This gives us directly the components of the S matrix.

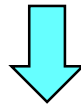Example (cont.)

Examining the components, we have:

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \left(\begin{bmatrix} \bar{Z}_{11} - 1 & \bar{Z}_{12} \\ \bar{Z}_{21} & \bar{Z}_{22} - 1 \end{bmatrix} \right) \left(\begin{bmatrix} \bar{Z}_{22} + 1 & -\bar{Z}_{12} \\ -\bar{Z}_{21} & \bar{Z}_{11} + 1 \end{bmatrix} \frac{1}{\Delta} \right)$$



$$S_{11} = \frac{1}{\Delta} \left((\bar{Z}_{11} - 1)(\bar{Z}_{22} + 1) - \bar{Z}_{12}\bar{Z}_{21} \right)$$

$$S_{12} = \frac{1}{\Delta} \left(-(\bar{Z}_{11} - 1)\bar{Z}_{12} + \bar{Z}_{12}(\bar{Z}_{11} + 1) \right)$$

$$S_{21} = \frac{1}{\Delta} \left(-(\bar{Z}_{22} - 1)\bar{Z}_{21} + \bar{Z}_{21}(\bar{Z}_{22} + 1) \right)$$

$$S_{22} = \frac{1}{\Delta} \left((\bar{Z}_{11} + 1)(\bar{Z}_{22} - 1) - \bar{Z}_{12}\bar{Z}_{21} \right)$$

Example (cont.)

Simplifying the terms S_{12} and S_{21} , we have:

$$S_{11} = \frac{1}{\Delta} \left((\bar{Z}_{11} - 1)(\bar{Z}_{22} + 1) - \bar{Z}_{12}\bar{Z}_{21} \right)$$

$$S_{12} = \frac{1}{\Delta} (2\bar{Z}_{12})$$

$$S_{21} = \frac{1}{\Delta} (2\bar{Z}_{21})$$

$$S_{22} = \frac{1}{\Delta} \left((\bar{Z}_{11} + 1)(\bar{Z}_{22} - 1) - \bar{Z}_{12}\bar{Z}_{21} \right)$$


This agrees with the table.

| Z |
|--|
| $\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$ |
| $\frac{2Z_{12}Z_0}{\Delta Z}$ |
| $\frac{2Z_{21}Z_0}{\Delta Z}$ |
| $\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$ |
| $\Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}$ |

Signal-Flow Graph

This is a way to graphically represent the S parameters.

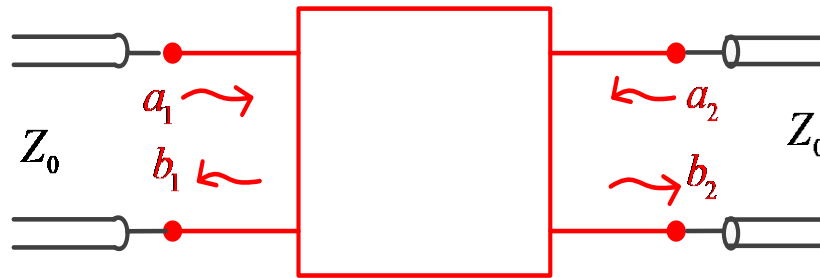Please see the Pozar book for more details.




The wave amplitudes are represented as nodes in the single-flow graph.

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

(wave amplitudes evaluated at $z_i = 0$)

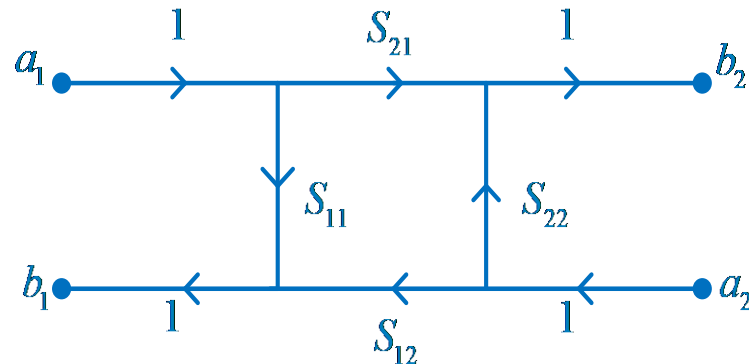

Rule: The value at each node is the sum of the values coming into the node from the various other nodes.