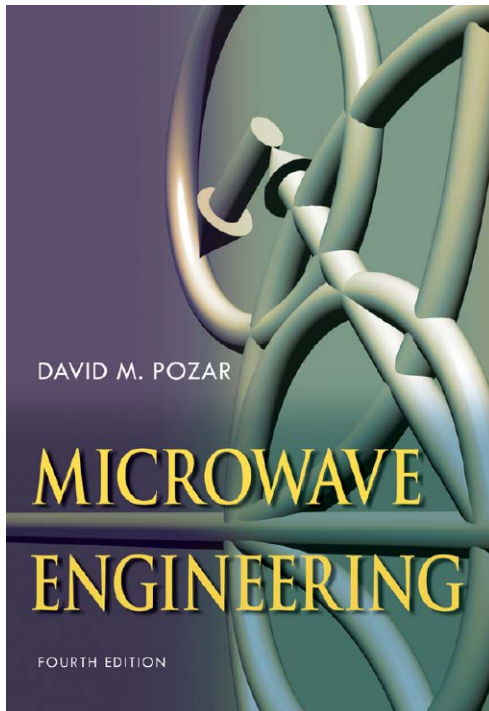


ECE 5317-6351

Microwave Engineering


Fall 2019

Prof. David R. Jackson
Dept. of ECE




Notes 18

Impedance Matching

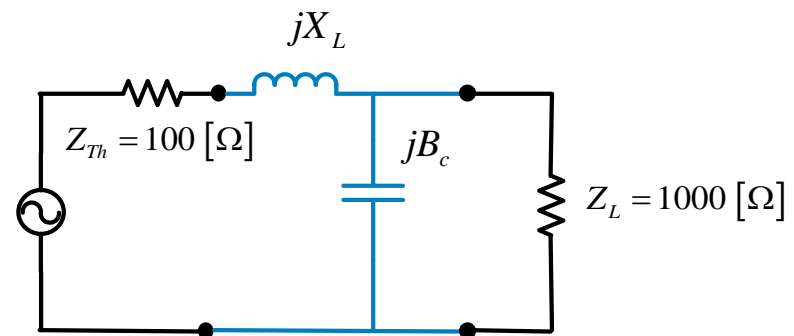

Impedance Matching

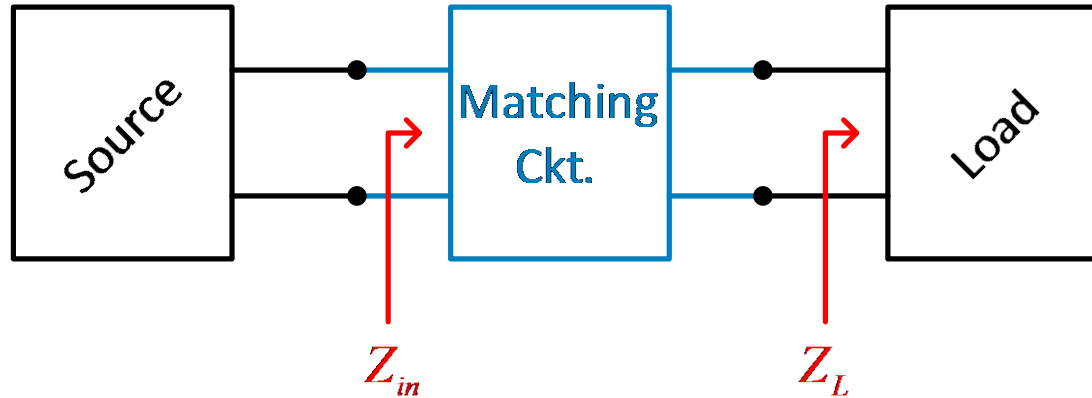

Impedance matching is used to:

- Maximize power from source to load
- Minimize reflections

We have $Z_L = R_L + jX_L$

We want $Z_{in} = R_{in} + jX_{in}$

↑
(usually zero)

Considerations:


- Complexity
- Bandwidth
- Implementation
- Adjustability



Two constraints

A matching circuit typically requires at least 2 degrees of freedom.

Impedance Matching (cont.)


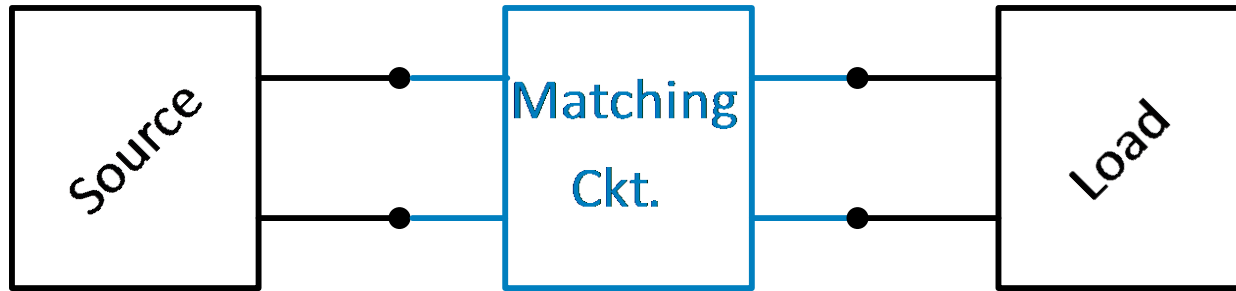


Matching Methods:

- 1) Lumped element matching circuits
- 2) Transmission line matching circuits
- 3) Quarter-wave impedance transformers


Lumped-Element Matching Circuits

Examples

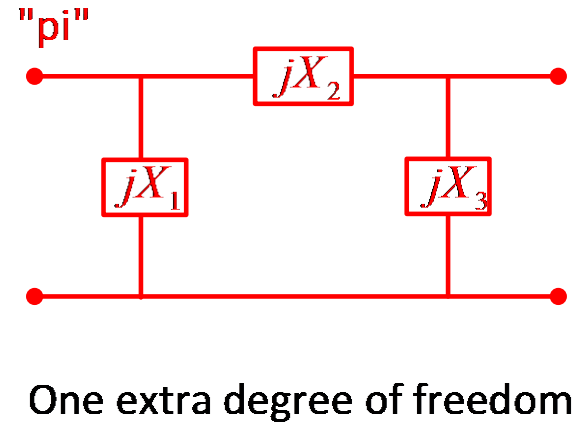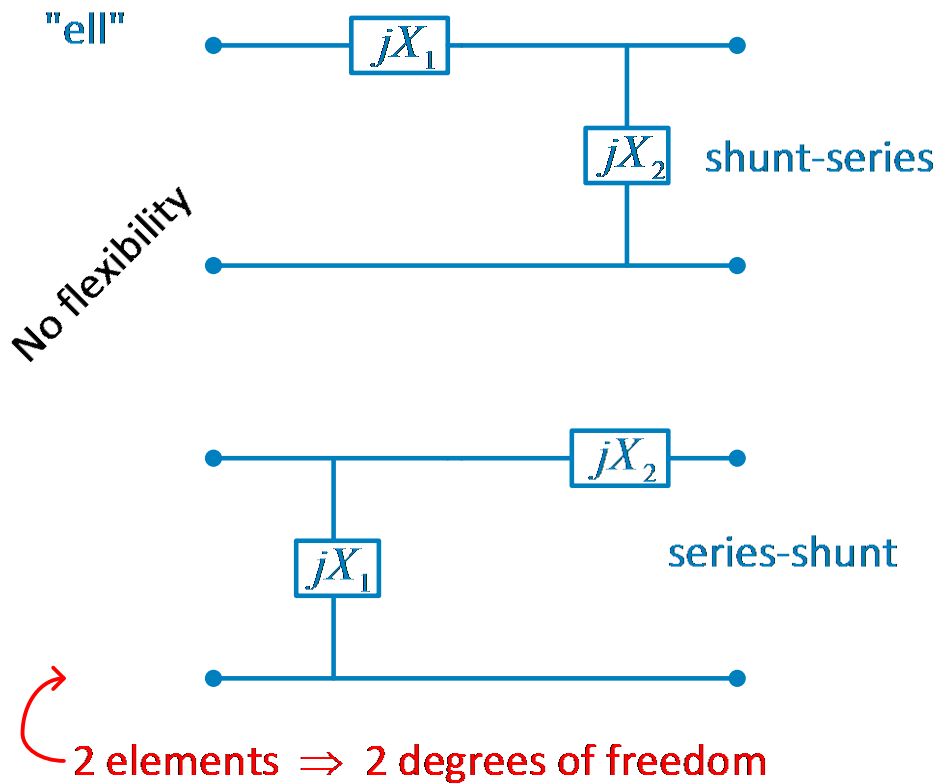


Lumped-Element Matching Circuits (cont.)

“tee”

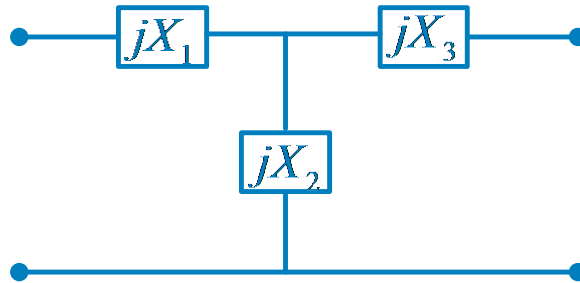

One extra degree of freedom

“ladder”

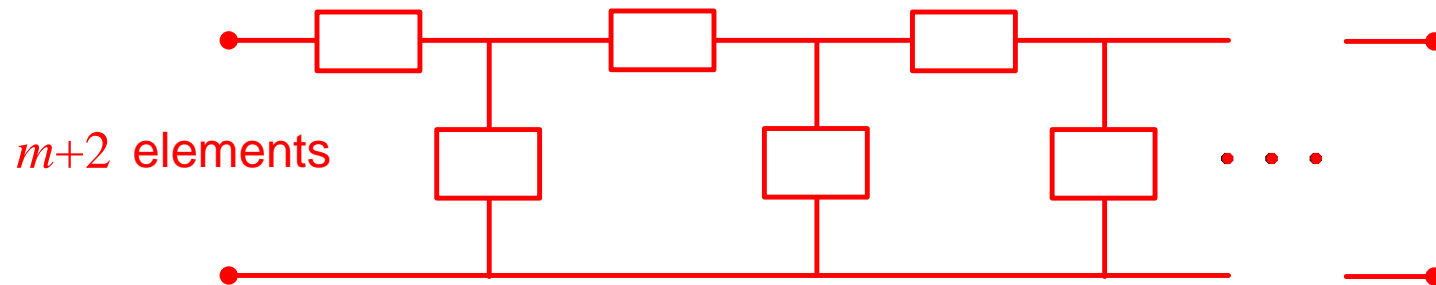


$m+2$ elements

m extra degrees of freedom


Smith Chart Review

Smith Chart
(Z-Chart)

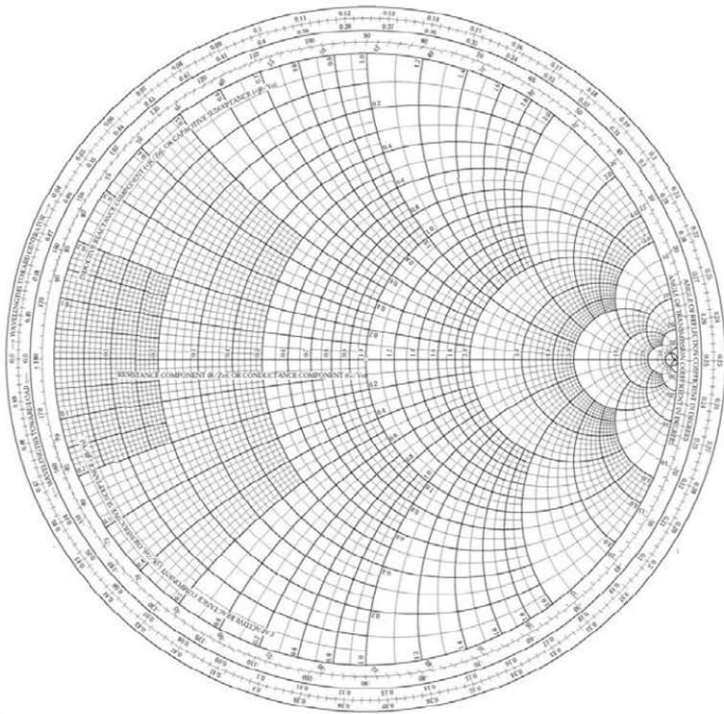

Γ plane

Short-hand version

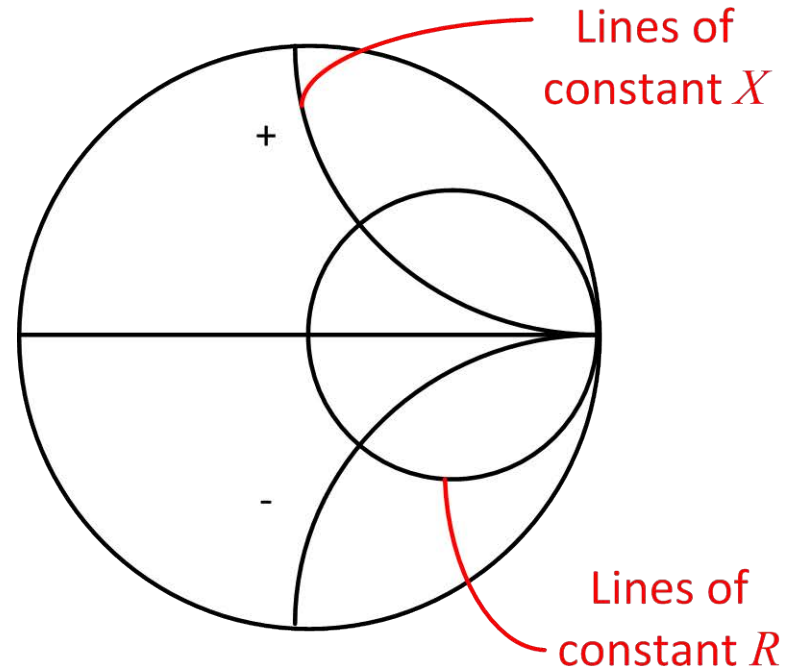


Lines of
constant X

Lines of
constant R


Smith Charts Review (cont.)

Smith Chart
(Y-Chart)

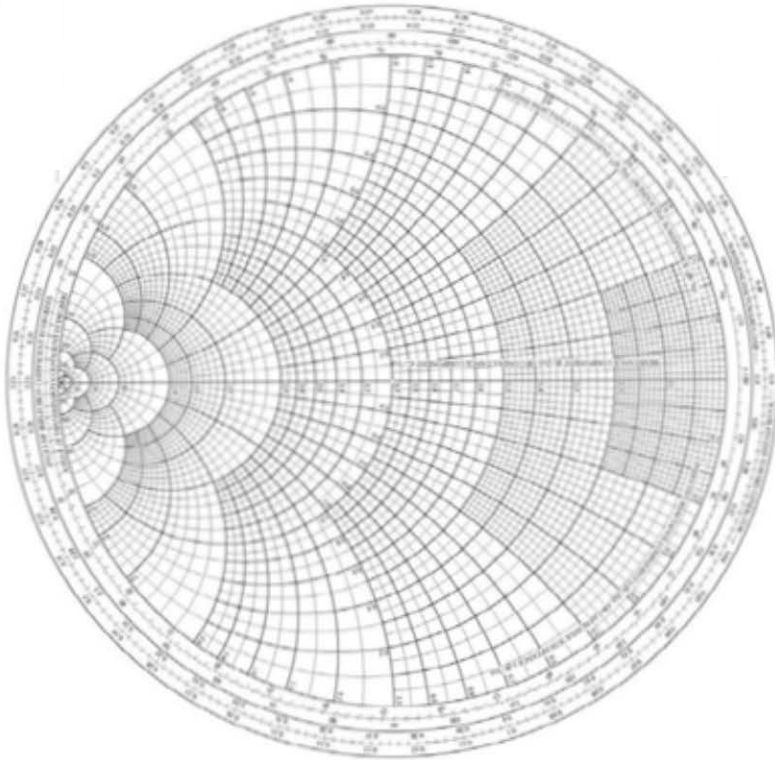

Γ plane

Lines of constant B

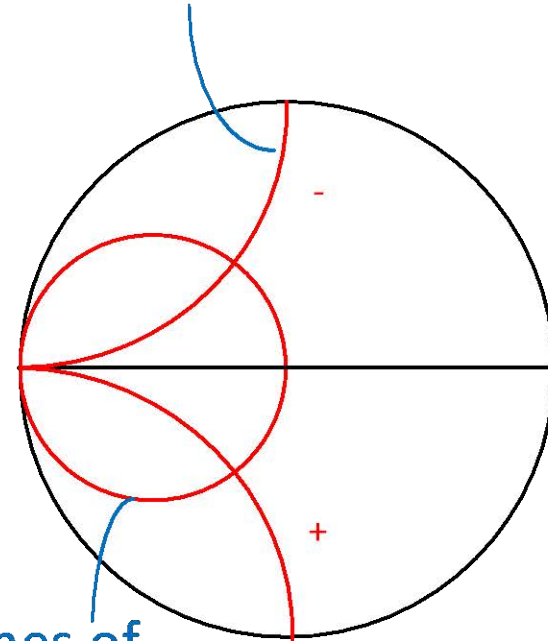


Lines of
constant G


Smith Charts Review (cont.)

ZY- Chart

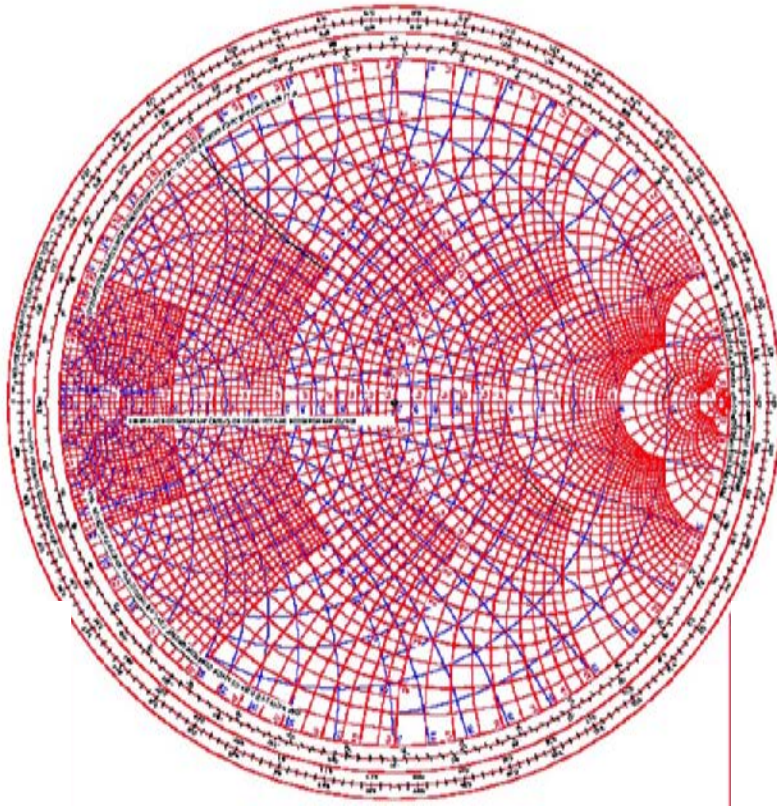NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES




Γ plane

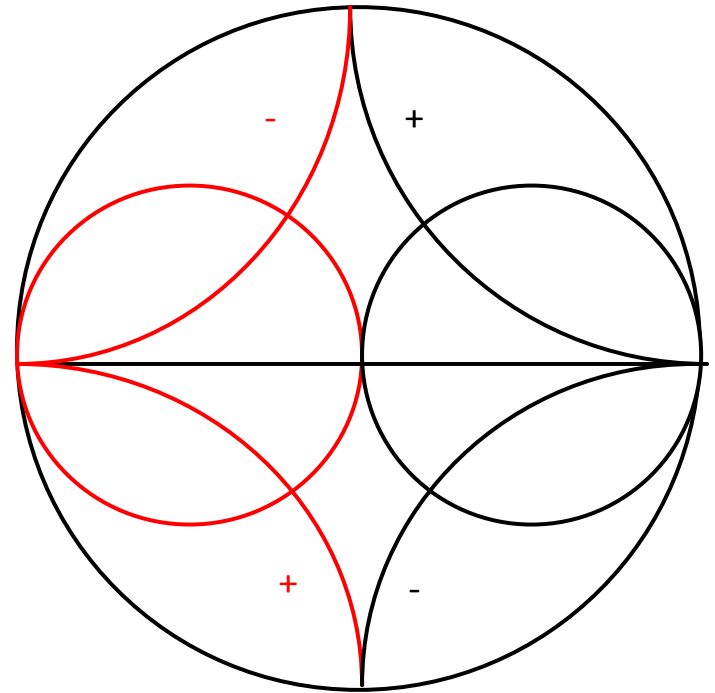

Series and Shunt Elements

Γ plane

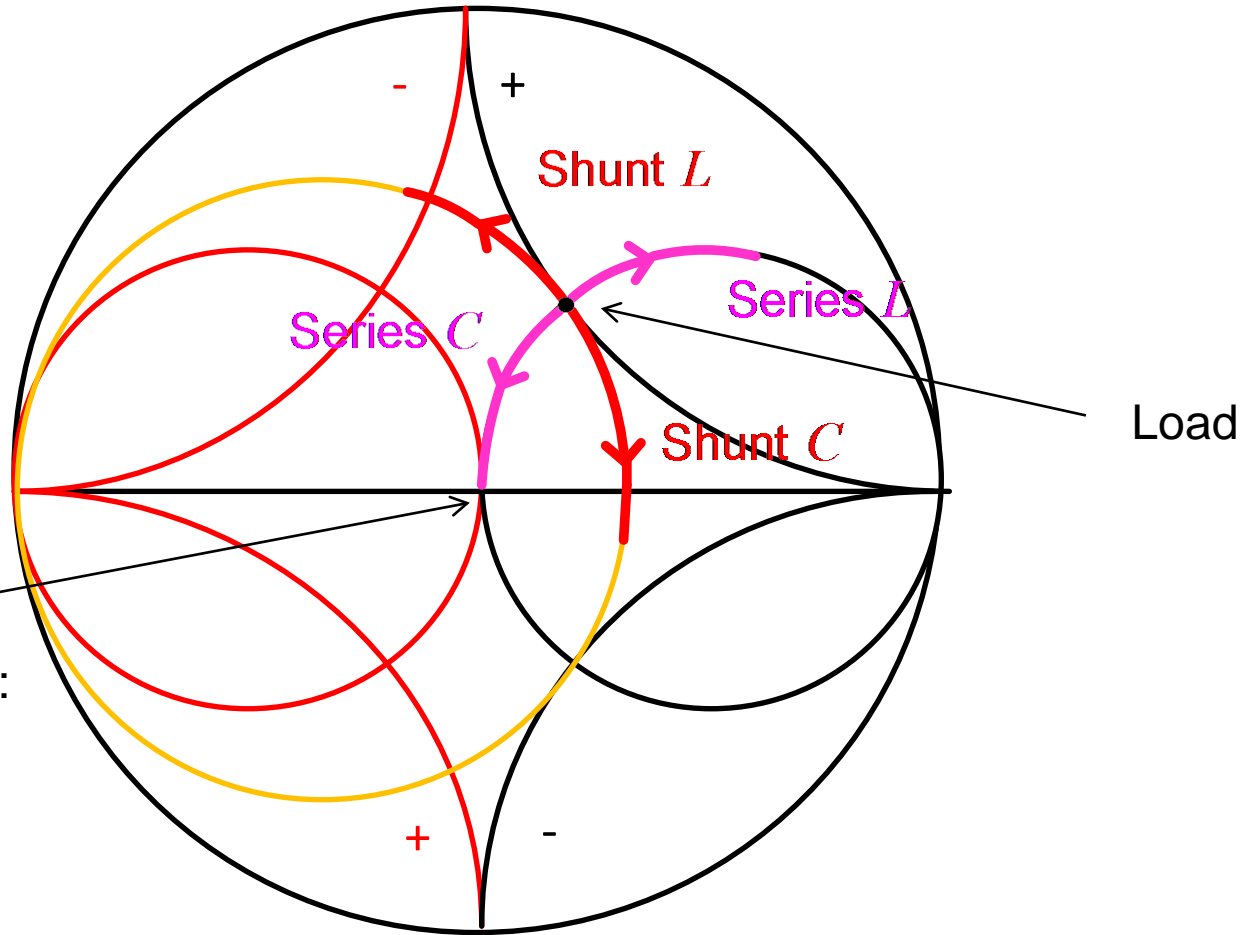

Center of Smith chart:

$$Z = Z_0, Y = Y_0 = 1/Z_0$$

$$Z_0 \equiv Z_{in}$$


Note:

The Smith chart is not actually being used as a transmission-line calculator but an impedance/admittance calculator. Hence, the normalizing impedance Z_0 is arbitrary. (Usually we choose it to be the desired input resistance R_{in} .)

High Impedance to Low Impedance


Use when $G_L < Y_{in}$

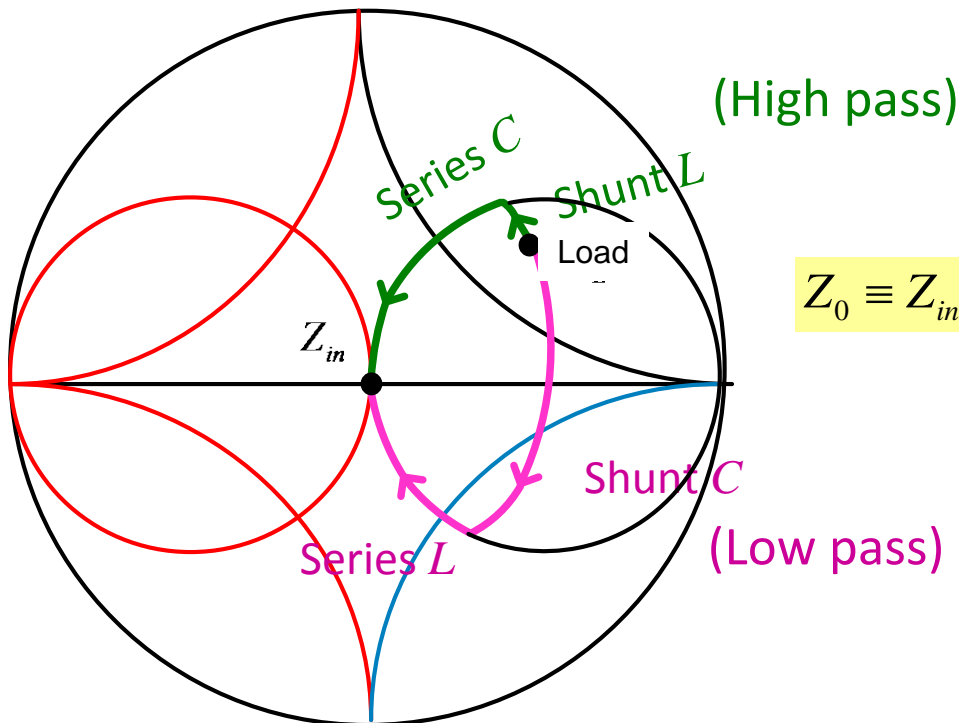(The load is outside of the red $G = 1$ circle.)



$$Z_0 \equiv Z_{in}$$

Shunt-series "ell"

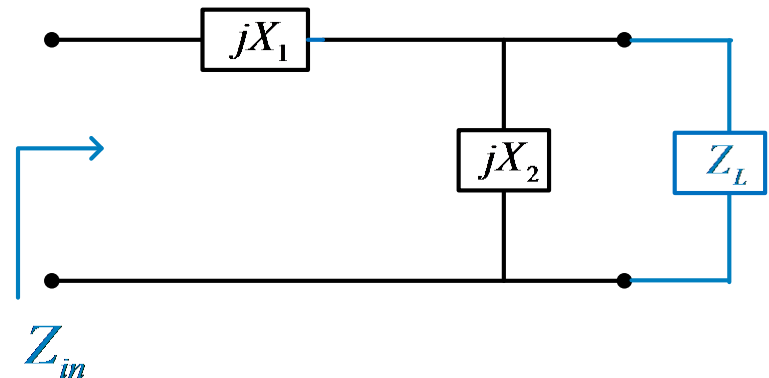


Two possibilities

The shunt element puts us on the $R = 1$ circle; the series element is used to "tune out" the unwanted reactance.

Low Impedance to High Impedance


Use when $R_L < R_{in}$

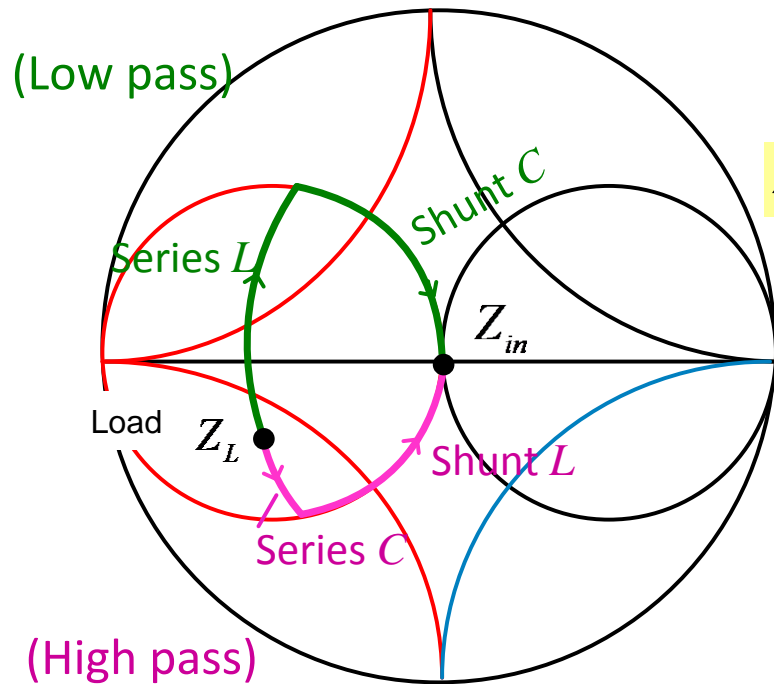(The load is outside of the black $R = 1$ circle.)



$$Z_0 \equiv Z_{in}$$

Series-shunt "ell"

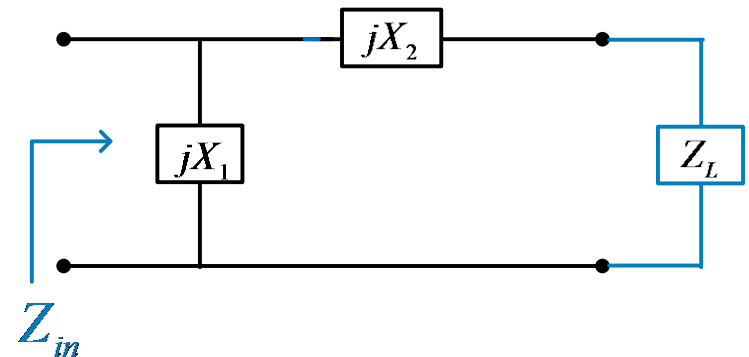

Two possibilities

The series element puts us on the $G = 1$ circle; the shunt element is used to "tune out" the unwanted susceptance.


Example

Use high impedance to low impedance matching.


We want $Z_{in} = 100 [\Omega]$

Choose normalizing impedance $100 [\Omega]$

IMPEDANCE AND ADMITTANCE COORDINATES

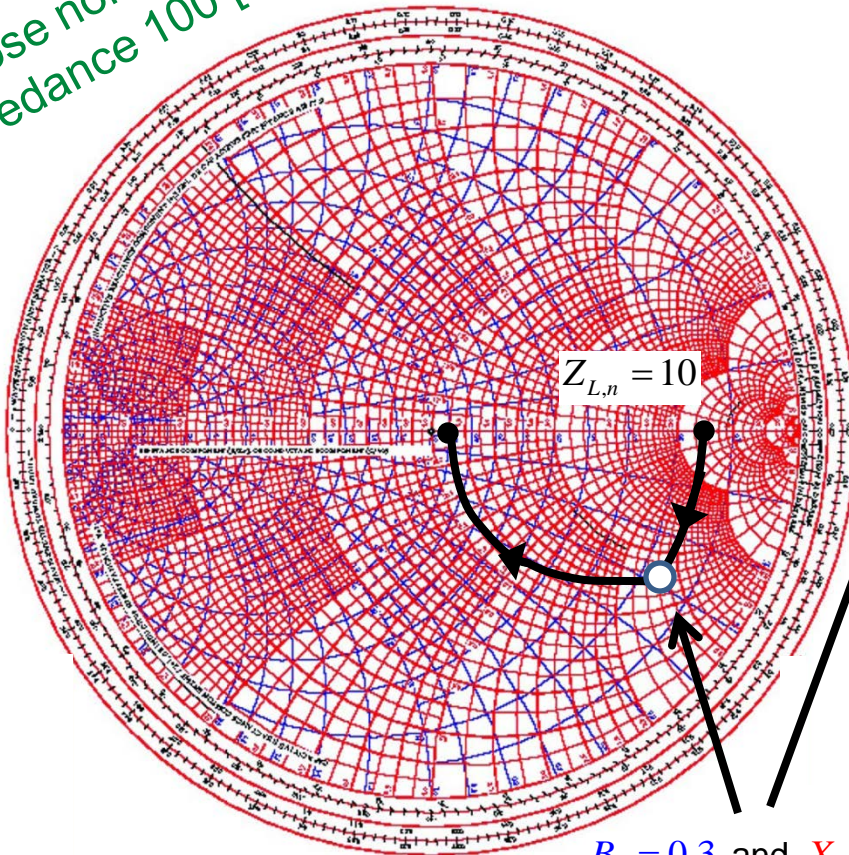

$B_n = 0.3$ and $X_n = -3.0$

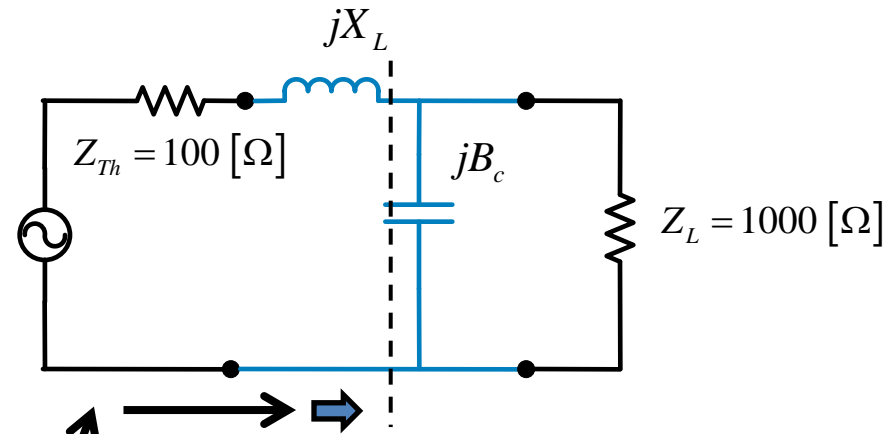

$$B_{C,n} = 0.3 \Rightarrow B_C = \frac{0.3}{100[\Omega]} = 3 \text{ [mS]}$$

$$X_C = -1/B_C = -333 [\Omega] \quad \left(X_C = -\frac{1}{\omega C} \right)$$



$$X_{L,n} = -X_n = 3 \Rightarrow X_L = 3(100[\Omega])$$

$$X_L = 300 [\Omega] \quad (X_L = \omega L)$$

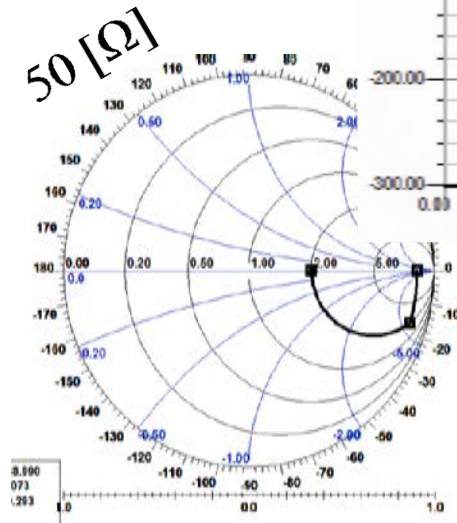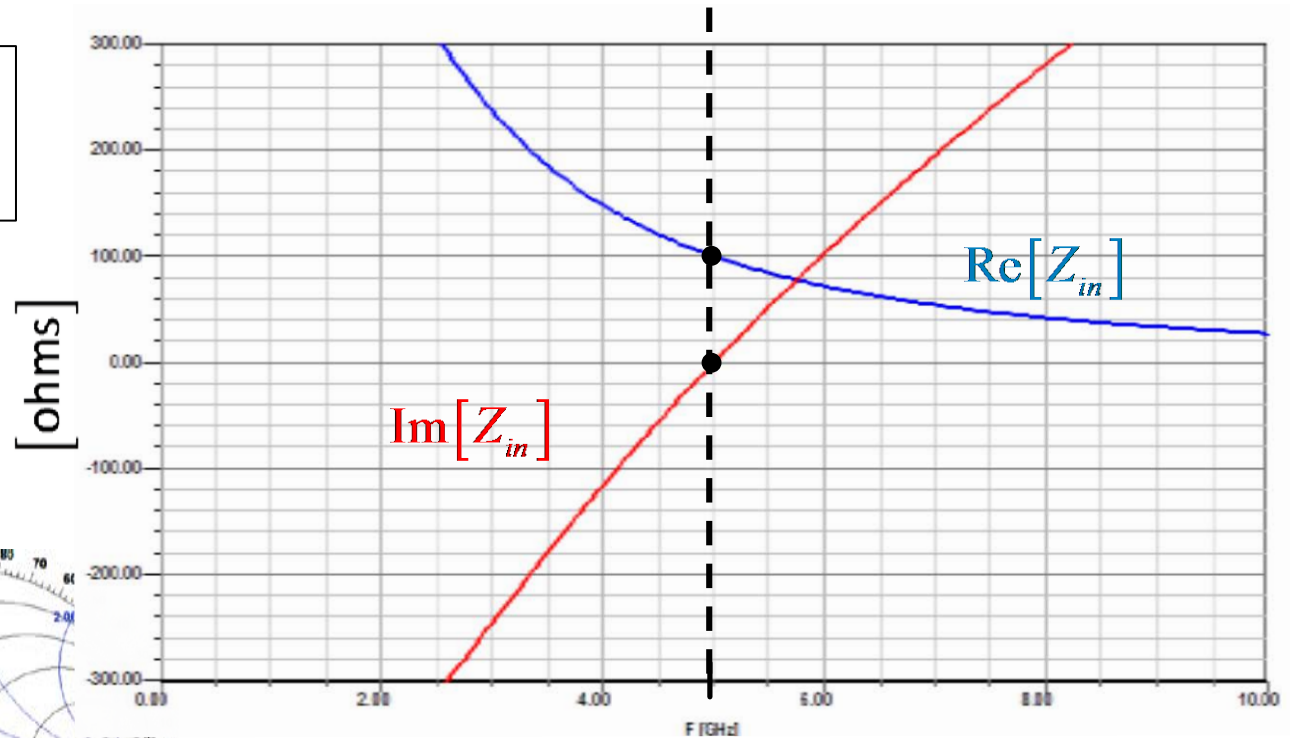Example (cont.)

Here, the design example was repeated using a 50 [Ω] normalizing impedance.

Note that the final normalized input impedance is 2.0.




5 GHz design frequency


$C = 0.096$ [pF]

$L = 9.55$ [nH]

Matching with a Pi Network

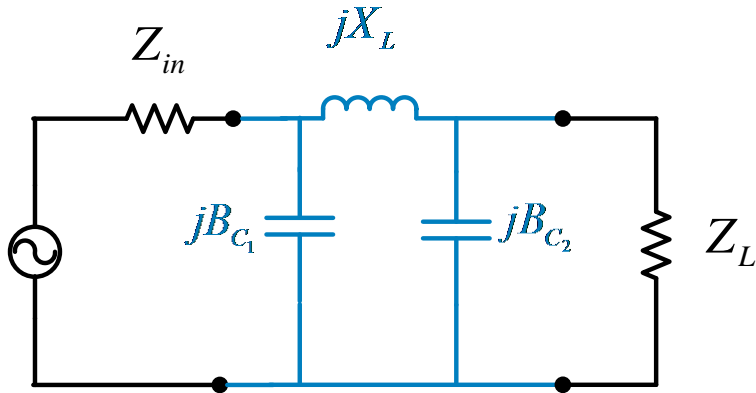

This works for low-high or high-low.

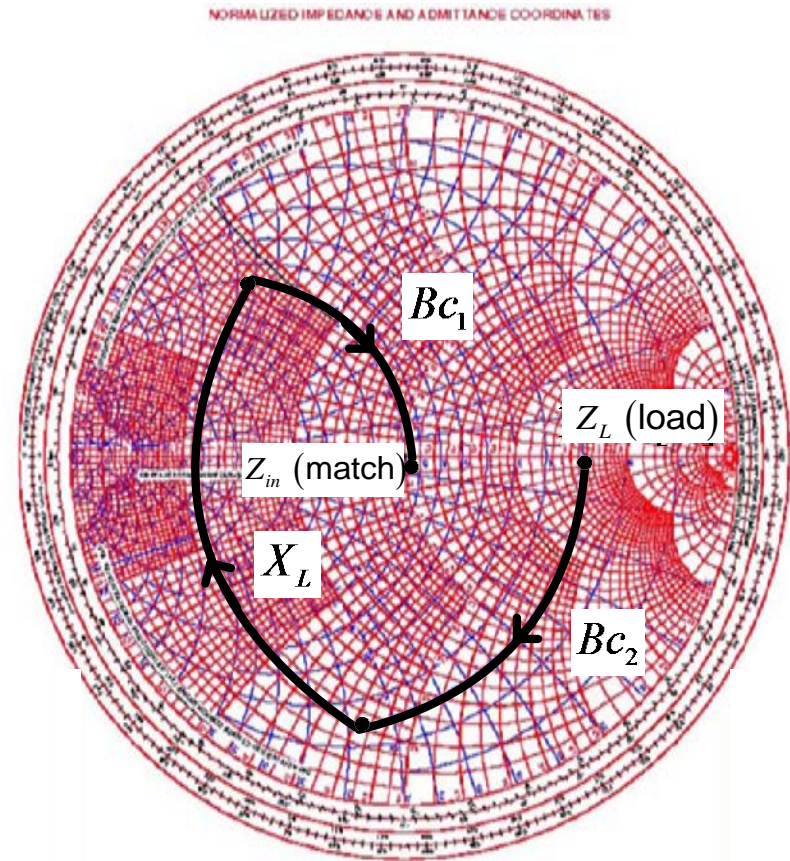

Note:

This solution is *not unique*. Different values for B_{C_2} could have been chosen.



Note:

We could have also used parallel inductors and a series capacitor, or other combinations.


Pi Network Example

(1000 Ω \rightarrow 100 Ω)

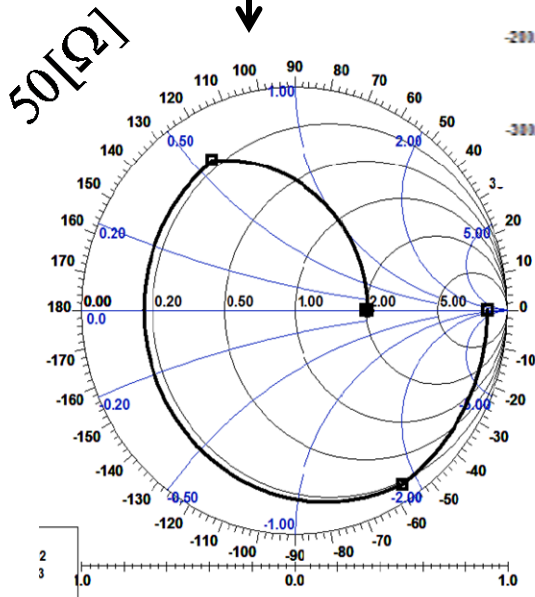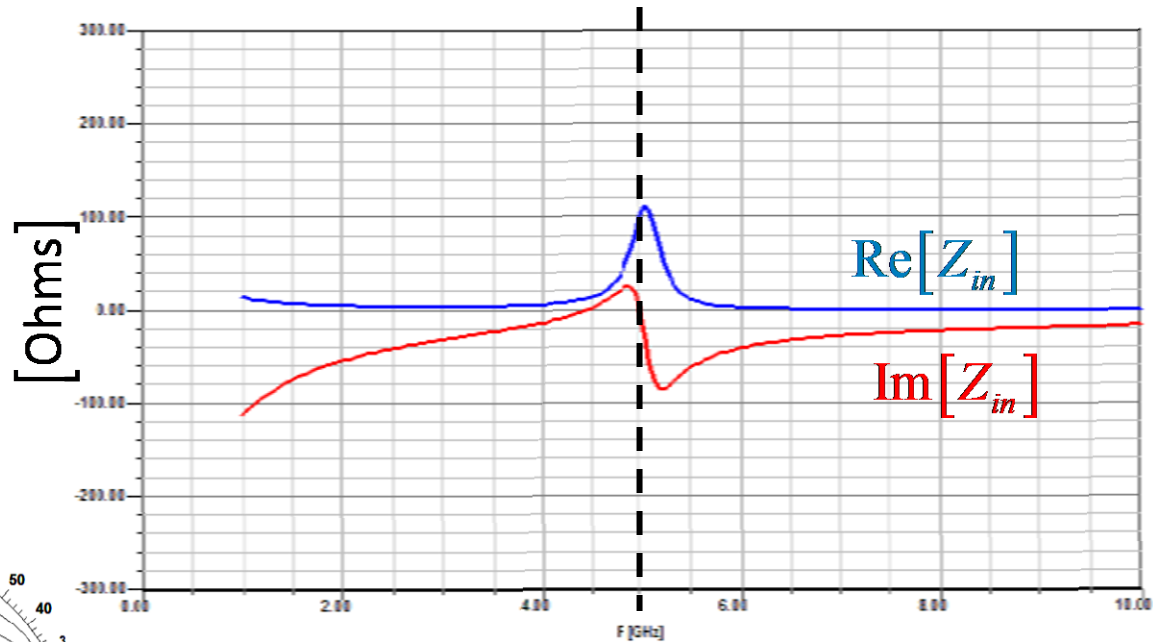Note that the final normalized input impedance is 2.0.



Design frequency = 5GHz

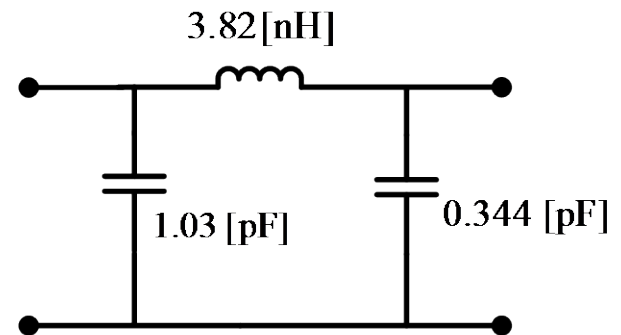

High Impedance to Low Impedance


Exact Solution

$$R_L > R_{in}$$

$$G_L = 1 / R_L$$

$$B_2 = -1 / X_2$$


Shunt-series "ell"

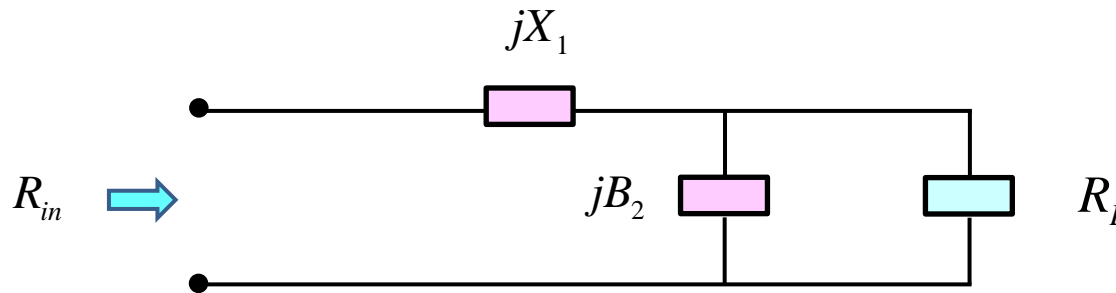

$$\operatorname{Re}\left(\frac{1}{G_L + jB_2}\right) = R_{in}$$




$$\frac{G_L}{G_L^2 + B_2^2} = R_{in}$$

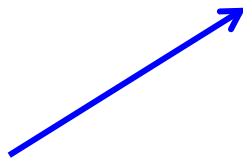

$$\frac{G_L^2 + B_2^2}{G_L} = G_{in}$$



$$G_L + \frac{B_2^2}{G_L} = G_{in}$$

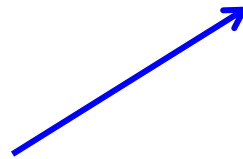

$$B_2 = \pm \sqrt{G_L (G_{in} - G_L)}$$

Then we choose:

$$X_1 = -\operatorname{Im}\left(\frac{1}{G_L + jB_2}\right) = \frac{B_2}{G_L^2 + B_2^2}$$

High Impedance to Low Impedance


Exact Solution

$$R_L > R_{in}$$

Summary

$$G_L = 1 / R_L$$

$$B_2 = -1 / X_2$$

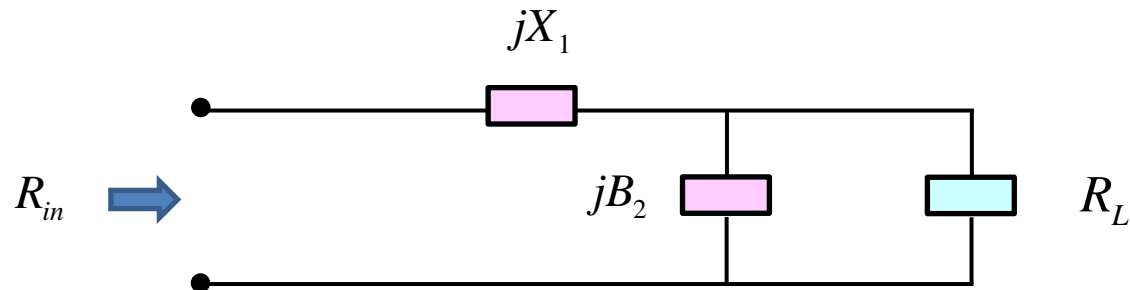

$$B_2 = \pm \sqrt{G_L (G_{in} - G_L)}$$

$$X_1 = \frac{B_2}{G_L^2 + B_2^2}$$

Transmission Line Matching


❖ Single-stub matching

- This has already been discussed.

❖ Double-stub matching

- This is an alternative matching method that gives more flexibility (details omitted – please see the Pozar book).

Quarter-Wave Transformer

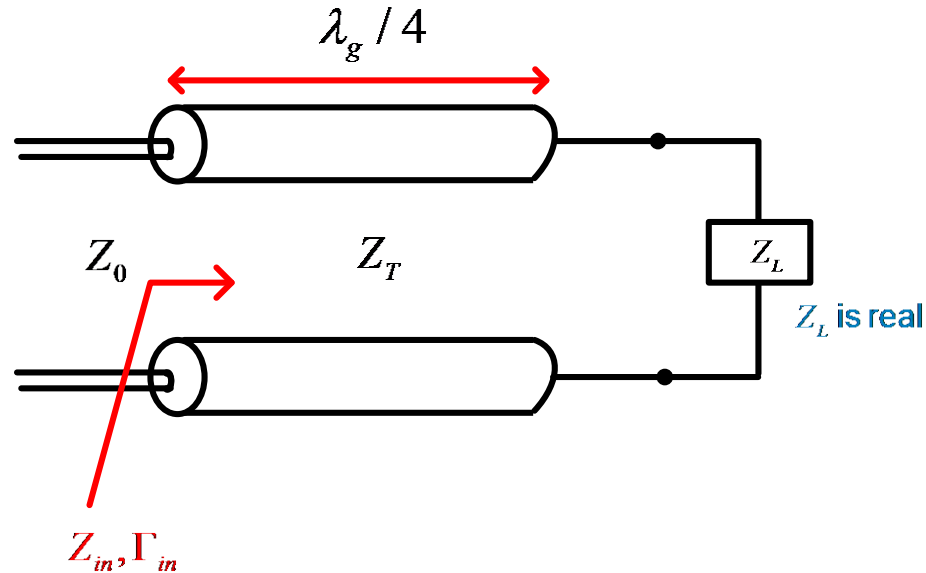

$$\text{@ } f = f_0$$

$$\beta l = \frac{2\pi}{\lambda_g} \frac{\lambda_g}{4} = \frac{\pi}{2}$$

$$\Rightarrow Z_{in} = \frac{Z_T^2}{Z_L}$$

$$\Gamma_{in} = 0 \quad \text{when} \quad Z_T = \sqrt{Z_0 Z_L}$$

Only true at f_0 where $l = \lambda_g / 4$

Note:

If Z_L is not real, we can always add a reactive load in series or parallel to make it real (or add a length of transmission line between the load and the transformer to get a real impedance).

Quarter-Wave Transformer (cont.)

At a general frequency:

$$\begin{aligned} Z_{in} &= Z_T \left(\frac{Z_L + jZ_T \tan \beta_T \ell}{Z_T + jZ_L \tan \beta_T \ell} \right) \\ &= Z_T \left(\frac{Z_L + jZ_T t}{Z_T + jZ_L t} \right) \quad t \equiv \tan \beta_T \ell \end{aligned}$$

After some algebra (omitted):

$$\Gamma = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_L - Z_0}{Z_L + Z_0 + j2t\sqrt{Z_0 Z_L}}$$

where we have used $Z_T = \sqrt{Z_0 Z_L}$

Quarter-Wave Transformer (cont.)


$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0 + j2t\sqrt{Z_0 Z_L}}$$

After some more algebra (omitted):

$$|\Gamma| = \frac{1}{\sqrt{1 + \left(\frac{4Z_0 Z_L}{(Z_L - Z_0)^2} \sec^2 \theta \right)}} \quad \theta \equiv \beta_T \ell$$

where we used $1 + t^2 = 1 + \tan^2 \beta_T l = \sec^2 \beta_T l = \sec^2 \theta$

Quarter-Wave Transformer (cont.)

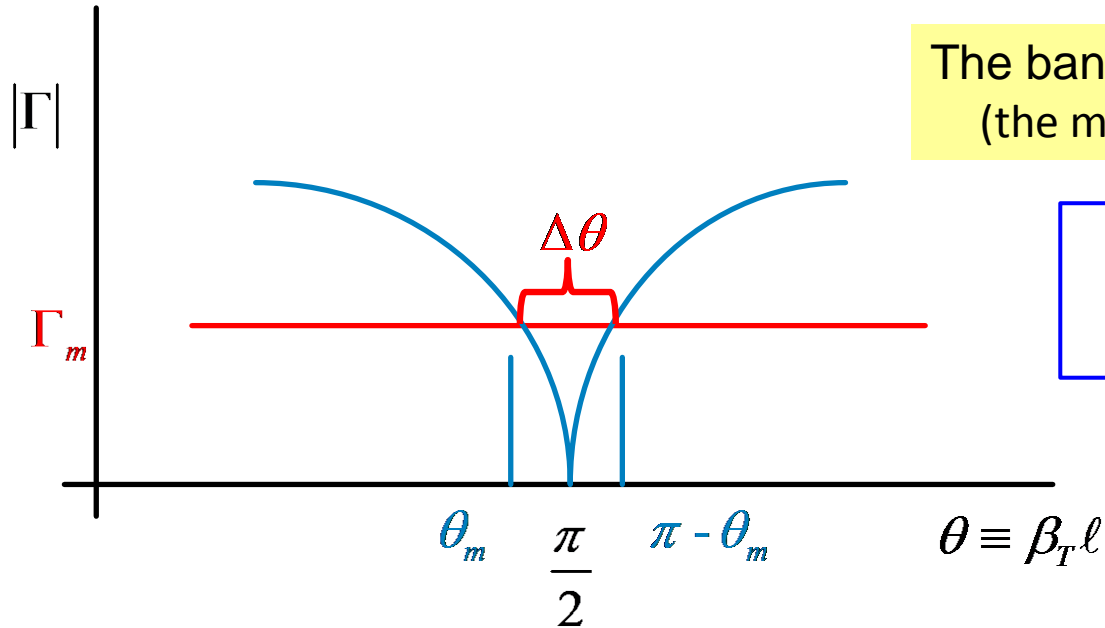

The bandwidth is defined by the limit Γ_m (the maximum acceptable value of Γ).

For example, using $\Gamma_m = 1/3$ corresponds to $\text{SWR} = 2.0$. This corresponds to $\Gamma_m = -9.54$ dB.

We set:

Bandwidth region of transformer:

$$\Delta\theta = (\beta_{2T} - \beta_{1T}) \ell = 2 \left(\frac{\pi}{2} - \theta_m \right)$$

$$\Gamma_m = \frac{1}{\sqrt{1 + \left[\frac{4Z_0 Z_L}{(Z_L - Z_0)^2} \sec^2 \theta_m \right]}}$$

Solving for θ_m :

$$\theta_m = \cos^{-1} \left(\frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \right) \frac{2\sqrt{Z_0 Z_L}}{|Z_L - Z_0|}$$

← Solve for θ_m

Note: $\cos^{-1} x \in (0, \pi/2)$

Quarter-Wave Transformer (cont.)

For TEM lines:

$$\theta = \beta_T l = \frac{\pi}{2} \frac{f}{f_0} \quad \Rightarrow \quad f = \theta \left(\frac{2f_0}{\pi} \right)$$

$$\Rightarrow f_m = \theta_m \left(\frac{2f_0}{\pi} \right)$$

$$\Rightarrow \text{BW} = \frac{\Delta f}{f_0} = \frac{2(f_0 - f_m)}{f_0} = 2 - \frac{2f_m}{f_0} = 2 - \frac{4\theta_m}{\pi} \quad (\text{relative bandwidth})$$

$$\text{BW} = 2 - \frac{4\theta_m}{\pi}$$


Note:
Multiply by 100 to get BW
in percent.

Hence, using θ_m from the previous slide,

$$\text{BW} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_0 Z_L}}{|Z_L - Z_0|} \right]$$

Quarter-Wave Transformer (cont.)

Summary

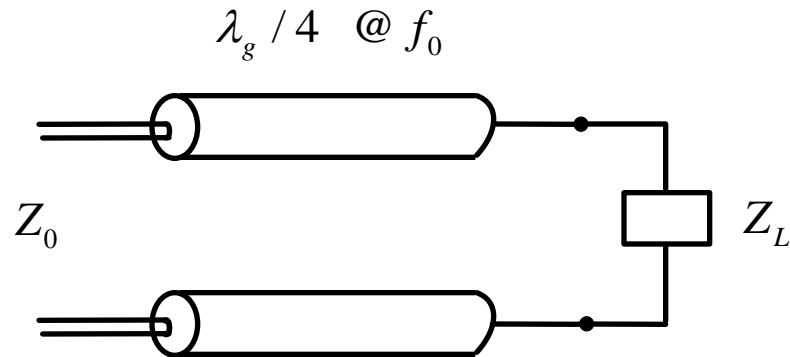


$$BW = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_0 Z_L}}{|Z_L - Z_0|} \right]$$

Smaller contrast between Z_0 and $Z_L \Rightarrow$ larger BW

Larger contrast between Z_0 and $Z_L \Rightarrow$ smaller BW

Example

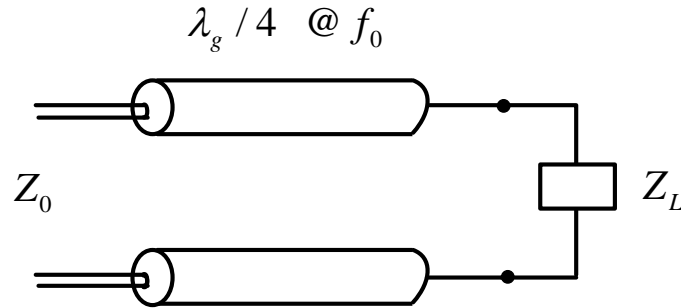

Given:

$$Z_L = 100 \text{ } [\Omega]$$

$$Z_0 = 50 \text{ } [\Omega]$$

We'll illustrate with two choices:

$$\Gamma_m = 1/3 \quad (\Gamma_m^{\text{dB}} = -9.54 \text{ [dB]}) \quad \Rightarrow \quad \text{BW} = 0.433 \text{ (43.3\%)}$$

$$\Gamma_m = 0.05 \quad (\Gamma_m^{\text{dB}} = -26.0 \text{ [dB]}) \quad \Rightarrow \quad \text{BW} = 0.060 \text{ (6.0\%)}$$

$$\text{BW} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_0 Z_L}}{|Z_L - Z_0|} \right]$$