

# ECE 5317-6351


# Microwave Engineering

**Fall 2019**

Prof. David R. Jackson  
Dept. of ECE

## Notes 21
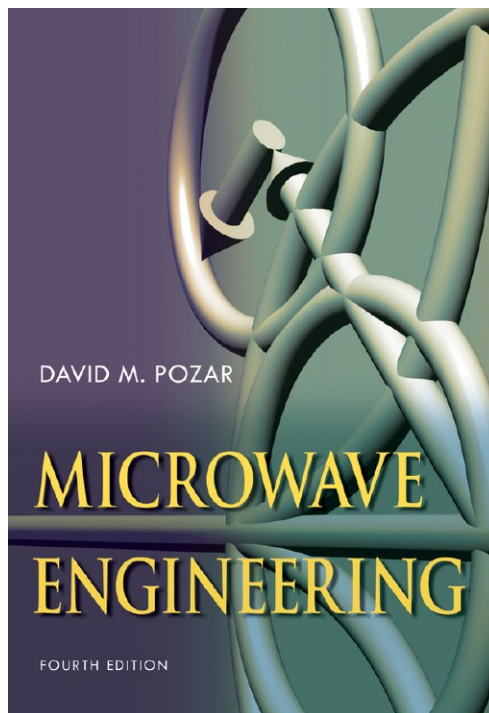
## Quadrature Coupler and Rat-Race Coupler




# Quadrature (90°) Coupler

“A quadrature coupler is one in which the input is split into two signals (usually with a goal of equal magnitudes) that are 90 degrees apart in phase. Types of quadrature couplers include branchline couplers (also known as quadrature hybrid\* couplers), Lange couplers and overlay couplers.”

Taken from “Microwaves 101”

[http://www.microwaves101.com/encyclopedia/Quadrature\\_couplers.cfm](http://www.microwaves101.com/encyclopedia/Quadrature_couplers.cfm)

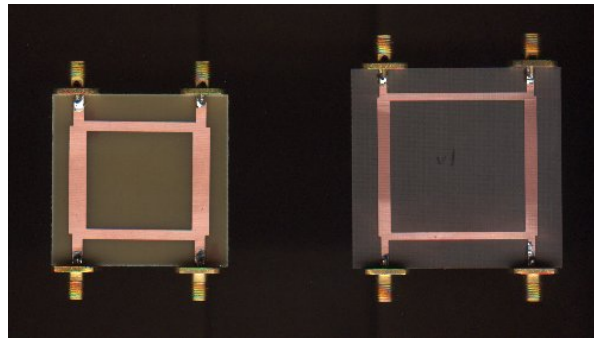
This coupler is very useful for obtaining circular polarization:  
There is a 90° phase difference between ports 2 and 3.



## Note:

The term “hybrid” denotes the fact that there is an equal (3 dB) power split to the output ports.

# Quadrature Coupler (cont.)

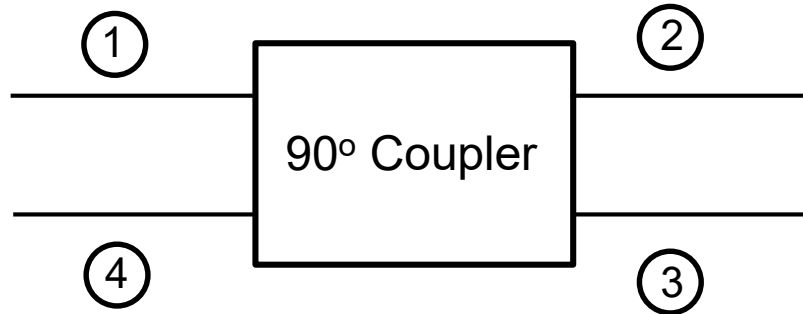


$$[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$

- The quadrature hybrid is a lossless 4-port (the  $S$  matrix is unitary ).
- All four ports are matched.
- The device is reciprocal (the  $S$  matrix is symmetric.)
- Port 4 is isolated from port 1, and ports 2 and 3 are isolated from each other.
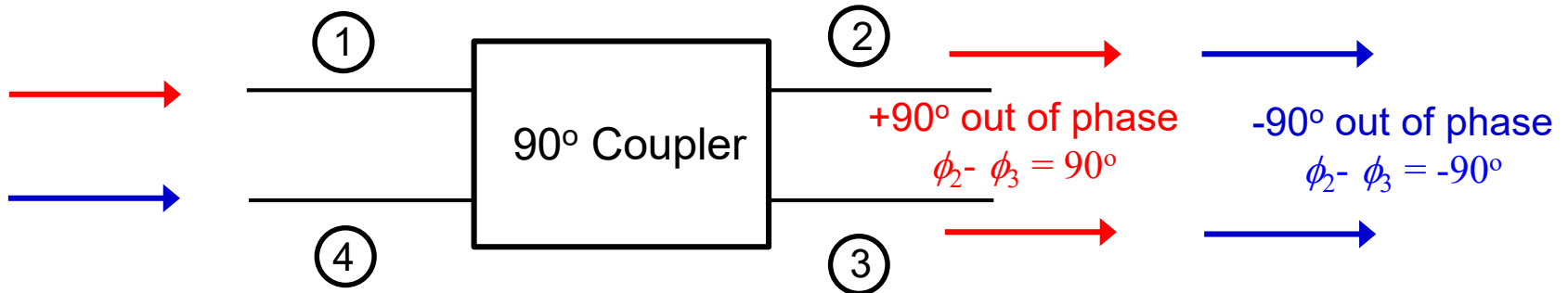
# Quadrature Coupler (cont.)

The quadrature coupler is usually used as a splitter:



**Note:** A matched load is usually placed on port 4.

- The signal from port 1 splits evenly between ports 2 and 3, with a 90° phase difference.

$$S_{21} = jS_{31}$$

Can be used to produce right-handed circular polarization.

- The signal from port 4 splits evenly between ports 2 and 3, with a -90° phase difference.


$$S_{24} = -jS_{34}$$

Can be used to produce left-handed circular polarization.

# Quadrature Coupler (cont.)
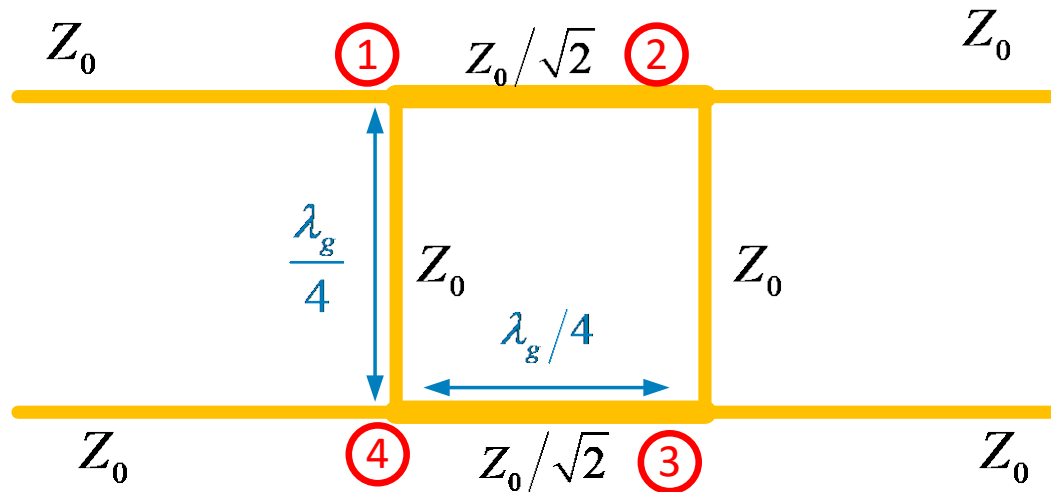
## Branch-Line Coupler

A microstrip realization of a quadrature hybrid (branch-line coupler) is shown here.




### Notes:

- We only need to study what happens when we excite port 1, since the structure is physically symmetric.
- We use even/odd mode analysis (exciting ports 1 and 4) to figure out what happens when we excite port 1.

**An analysis of the branch-line coupler is given in the Appendix.**

# Quadrature Coupler (cont.)

## Summary

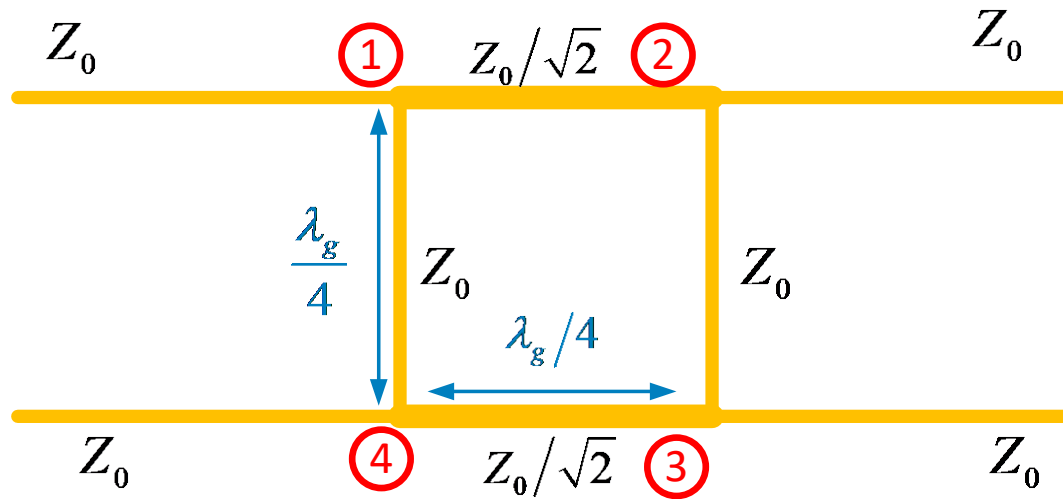

$$[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$


The input power to port 1 divides evenly between ports 2 and 3, with ports 2 and 3 being  $90^\circ$  out of phase.

**Note:** A matched load is usually placed on port 4.
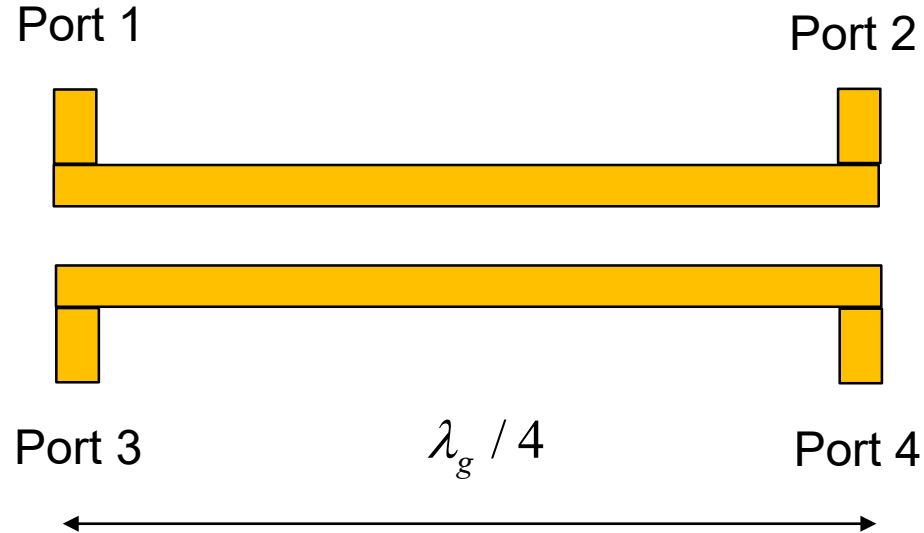
# Quadrature Coupler (cont.)

A coupled-line coupler is one that uses coupled lines (microstrip, stripline) with no direct connection between all of the ports.

Please see the Pozar book for more details.



This coupler has a  $90^\circ$  phase difference between the output ports (ports 2 and 3), and can be used to obtain an equal (-3 dB) power split or another split ratio.

# Quadrature Coupler (cont.)

Circularly-polarized microstrip antennas can be fed with a 90° coupler.



One feed port produces RHCP, the other feed port produced LHCP.

**Note:** This is a better way (higher bandwidth) to get CP than with a simple 90° delay line.




# Rat-Race Ring Coupler (180° Coupler)

“Applications of rat-race couplers are numerous, and include mixers and phase shifters. The rat-race gets its name from its circular shape, shown below.”


Taken from “Microwaves 101”

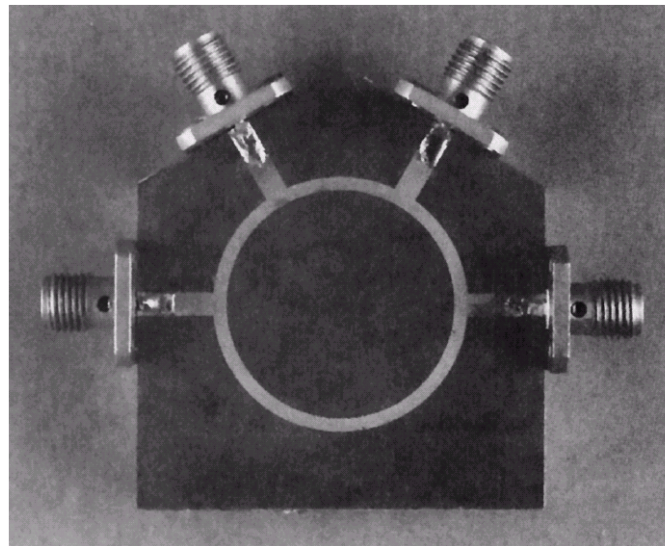[http://www.microwaves101.com/encyclopedia/ratrace\\_couplers.cfm](http://www.microwaves101.com/encyclopedia/ratrace_couplers.cfm)



Photograph of a  
microstrip ring coupler  
Courtesy of M. D. Abouzahra, MIT  
Lincoln Laboratory

# Rat-Race Coupler (cont.)

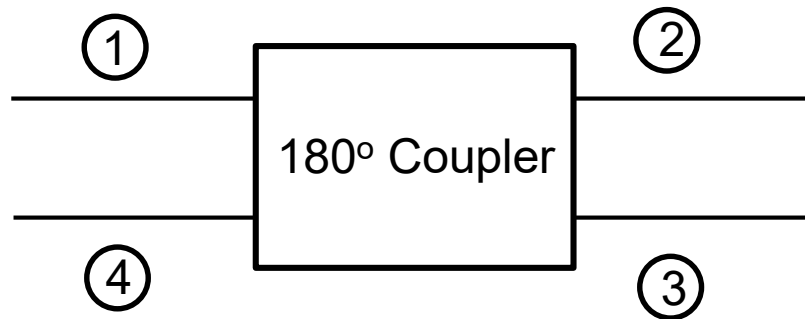


$$[S] = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$

- The rat race is a lossless 4-port (the  $S$  matrix is unitary).
- All four ports are matched.
- The device is reciprocal (the  $S$  matrix is symmetric).
- Port 4 is isolated from port 1, and ports 2 and 3 are isolated from each other.

# Rat-Race Coupler (cont.)

The rat race can be used as a splitter:

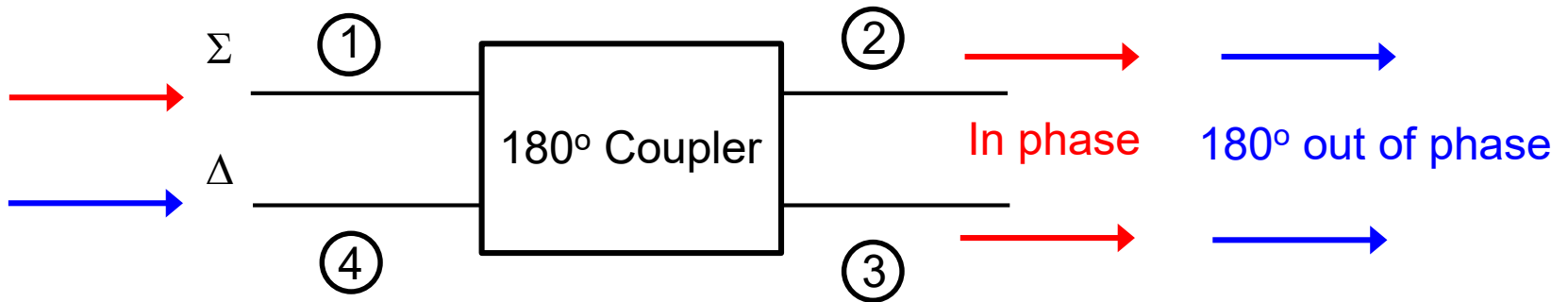

**Note:** A matched load is usually placed on port 4.

- The signal from the “sum port”  $\Sigma$  (port 1) splits evenly between ports 2 and 3, in phase. This could be used as a power splitter (alternative to Wilkinson).


$$S_{21} = S_{31}$$

- The signal from the “difference port”  $\Delta$  (port 4) splits evenly between ports 1 and 2, 180° out of phase. This could be used as a balun.

$$S_{24} = -S_{34}$$

# Rat-Race Coupler (cont.)

The rat race can be used as a combiner:

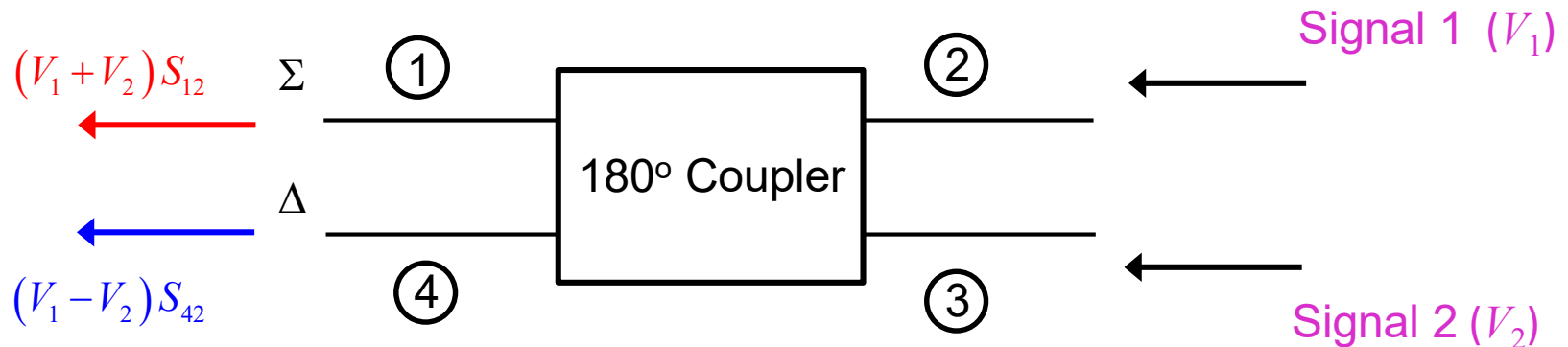

- The signal from the sum port  $\Sigma$  (port 1) is the sum of the input signals 1 and 2.

$$S_{12} = S_{13}$$


- The signal from the difference port  $\Delta$  (port 4) is the difference of the input signals 1 and 2.

$$S_{42} = -S_{43}$$
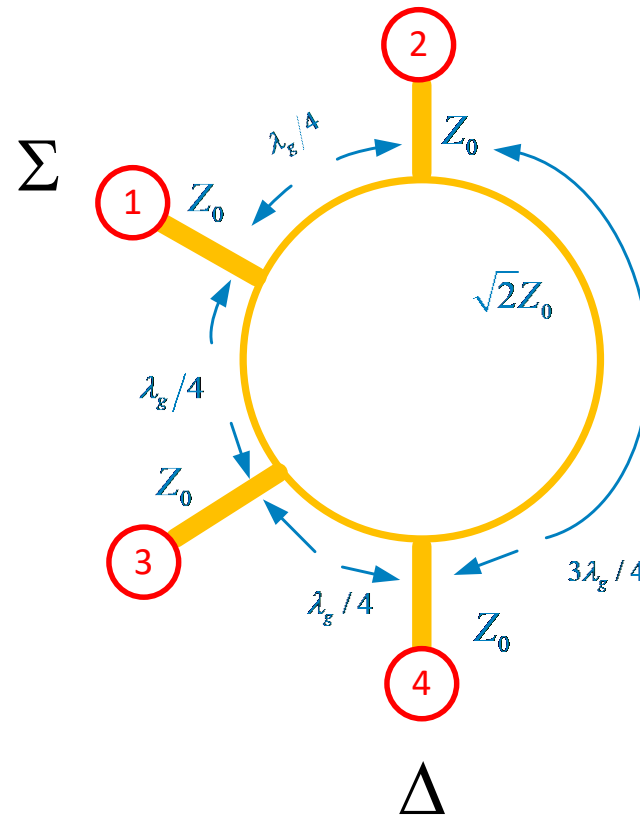
# Rat-Race Coupler (cont.)

A microstrip realization is shown here.


$$[S] = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$



An analysis of the rat-race coupler is given in the Appendix.
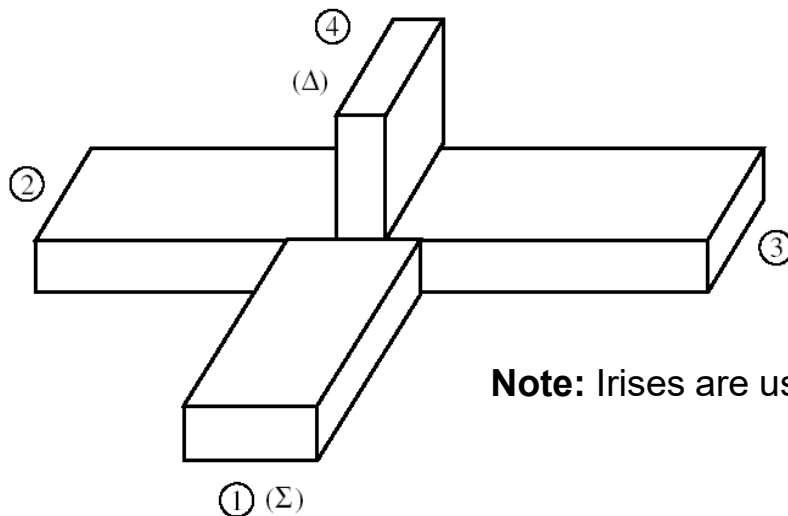
# Magic T

A waveguide realization of a 180° coupler is shown here, called a “Magic T.”



“Magic T”

**Note:** Irises are usually used to obtain matching at the ports.

IEEE Microwave Theory and Techniques Society


$$[S] = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$



Note the logo!
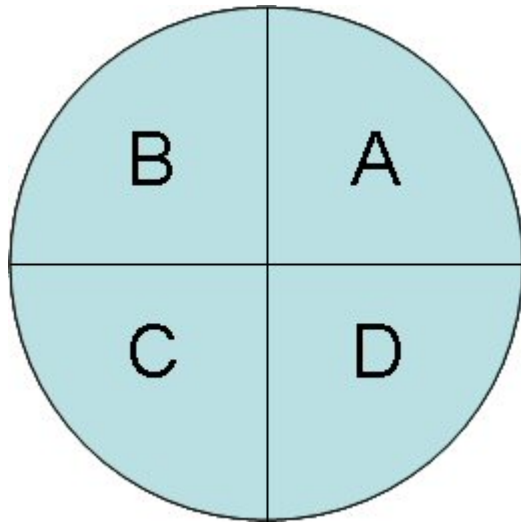
# Monopulse Radar

Rat-Race couplers are often used in monopulse radar.




Four antennas


$$\Sigma = A + B + C + D$$

$$\Delta_{AZ} = (B + C) - (A + D)$$


$$\Delta_{EL} = (C + D) - (B + A)$$

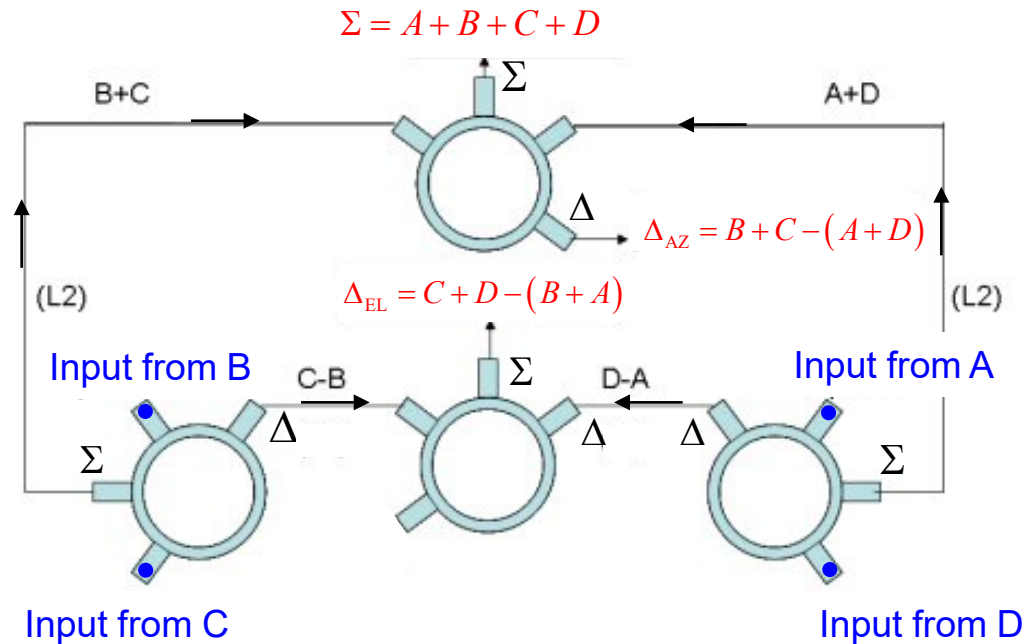

Rat-Race:

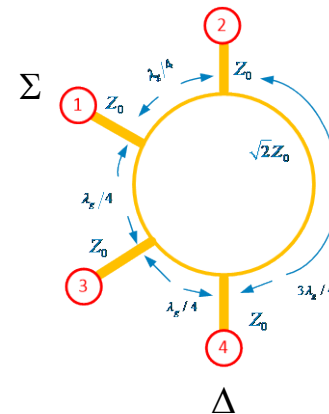

# Monopulse Radar (cont.)

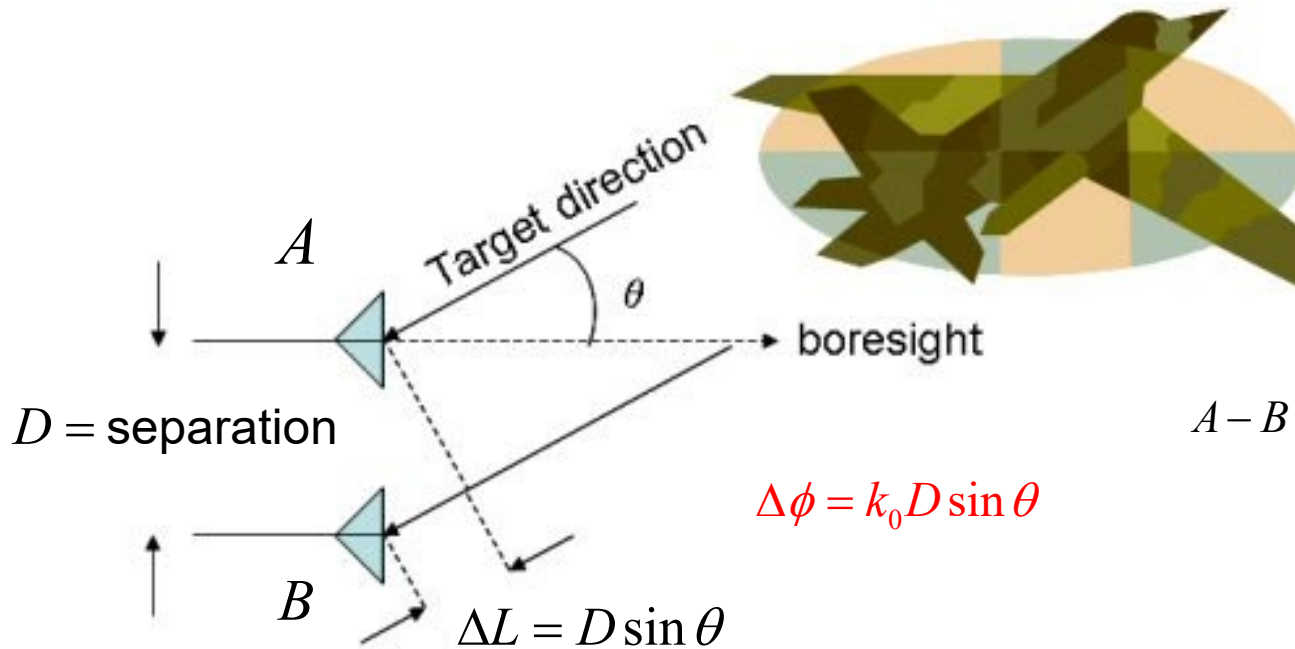

$$\begin{aligned}
 A - B &= 1 - e^{-j\Delta\phi} \\
 &= e^{-j\Delta\phi/2} (e^{+j\Delta\phi/2} - e^{-j\Delta\phi/2}) \\
 &= e^{-j\Delta\phi/2} (2j \sin(\Delta\phi/2))
 \end{aligned}$$



The difference signals are used to determine the azimuth and elevation of the target.


The difference between the two antenna signals maps into the phase difference  $\Delta\phi$ , which maps into the angle  $\theta$ .



# Appendix A


Here we analyze the quadrature coupler.

Port 1 Excitation  
"even" analysis

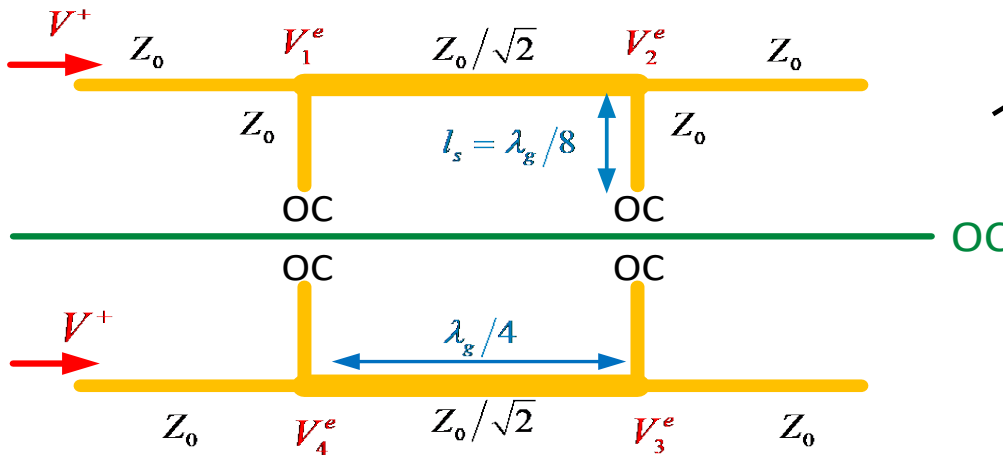

$$V_3^e = V_2^e$$

$$V_4^e = V_1^e$$

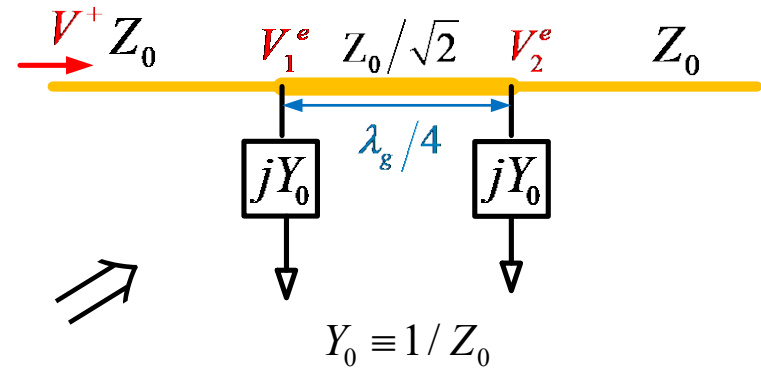


Input admittance of open-circuited stub:

$$\begin{aligned} Y_s &= jY_0 \tan(\beta_s l_s) \\ &= jY_0 \tan(\pi / 4) \\ &= jY_0 \end{aligned}$$


# Appendix A (cont.)

Port 1 Excitation  
“odd” problem

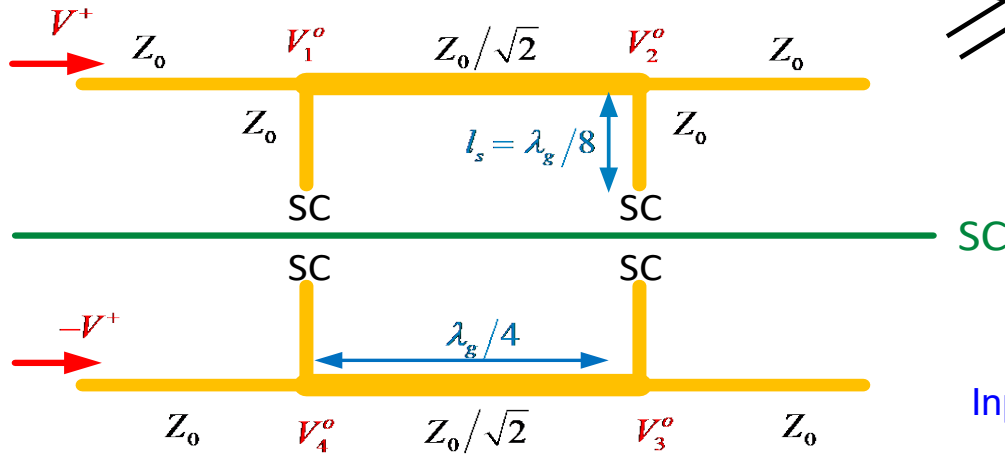

$$V_3^o = -V_2^o$$

$$V_4^o = -V_1^o$$

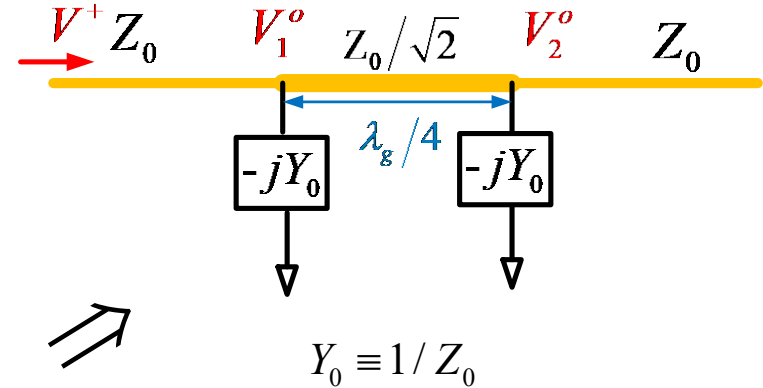


Input admittance of short-circuited stub:

$$\begin{aligned} Y_s &= -jY_0 \cot(\beta_s l_s) \\ &= -jY_0 \cot(\pi / 4) \\ &= -jY_0 \end{aligned}$$
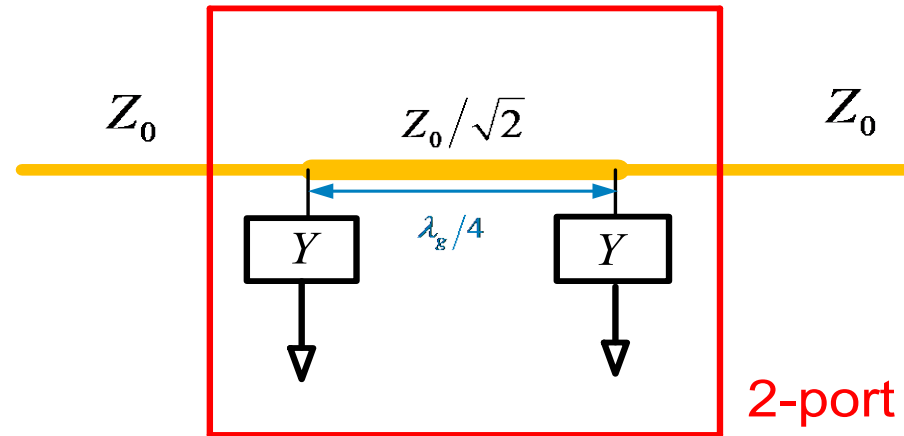
# Appendix A (cont.)

Consider the general case:

$$Y_s = \pm jY_0 \begin{pmatrix} + \text{ for even} \\ - \text{ for odd} \end{pmatrix}$$



$$[ABCD]_Y = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

Shunt load on line

$$[ABCD]_{\lambda/4} = \begin{bmatrix} 0 & \frac{jZ_0}{\sqrt{2}} \\ \frac{j\sqrt{2}}{Z_0} & 0 \end{bmatrix}$$

Quarter-wave line

In general:

$$[ABCD]^{line} = \begin{bmatrix} \cos(\beta\ell) & jZ_0^{line} \sin(\beta\ell) \\ (j/Z_0^{line}) \sin(\beta\ell) & D = \cos(\beta\ell) \end{bmatrix}$$

Here:  $Z_0^{line} = Z_0 / \sqrt{2}$   
 $\beta\ell = \pi / 2$

$$\Rightarrow [ABCD] = [ABCD]_Y [ABCD]_{\lambda/4} [ABCD]_Y$$

# Appendix A (cont.)

Hence we have:

$$\begin{aligned} [ABCD] &= \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} 0 & \frac{jZ_0}{\sqrt{2}} \\ \frac{j\sqrt{2}}{Z_0} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \\ &= \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} \frac{jZ_0 Y}{\sqrt{2}} & \frac{jZ_0}{\sqrt{2}} \\ \frac{j\sqrt{2}}{Z_0} & 0 \end{bmatrix} \\ &= \begin{bmatrix} \frac{jZ_0 Y}{\sqrt{2}} & \frac{jZ_0}{\sqrt{2}} \\ \frac{jZ_0 Y^2}{\sqrt{2}} + \frac{j\sqrt{2}}{Z_0} & \frac{jZ_0 Y}{\sqrt{2}} \end{bmatrix} \end{aligned}$$
$$Y = \pm jY_0 = \pm \frac{j}{Z_0} \begin{pmatrix} + \text{ for even} \\ - \text{ for odd} \end{pmatrix}$$

# Appendix A (cont.)

Continuing with the algebra, we have:

$$\begin{aligned} [ABCD] &= \frac{1}{\sqrt{2}} \begin{bmatrix} jZ_0 \left( \pm \frac{j}{Z_0} \right) & jZ_0 \\ jZ_0 \left( \pm \frac{j}{Z_0} \right)^2 + \frac{j2}{Z_0} & jZ_0 \left( \pm \frac{j}{Z_0} \right) \end{bmatrix} \\ &= \frac{1}{\sqrt{2}} \begin{bmatrix} j(\pm j) & jZ_0 \\ -j \left( \frac{1}{Z_0} \right) + \frac{j2}{Z_0} & j(\pm j) \end{bmatrix} \\ &= \frac{1}{\sqrt{2}} \begin{bmatrix} \mp 1 & jZ_0 \\ j \left( \frac{1}{Z_0} \right) & \mp 1 \end{bmatrix} \end{aligned}$$

# Appendix A (cont.)

Hence we have:

$$[ABCD]_e = \frac{1}{\sqrt{2}} \begin{bmatrix} \mp 1 & jZ_0 \\ j\left(\frac{1}{Z_0}\right) & \mp 1 \end{bmatrix}$$

Convert this to  $S$  parameters (use Table 4.2 in Pozar):

$$[S]_e = \begin{bmatrix} 0 & \frac{\mp 1 - j}{\sqrt{2}} \\ \frac{\mp 1 - j}{\sqrt{2}} & 0 \end{bmatrix}$$

**Note:**


We are describing a two-port device here, in the even and odd mode cases.

This is a 2×2 matrix, not a 4×4 matrix.

# Appendix A (cont.)

Adding even and odd mode cases together:

$$V_1^+ = V^+ + V^-$$

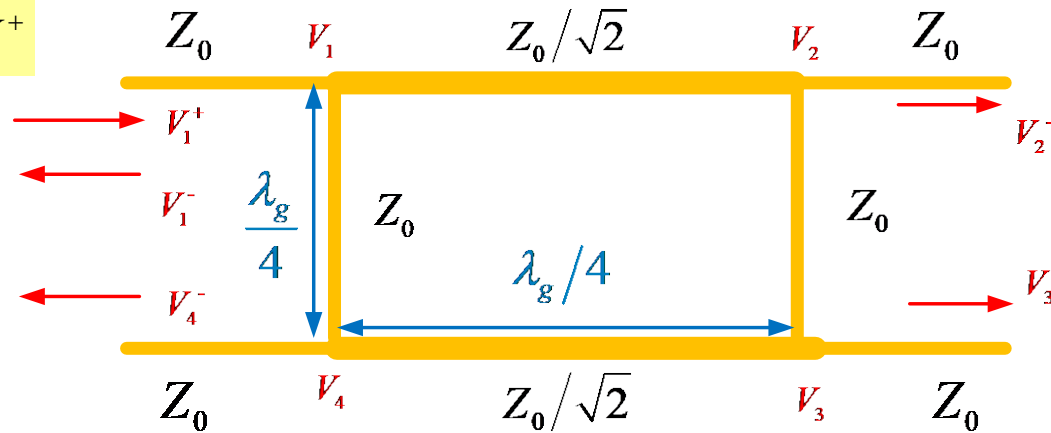

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{a_2=a_3=a_4=0} \Rightarrow S_{11} = \frac{V_1^{-e} + V_1^{-o}}{V^+ + V^+} = \frac{V_1^{-e} + V_1^{-o}}{2V^+} = \frac{1}{2} \left( \frac{V_1^{-e}}{V^+} + \frac{V_1^{-o}}{V^+} \right)$$

$$= \frac{1}{2} (S_{11}^e + S_{11}^o) = 0 + 0$$

Hence


$$S_{11} = 0$$

By symmetry:

$$S_{11} = S_{22} = S_{33} = S_{44} = 0$$

# Appendix A (cont.)

$$V_1^+ = V^+ + V^+$$

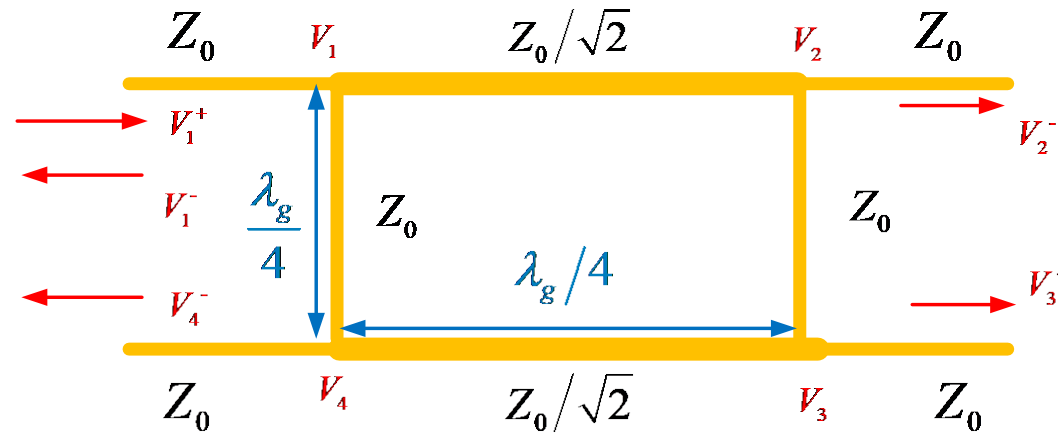

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{a_2=a_3=a_4=0} \Rightarrow S_{21} = \frac{V_2^{-e} + V_2^{-o}}{V^+ + V^+} = \frac{V_2^{-e} + V_2^{-o}}{2V^+} = \frac{1}{2} (S_{21}^e + S_{21}^o)$$

$$= \frac{1}{2} \left[ \left( \frac{-1-j}{\sqrt{2}} \right) + \left( \frac{1-j}{\sqrt{2}} \right) \right]$$

$$= \frac{-j}{\sqrt{2}}$$


By symmetry and reciprocity:

$$S_{21} = S_{12} = S_{43} = S_{34} = \frac{-j}{\sqrt{2}}$$



# Appendix A (cont.)

$$V_1^+ = V^+ + V^+$$

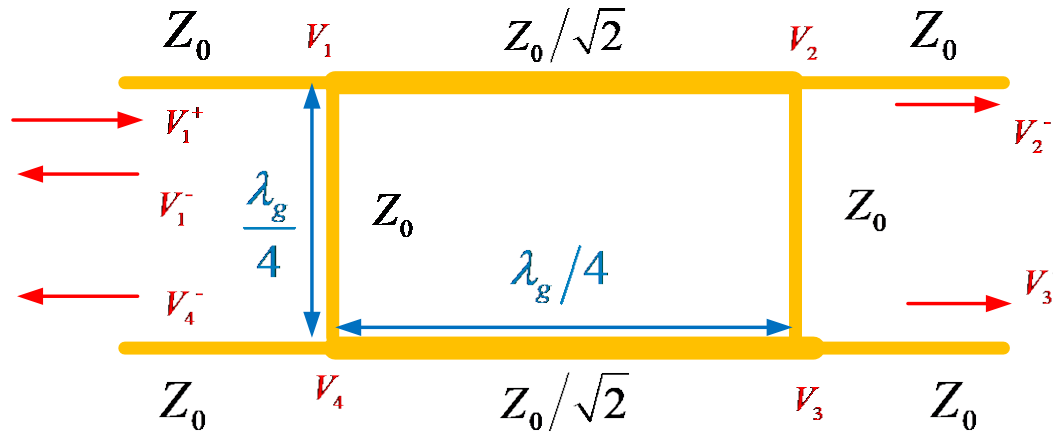

$$S_{31} = \left. \frac{V_3^-}{V_1^+} \right|_{a_2=a_3=a_4=0} \Rightarrow S_{31} = \frac{V_3^{-e} + V_3^{-o}}{V^+ + V^+} = \frac{V_3^{-e} + V_3^{-o}}{2V^+} = \frac{V_2^{-e} - V_2^{-o}}{2V^+} = \frac{1}{2} (S_{21}^e - S_{21}^o)$$

$$= \frac{1}{2} \left[ \left( \frac{-1-j}{\sqrt{2}} \right) - \left( \frac{1-j}{\sqrt{2}} \right) \right]$$


$$= \frac{-1}{\sqrt{2}}$$

By symmetry and reciprocity:

$$S_{31} = S_{13} = S_{24} = S_{42} = \frac{-1}{\sqrt{2}}$$

# Appendix A (cont.)

$$V_1^+ = V^+ + V^+$$

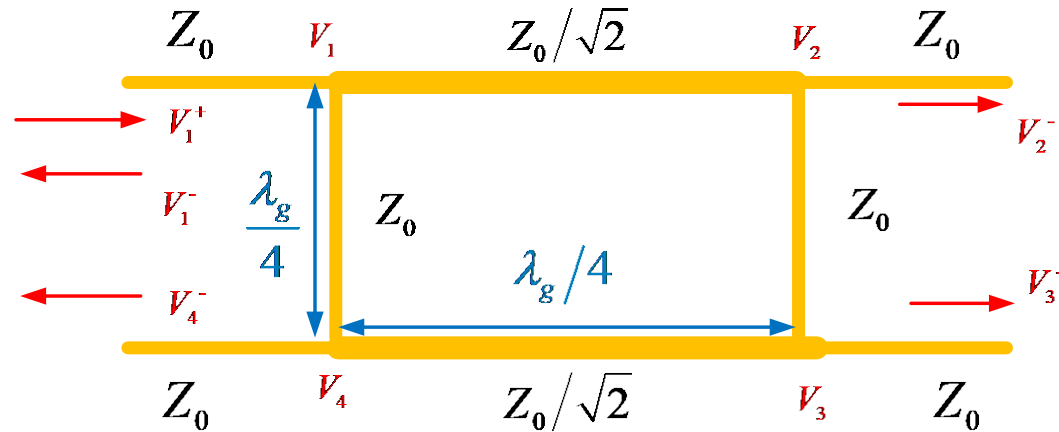


$$S_{41} = \left. \frac{V_4^-}{V_1^+} \right|_{a_2=a_3=a_4=0} \Rightarrow S_{41} = \frac{V_4^{-e} + V_4^{-o}}{V^+ + V^+} = \frac{V_4^{-e} + V_4^{-o}}{2V^+} = \frac{V_1^{-e} - V_1^{-o}}{2V^+} = \frac{1}{2}(S_{11}^e - S_{11}^o) = 0$$


By symmetry and reciprocity:  $S_{41} = S_{14} = S_{23} = S_{32} = 0$
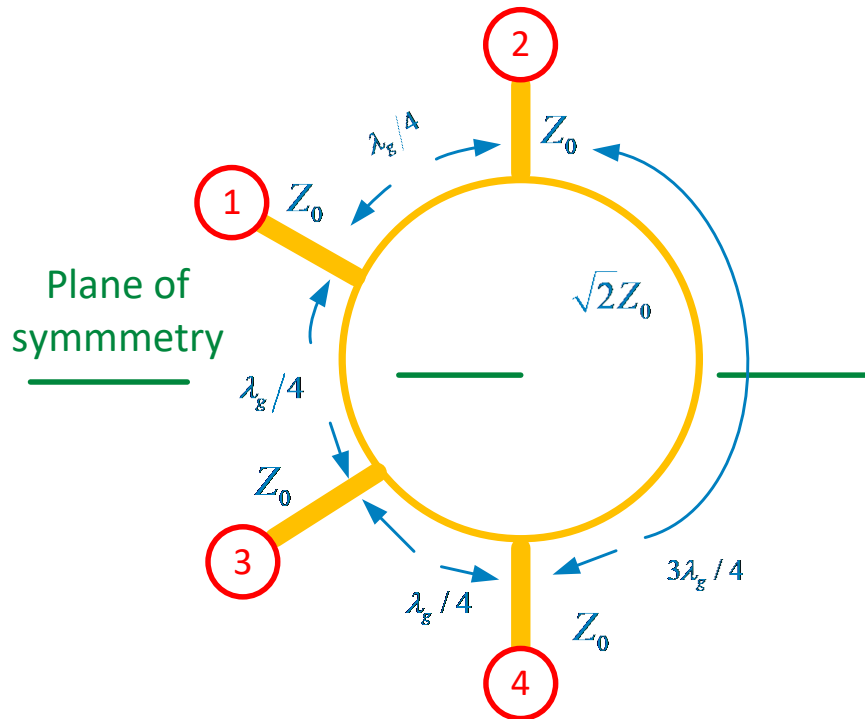
# Appendix B

Here we analyze the Rat-Race Ring coupler.




Layout

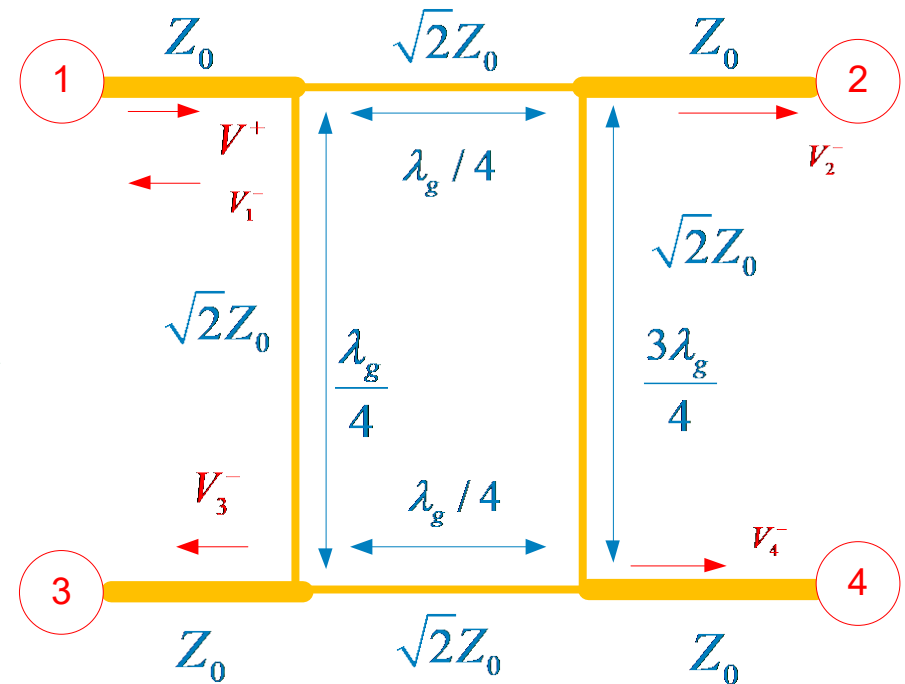

Schematic


# Appendix B (cont.)

Port 1 Excitation  
"even" problem

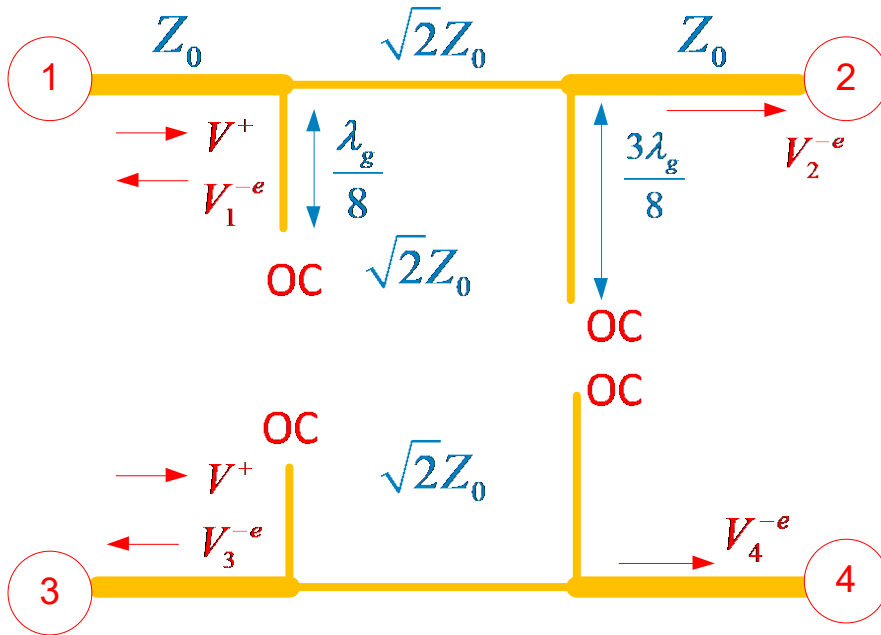

$$Y_0 = 1/Z_0$$

$$Y_{0s} = Y_0 / \sqrt{2}$$

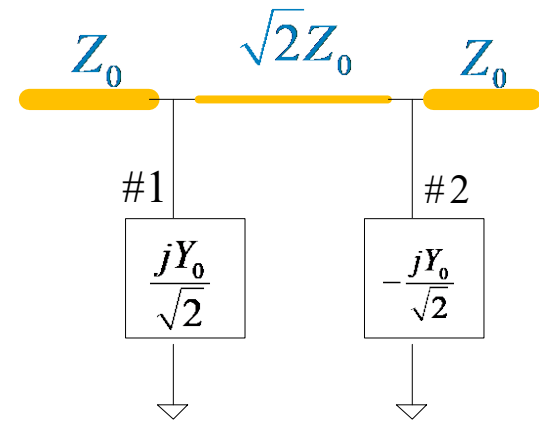


$$\begin{aligned} Y_{s1} &= jY_{0s1} \tan(\beta_s l_{s1}) \\ &= j(Y_0 / \sqrt{2}) \tan(\pi / 4) \\ &= jY_0 / \sqrt{2} \end{aligned}$$

$$\begin{aligned} Y_{s2} &= jY_{0s2} \tan(\beta_s l_{s2}) \\ &= j(Y_0 / \sqrt{2}) \tan(3\pi / 4) \\ &= -jY_0 / \sqrt{2} \end{aligned}$$


# Appendix B (cont.)

Port 1 Excitation  
"odd" problem

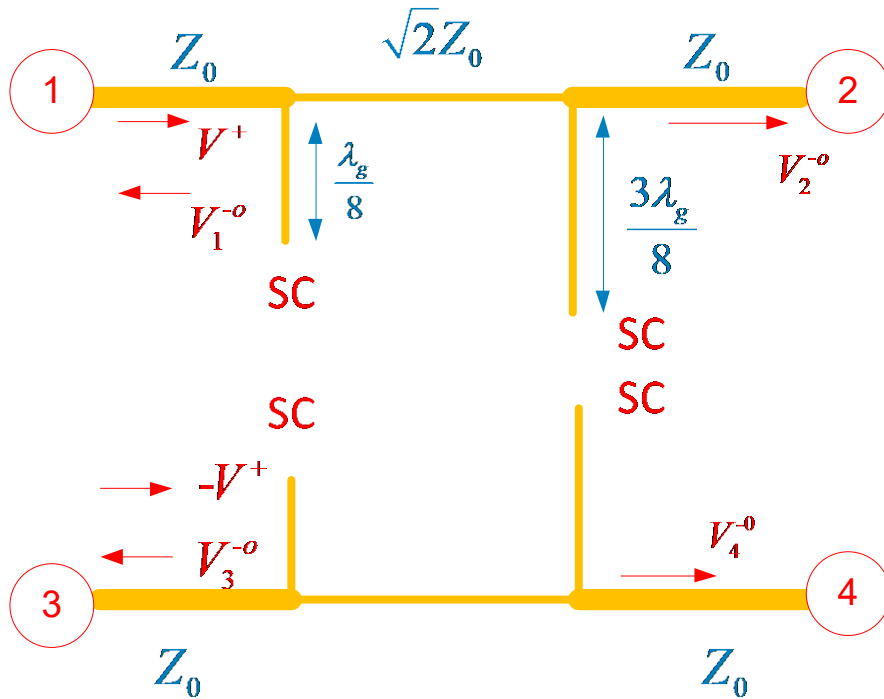

$$Y_0 = 1/Z_0$$

$$Y_{0s} = Y_0 / \sqrt{2}$$

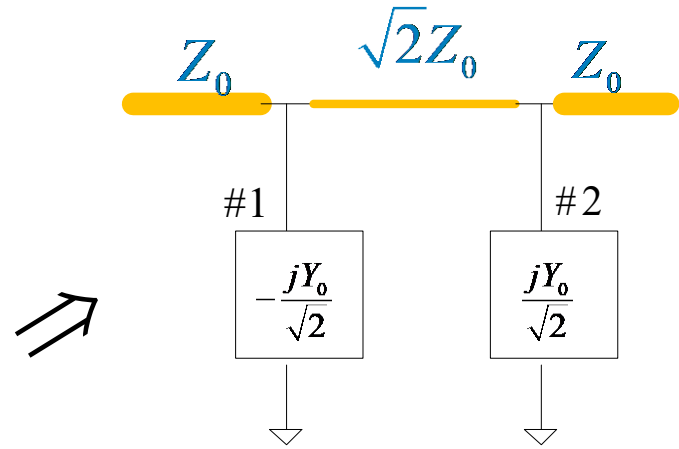

$$\begin{aligned} Y_{s1} &= -jY_{0s1} \cot(\beta_s l_s) \\ &= -j(Y_0 / \sqrt{2}) \cot(\pi / 4) \\ &= -jY_0 / \sqrt{2} \end{aligned}$$

$$\begin{aligned} Y_{s1} &= -jY_{0s2} \cot(\beta_s l_s) \\ &= -j(Y_0 / \sqrt{2}) \cot(3\pi / 4) \\ &= jY_0 / \sqrt{2} \end{aligned}$$

# Appendix B (cont.)

Proceeding as for the 90° coupler, we have:

$$\begin{aligned} [ABCD]_e &= \begin{bmatrix} 1 & 0 \\ \frac{\pm jY_0}{\sqrt{2}} & 1 \end{bmatrix} \begin{bmatrix} 0 & j\sqrt{2}Z_0 \\ j\frac{1}{\sqrt{2}Z_0} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \mp \frac{jY_0}{\sqrt{2}} & 1 \end{bmatrix} \\ &= \begin{bmatrix} 1 & 0 \\ \frac{\pm jY_0}{\sqrt{2}} & 1 \end{bmatrix} \begin{bmatrix} \pm 1 & j\sqrt{2}Z_0 \\ j\frac{1}{\sqrt{2}Z_0} & 0 \end{bmatrix} \\ &= \begin{bmatrix} \pm 1 & j\sqrt{2}Z_0 \\ j\frac{\sqrt{2}}{Z_0} & \mp 1 \end{bmatrix} \end{aligned}$$

# Appendix B (cont.)

Converting from the  $ABCD$  matrix to the  $S$  matrix, we have:

$$[ABCD]_0^e = \begin{bmatrix} \pm 1 & j\sqrt{2}Z_0 \\ j\frac{\sqrt{2}}{Z_0} & \mp 1 \end{bmatrix}$$

**Note:**

We are describing a two-port device here, in the even and odd mode cases.

This is a 2×2 matrix, not a 4×4 matrix.



Use Table 4.2 in Pozar

$$[S]_0^e = \frac{-j}{\sqrt{2}} \begin{bmatrix} \pm 1 & 1 \\ 1 & \mp 1 \end{bmatrix}$$

# Appendix B (cont.)

For the  $S$  parameters coming from port 1 excitation, we then have:

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{a_2=a_3=a_4=0}$$

$$S_{11} = S_{33} = 0$$

(symmetry)

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{a_2=a_3=a_4=0}$$

$$S_{21} = S_{12} = S_{34} = S_{43} = \frac{-j}{\sqrt{2}}$$

(symmetry and reciprocity)

$$\begin{aligned} S_{11} &= \frac{V_1^{-e} + V_1^{-o}}{2V^+} = \frac{1}{2}(S_{11}^e + S_{11}^o) \\ &= \frac{1}{2}\left(\frac{-j}{\sqrt{2}} + \frac{j}{\sqrt{2}}\right) \\ &= 0 \end{aligned}$$

$$\begin{aligned} S_{21} &= \frac{V_2^{-e} + V_2^{-o}}{2V^+} = \frac{1}{2}(S_{21}^e + S_{21}^o) \\ &= \frac{1}{2}\left(\frac{-j}{\sqrt{2}} + \frac{-j}{\sqrt{2}}\right) \\ &= \frac{-j}{\sqrt{2}} \end{aligned}$$



# Appendix B (cont.)

$$S_{31} = \left. \frac{V_3^-}{V_1^+} \right|_{a_2=a_3=a_4=0}$$

$$S_{31} = S_{13} = -\frac{j}{\sqrt{2}}$$

(symmetry)

$$\begin{aligned} S_{31} &= \frac{V_3^{-e} + V_3^{-o}}{2V^+} = \frac{1}{2}(S_{11}^e - S_{11}^o) \\ &= \frac{1}{2} \left( \frac{-j}{\sqrt{2}} - \frac{j}{\sqrt{2}} \right) \\ &= \frac{-j}{\sqrt{2}} \end{aligned}$$

Similarly, exciting port 2, and using symmetry and reciprocity, we have the following results (derivation omitted):

$$S_{22} = S_{44} = 0$$

$$S_{23} = S_{32} = S_{14} = S_{41} = 0$$

$$S_{24} = S_{42} = \frac{j}{\sqrt{2}}$$