

# ECE 5317-6351


# Microwave Engineering

**Fall 2019**

Prof. David R. Jackson  
Dept. of ECE


## **Notes 22**
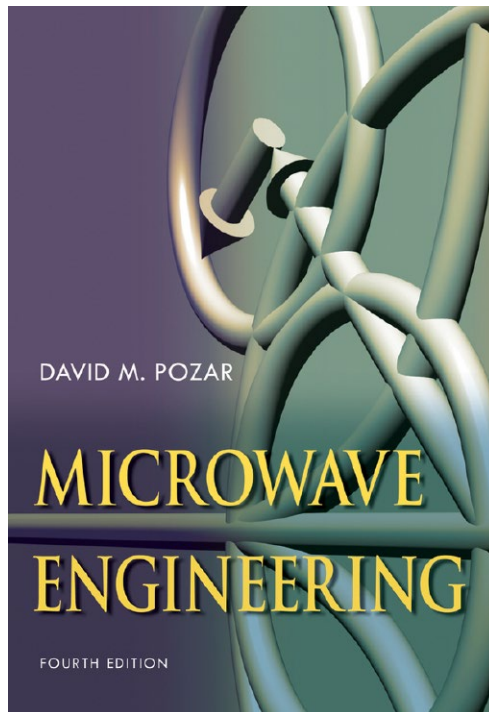
### **Filter Design Part 1: Insertion Loss Method**



# Filters

Consider the following circuit:

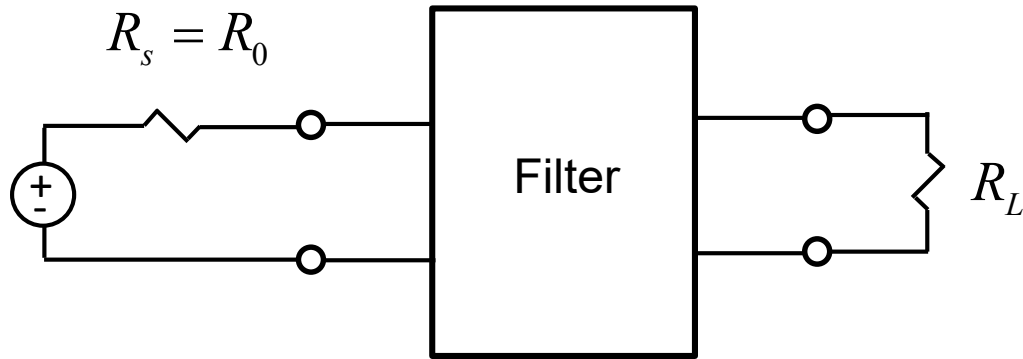


This is the basic filter circuit that we will study.

The filter is assumed to be lossless (consists of  $L$  and  $C$  elements).
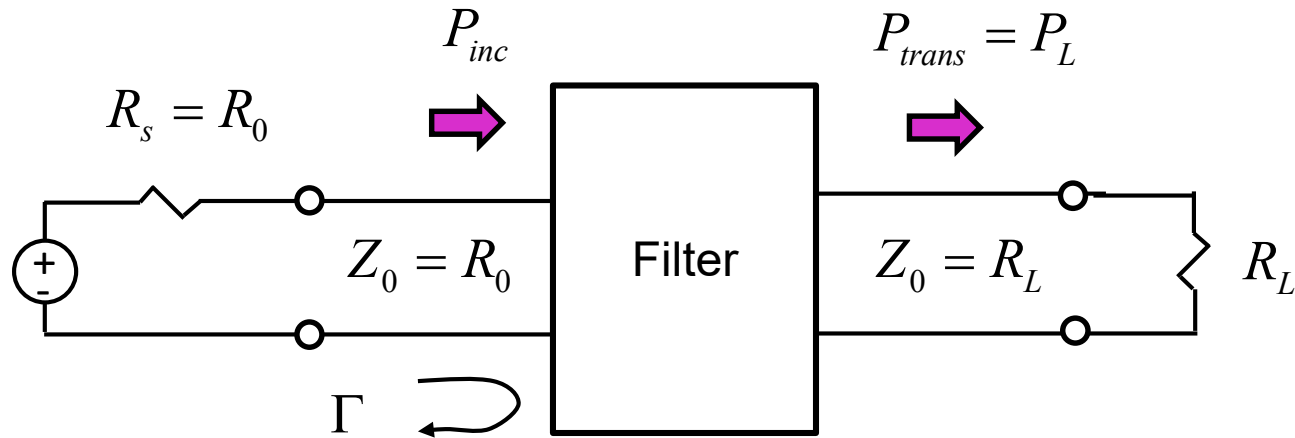
# Filters (cont.)

We can think of transmission lines connected at the input and output of the filter.



Power loss ratio:

$$P_{LR} \equiv \frac{P_{inc}}{P_L}$$

$$\Gamma = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

Lossless filter:

$$P_L = P_{in} = P_{inc} (1 - |\Gamma|^2)$$

$$P_{LR} = \frac{P_{inc}}{P_{inc} (1 - |\Gamma|^2)} = \frac{1}{(1 - |\Gamma|^2)}$$


# Filters (cont.)

Also

$$|S_{21}|^2 = \frac{P_2^-}{P_1^+} = \frac{P_{trans}}{P_{inc}} = \frac{P_L}{P_{inc}} = \frac{1}{P_{LR}} \quad \Rightarrow \quad P_{LR} = \frac{1}{|S_{21}|^2}$$

Insertion Loss (dB):  $IL \equiv 10 \log_{10} P_{LR} = -20 \log_{10} |S_{21}|$

From conservation of energy:  $|S_{21}|^2 = 1 - |S_{11}|^2$

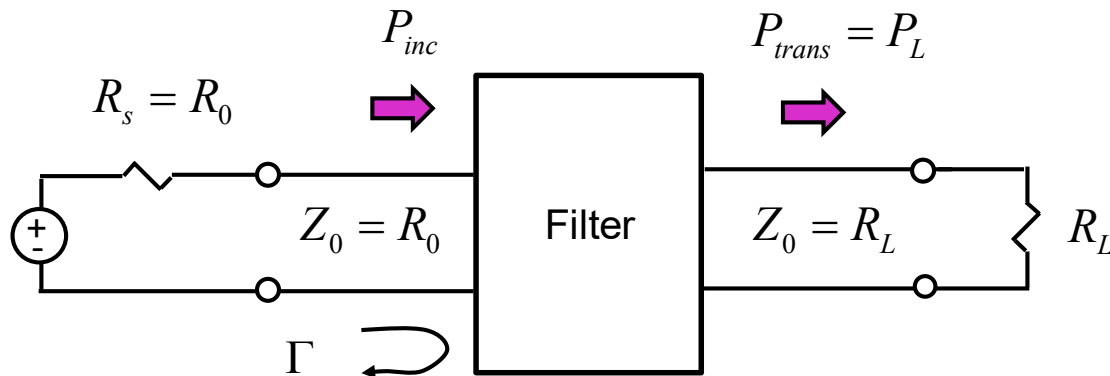


# Filters (cont.)

The “insertion loss method” aims at designing a filter to achieve a particular type of response for the function  $P_{LR}(\omega)$ .

$$P_{LR} = \frac{P_{inc}}{P_L} = \frac{1}{(1 - |\Gamma|^2)} = \frac{1}{|S_{21}|^2}$$


$$IL \equiv 10 \log_{10} P_{LR} = -20 \log_{10} |S_{21}|$$

$$|S_{11}|^2 = 1 - |S_{21}|^2$$

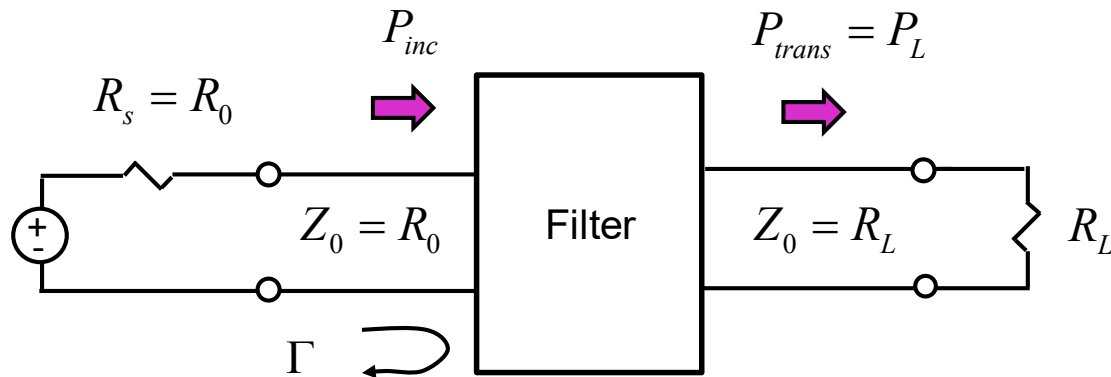

# Low-Pass Filter

## Ideal low-pass filter response

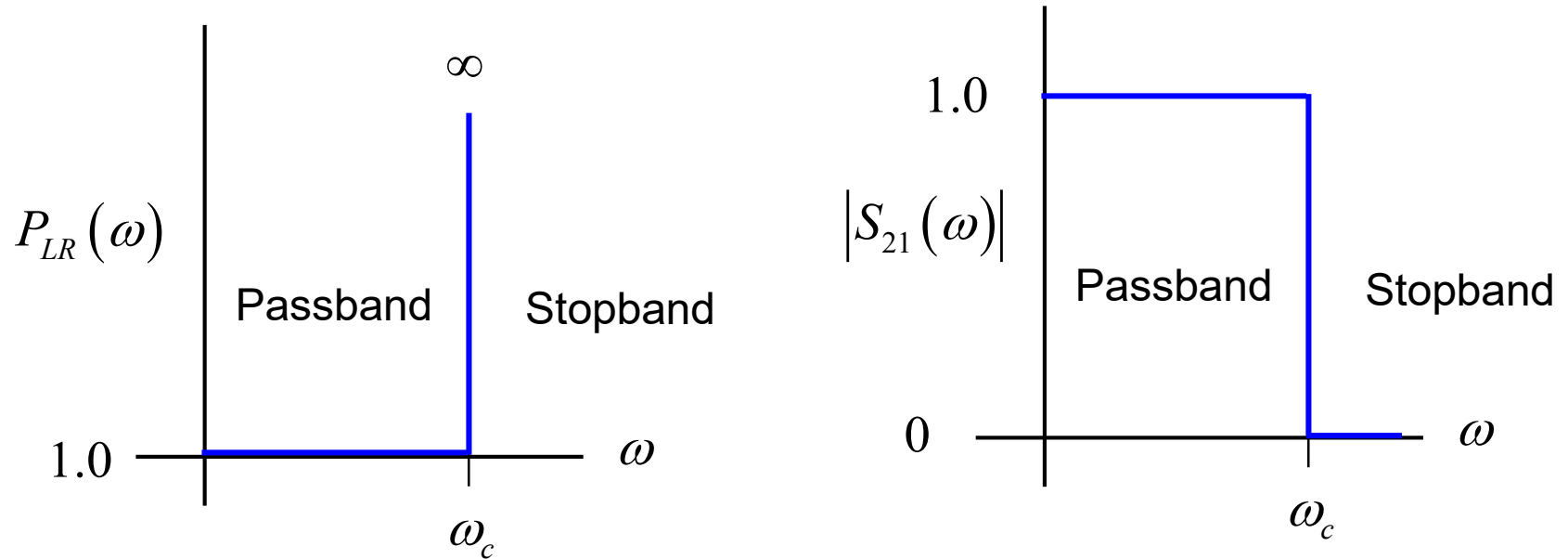

Recall: 
$$P_{LR} = \frac{1}{|S_{21}|^2}$$

# Filters (cont.)

## Types of filters:

- ❖ Low-pass
- ❖ High-pass
- ❖ Bandpass
- ❖ Bandstop

## Approach:

Design the low-pass filter first. The other types of filters come from this by using a frequency transformation.  
(This is discussed in the next set of notes.)

# Filters (cont.)

Common types of filters:

- ❖ Butterworth (binomial)\*
- ❖ Chebyshev (type I)\*
- ❖ Chebyshev (type II)
- ❖ Linear phase\*\*
- ❖ Elliptic

\*Discussed in this set of notes and the next set of notes.

\*\* Discussed in the next set of notes.



# Note on Reflection Coefficient

## Property of the Power Loss Function

$$\Gamma(-\omega) = \Gamma^*(\omega) \quad \text{(This property holds for the Fourier transform of any real-valued signal. A reflected time-domain signal must be real valued.)}$$

$$\Rightarrow \Gamma_R(-\omega) + j\Gamma_I(-\omega) = \Gamma_R(\omega) - j\Gamma_I(\omega)$$

$$\Rightarrow \left\{ \begin{array}{l} \Gamma_R(\omega) = \text{even function of } \omega \\ \Gamma_I(\omega) = \text{odd function of } \omega \end{array} \right.$$


$$\Rightarrow |\Gamma(\omega)|^2 = \text{even function of } \omega$$

$$\Rightarrow P_{LR}(\omega) = \text{even function of } \omega$$

(When we design a filter, we have to keep this in mind!)

# Low-Pass Filter

Low-pass filter response:

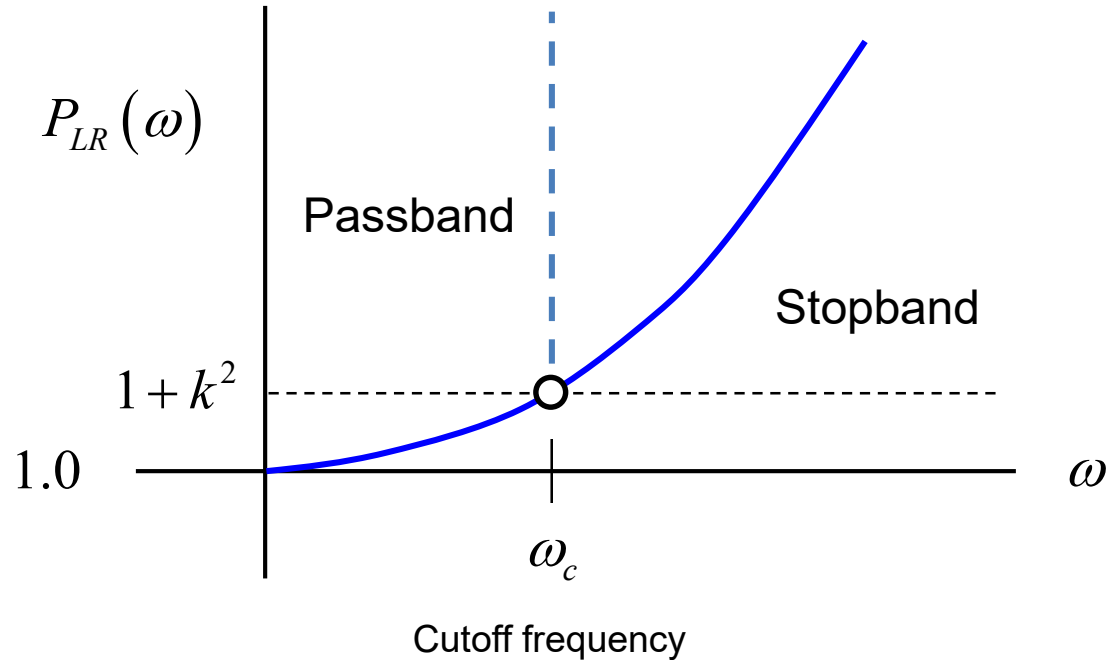


The constant  $k$  is somewhat arbitrary, and defines the cutoff frequency.

$$P_{LR}(\omega_c) = 1 + k^2$$

# Low-Pass Filter


Normalized low-pass filter response:

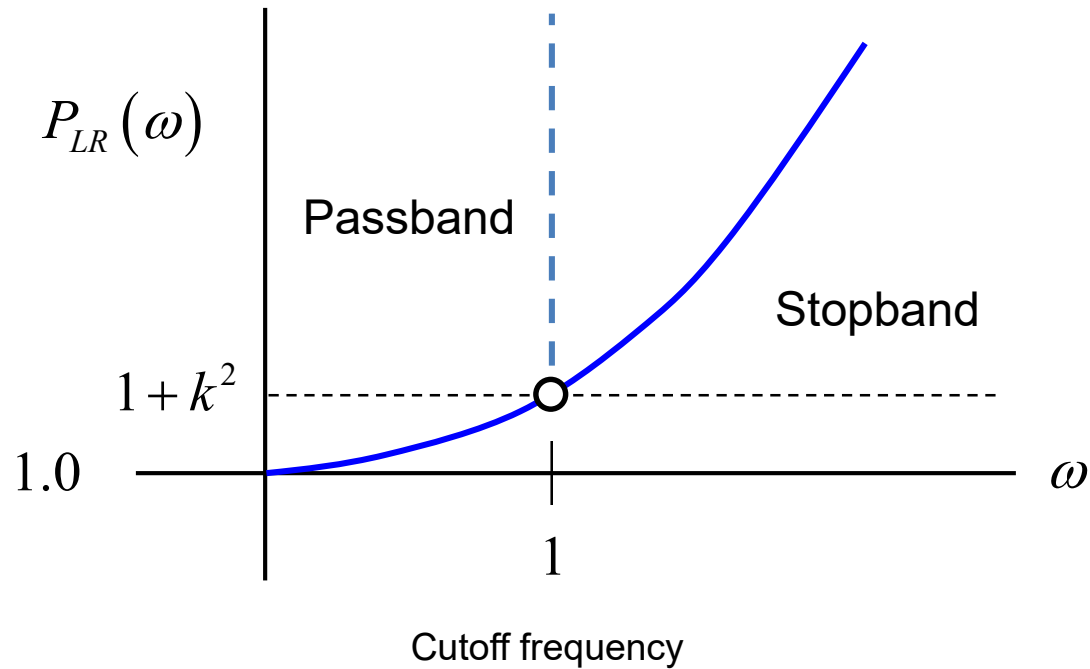

We design the normalized low-pass filter first ( $\omega_c = 1$ ), and then use scaling and frequency transformation to obtain the final filter (low-pass, high-pass, bandpass, bandstop).  
**(This is done in the next set of notes.)**

# Low-Pass Filter

Low-pass filter responses:

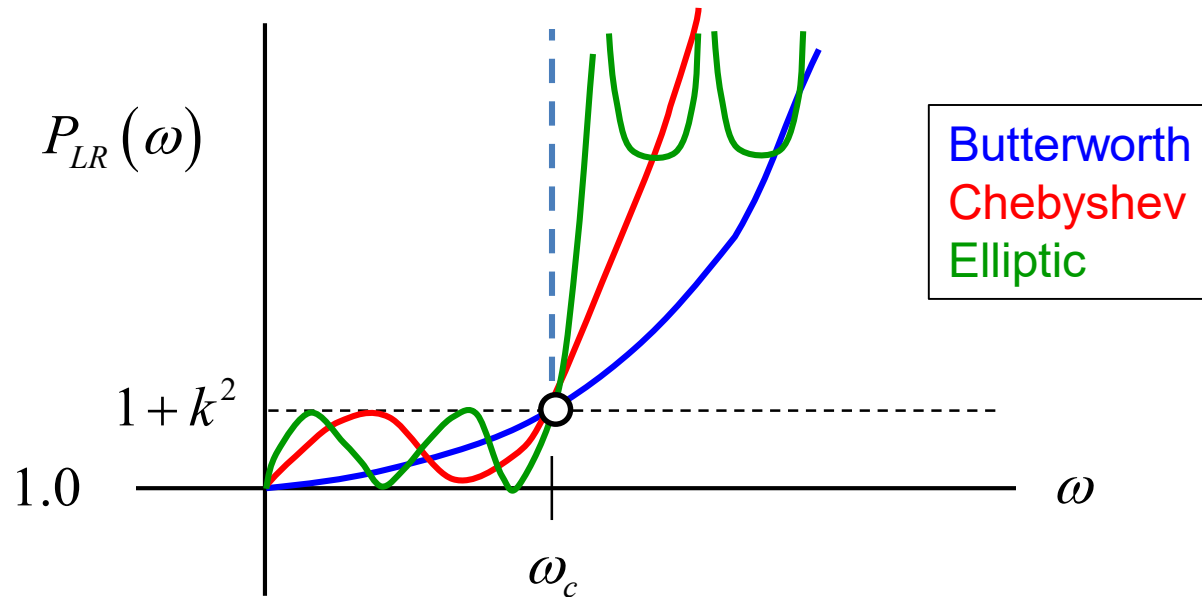

**Note:**

The Chebyshev response shown is called “type 1”, with ripple in the passband. The “type 2” Chebyshev response has ripple in the stopband.

# Low-Pass Filter

## Comments:


- The Butterworth design has the flattest response.
- The Chebyshev (type 1) design has a constant ripple in the passband.
- The Chebyshev (type 2) has a constant ripple in the stopband.
- The elliptic filter has ripple in both the passband and the stopband.

The elliptic filter has the sharpest transition from the passband to the stopband, for given levels of ripple in the passband and stopband.


# Low-Pass Filter

## Comparison of Filter Responses


Butterworth

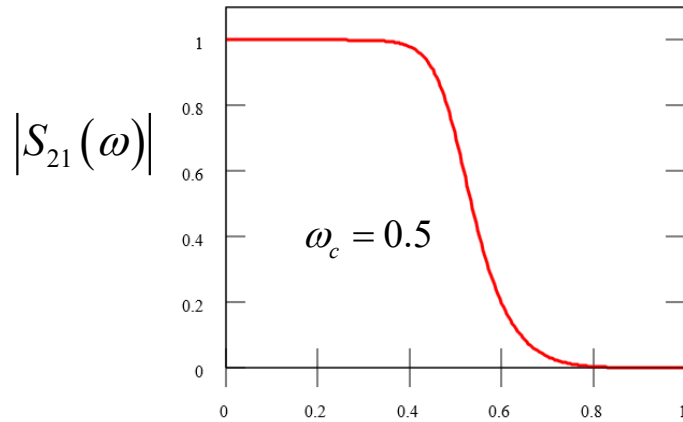


Chebyshev (type 1)

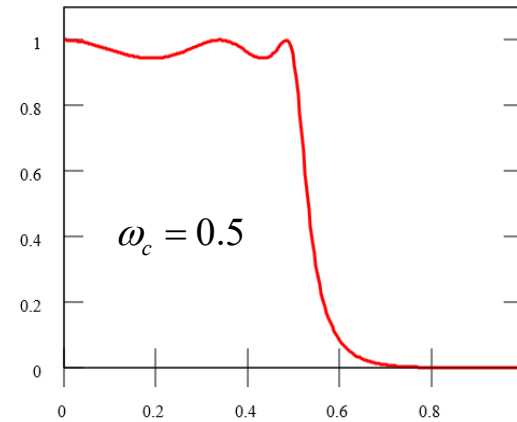

Chebyshev (type 2)

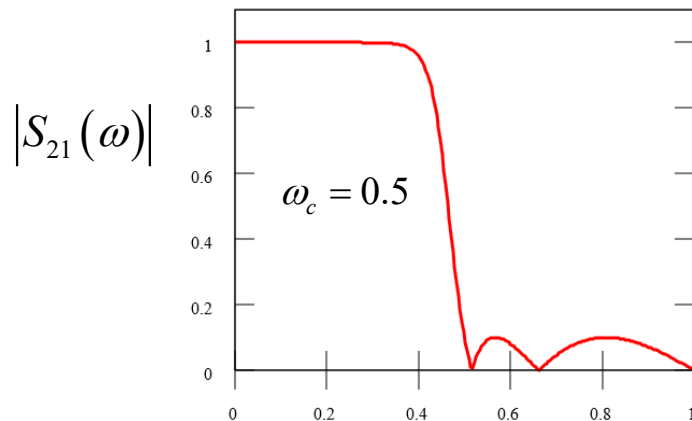

Elliptic

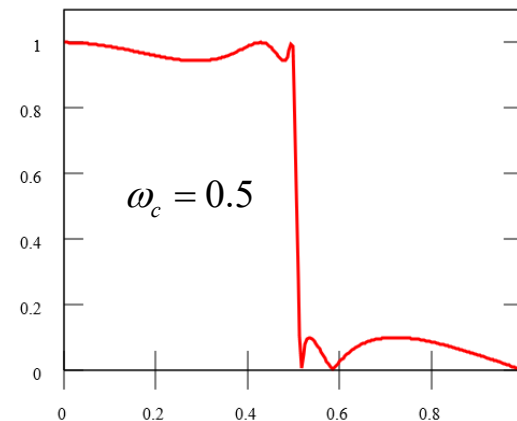

# Butterworth Low-Pass Filter

Choose:

$$P_{LR}(\omega) = 1 + k^2 \left( \frac{\omega}{\omega_c} \right)^{2N}$$

$N$  = order of the filter\*

- The first  $N-1$  derivatives of  $P_{LR}$  with respect to  $\omega$  are zero.

At the band edge:  $P_{LR}(\omega_c) = 1 + k^2$

Common choice:  $k = 1$  ( $P_{LR}(\omega_c) = 2$ ,  $IL(\omega_c) = 3 \text{ dB}$ )

\* As seen later, this will also be the number of  $(L, C)$  elements in the filter.

# Butterworth Low-Pass Filter (cont.)

High-frequency limit:  $\omega / \omega_c \rightarrow \infty$

$$P_{LR}(\omega) \sim k^2 \left( \frac{\omega}{\omega_c} \right)^{2N}$$

Hence

$$\text{IL} \equiv 10 \log_{10} P_{LR} \sim 10 \log_{10} \left( k^2 \left( \frac{\omega}{\omega_c} \right)^{2N} \right)$$

so

$$\text{IL}(\omega) \sim 20 \log_{10} k + 20N \log_{10} \left( \frac{\omega}{\omega_c} \right)$$

**Conclusion:** IL increases at  $20N$  dB/decade in the stopband.



# Chebyshev Low-Pass Filter

Choose:

$$P_{LR}(\omega) = 1 + k^2 T_N^2\left(\frac{\omega}{\omega_c}\right) \quad N = \text{order of the filter}^*$$

- There is equal ripple in the passband.

At the band edge:  $P_{LR}(\omega_c) = 1 + k^2$  Note:  $T_n(1) = 1$

Ripple level:  $1 + k^2$  (dB =  $10 \log_{10}(1 + k^2)$ )

$$T_n(x) \equiv \begin{cases} \cos(n \cos^{-1} x), & |x| \leq 1 \\ \cosh(n \cosh^{-1} x), & |x| \geq 1 \end{cases}$$
$$\begin{aligned} T_1(x) &= x \\ T_2(x) &= 2x^2 - 1 \\ T_3(x) &= 4x^3 - 3x \\ &\vdots \\ T_n(x) &= 2xT_{n-1}(x) - T_{n-2}(x) \end{aligned}$$

\* As seen later, this will also be the number of (L,C) elements in the filter.

# Chebyshev Low-Pass Filter (cont.)

High-frequency limit:  $\omega / \omega_c \rightarrow \infty$

$$P_{LR}(\omega) \sim \frac{k^2}{4} 2^{2N} \left( \frac{\omega}{\omega_c} \right)^{2N}$$

Note:  $T_n(x) \sim 2^{n-1} x^n, x \rightarrow \infty$

Hence

$$\begin{aligned} \text{IL} &\equiv 10 \log_{10} P_{LR} \sim 10 \log_{10} \left( \frac{k^2}{4} \right) + 20N \log_{10} (2) + 20N \log_{10} \left( \frac{\omega}{\omega_c} \right) \\ &= 20 \log_{10} (k) - 10 \log_{10} (4) + 20N \log_{10} (2) + 20N \log_{10} \left( \frac{\omega}{\omega_c} \right) \end{aligned}$$

so

$$\text{IL} \sim 20 \log_{10} (k) + 20(N-1) \log_{10} (2) + 20N \log_{10} \left( \frac{\omega}{\omega_c} \right)$$

# Chebyshev Low-Pass Filter (cont.)

## Comparison:

Butterworth: 
$$IL(\omega) \sim 20 \log_{10} k + 20N \log_{10} \left( \frac{\omega}{\omega_c} \right)$$


Chebyshev: 
$$IL \sim 20 \log_{10} (k) + 20(N-1) \log_{10} (2) + 20N \log_{10} \left( \frac{\omega}{\omega_c} \right)$$

### Conclusion:

In the stopband, the IL is larger than for the Chebyshev filter, but it increases at the same rate for both filters.

# Two Element Low-Pass Filter

Original circuit:

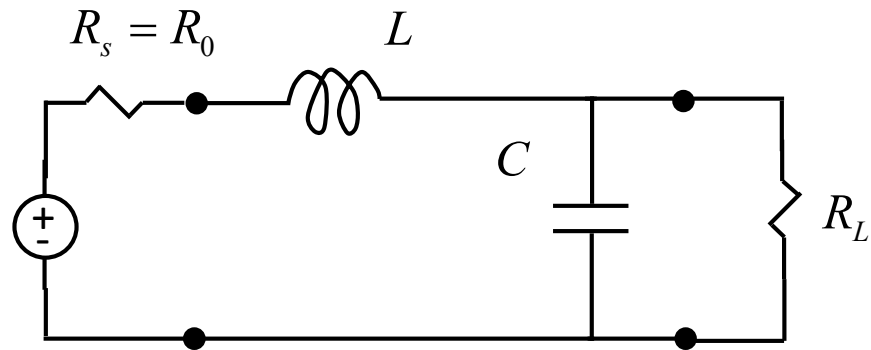


Normalize impedances by  $R_0$ :

$$R_{Ln} = R_L / R_0$$

$$L_n = L / R_0$$


$$C_n = CR_0$$

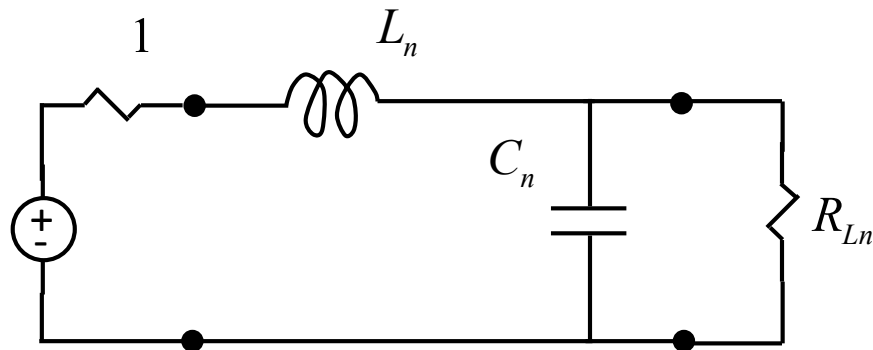This normalization does not change the reflection coefficient.



# Two Element Low-Pass Filter (cont.)

Normalized circuit:

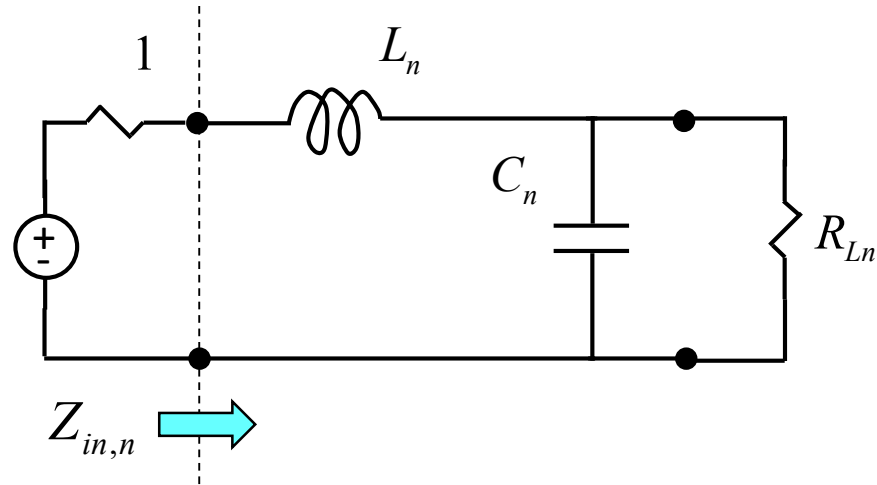

$$Z_{in,n} = j\omega L_n + \frac{1}{j\omega C_n + \frac{1}{R_{Ln}}}$$
$$= j\omega L_n + \frac{R_{Ln}}{1 + j\omega R_{Ln} C_n}$$

$$\Gamma_n = \frac{Z_{in,n} - 1}{Z_{in,n} + 1}$$

$$P_{LR} = \frac{1}{(1 - |\Gamma|^2)}$$

# Two Element Low-Pass Filter (cont.)

After some algebra:

$$P_{LR} = \left( 1 + \frac{(1 - R_{Ln})^2}{4R_{Ln}} \right) + \omega^2 \left( \left( \frac{1}{4R_{Ln}} \right) (R_{Ln}^2 C_n^2 + L_n^2 - 2L_n C_n R_{Ln}^2) \right) \\ + \omega^4 \left( \frac{1}{4R_{Ln}} \right) (L_n^2 C_n^2 R_{Ln}^2)$$

or

$$P_{LR} = \left( 1 + \frac{(1 - R_{Ln})^2}{4R_{Ln}} \right) + \left( \frac{\omega}{\omega_c} \right)^2 \left( \left( \frac{\omega_c^2}{4R_{Ln}} \right) (R_{Ln}^2 C_n^2 + L_n^2 - 2L_n C_n R_{Ln}^2) \right) \\ + \left( \frac{\omega}{\omega_c} \right)^4 \left( \left( \frac{\omega_c^4}{4R_{Ln}} \right) (L_n^2 C_n^2 R_{Ln}^2) \right)$$

$\omega_c$  = specified cutoff frequency

# Two Element Low-Pass Filter (cont.)

Hence we have:

$$P_{LR} = A_0 + A_2 \left( \frac{\omega}{\omega_c} \right)^2 + A_4 \left( \frac{\omega}{\omega_c} \right)^4$$

where

$$A_0 = \left( 1 + \frac{(1 - R_{Ln})^2}{4R_{Ln}} \right)$$

$$A_2 = \left( \frac{\omega_c^2}{4R_{Ln}} \right) (R_{Ln}^2 C_n^2 + L_n^2 - 2L_n C_n R_{Ln}^2)$$

$$A_4 = \left( \frac{\omega_c^4}{4R_{Ln}} \right) (L_n^2 C_n^2 R_{Ln}^2)$$

# Two Element Low-Pass Butterworth

$$P_{LR} = A_0 + A_2 \left( \frac{\omega}{\omega_c} \right)^2 + A_4 \left( \frac{\omega}{\omega_c} \right)^4$$

Choose Butterworth response ( $k = 1$ ):

$$P_{LR} = 1 + \left( \frac{\omega}{\omega_c} \right)^{2N} \Rightarrow N = 2$$

Hence

$$A_0 = \left( 1 + \frac{(1 - R_{Ln})^2}{4R_{Ln}} \right) = 1$$

$$A_2 = \left( \frac{\omega_c^2}{4R_{Ln}} \right) (R_{Ln}^2 C_n^2 + L_n^2 - 2L_n C_n R_{Ln}^2) = 0$$

$$A_4 = \left( \frac{\omega_c^4}{4R_{Ln}} \right) (L_n^2 C_n^2 R_{Ln}^2) = 1$$

**Note:**  
The order  $N$  of the filter is the same as the number of  $(L, C)$  elements.



# Two Element Low-Pass Butterworth (cont.)

Three equations:

$$A_0 = \left( 1 + \frac{(1 - R_{Ln})^2}{4R_{Ln}} \right) = 1$$

$$A_2 = \left( \frac{\omega_c^2}{4R_{Ln}} \right) (R_{Ln}^2 C_n^2 + L_n^2 - 2L_n C_n R_{Ln}^2) = 0$$

$$A_4 = \left( \frac{\omega_c^4}{4R_{Ln}} \right) (L_n^2 C_n^2 R_{Ln}^2) = 1$$

Solution:

$A_0$  equation:

$$R_{Ln} = 1$$

$A_2$  equation:

$$L_n = C_n$$

$A_4$  equation:

$$L_n = C_n = \frac{\sqrt{2}}{\omega_c}$$

# Two Element Low-Pass Butterworth (cont.)

Unnormalizing:

$$R_{Ln} = R_L / R_0$$

$$L_n = L / R_0$$

$$C_n = CR_0$$



$$R_L = R_{Ln} R_0$$

$$L = L_n R_0$$

$$C = C_n / R_0$$

where

$$R_{Ln} = 1$$


$$L_n = C_n = \sqrt{2} / \omega_c$$

Hence:

$$R_L = R_0$$

$$L = R_0 \frac{\sqrt{2}}{\omega_c}$$
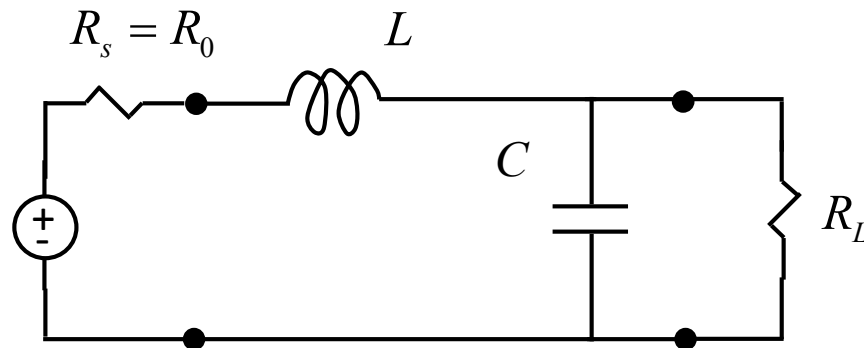
$$C = \frac{1}{R_0} \frac{\sqrt{2}}{\omega_c}$$



# Two Element Low-Pass Butterworth (cont.)

## Example


Design a low-pass Butterworth filter

$$N = 2$$

$$k = 1$$

$$f_c = 1 \text{ GHz}$$

$$R_0 = R_L = 50 \Omega$$

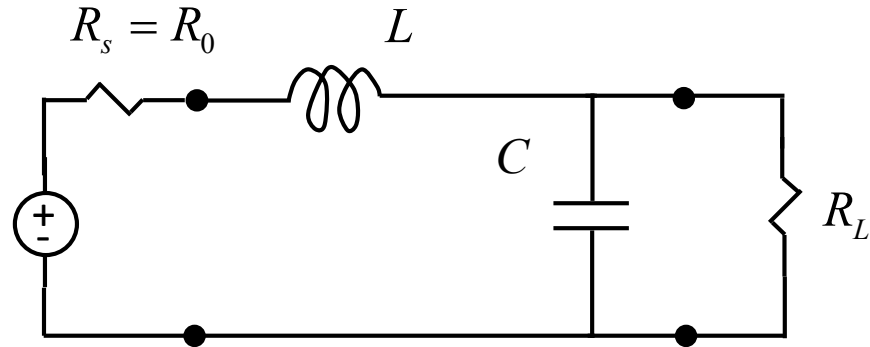


Recall:  $k = 1 \Rightarrow P_{LR}(\omega_c) = 2 \Rightarrow \text{IL}(\omega_c) = 3 \text{ dB}$

$$R_L = R_0$$

$$L = R_0 \frac{\sqrt{2}}{\omega_c}$$
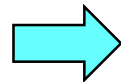
$$C = \frac{1}{R_0} \frac{\sqrt{2}}{\omega_c}$$



$$R_L = R_0 = 50 [\Omega]$$

$$L = 50 \frac{\sqrt{2}}{2\pi 10^9} [\text{H}]$$

$$C = \frac{1}{50} \frac{\sqrt{2}}{2\pi 10^9} [\text{F}]$$


$$R_L = R_0 = 50 [\Omega]$$

$$L = 11.25 [\text{nH}]$$

$$C = 4.50 [\text{pF}]$$


# Two Element Low-Pass Butterworth (cont.)

## Results from Ansys Designer

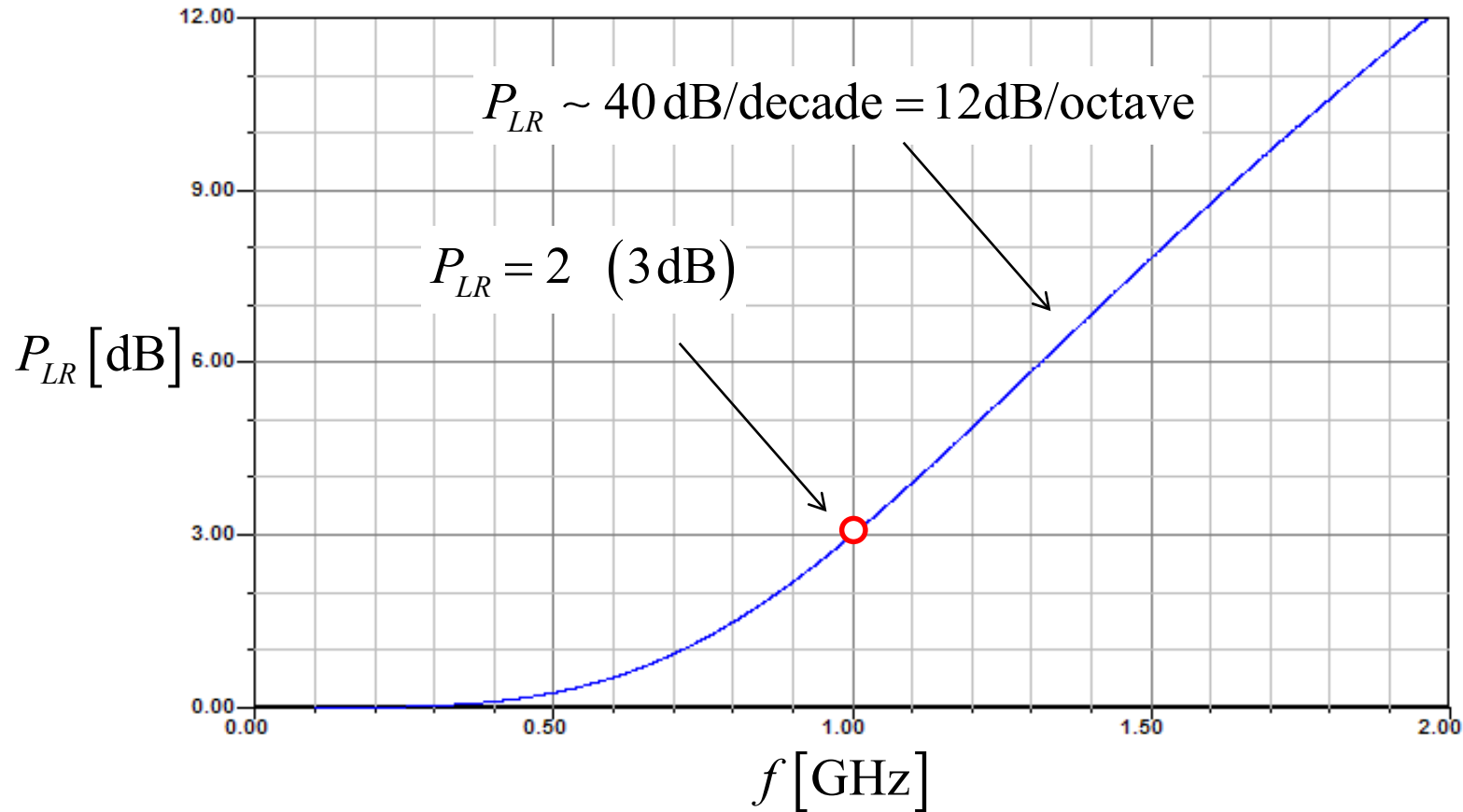

# Two Element Low-Pass Butterworth (cont.)

## Results from Ansys Designer

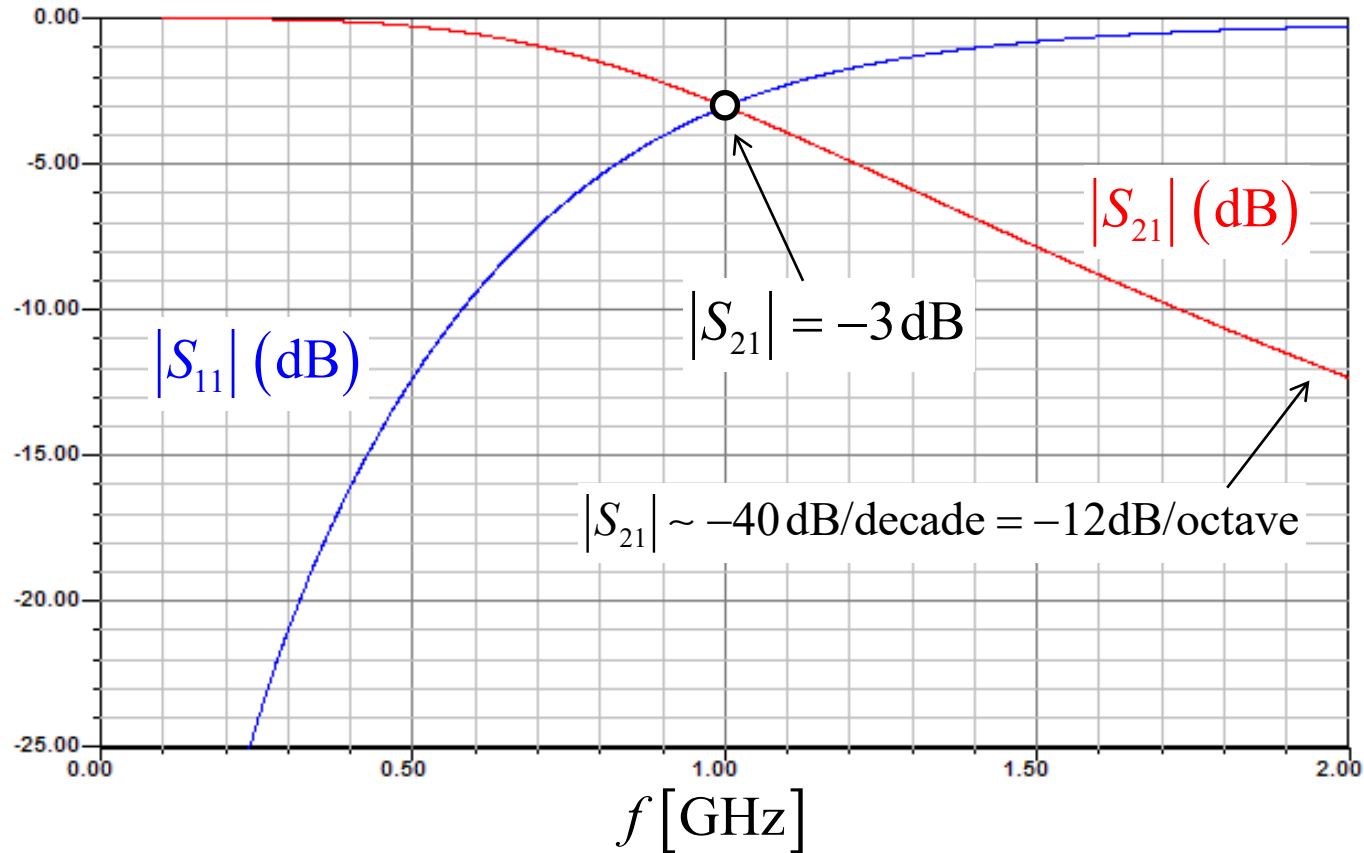

Recall:  $IL = -S_{21}^{\text{dB}}$ ,  $|S_{11}|^2 = 1 - |S_{21}|^2$  (lossless)

# Two Element Low-Pass Chebyshev

$$P_{LR} = A_0 + A_2 \left( \frac{\omega}{\omega_c} \right)^2 + A_4 \left( \frac{\omega}{\omega_c} \right)^4$$

Choose Chebyshev response (arbitrary  $k$  value):

$$P_{LR}(\omega) = 1 + k^2 T_N^2 \left( \frac{\omega}{\omega_c} \right) \Rightarrow N = 2$$

so

$$P_{LR}(\omega) = 1 + k^2 \left( 4 \left( \frac{\omega}{\omega_c} \right)^4 - 4 \left( \frac{\omega}{\omega_c} \right)^2 + 1 \right)$$

Note:

$$T_2(x) = 2x^2 - 1$$

$$T_2^2(x) = 4x^4 - 4x^2 + 1$$

Hence:

$$A_0 = 1 + k^2$$

$$A_2 = -4k^2$$

$$A_4 = 4k^2$$

# Two Element Low-Pass Chebyshev (cont.)

Hence:

$$A_0 = \left( 1 + \frac{(1 - R_{Ln})^2}{4R_{Ln}} \right) = 1 + k^2$$

$$A_2 = \left( \frac{\omega_c^2}{4R_{Ln}} \right) (R_{Ln}^2 C_n^2 + L_n^2 - 2L_n C_n R_{Ln}^2) = -4k^2$$

$$A_4 = \left( \frac{\omega_c^4}{4R_{Ln}} \right) (L_n^2 C_n^2 R_{Ln}^2) = 4k^2$$

Solution (please see the Appendix):

$$R_{Ln} = 1 + 2k^2 \pm 2k\sqrt{1 + k^2}$$

$$L_n C_n = 4 \left( \frac{k}{\omega_c^2} \right) \frac{1}{\sqrt{R_{Ln}}}$$

$$C_n^2 = \frac{1}{2R_{Ln}^2} \left( 2pR_{Ln}^2 - 4k^2 \left( \frac{4R_{Ln}}{\omega_c^2} \right) \pm \sqrt{\left( 4k^2 \left( \frac{4R_{Ln}}{\omega_c^2} \right) - 2pR_{Ln}^2 \right)^2 - 4R_{Ln}^2 p^2} \right)$$

# Appendix

## Chebyshev solution:

$$A_0 = \left( 1 + \frac{(1 - R_{Ln})^2}{4R_{Ln}} \right) = 1 + k^2$$

$$A_2 = \left( \frac{\omega_c^2}{4R_{Ln}} \right) (R_{Ln}^2 C_n^2 + L_n^2 - 2L_n C_n R_{Ln}^2) = -4k^2$$

$$A_4 = \left( \frac{\omega_c^4}{4R_{Ln}} \right) (L_n^2 C_n^2 R_{Ln}^2) = 4k^2$$

## $A_0$ equation:

$$1 + \frac{(1 - R_{Ln})^2}{4R_{Ln}} = 1 + k^2$$

$$\Rightarrow \frac{(1 - R_{Ln})^2}{4R_{Ln}} = k^2$$

$$\Rightarrow (1 - R_{Ln})^2 = k^2 4R_{Ln}$$

$$1 - 2R_{Ln} + R_{Ln}^2 = k^2 4R_{Ln}$$

$$\Rightarrow R_{Ln}^2 - R_{Ln} (2 + 4k^2) + 1 = 0$$

$$\Rightarrow R_{Ln} = 1 + 2k^2 \pm 2k\sqrt{1 + k^2}$$

**Note:**

$R_L \neq R_0$  for  $N = \text{even}$ .

(It turns out that  $R_L = R_0$  for  $N = \text{odd}$ .)



# Appendix (cont.)


$$A_0 = \left( 1 + \frac{(1 - R_{Ln})^2}{4R_{Ln}} \right) = 1 + k^2$$

$$A_2 = \left( \frac{\omega_c^2}{4R_{Ln}} \right) (R_{Ln}^2 C_n^2 + L_n^2 - 2L_n C_n R_{Ln}^2) = -4k^2$$

$$A_4 = \left( \frac{\omega_c^4}{4R_{Ln}} \right) (L_n^2 C_n^2 R_{Ln}^2) = 4k^2$$

$A_4$  equation:

$$L_n^2 C_n^2 = 16 \left( \frac{k^2}{\omega_c^4} \right) \frac{1}{R_{Ln}}$$

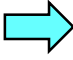
$$L_n C_n = 4 \left( \frac{k}{\omega_c^2} \right) \frac{1}{\sqrt{R_{Ln}}}$$

# Appendix (cont.)

$$A_0 = \left( 1 + \frac{(1 - R_{Ln})^2}{4R_{Ln}} \right) = 1 + k^2$$

$$A_2 = \left( \frac{\omega_c^2}{4R_{Ln}} \right) (R_{Ln}^2 C_n^2 + L_n^2 - 2L_n C_n R_{Ln}^2) = -4k^2$$

$$A_4 = \left( \frac{\omega_c^4}{4R_{Ln}} \right) (L_n^2 C_n^2 R_{Ln}^2) = 4k^2$$

$A_2$  equation:

$$\left( \frac{\omega_c^2}{4R_{Ln}} \right) (R_{Ln}^2 C_n^2 + L_n^2 - 2L_n C_n R_{Ln}^2) = -4k^2$$

$$\Rightarrow (R_{Ln}^2 C_n^2 + L_n^2 - 2L_n C_n R_{Ln}^2) = -4k^2 \left( \frac{4R_{Ln}}{\omega_c^2} \right)$$

$$\Rightarrow (R_{Ln}^2 C_n^2 + L_n^2) = -4k^2 \left( \frac{4R_{Ln}}{\omega_c^2} \right) + 2(L_n C_n) R_{Ln}^2 \quad (\text{The RHS is known.})$$

# Appendix (cont.)

$A_2$  equation (cont.):

$$\left(R_{Ln}^2 C_n^2 + L_n^2\right) = -4k^2 \left(\frac{4R_{Ln}}{\omega_c^2}\right) + 2pR_{Ln}^2 \quad \left(p \equiv L_n C_n = 4 \left(\frac{k}{\omega_c^2}\right) \frac{1}{\sqrt{R_{Ln}}}\right)$$

$$\Rightarrow \left(R_{Ln}^2 C_n^2 + \frac{p^2}{C_n^2}\right) = -4k^2 \left(\frac{4R_{Ln}}{\omega_c^2}\right) + 2pR_{Ln}^2$$

$$\Rightarrow \left(R_{Ln}^2 C_n^4 + p^2\right) = C_n^2 \left(-4k^2 \left(\frac{4R_{Ln}}{\omega_c^2}\right) + 2pR_{Ln}^2\right)$$

$$\Rightarrow R_{Ln}^2 x^2 + x \left(4k^2 \left(\frac{4R_{Ln}}{\omega_c^2}\right) - 2pR_{Ln}^2\right) + p^2 = 0 \quad (x \equiv C_n^2)$$

$$\Rightarrow x = \frac{1}{2R_{Ln}^2} \left(2pR_{Ln}^2 - 4k^2 \left(\frac{4R_{Ln}}{\omega_c^2}\right) \pm \sqrt{\left(4k^2 \left(\frac{4R_{Ln}}{\omega_c^2}\right) - 2pR_{Ln}^2\right)^2 - 4R_{Ln}^2 p^2}\right)$$