

# ECE 5317-6351


# Microwave Engineering

**Fall 2019**

Prof. David R. Jackson  
Dept. of ECE

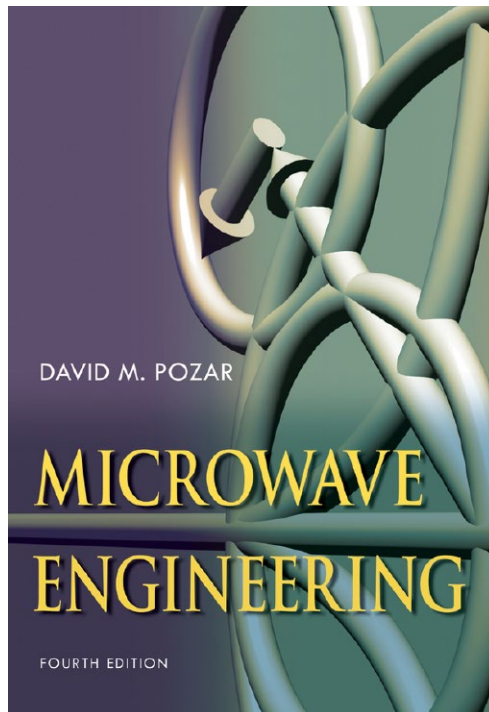**Notes 24**

**Filter Design Part 3:  
Transmission Line Filters**



# Filter Design Using Transmission Lines

In this set of notes we examine filter design using transmission Lines

## Recipe:

- We start with a lumped-element design.
- We can use low and high impedance lines to approximate lumped elements: works for series  $L$  and shunt  $C$  elements (what you need in a low-pass design).
- We can also apply Richard's transformation to change any lumped element design into one with transmission lines.
- We can also use the Kuroda identities to change series TL elements into parallel ones (more convenient for microstrip implementation).


# Approximate Realization of Lumped Elements

## Approximate method:

- Narrow and wide sections of microstrip line can be used to approximately realize series lumped  $L$  and shunt  $C$  elements.
- Although approximate, this is a simple technique.
- This works well for low-pass filters (where we need series  $L$  and shunt  $C$  elements).
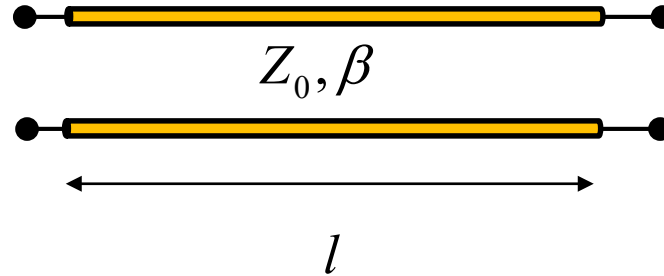
# Approximate Realization of Lumped Elements (cont.)


Consider a section of transmission line (e.g., microstrip line):



$$Z_{11} = Z_{22} = -jZ_0 \cot(\beta l)$$

$$Z_{21} = Z_{12} = -jZ_0 / \sin(\beta l)$$

Model:

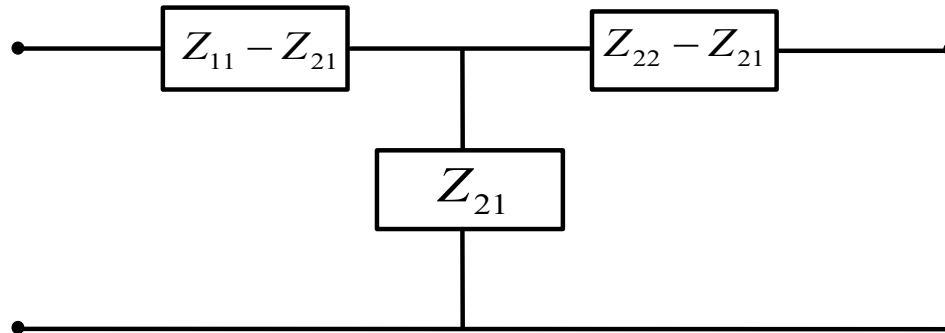

# Approximate Realization of Lumped Elements (cont.)

Element values in the model:

$$Z_{11} - Z_{21} = jZ_0 \tan(\beta l / 2)$$

$$Z_{21} = -jZ_0 / \sin(\beta l)$$


Details of calculation:

$$Z_{11} - Z_{21} = -jZ_0 (\cot(\beta l) - 1 / \sin(\beta l))$$

$$= -jZ_0 \left( \frac{\cos(\beta l) - 1}{\sin(\beta l)} \right)$$


$$= jZ_0 \tan(\beta l / 2)$$

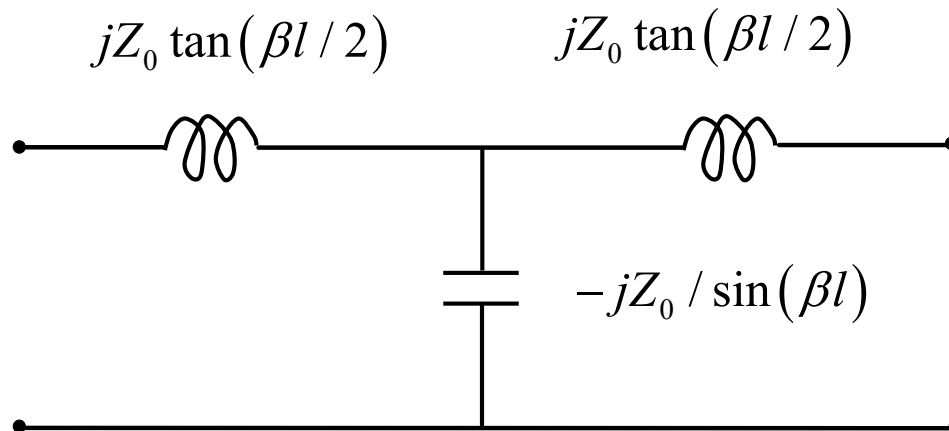**Note:**  $\tan(x/2) = \frac{1 - \cos x}{\sin x}$



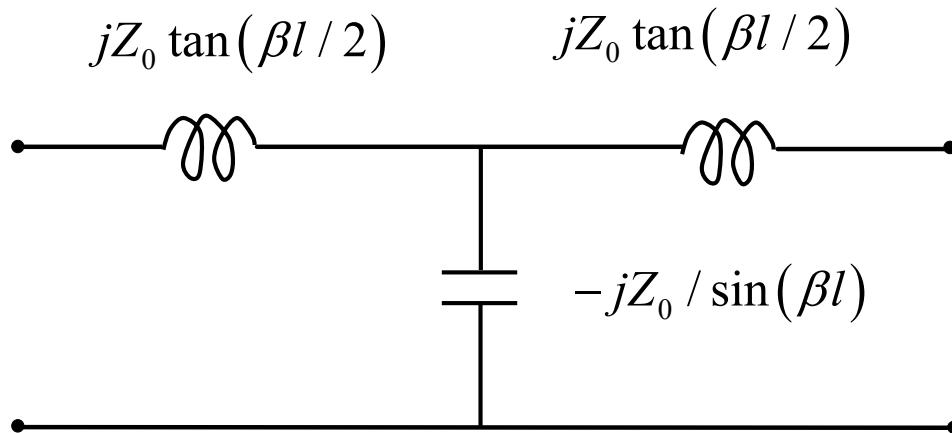
# Approximate Realization of Lumped Elements (cont.)

Assume:  $Z_0 \gg 1$ ,  $\beta l \ll 1$  (narrow and short microstrip line)



$$\Rightarrow \omega L = Z_0 (\beta l)$$


$$jZ_0 (\beta l) \Omega$$

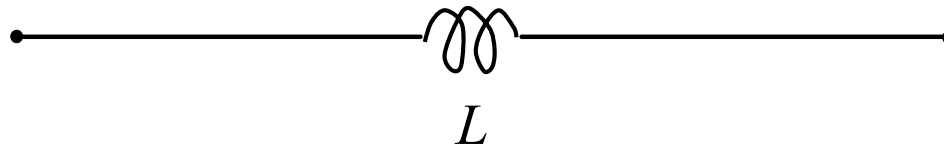


Series inductor
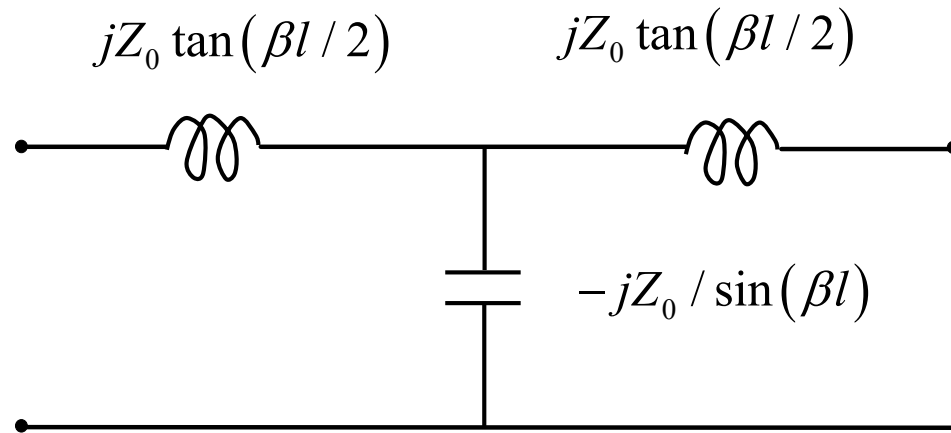
# Approximate Realization of Lumped Elements (cont.)

Assume:  $Z_0 \ll 1$ ,  $\beta l \ll 1$  (wide and short microstrip line)


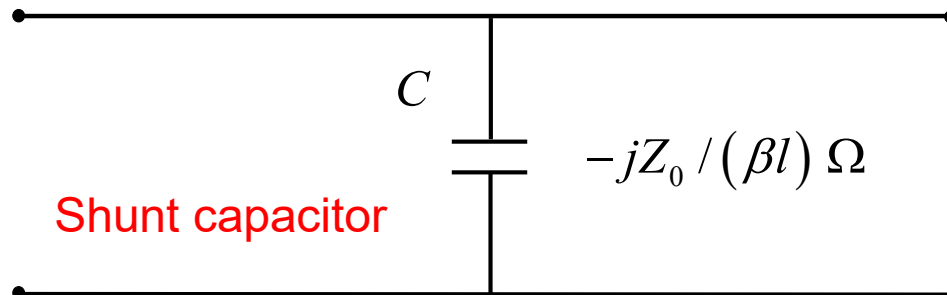
$$\Rightarrow \frac{1}{\omega C} = Z_0 / (\beta l)$$



# Approximate Realization of Lumped Elements (cont.)

From the previous derivation:

$$\left. \begin{aligned} \omega L &= Z_0^{high} (\beta l) \\ \frac{1}{\omega C} &= Z_0^{low} / (\beta l) \end{aligned} \right\} \begin{aligned} &\text{Solve for the lengths of the lines that are needed} \\ &\text{Choose: } \omega = \omega_c \end{aligned}$$

$$\text{Series inductors: } \omega_c L = Z_{high} (\beta l)_{\omega_c}$$

$$\text{Shunt capacitors: } \frac{1}{\omega_c C} = Z_{low} / (\beta l)_{\omega_c}$$




$$\text{Narrow lines (series inductors): } (\beta l)_{\omega_c} = \frac{\omega_c L}{Z_{high}}$$

$$\text{Wide lines (shunt capacitors): } (\beta l)_{\omega_c} = \omega_c C Z_{low}$$


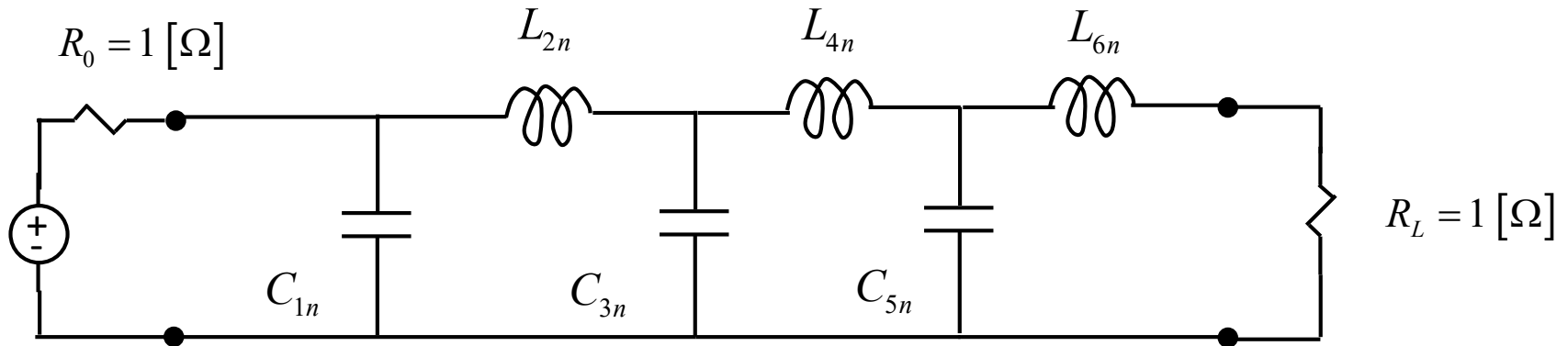
# Example

Design an  $N = 6$  Butterworth stepped-impedance low-pass filter for a matched  $50\ \Omega$  load with a cutoff frequency of 2.5 GHz. Choose  $Z_{low} = 20\ \Omega$ ,  $Z_{high} = 120\ \Omega$ .



Choose type “a”

From table:

$$g_1 = C_{1n} = 0.517$$

$$g_2 = L_{2n} = 1.414$$

$$g_3 = C_{3n} = 1.932$$


$$g_4 = L_{4n} = 1.932$$

$$g_5 = C_{5n} = 1.414$$

$$g_6 = L_{6n} = 0.517$$

# Example (cont.)

De-normalized filter:

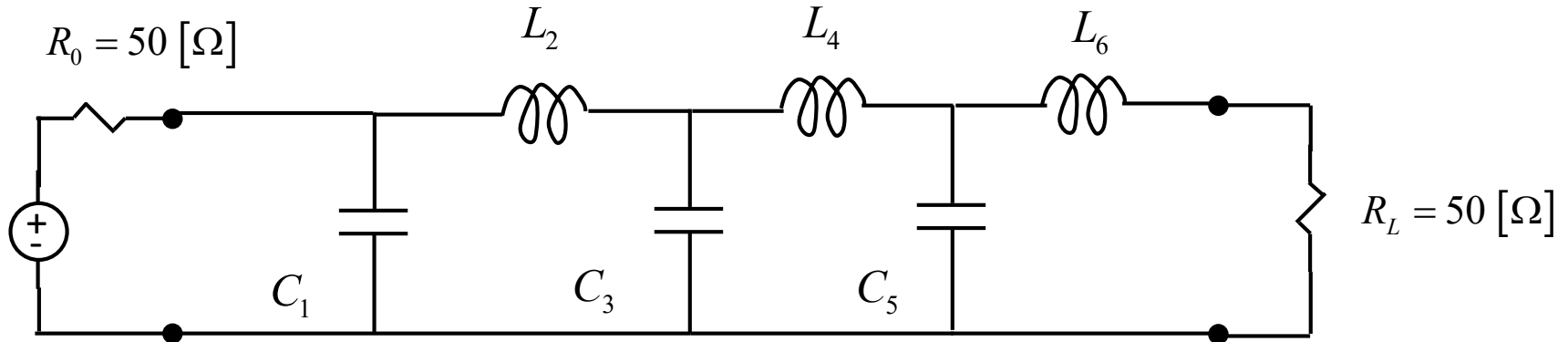

$$C_{1n} = 0.517 \text{ [F]}$$

$$L_{2n} = 1.414 \text{ [H]}$$

$$C_{3n} = 1.932 \text{ [F]}$$


$$L_{4n} = 1.932 \text{ [H]}$$

$$C_{5n} = 1.414 \text{ [F]}$$

$$L_{6n} = 0.517 \text{ [H]}$$

$$L = (L_n R_0) / \omega_c$$

$$C = (C_n / R_0) / \omega_c$$

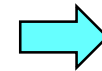

$$C_1 = 0.658 \text{ [pF]}$$

$$L_2 = 4.5 \text{ [nH]}$$


$$C_3 = 2.46 \text{ [pF]}$$

$$L_4 = 6.15 \text{ [nH]}$$

$$C_5 = 1.80 \text{ [pF]}$$

$$L_6 = 1.65 \text{ [nH]}$$

# Example (cont.)

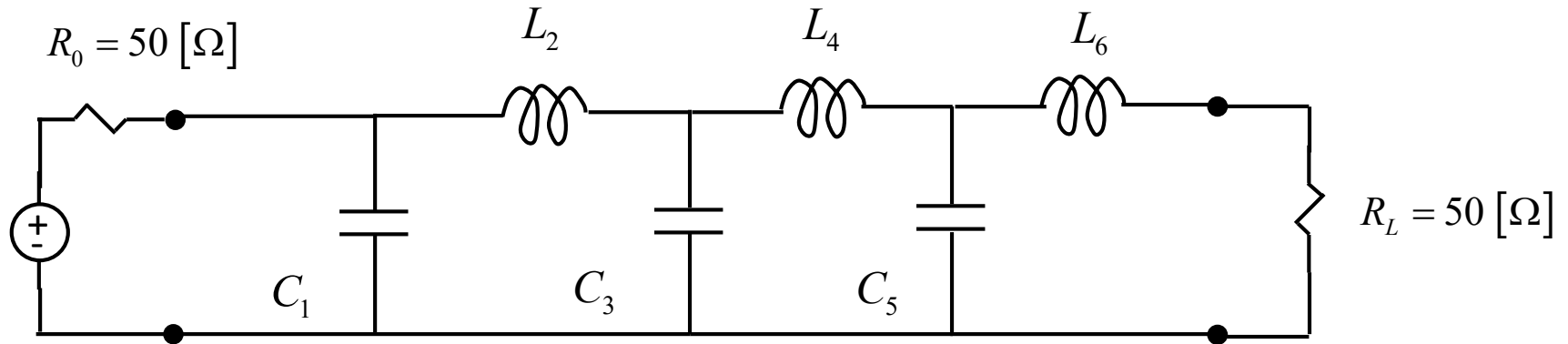

Choice:

$$Z_{low} = 20 \Omega$$

$$Z_{high} = 120 \Omega$$

$$C_1 = 0.658 \text{ [pF]}$$

$$L_2 = 4.5 \text{ [nH]}$$

$$C_3 = 2.46 \text{ [pF]}$$

$$L_4 = 6.15 \text{ [nH]}$$

$$C_5 = 1.80 \text{ [pF]}$$

$$L_6 = 1.65 \text{ [nH]}$$

$$(\beta l)_{\omega_c} = \frac{\omega_c L}{Z_{high}} \quad (\#2, \#4, \#6)$$

$$(\beta l)_{\omega_c} = \omega_c C Z_{low} \quad (\#1, \#3, \#5)$$



$$(\beta l)_1 = 0.207 \text{ [rad]} \quad (11.8^\circ)$$

$$(\beta l)_2 = 0.589 \text{ [rad]} \quad (11.8^\circ)$$

$$(\beta l)_3 = 0.773 \text{ [rad]} \quad (44.3^\circ)$$


$$(\beta l)_4 = 0.805 \text{ [rad]} \quad (46.1^\circ)$$

$$(\beta l)_5 = 0.565 \text{ [rad]} \quad (32.4^\circ)$$

$$(\beta l)_6 = 0.215 \text{ [rad]} \quad (12.3^\circ)$$

# Example (cont.)

## Microstrip Realization

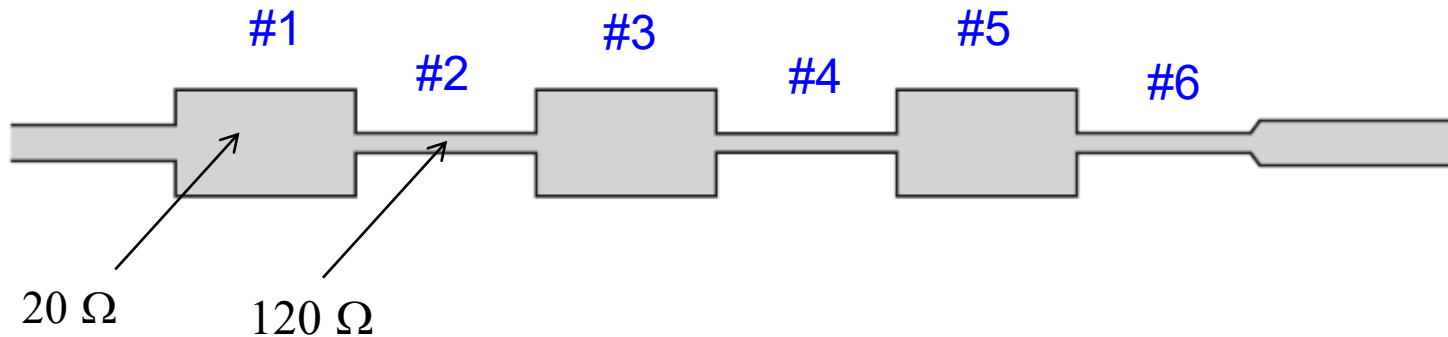

(not drawn to scale)

Figure 8.40 from Pozar

**Note:**

TX line can first be used to find the line widths (from the chosen  $Z_0$  values), and then used to find the line lengths (from the calculated electrical lengths).

# Example (cont.)

## Microstrip Realization

$$h = 1.58 \text{ [mm]}, \varepsilon_r = 4.2, \tan \delta = 0.02$$

Section	$Z_i = Z_\ell$ or $Z_h$ ( $\Omega$ )	$\beta\ell_i$ (deg)	$W_i$ (mm)	$\ell_i$ (mm)
1	20	11.8	11.3	2.05
2	120	33.8	0.428	6.63
3	20	44.3	11.3	7.69
4	120	46.1	0.428	9.04
5	20	32.4	11.3	5.63
6	120	12.3	0.428	2.41

From p. 425 of Pozar

# Example (cont.)

## Results


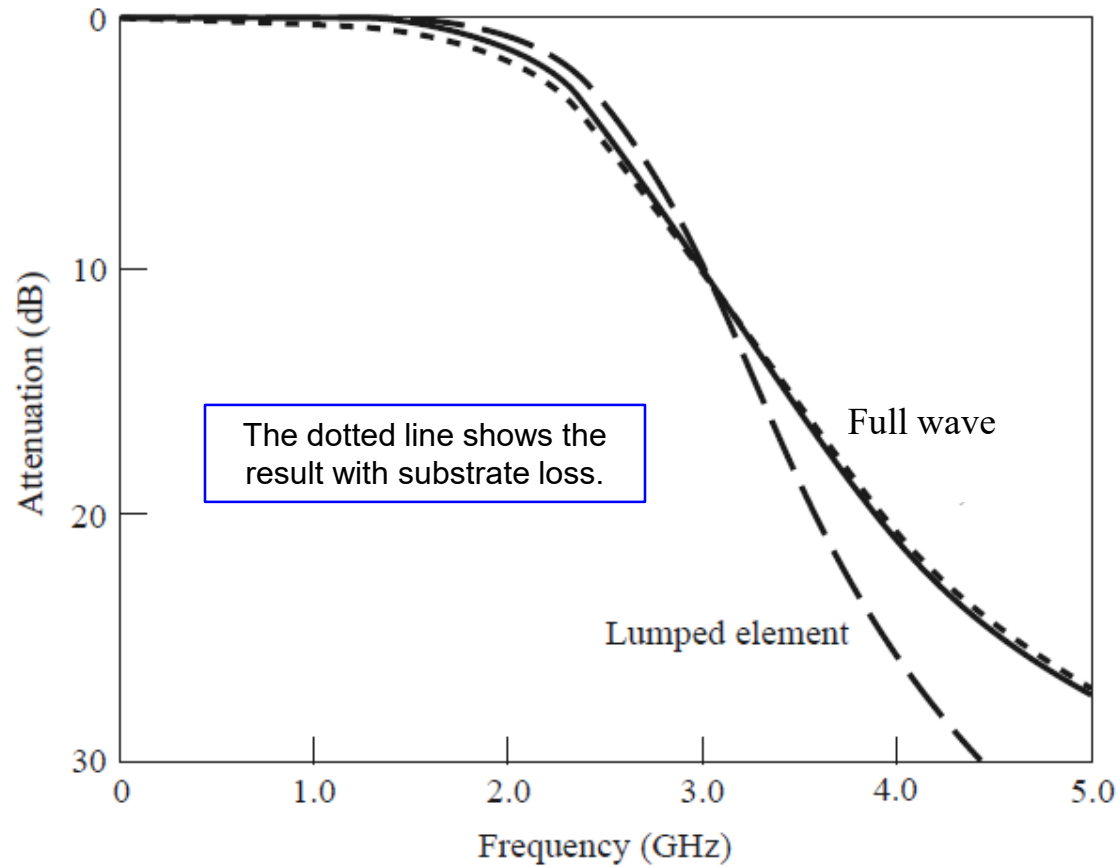


Figure 8.41 from Pozar

# Example (cont.)

Figure of an Actual Low-Pass Filter

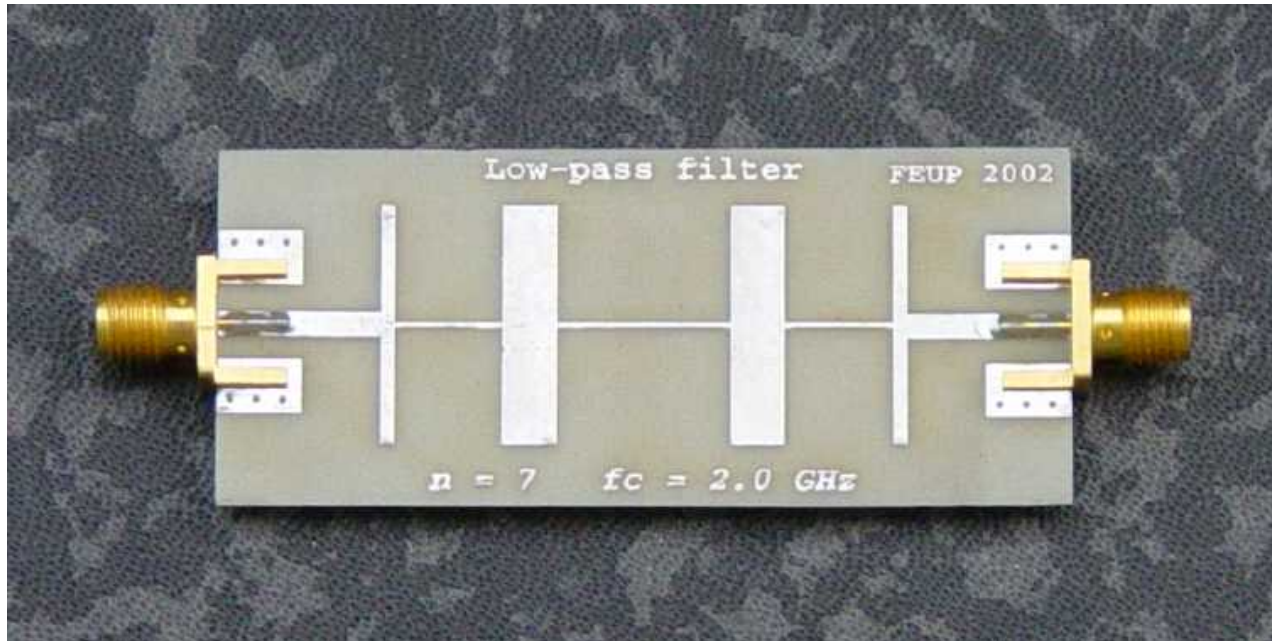

# Richard's Transformation

## Richard's transformation

### Main idea:

Short-circuited and open-circuited transmission lines are chosen to mimic the performance of the lumped  $L$  and  $C$  elements, respectively.

Richard's transformation:

$$\Omega(\omega) \equiv \omega_c \tan(\beta l) = \omega_c \tan(\omega \sqrt{\mu \epsilon} l)$$

$\Omega$  = radian frequency in lumped-element design

$\omega$  = radian frequency in transmission line design

Require:  $\Omega(\omega_c) = \omega_c \Rightarrow \tan(\omega_c \sqrt{\mu \epsilon} l) = 1 \quad (l = \lambda_g / 8 @ \omega_c)$


(The lumped-element and transmission-line circuits will have the same cutoff frequency.)


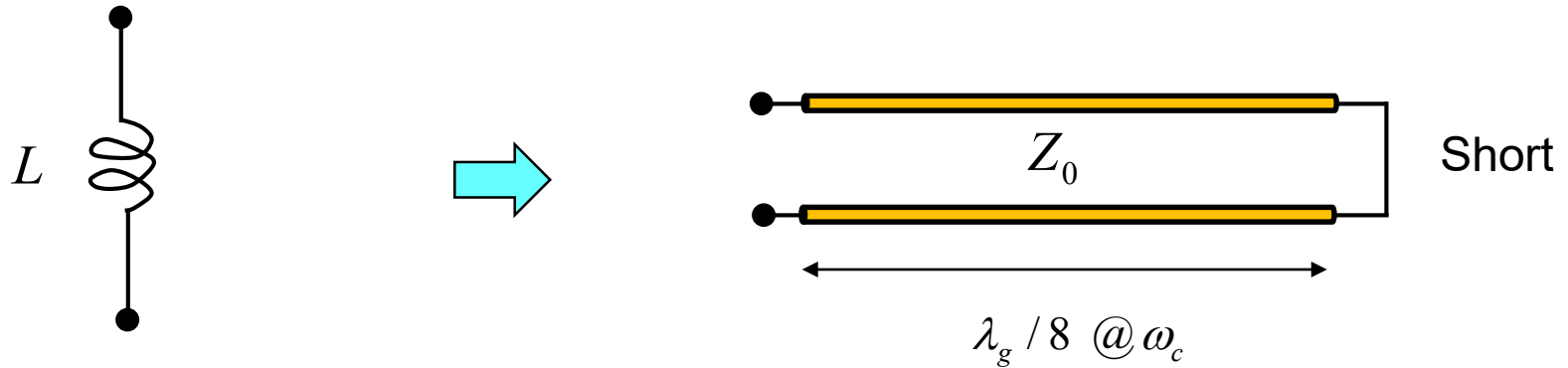
# Richard's Transformation (cont.)

At any frequency  $\omega$ , TLs can behave the same as lumped elements at frequency  $\Omega$ .

Equivalent TL model for a lumped inductor:



Require:  $j\Omega L = jZ_0 \tan(\beta l)$  (same impedance property)


$$\Rightarrow j\omega_c \tan(\beta l) L = jZ_0 \tan(\beta l)$$

$$\Rightarrow Z_0 = \omega_c L$$

The inductor then has the same impedance at any frequency  $\Omega$  as does the short-circuited transmission line at corresponding frequency  $\omega$ .
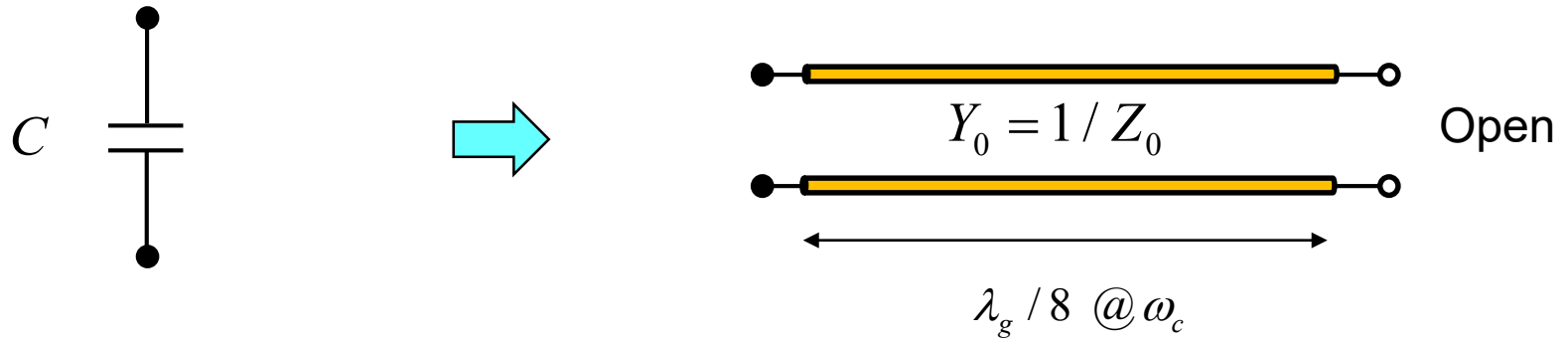
# Richard's Transformation (cont.)

Equivalent TL model for a lumped capacitor:



Require:  $j\Omega C = jY_0 \tan(\beta l)$  (same admittance property)

$$\Rightarrow j\omega_c \tan(\beta l) C = jY_0 \tan(\beta l)$$


$$\Rightarrow Y_0 = \omega_c C$$

The capacitor then has the same admittance at any frequency  $\Omega$  as does the open-circuited transmission line at corresponding frequency  $\omega$ .

# Richard's Transformation (cont.)
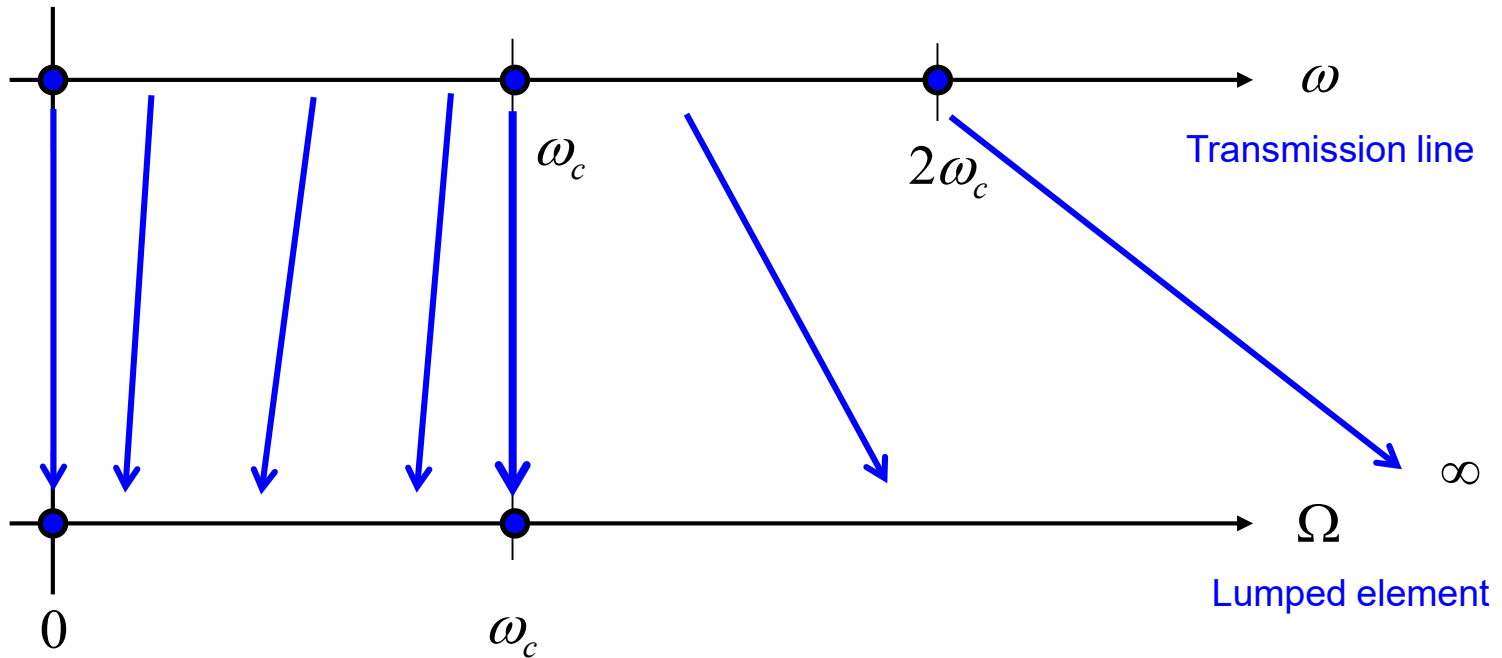
## Illustration of Mapping

$$\Omega(\omega) \equiv \omega_c \tan(\beta l) = \omega_c \tan(\omega \sqrt{\mu \epsilon} l)$$




$$@ \omega_c : \beta l = \frac{\pi}{4} \Rightarrow \tan(\beta l) = 1$$

$$@ 2\omega_c : \beta l = \frac{\pi}{2} \Rightarrow \tan(\beta l) = \infty$$


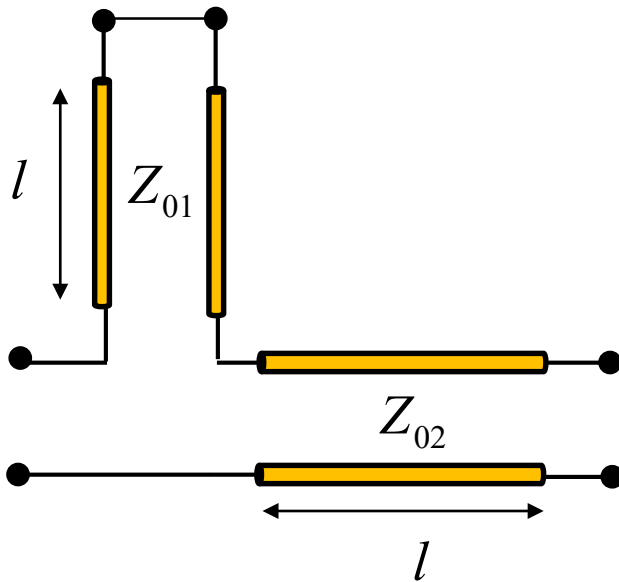
# Kuroda's Identities

Kuroda's Identity #2 is useful for transforming a series shorted TL into a parallel open-circuited TL.

**Note:** The TLs all have the same electrical length.



Line with series shorted stub

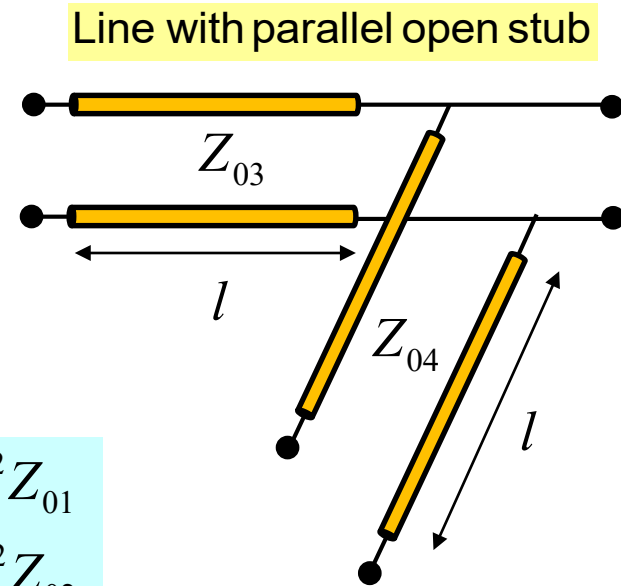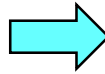

Line with parallel open stub

$$Z_{03} = n^2 Z_{01}$$

$$Z_{04} = n^2 Z_{02}$$

where

$$n^2 = 1 + \frac{Z_{02}}{Z_{01}}$$

Please see the  
Pozar book for a  
derivation.


# Example

Design an  $N = 3$  Chebyshev low-pass filter for a matched  $50 \Omega$  load with 3.0 dB of ripple in the passband and a cutoff frequency of 4.0 GHz.

Choose type “ $b$ ” low-pass prototype:

$$N = 3 = \text{odd}$$

$$\Rightarrow g_4 = 1$$

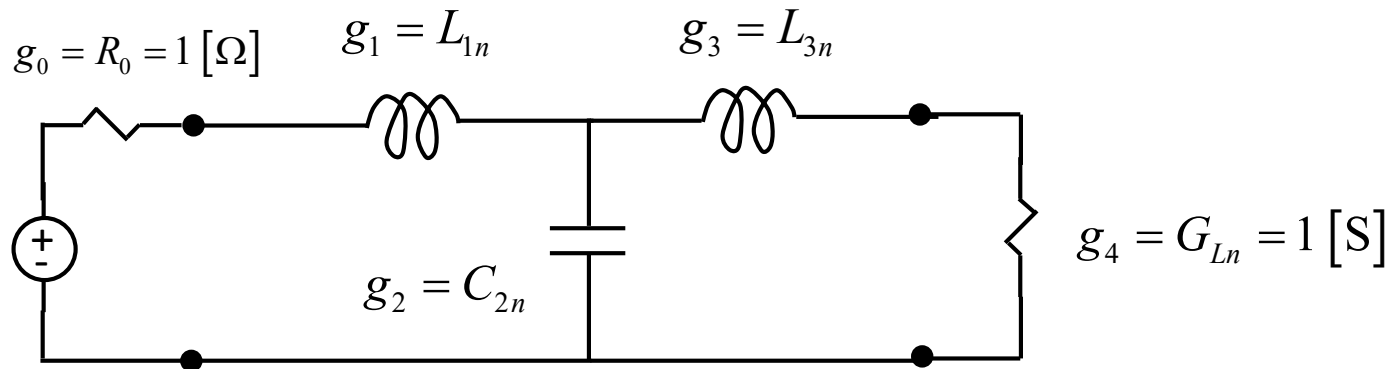

From table:


$$g_1 = L_{1n} = 3.3487$$

$$g_2 = C_{2n} = 0.7117$$

$$g_3 = L_{3n} = 3.3487$$

# Example (cont.)

Final lumped-element design:

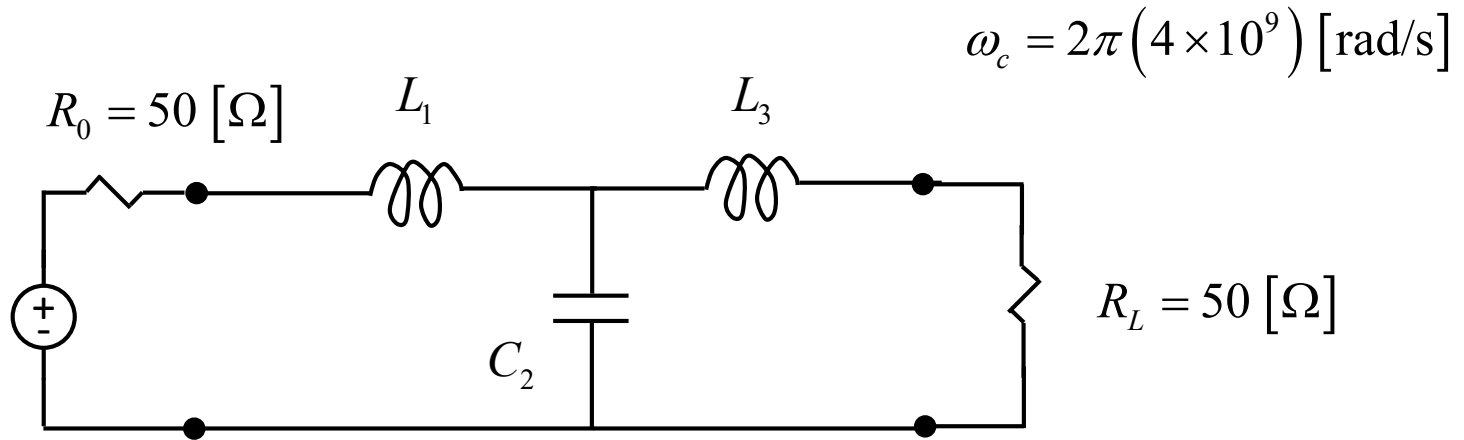

From table:

$$L_{1n} = 3.3487 \text{ [H]}$$

$$C_{2n} = 0.7117 \text{ [F]}$$

$$L_{3n} = 3.3487 \text{ [H]}$$

Denormalization:

$$L = (L_n R_0) / \omega_c$$

$$C = (C_n / R_0) / \omega_c$$

Lumped elements:


$$L_1 = 6.66 \text{ [nH]}$$

$$C_2 = 0.566 \text{ [pF]}$$

$$L_3 = 6.66 \text{ [nH]}$$
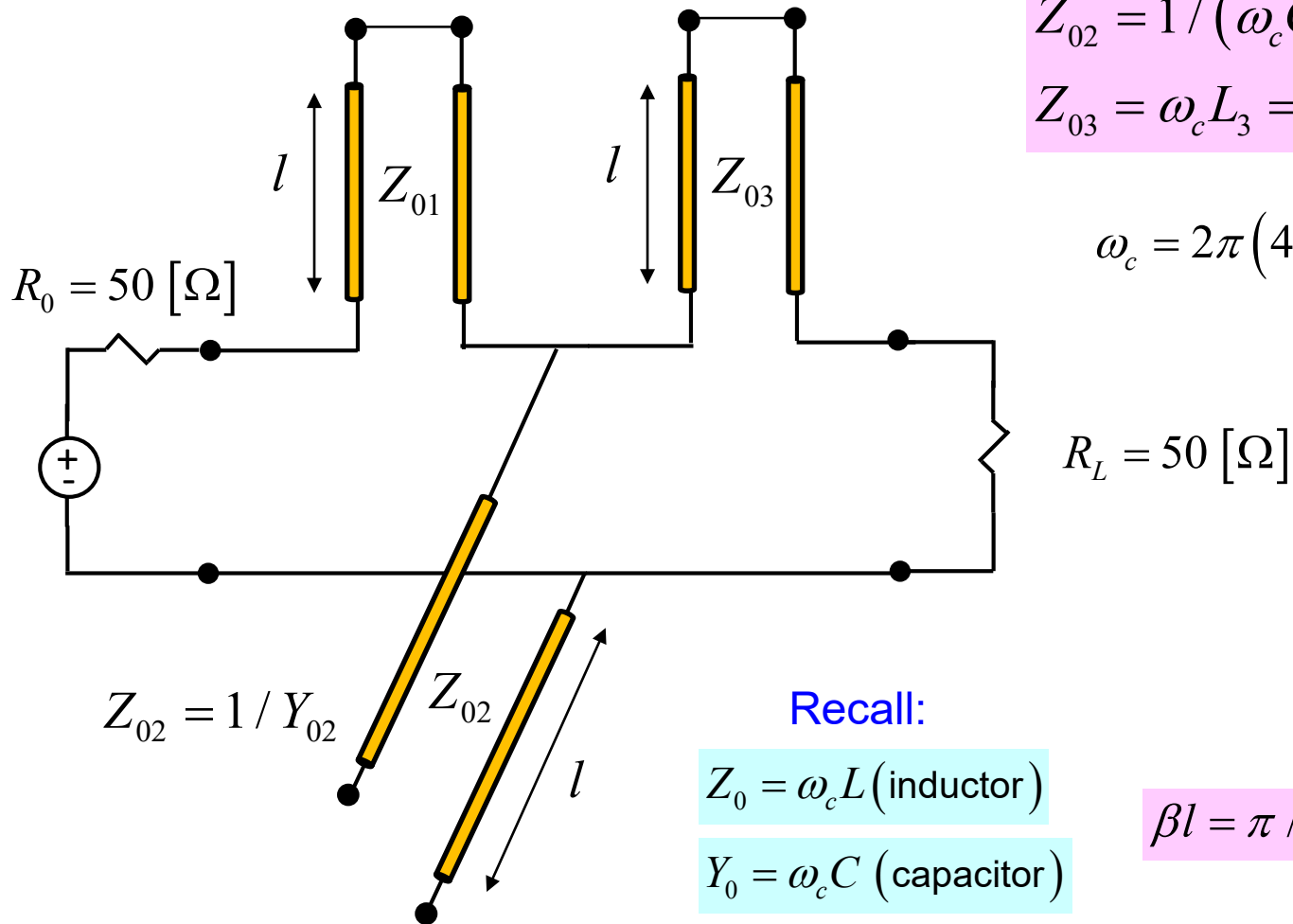
# Example (cont.)

Convert to TLs (Richard's transformation):



$$Z_{01} = \omega_c L_1 = 167.4 \text{ [}\Omega\text{]}$$

$$Z_{02} = 1 / (\omega_c C_2) = 70.3 \text{ [}\Omega\text{]}$$

$$Z_{03} = \omega_c L_3 = 167.4 \text{ [}\Omega\text{]}$$

$$\omega_c = 2\pi (4 \times 10^9) \text{ [rad/s]}$$

Recall:


$$Z_0 = \omega_c L \text{ (inductor)}$$

$$Y_0 = \omega_c C \text{ (capacitor)}$$

$$\beta l = \pi / 4 \text{ @ } 4 \text{ [GHz]}$$
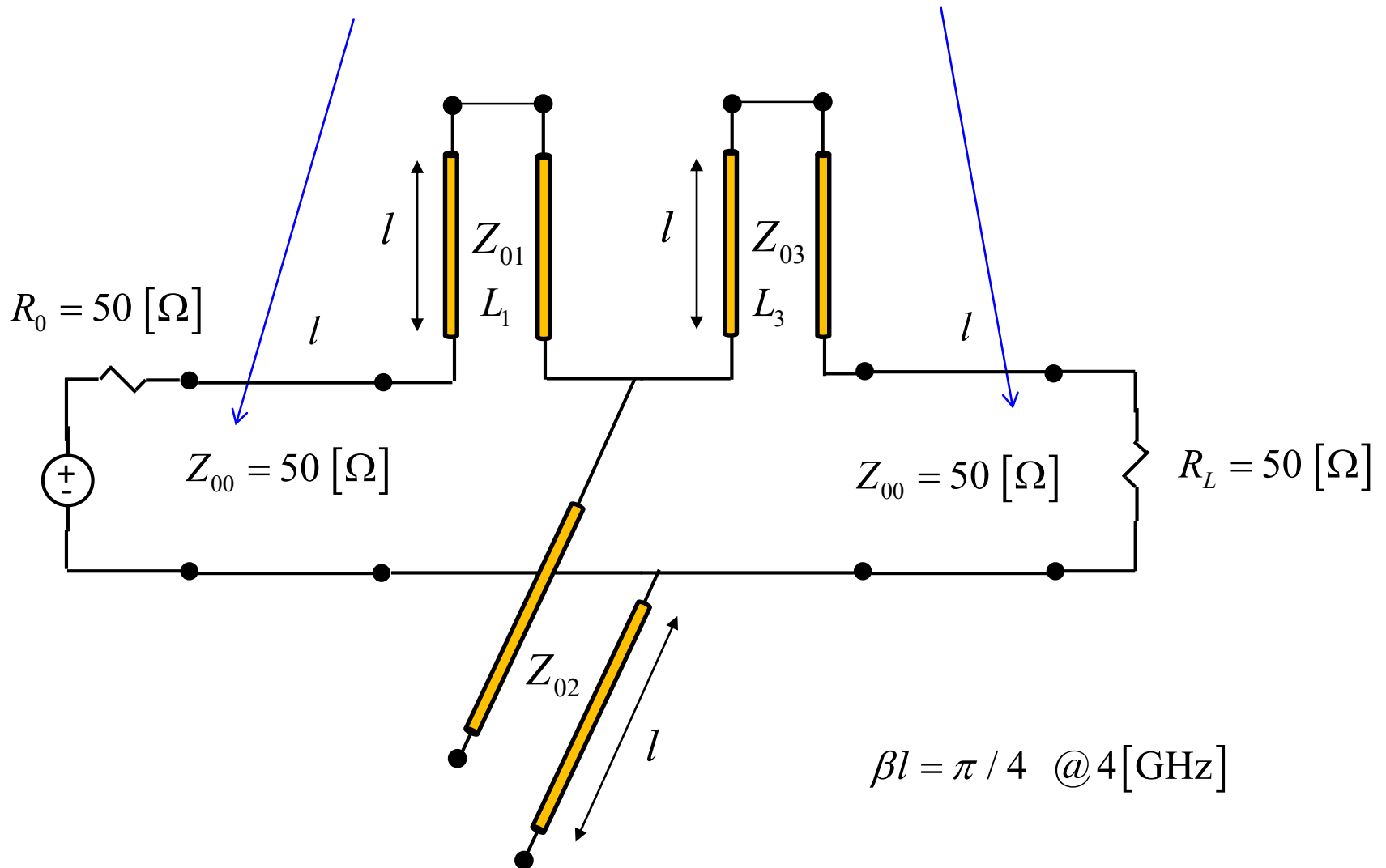
# Example (cont.)

Add extra 50  $\Omega$  transmission lines.




These extra lines do not affect the filter performance.


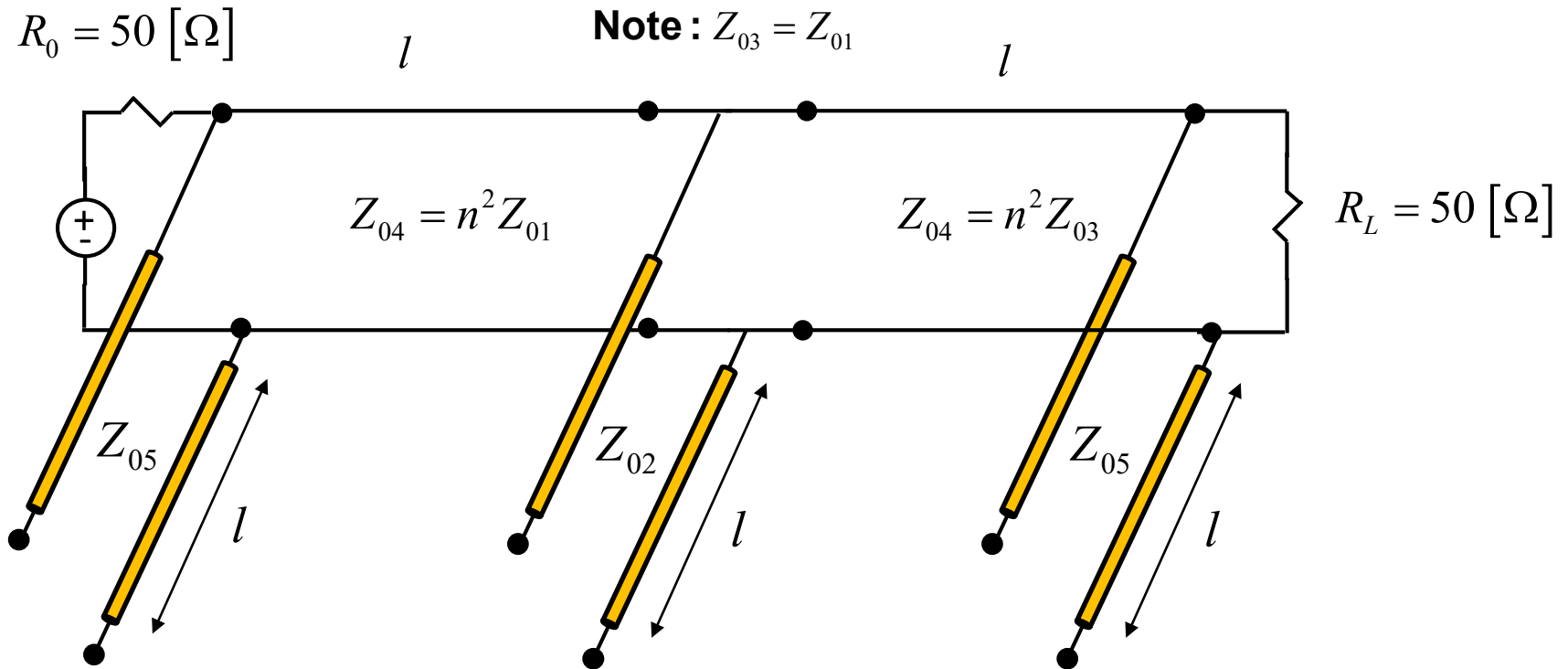
# Example (cont.)

Apply the Kuroda identity #2:

$$\beta l = \pi / 4 \quad @ 4 [\text{GHz}]$$



$$n^2 = 1 + \frac{Z_{00}}{Z_{03}} = 1.299$$


$$Z_{04} = n^2 Z_{01}$$

$$Z_{05} = n^2 Z_{00}$$

# Example (cont.)
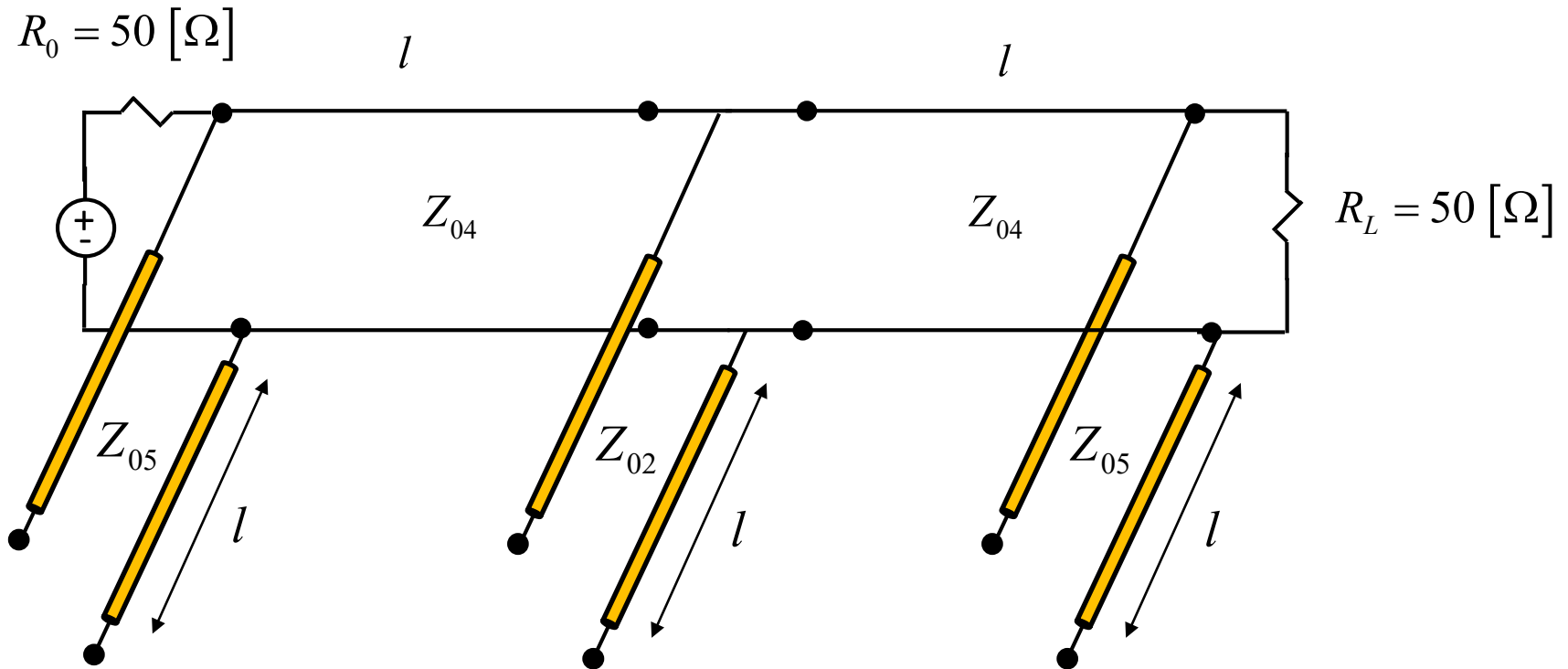
## Final Design

$$\beta l = \pi / 4 \quad @ 4 [\text{GHz}]$$



$$Z_{02} = 70.3 [\Omega]$$

$$Z_{04} = 217.5 [\Omega]$$

$$Z_{05} = 64.9 [\Omega]$$

# Example (cont.)

## Microstrip Realization


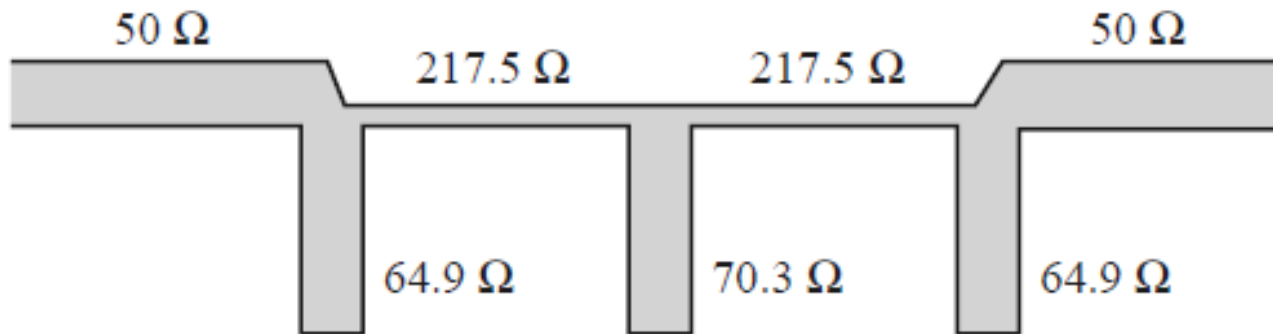


Figure 8.36 from Pozar

# Example (cont.)

## Results

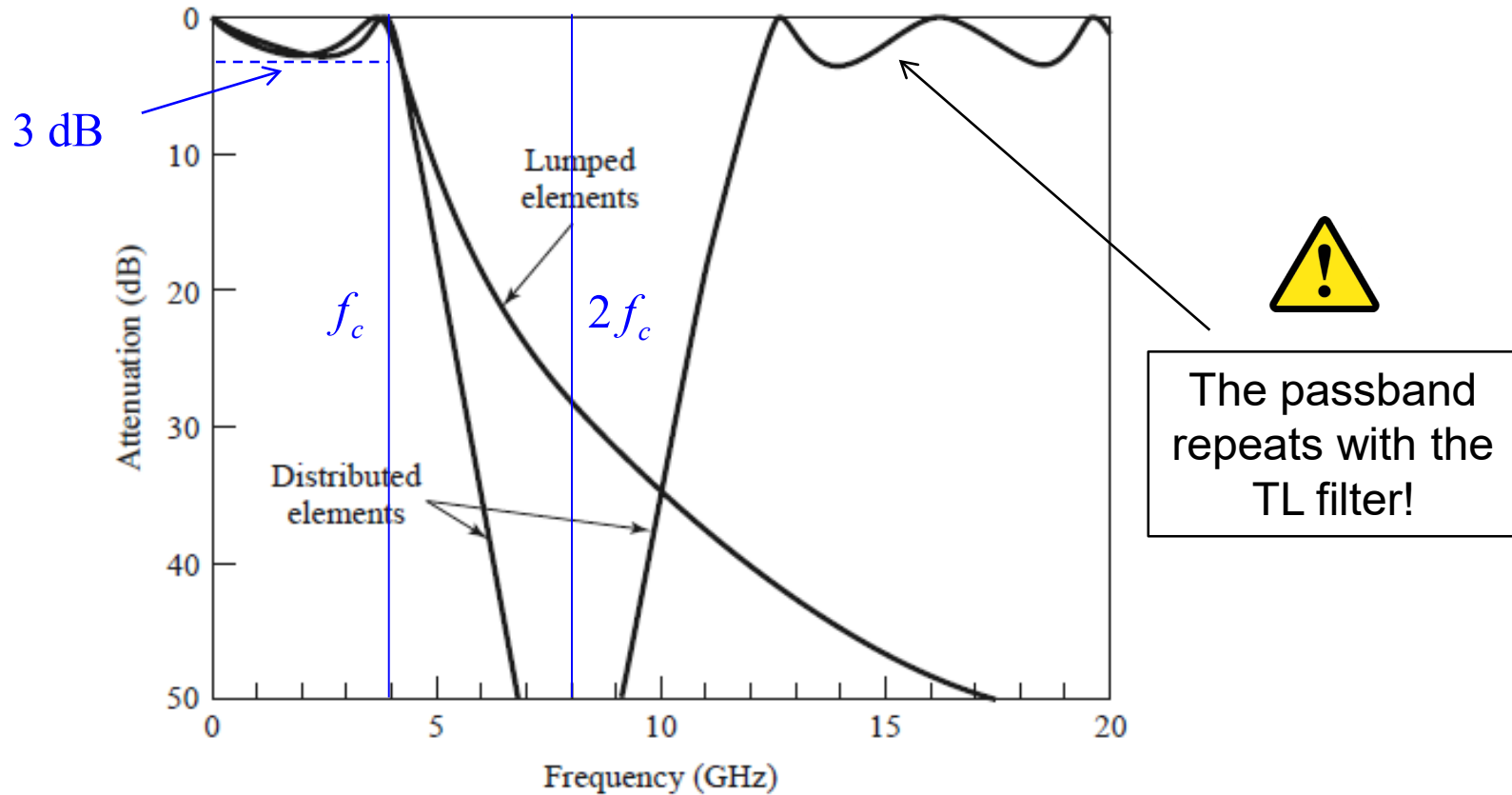

$$IL = \text{attenuation}_{\text{dB}} = -|S_{21}|_{\text{dB}}$$

Figure 8.37 from Pozar