

# ECE 5317-6351



## Microwave Engineering

Fall 2019


Prof. David R. Jackson  
Dept. of ECE

### Notes 5

### Smith Charts

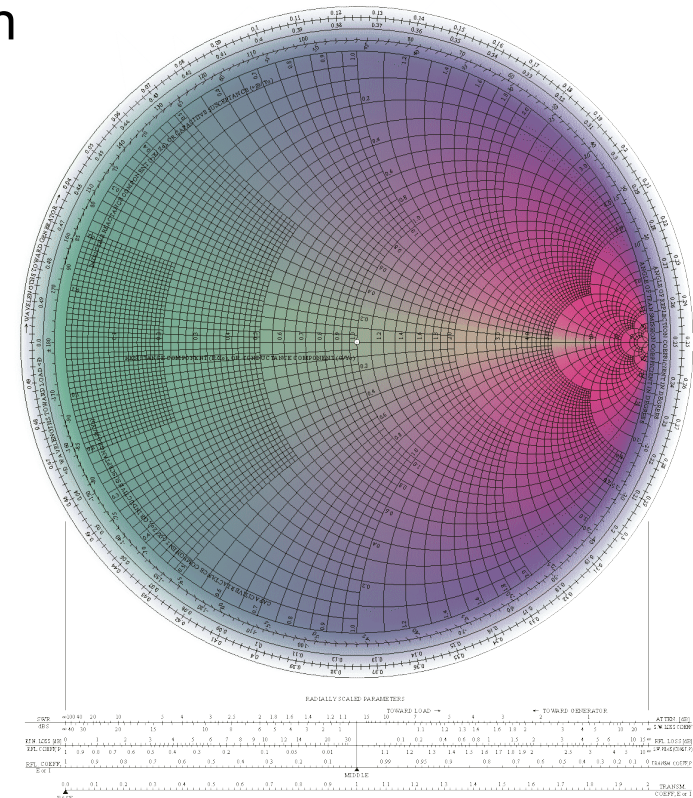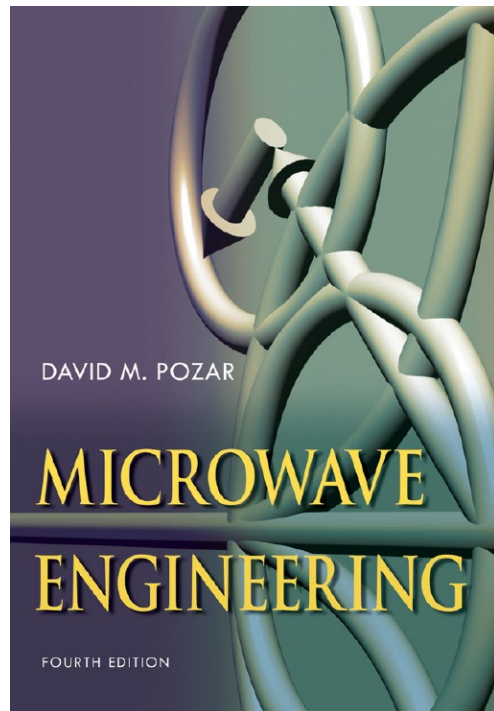

# Generalized Reflection Coefficient

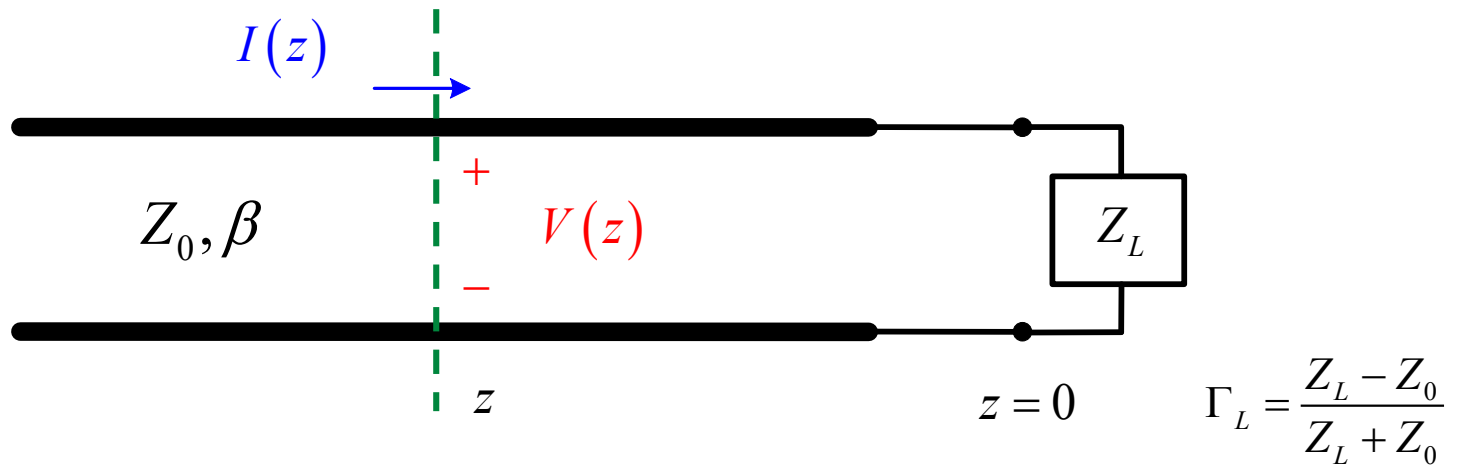

Recall:

$$V(z) = V_0^+ e^{-\gamma z} (1 + \Gamma_L e^{+2\gamma z}) = V_0^+ e^{-\gamma z} (1 + \Gamma(z))$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} (1 - \Gamma_L e^{+2\gamma z}) = \frac{V_0^+}{Z_0} e^{-\gamma z} (1 - \Gamma(z))$$

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \left( \frac{1 + \Gamma_L e^{+2\gamma z}}{1 - \Gamma_L e^{+2\gamma z}} \right) = Z_0 \left( \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \right)$$

Generalized reflection Coefficient:  $\Gamma(z) = \Gamma_L e^{+2\gamma z}$

# Generalized Reflection Coefficient (cont.)

Different forms for  $\Gamma(z)$

$$\begin{aligned}\Gamma(z) &= \Gamma_L e^{+2\gamma z} \\ &= |\Gamma_L| e^{j\phi_L} e^{+2\gamma z} \\ &= \Gamma_R(z) + j\Gamma_I(z)\end{aligned}$$

Lossless transmission line ( $\alpha = 0$ )

$$\Gamma(z) = |\Gamma_L| e^{j(\phi_L + 2\beta z)}$$

Magnitude property of  $\Gamma(z)$

$$\text{Re}\{Z_L\} \geq 0 \Rightarrow |\Gamma_L| \leq 1$$


**Proof:**

$$\begin{aligned}\Gamma_L &= \frac{(R_L + jX_L) - Z_0}{(R_L + jX_L) + Z_0} \\ &= \frac{(R_L - Z_0) + jX_L}{(R_L + Z_0) + jX_L}\end{aligned}$$

$$\Rightarrow |\Gamma_L|^2 = \frac{(R_L - Z_0)^2 + X_L^2}{(R_L + Z_0)^2 + X_L^2} \leq 1$$

# Complex $\Gamma$ Plane

$$\begin{aligned}
 \Gamma &= \Gamma(z) \\
 &= \Gamma_R(z) + j\Gamma_I(z) \\
 &= \Gamma_L e^{j(2\beta z)} \\
 &= |\Gamma_L| e^{j(\phi_L + 2\beta z)} \\
 &= |\Gamma_L| e^{j(\phi_L - 2\beta d)} \\
 &= \Gamma_L e^{-j(2\beta d)}
 \end{aligned}$$

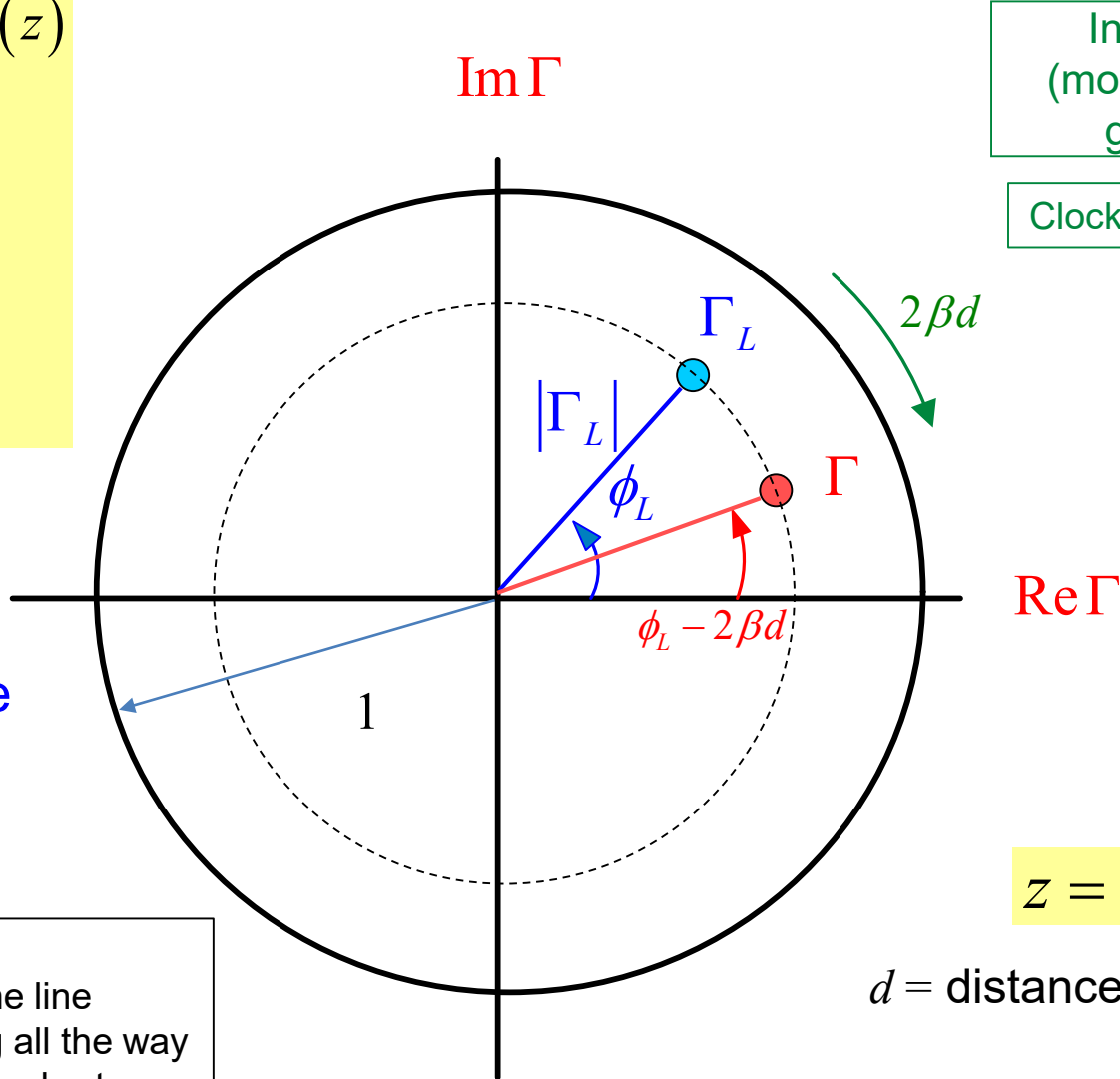

Increasing  $d$   
(moving towards  
generator)

Clockwise movement!

Lossless line

$$z = -d$$

$d$  = distance from load

**Note:**  
Going  $\lambda/2$  on the line  
corresponds to going all the way  
around the Smith chart.

# Z Chart

Start with

$$Z(z) = Z_0 \left( \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \right)$$

The Z chart is the “usual” Smith chart.

Define

$$Z_n(z) \equiv \frac{Z(z)}{Z_0} = \left( \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \right)$$

$$Z_n = R_n + jX_n$$

Hence we have:

$$R_n + jX_n = \left( \frac{1 + (\Gamma_R + j\Gamma_I)}{1 - (\Gamma_R + j\Gamma_I)} \right)$$

**Note:**


The  $z$  dependence is being suppressed here.

Next, multiply both sides by the RHS denominator term and equate real and imaginary parts. Then solve the resulting equations for  $\Gamma_R$  and  $\Gamma_I$  in terms of  $R_n$  or  $X_n$ . This gives two equations.

# Z Chart (cont.)

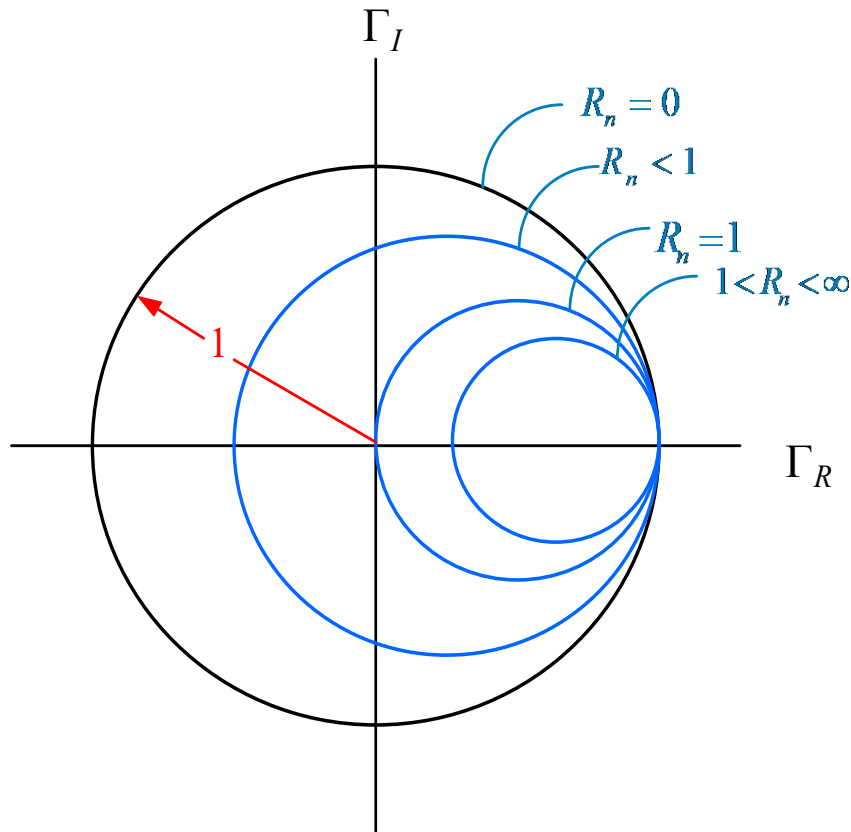1) Equation #1:

$$\left( \Gamma_R - \frac{R_n}{1 + R_n} \right)^2 + \Gamma_I^2 = \left( \frac{1}{1 + R_n} \right)^2$$



Equation for a circle in the  $\Gamma$  plane


$$\text{Center} = \left( \frac{R_n}{1 + R_n}, 0 \right)$$

$$\text{Radius} = \frac{1}{1 + R_n}$$

# Z Chart (cont.)
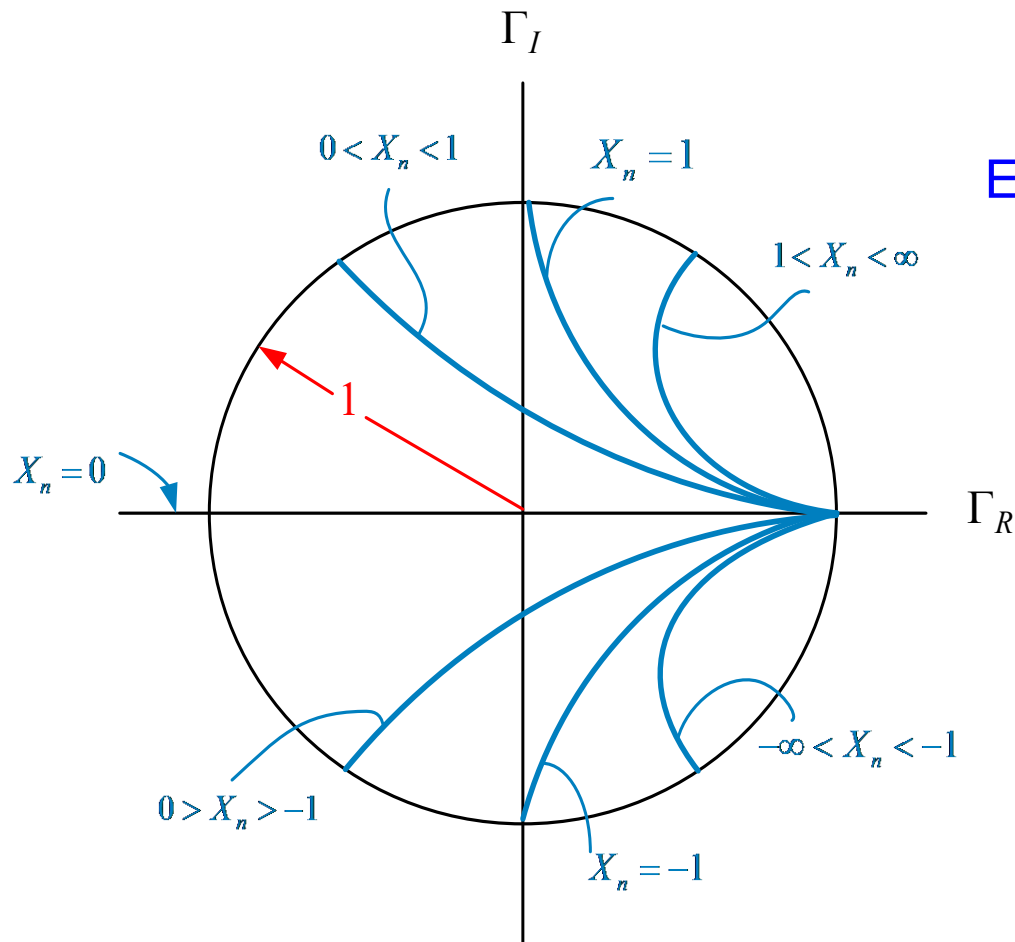
## 2) Equation #2:

$$(\Gamma_R - 1)^2 + \left( \Gamma_I - \frac{1}{X_n} \right)^2 = \left( \frac{1}{X_n} \right)^2$$




Equation for a circle in the  $\Gamma$  plane

$$\text{Center} = \left( 1, \frac{1}{X_n} \right)$$

$$\text{Radius} = \frac{1}{|X_n|}$$


# Z Chart (cont.)

Smith Chart  
(Z-Chart)

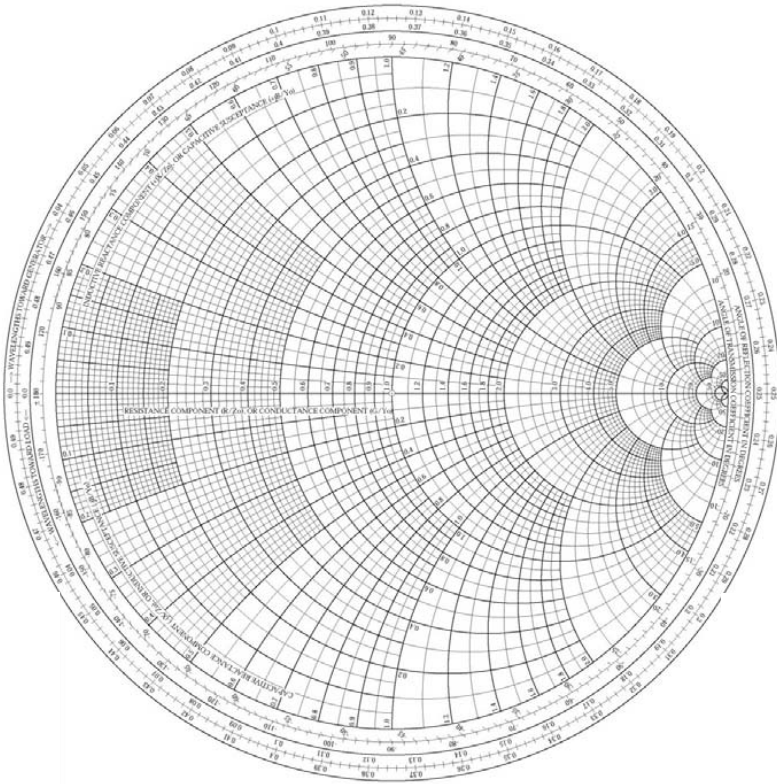

$\Gamma$  plane


Short-hand version

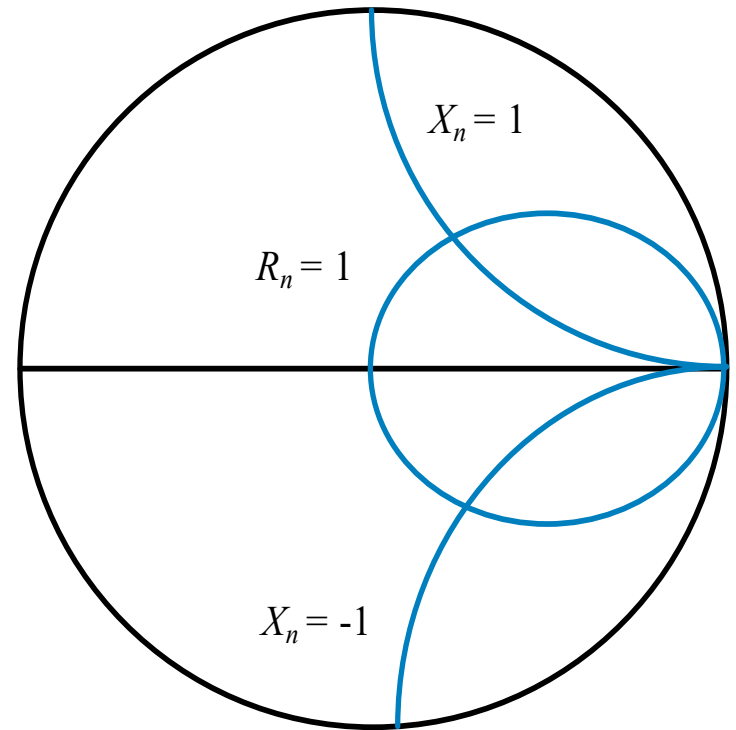

$\Gamma$  plane



# Z Chart (cont.)

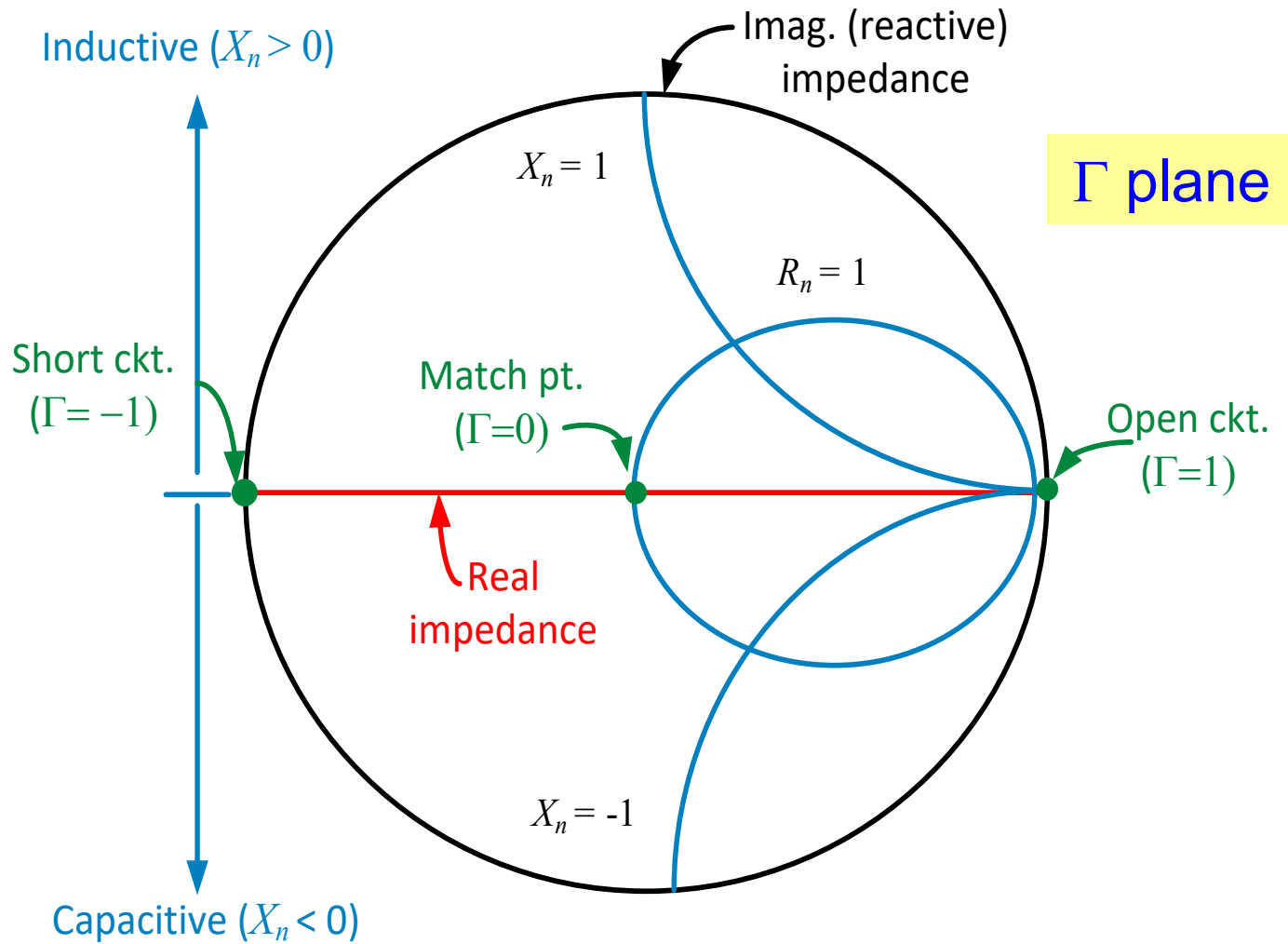

# Admittance Calculations with the Z Chart

Note: 
$$Y(z) = \frac{1}{Z(z)} = \frac{1}{Z_0} \left( \frac{1 - \Gamma(z)}{1 + \Gamma(z)} \right)$$

$$= Y_0 \left( \frac{1 + (-\Gamma(z))}{1 - (-\Gamma(z))} \right) \quad (Y_0 \equiv 1 / Z_0)$$

$$\Rightarrow Y_n(z) \equiv \frac{Y(z)}{Y_0} = \left( \frac{1 + (-\Gamma(z))}{1 - (-\Gamma(z))} \right) = G_n(z) + jB_n(z)$$

Define:

$$\Gamma'(z) \equiv -\Gamma(z)$$


$$Y_n(z) = \left( \frac{1 + \Gamma'}{1 - \Gamma'} \right)$$

**Conclusion:**

The same Smith chart can be used as an admittance calculator.

Same mathematical form as for  $Z_n$ : 
$$Z_n(z) = \left( \frac{1 + \Gamma}{1 - \Gamma} \right)$$
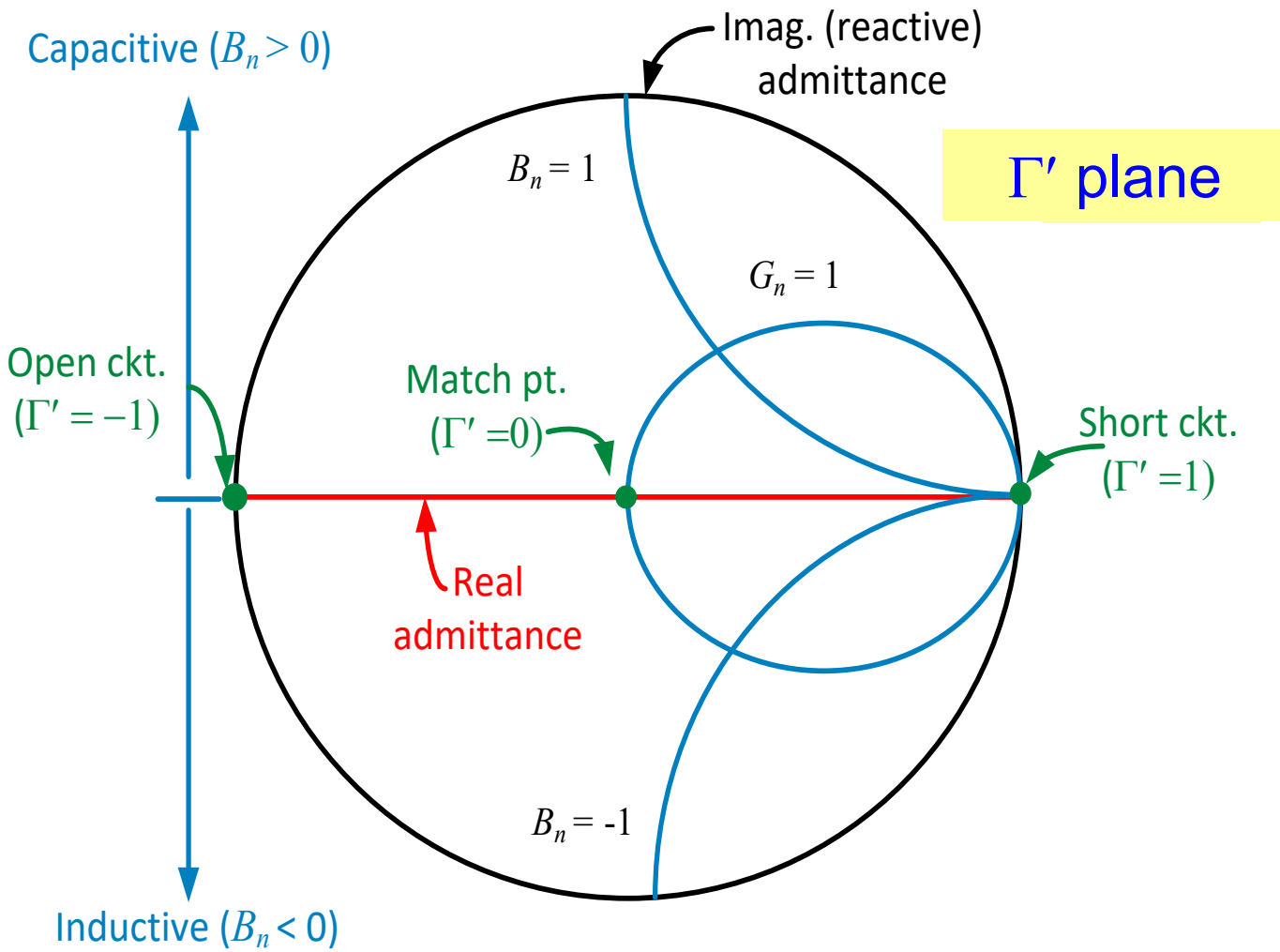
# Admittance Calculations with the Z Chart (cont.)




# Impedance or Admittance Calculations with the Z Chart

Normalized impedance or admittance coordinates

The Smith chart can be used for either impedance or admittance calculations, as long as we are consistent.

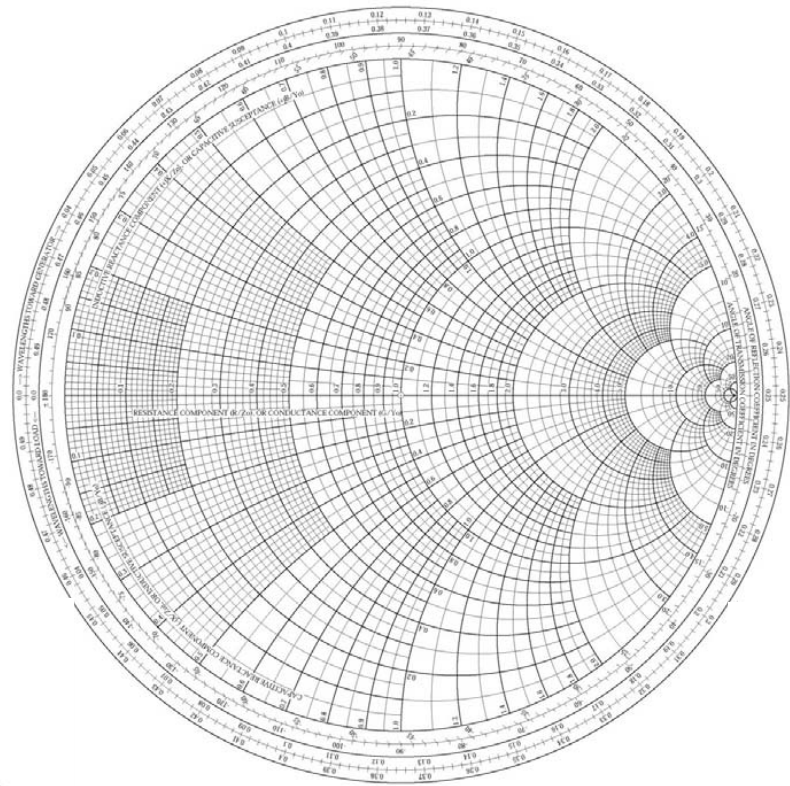The complex plane is either the  $\Gamma$  plane or the  $\Gamma'$  plane.



# Y Chart

As an **alternative** way to do admittance calculations, we can continue to use the **original  $\Gamma$  plane**, and add admittance curves to the chart.

$$Y_n(z) = \left( \frac{1 + (-\Gamma(z))}{1 - (-\Gamma(z))} \right) = G_n(z) + jB_n(z)$$

Compare with previous Smith chart derivation, which started with this equation:


$$Z_n(z) = \left( \frac{1 + (\Gamma(z))}{1 - (\Gamma(z))} \right) = R_n(z) + jX_n(z)$$

$$\left. \begin{array}{l} R_n(z) \rightarrow G_n(z) \\ X_n(z) \rightarrow B_n(z) \end{array} \right\} \Rightarrow \Gamma(z) \rightarrow -\Gamma(z) \quad (\text{rotation of } 180^\circ)$$

**Examples:**  $R_n = 1$  circle, rotated  $180^\circ$ , becomes  $G_n = 1$  circle.  
 $X_n = 1$  circle, rotated  $180^\circ$ , becomes  $B_n = 1$  circle.

**Side note:** A  $180^\circ$  rotation on a Smith chart makes a normalized impedance become its reciprocal.


# Y Chart (cont.)

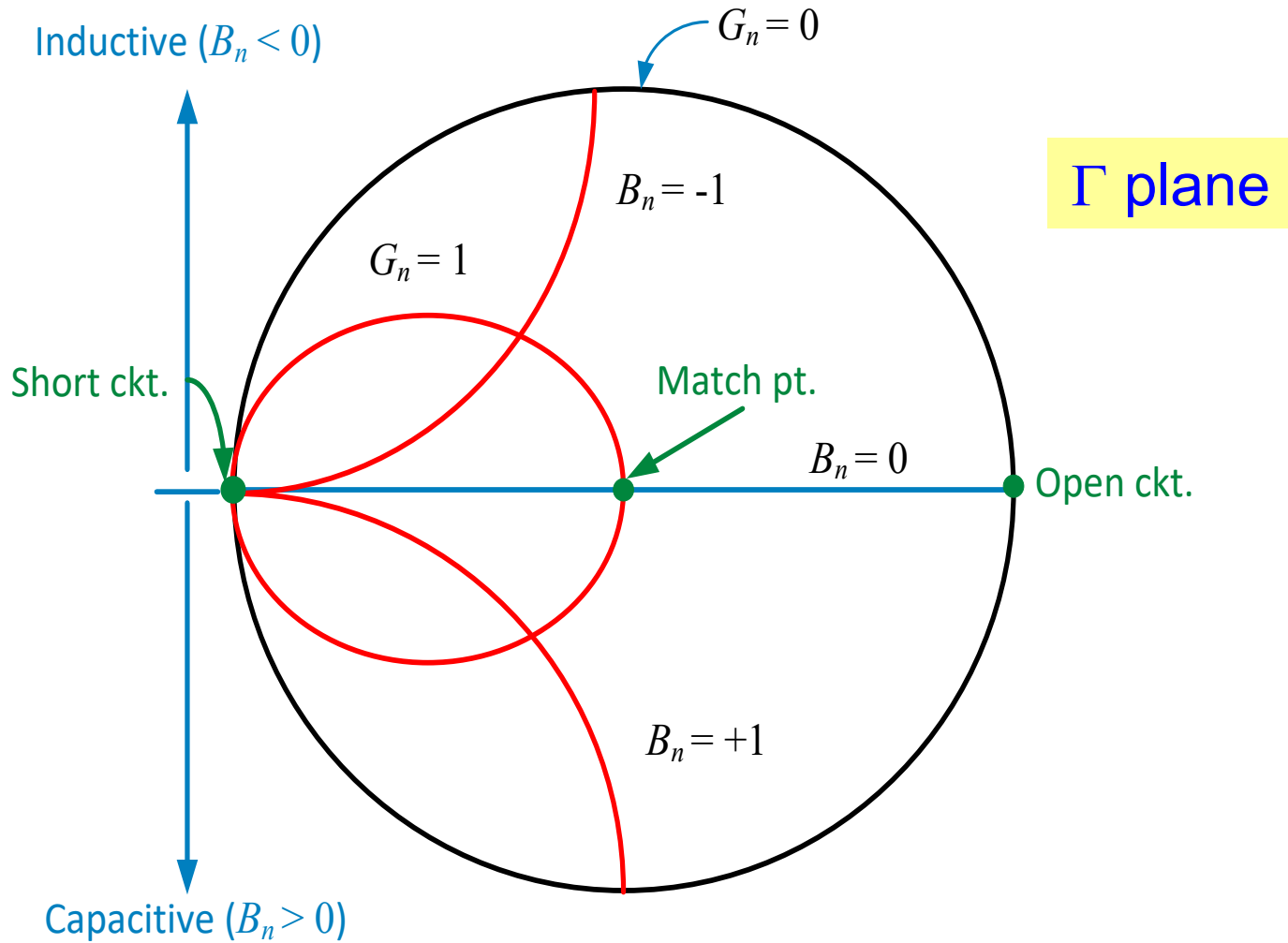


**The Y chart is the “mirror image” of the usual Smith chart.**

# Y Chart (cont.)

Smith Chart  
(Y-Chart)

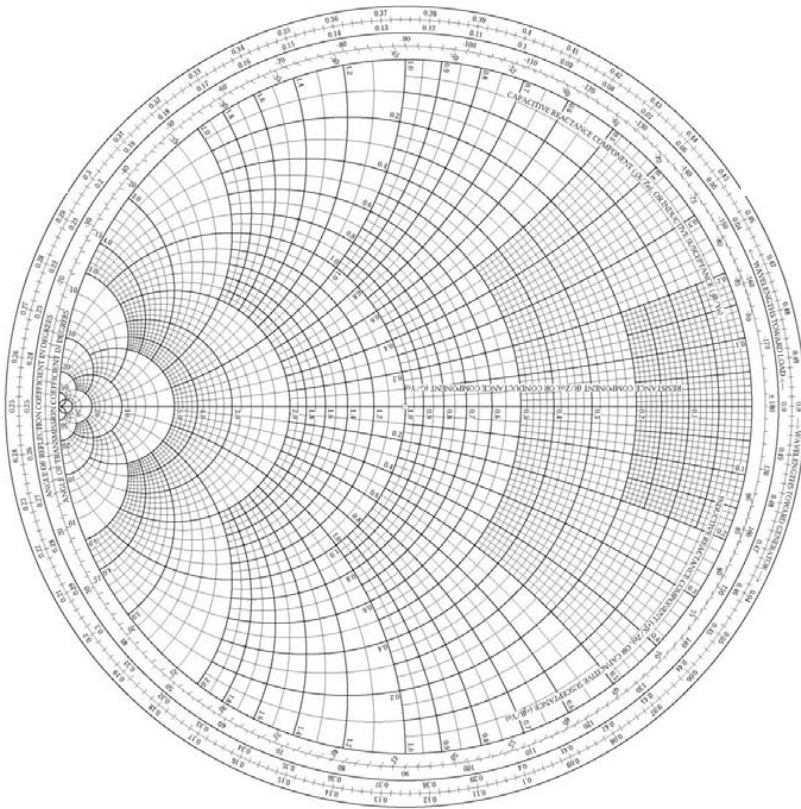

Short-hand version

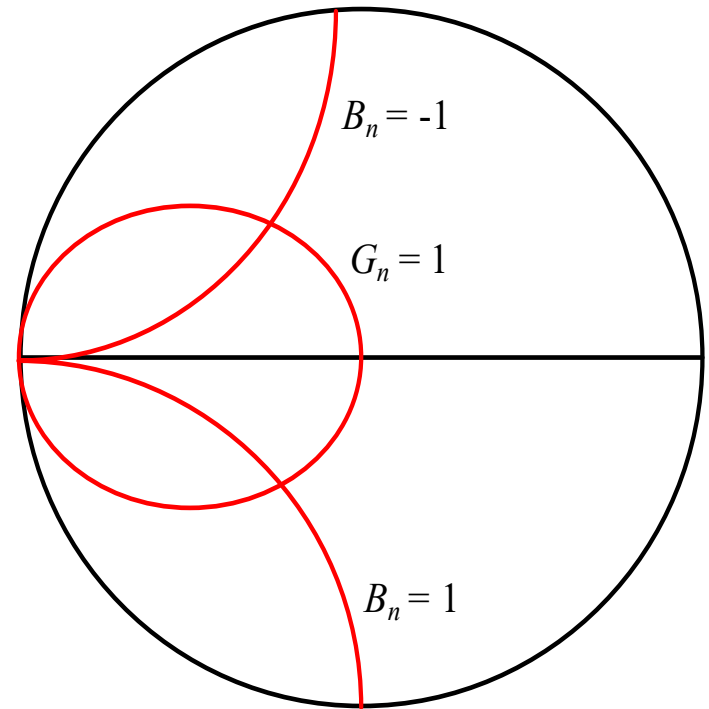


$\Gamma$  plane



# All Four Possibilities for Smith Charts

Z chart, used for impedance


1

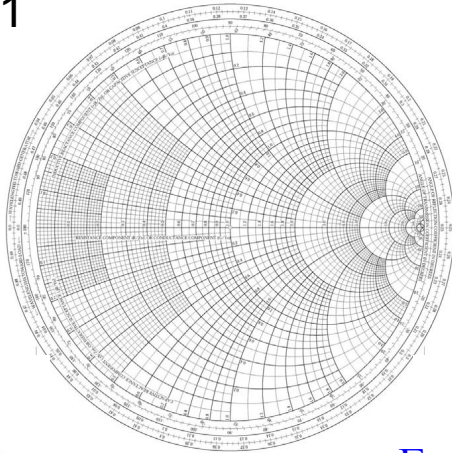

$\Gamma$  plane

Z chart, used for admittance

2

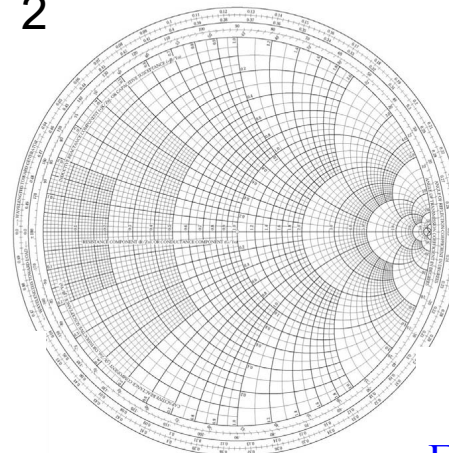

$\Gamma'$  plane


The first two are the most common.

The third is sometimes convenient.

The fourth is almost never used.

Y chart, used for admittance


3

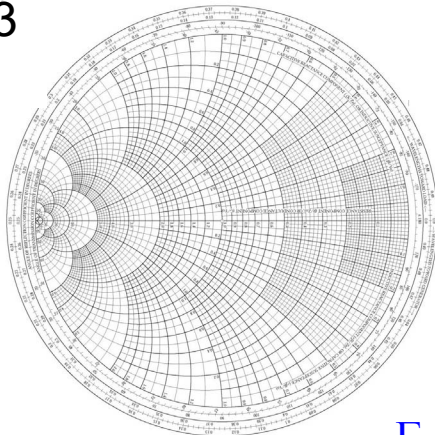

$\Gamma$  plane

Y chart, used for impedance

4

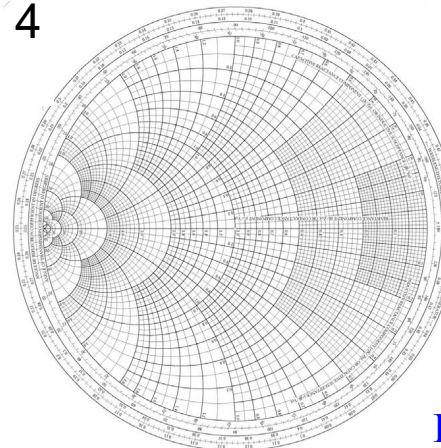


$\Gamma'$  plane



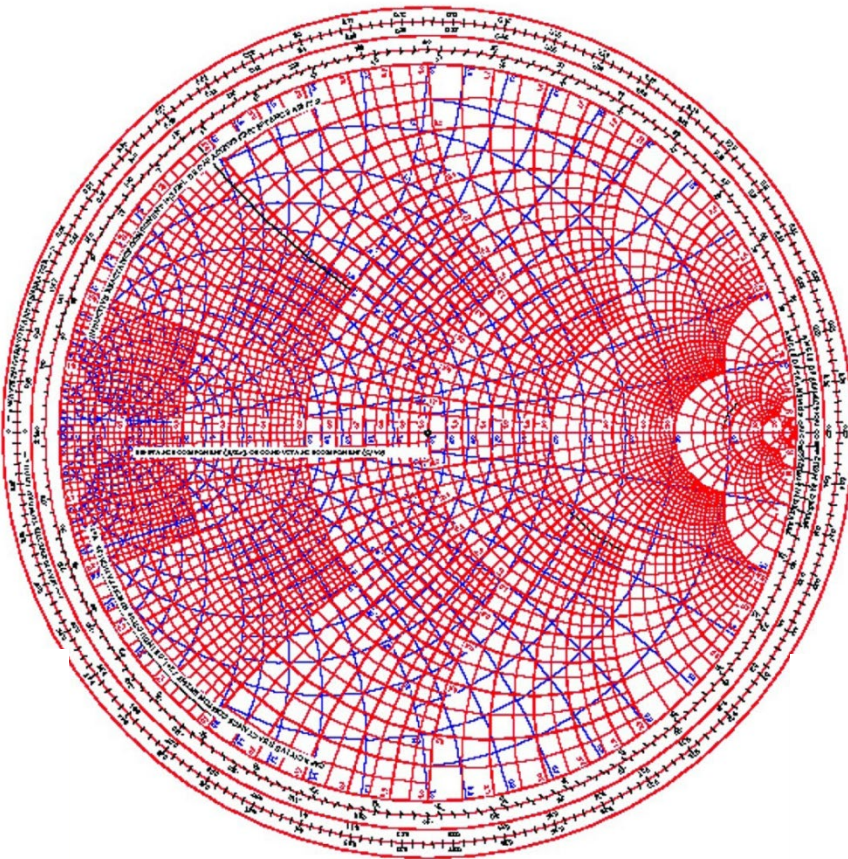
# ZY Chart

NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



Short-hand version

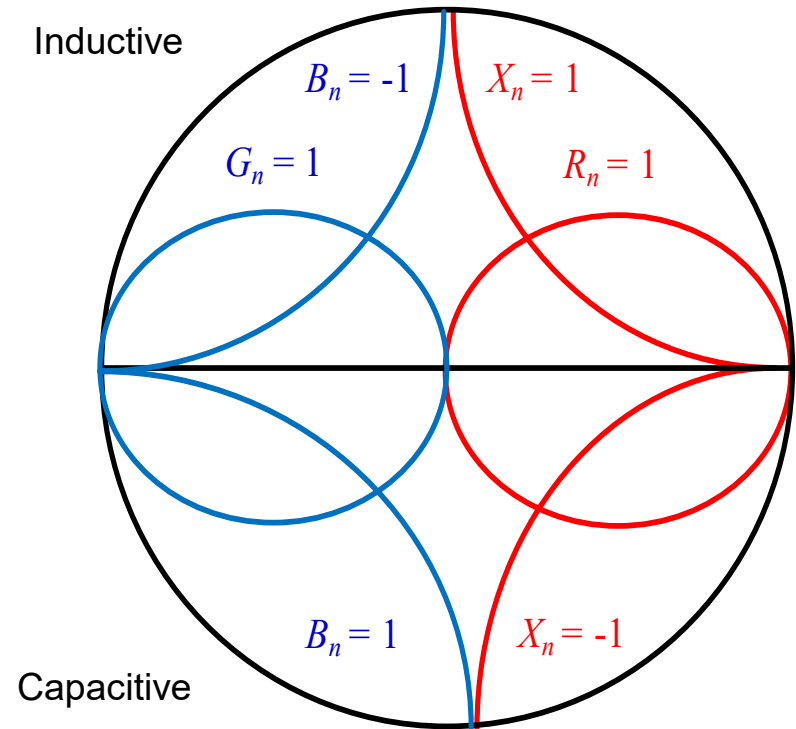

$\Gamma$  plane

This is convenient for doing matching problems that involve both series and shunt elements (done later).

# Standing Wave Ratio

The SWR is given by the value of  $R_n$  on the positive real axis of the Smith chart ( $R_n^{\max}$ ).


Proof:

$$\text{SWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

$$\begin{aligned} Z_n &= \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \\ &= \frac{1 + \Gamma_L e^{+2j\beta z}}{1 - \Gamma_L e^{+2j\beta z}} \\ &= \frac{1 + |\Gamma_L| e^{j\phi_L} e^{+2j\beta z}}{1 - |\Gamma_L| e^{j\phi_L} e^{+2j\beta z}} \end{aligned}$$

$$\phi_L + 2\beta z = 0 \Rightarrow R_n^{\max} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

Smith Chart  
(Z-Chart)

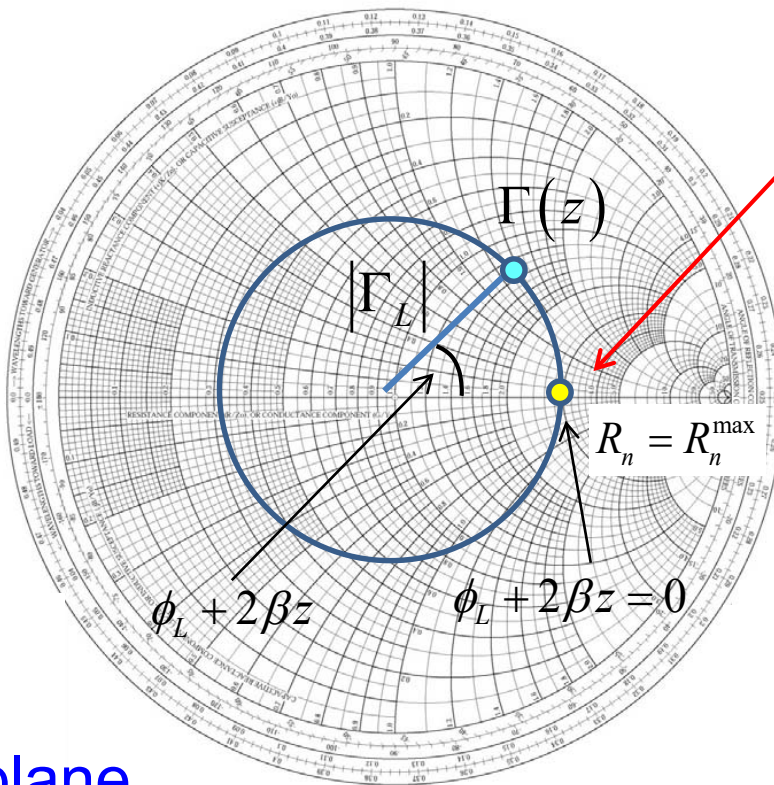

$\Gamma$  plane

# Electronic Smith Chart

At this link:

<http://www.sss-mag.com/topten5.html>

Download the following zip file:

smith\_v191.zip

Extract the following files:

smith.exe

mith.hlp

smith.pdf



This is the application file


# Example 1

$$Z_0 = 50 \Omega$$


$$Z_L = 100 + j50 \Omega$$

Find  $Z(-d)$  at  $d / \lambda_g = 1/4, 3/8, 1/2$

Use the  $Z$  chart.

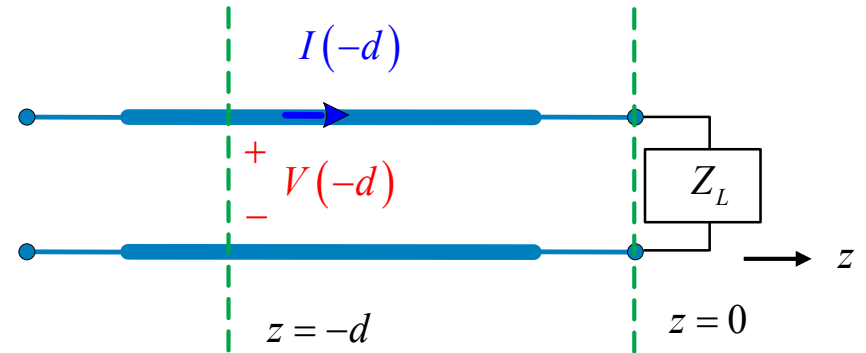

$$Z_{L,n} = \frac{Z_L}{Z_0} = 2 + j1$$

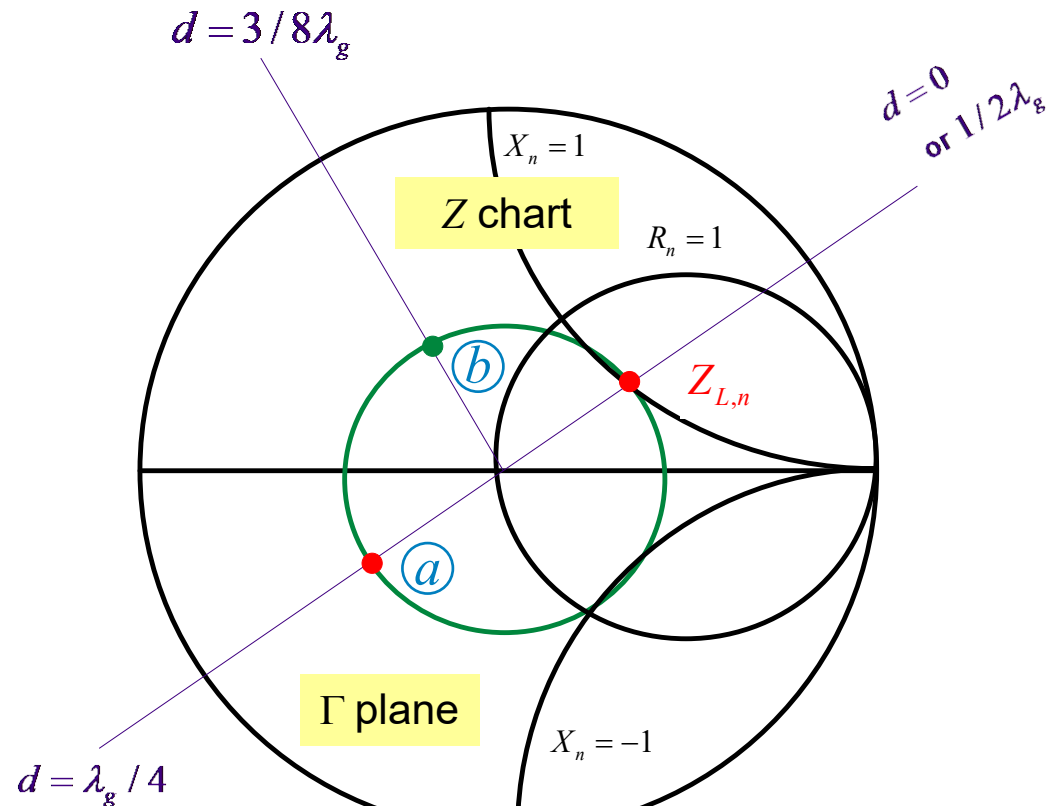

(a)

$$d = \lambda_g / 4$$

$$Z_n \approx 0.4 - j0.2$$

$$\Rightarrow Z(-\lambda_g / 4) \approx 20 - j10 \Omega$$

# Example 1 (cont.)


(b)

$$d = 3/8\lambda_g$$

$$Z_n \approx 0.5 + j0.5$$

$$\Rightarrow Z(-3/8\lambda_g) \approx 25 + j25\Omega$$

Note:  $3/8 + 0.212 - 0.5 = 0.087$

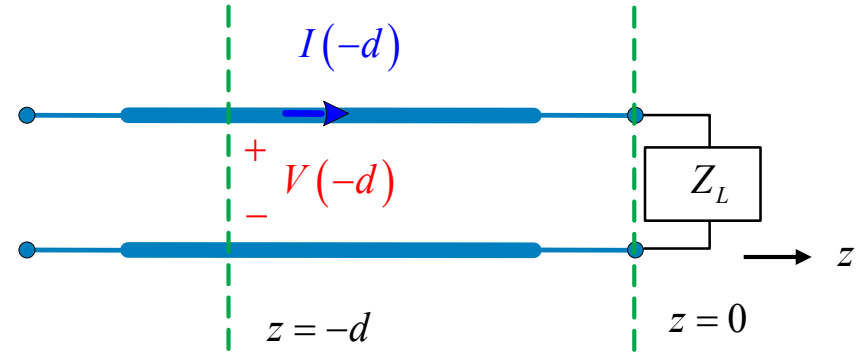


(c)

$$d = \lambda_g / 2$$

$$Z_n \approx 2 + j1$$
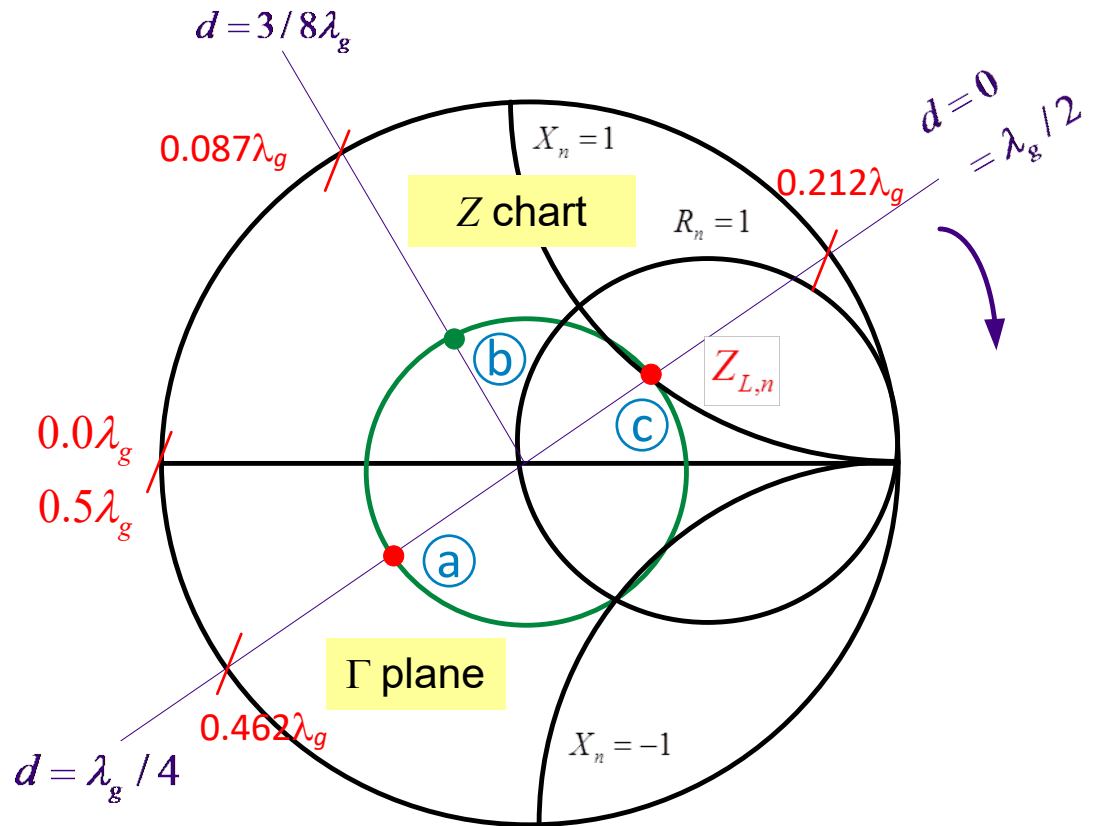
$$\Rightarrow Z(-\lambda_g / 2) = 100 + j50\Omega$$



# Example 2

$$Z_0 = 50 \Omega \quad (Y_0 = 20 \text{ mS})$$

$$Y_L = 8 \text{ mS} - j4 \text{ mS}$$

Find  $Y(-d)$  at  $d / \lambda_g = 1/4, 3/8, 1/2$

Use the  $Y$  chart.



$$Y_{L,n} = \frac{Y_L}{Y_0} = 0.4 - j0.2$$

(a)

$$d = \lambda_g / 4$$

$$Y_n \approx 2 + j1$$
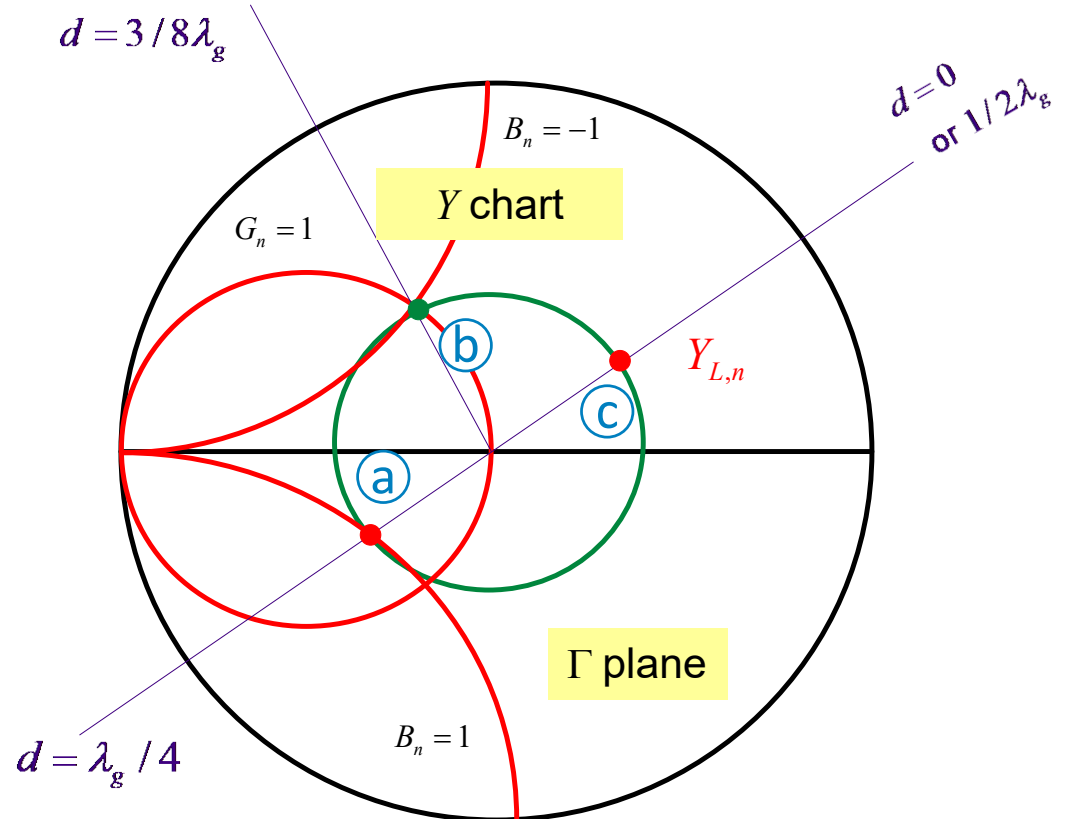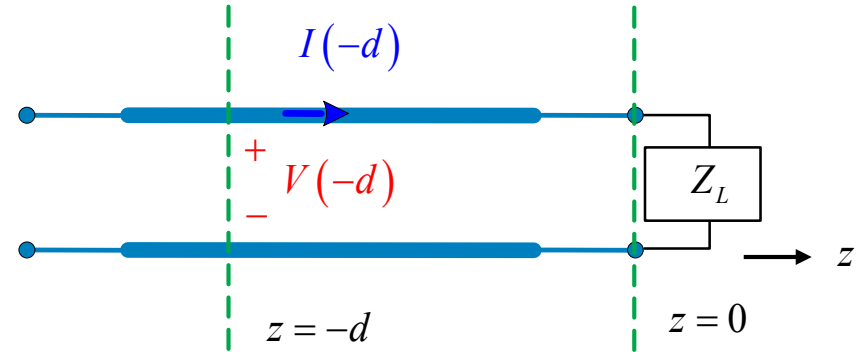
$$\Rightarrow Y(-\lambda_g / 4) \approx 40 \text{ mS} + j20 \text{ mS}$$




# Example 2 (cont.)

(b)

$$d = 3/8\lambda_g$$

$$Y_n \approx 1 - j1$$
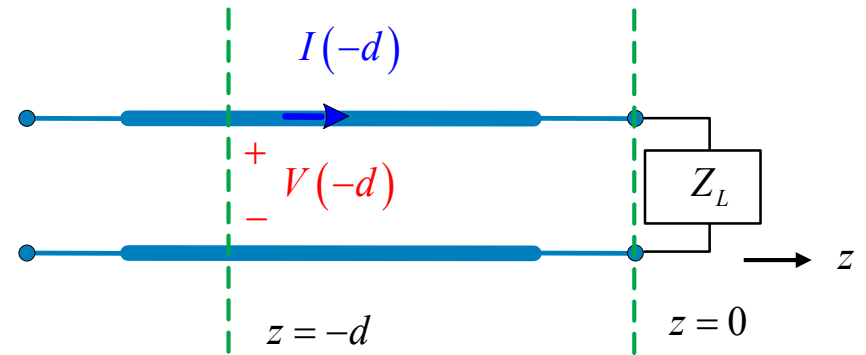
$$\Rightarrow Y(-3/8\lambda_g) \approx 20\text{mS} - j20\text{mS}$$




(c)

$$d = \lambda_g / 2$$

$$Y_n \approx 0.4 - j0.2$$
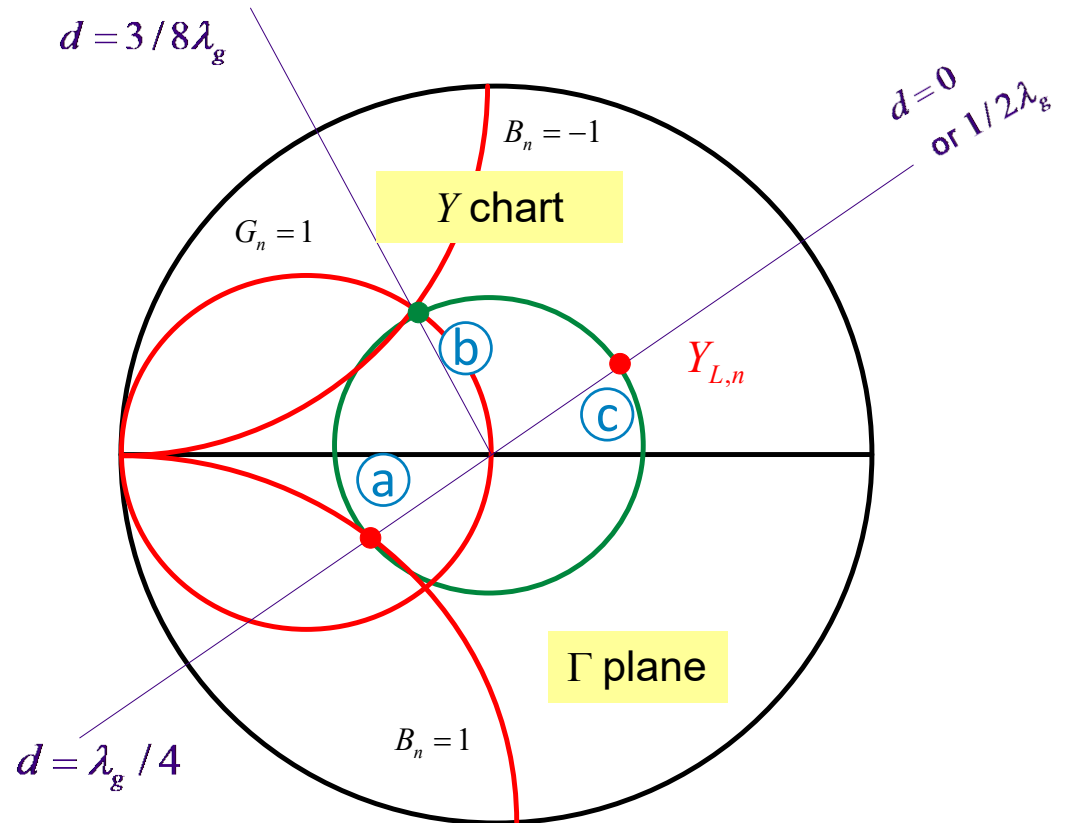
$$\Rightarrow Y(-\lambda_g / 2) = 8\text{mS} - j4\text{mS}$$




# Example 3

Use a short-circuited section of air-filled TEM,  $50\ \Omega$  transmission line ( $\beta = k_0$ ,  $\lambda_g = \lambda_d = \lambda_0$ ) to create an impedance of  $Z_{in} = -j25\ \Omega$  at  $f = 10\ \text{GHz}$ .

Use the  $Z$  chart.


$$Z_{in,n} = -j \frac{25}{50} = -j(0.5)$$

Z chart

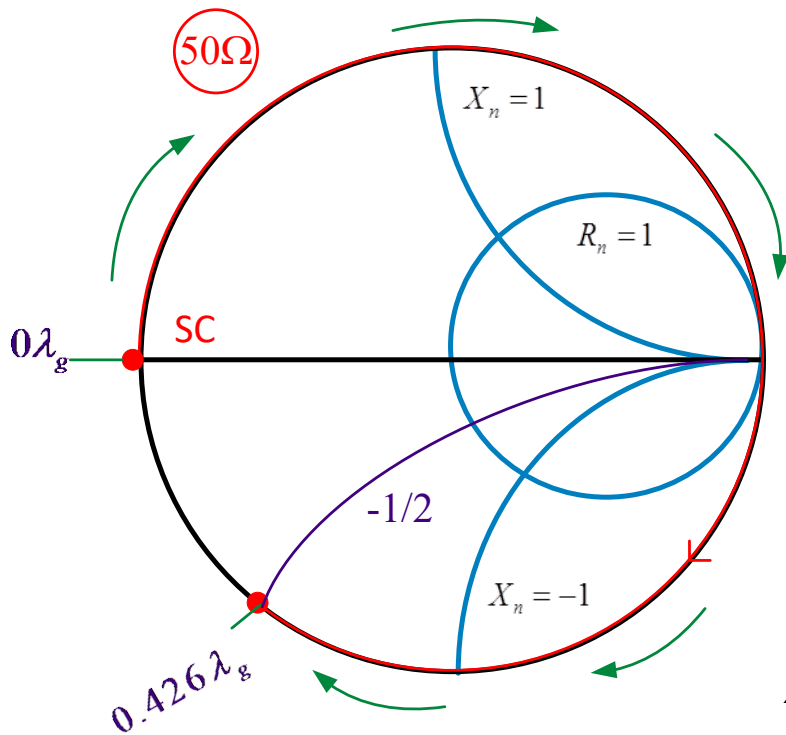

$\Gamma$  plane

$$Z_{in} = -j25\ \Omega$$

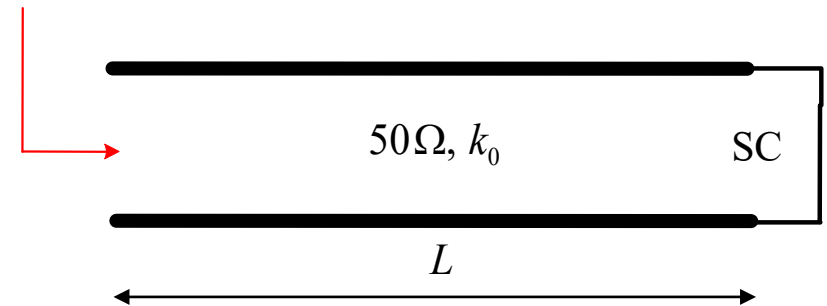

$$L = 0.426\lambda_g - 0\lambda_g = 0.426\lambda_g = 0.426\lambda_0$$

$$\lambda_0 = \frac{c}{f} = \frac{2\pi}{k_0} = \frac{2\pi}{\omega\sqrt{\mu_0\epsilon_0}} \quad \lambda_0 = 3.0\ \text{cm}$$


$$\Rightarrow L = 1.28\ \text{cm}$$




# Example 4

Use an open-circuited section of  $75 \Omega$  ( $Y_0 = 1/75 \text{ S}$ ) air-filled transmission line at  $f = 10 \text{ GHz}$  to create an admittance of  $Y_{in} = j1/75 \text{ S}$ :

Use the  $Y$  chart.

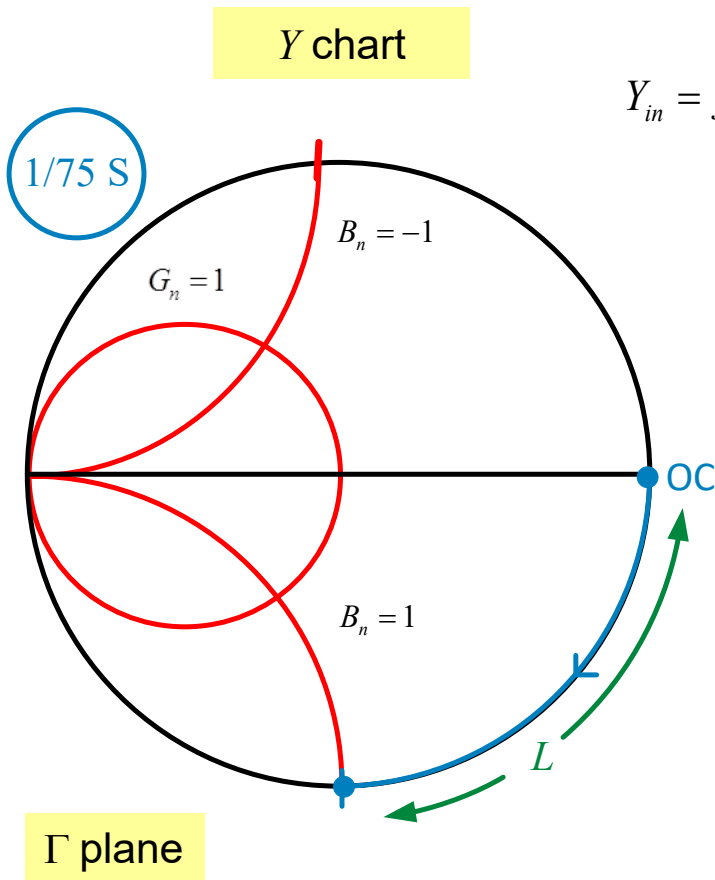
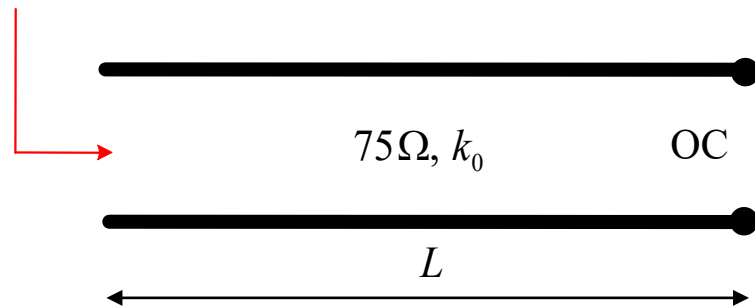
$$Y_{in} = j(1/75) \text{ S} \Rightarrow Y_{in,n} = j(1)$$



$$L = 0.125 \lambda_g = 0.125 \lambda_0 \quad \lambda_0 = 3.0 \text{ cm}$$


$$\Rightarrow L = 0.375 \text{ cm}$$

# Example 5

$$Z_0 = 50 \Omega$$

$$Z_L = 100 + j100 \Omega$$

## Single-stub matching

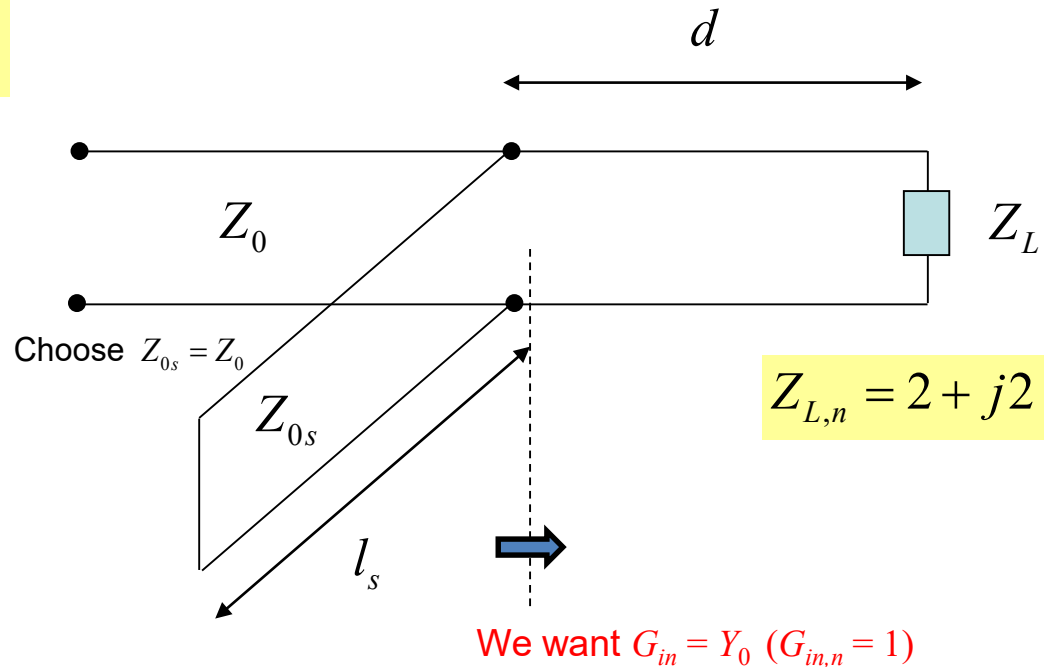

In this example we will use the “usual” Smith chart ( $Z$  chart), but as an admittance calculator.

$$Y_{L,n} = \frac{1}{2 + j2} = 0.25 - j(.25)$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_{Ln} - 1}{Z_{Ln} + 1} \quad \longrightarrow \quad \Gamma_L = 0.62 e^{j\pi/6} = 0.62 \angle 30^\circ$$

# Example 5 (cont.)

$$0.041\lambda + 0.178\lambda = 0.219\lambda_g$$


$$0.041\lambda + 0.322\lambda = 0.363\lambda_g$$

Solution:

Add  $Y_n = -j1.57$  at  $d = 0.219\lambda_g$

or  $Y_n = +j1.57$  at  $d = 0.363\lambda_g$

(We'll use the first choice.)

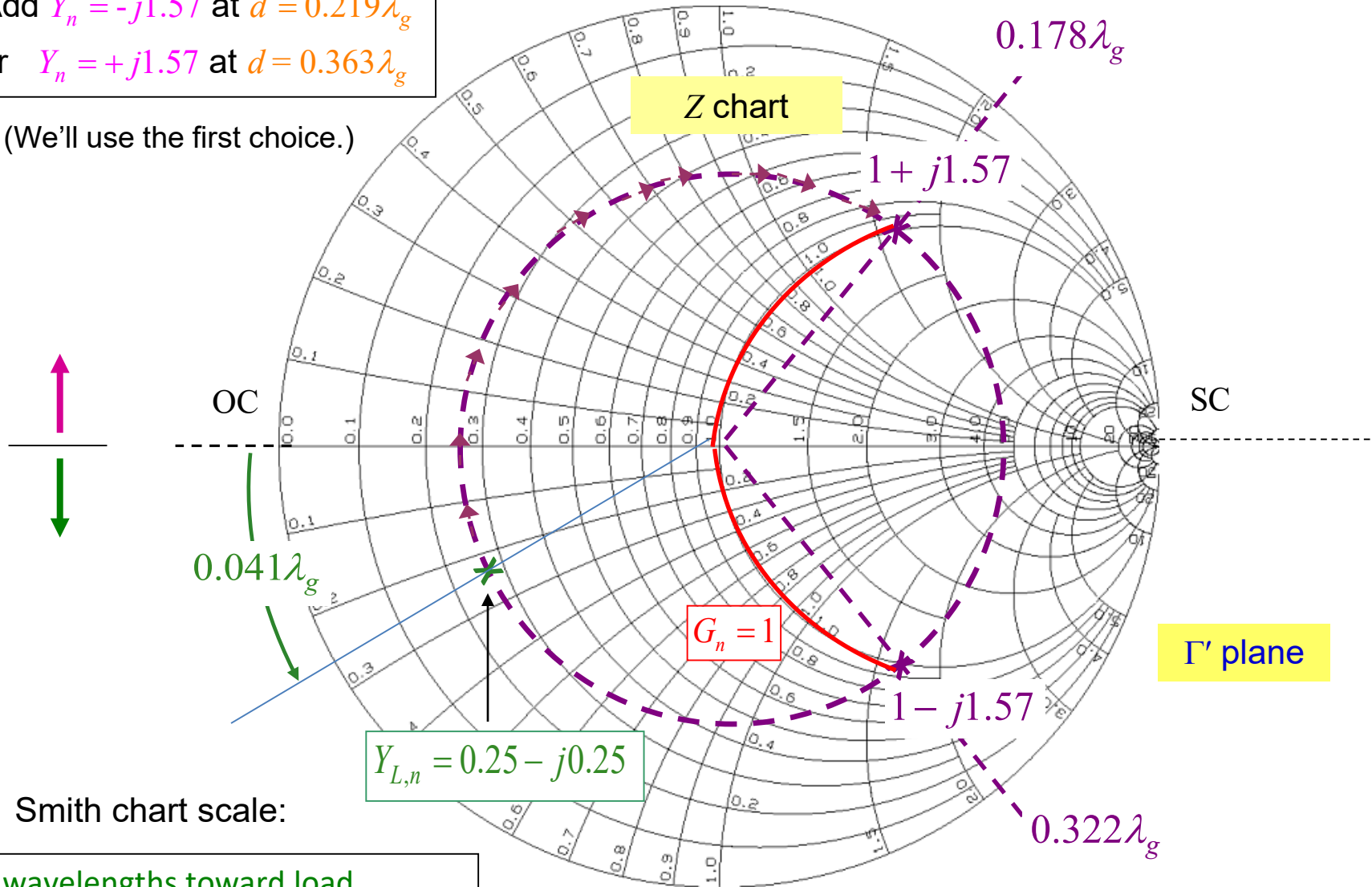

Smith chart scale:

wavelengths toward load

wavelengths toward generator

# Example 5 (cont.)

From the Smith chart:

$$l_s = 0.09\lambda_g$$

Analytically:

$$Z_{in}^{SC} = jZ_0 \tan(\beta l_s)$$

$$Y_{in}^{SC} = -jY_0 \cot(\beta l_s)$$


$$B_{s,n} = -\cot(\beta l_s)$$

$$-1.57 = -\cot \beta l_s$$

$$\cot \beta l_s = 1.57; \quad \tan \beta l_s = \frac{1}{1.57} = 0.637$$

$$\beta l_s = \frac{2\pi}{\lambda_g} l_s = \tan^{-1}(0.637) = 0.567 \text{ [rad]}$$

$$l_s = 0.0903\lambda_g$$

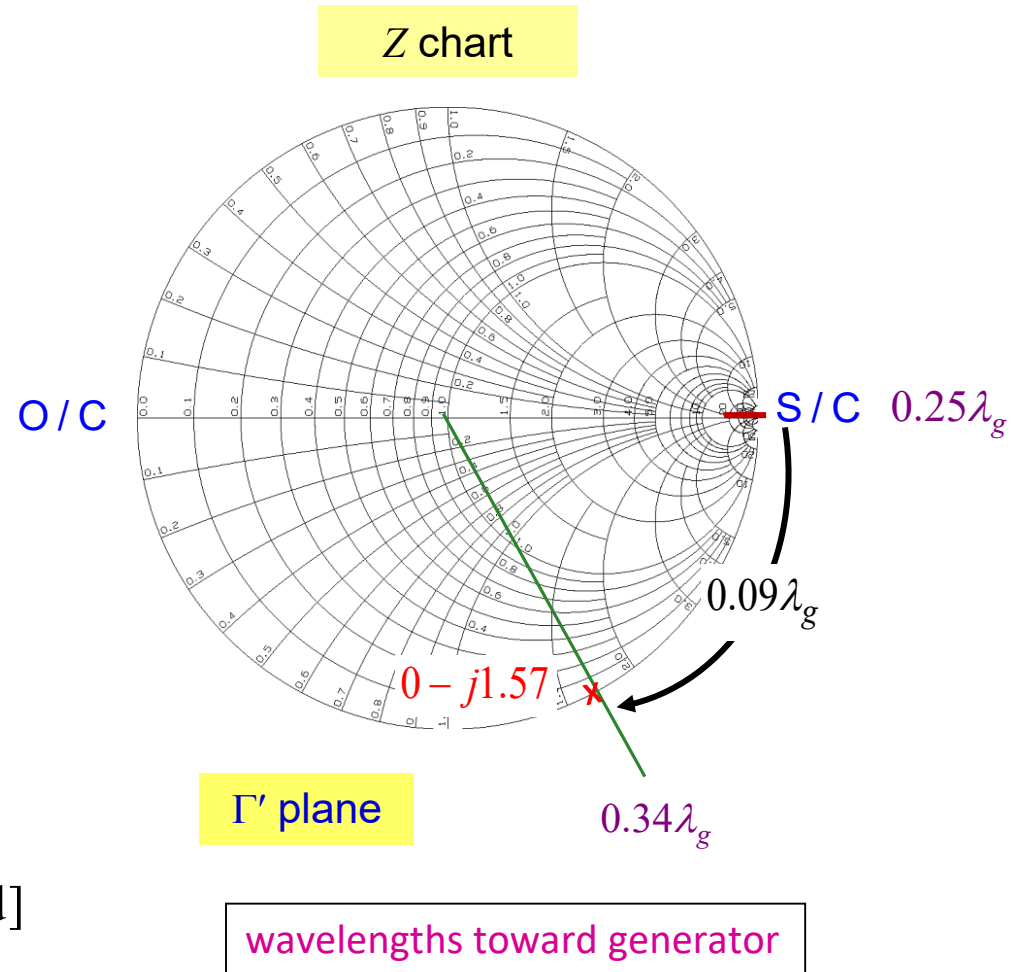

# Example 5 (cont.)

$$Z_0 = 50 \Omega$$

$$Z_L = 100 + j100 \Omega$$

**Summary:**

$$d = 0.219\lambda_g$$

$$l_s = 0.09\lambda_g$$

