

Signature: Solution Key

DO NOT OPEN THIS BOOKLET UNTIL INSTRUCTED TO DO SO.

EXAM 2
ELEE 2335
March 15, 1986


INSTRUCTIONS:

1. Sign your name on the upper left of this page.
2. All work is to be done in the spaces provided in this booklet. Use the backs if necessary. Indicate clearly where your work and answers may be found. Enclose your final answers in a box. No credit will be given unless the necessary work is shown. No crib sheets are allowed.
3. Show all of your units explicitly, both in your final answer and in your intermediate steps. Units in exam questions are placed within square brackets.
4. If your answers and work are not in ink, there will be no provision for changing your grade once the exam is returned to you. Do not use red ink.

1. 20
2. 15
3. 15
4. 10
5. 10
6. 15
7. 15
Bonus. 10

110

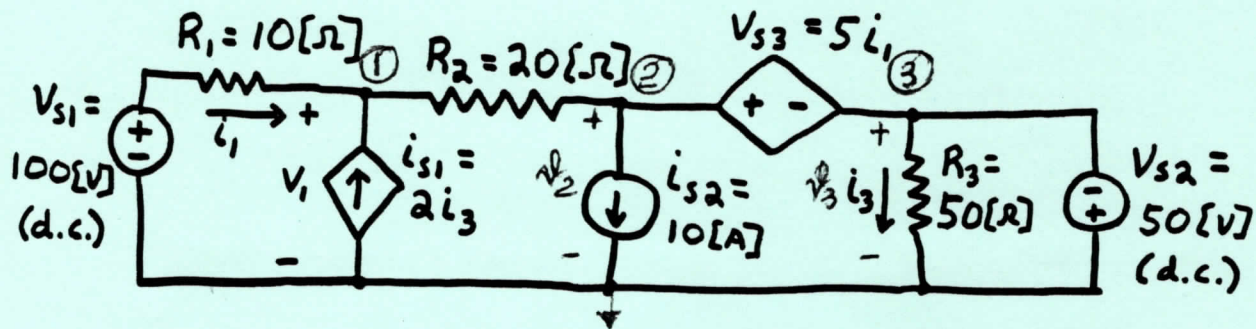1. (20 Points) Apply the node voltage method to determine the voltage v_1 in the following circuit.




$$\begin{aligned}
 (1) \quad & \text{Node \# 1: } \frac{v_1 - 100}{10} - i_{s1} + \frac{v_1 - v_2}{20} = 0. \\
 (2) \quad & \text{--- \# 2+3: } v_2 - v_3 - v_{s3} = v_2 - v_3 - 5i_1 = 0 \\
 & \text{--- \# 3: } v_3 = -v_{s2} = -50 \text{ [V]}. \\
 & i_{s1}: i_{s1} = 2i_3 = 2 \frac{v_3}{R_3} = 2 \frac{v_3}{50} = \frac{v_3}{25} = -2 \text{ [A]}. \\
 & v_{s3}: v_{s3} = 5i_1 = 5 \frac{v_{s1} - v_1}{10} = 5 \frac{100 - v_1}{10} = 50 - 0.5v_1
 \end{aligned}$$


$$\begin{aligned}
 (1) \quad & \left\{ \frac{v_1 - 100}{10} + 2 + \frac{v_1 - v_2}{20} = 0 \right. \\
 (2) \quad & \left. \begin{aligned} & v_2 + 50 - (50 - 0.5v_1) = 0 \\ & v_2 + 0.5v_1 = 0; \quad v_2 = -0.5v_1 \end{aligned} \right\}
 \end{aligned}$$

$$(1) \quad 3v_1 - v_2 = 160 \Rightarrow 3v_1 - (-0.5v_1) = 160; \quad \underline{v_1 = \frac{160}{3.5} = 45.714286 \text{ [V]}}$$

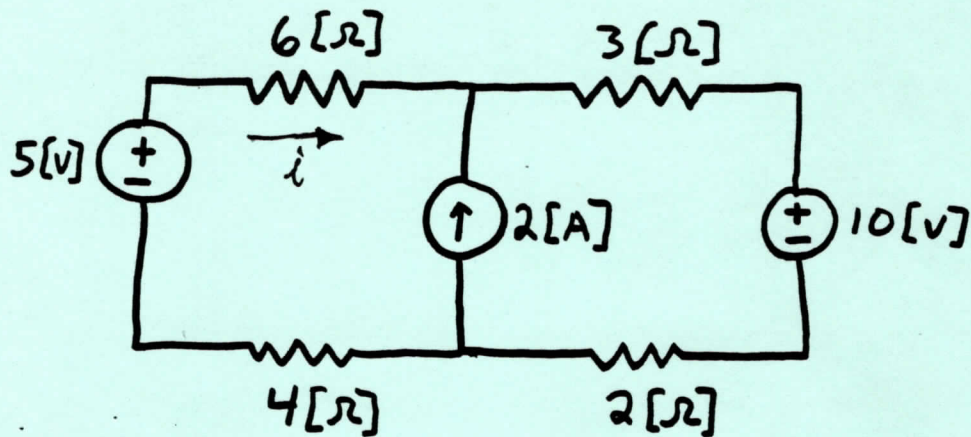2. (15 Points) In the circuit given, determine the value of the current i using the mesh current technique.



SOLUTION

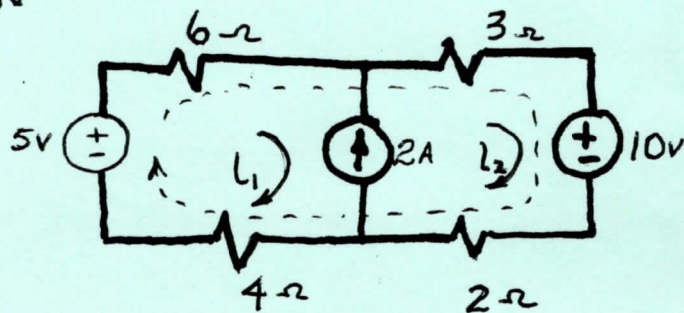

USING THE SUPERMESH CONCEPT

$$5 - 6l_1 - 3l_2 - 10 - 2l_2 - 4l_1 = 0 \quad ; \quad l_2 - l_1 = 2A$$

$$10l_1 + 5l_2 = -5$$

$$\therefore 10l_1 + 5(2 + l_1) = -5$$


$$15l_1 = -15$$

$$l_1 = -1A$$


SINCE $L = l_1$,

$$L = -1 \text{ AMP}$$

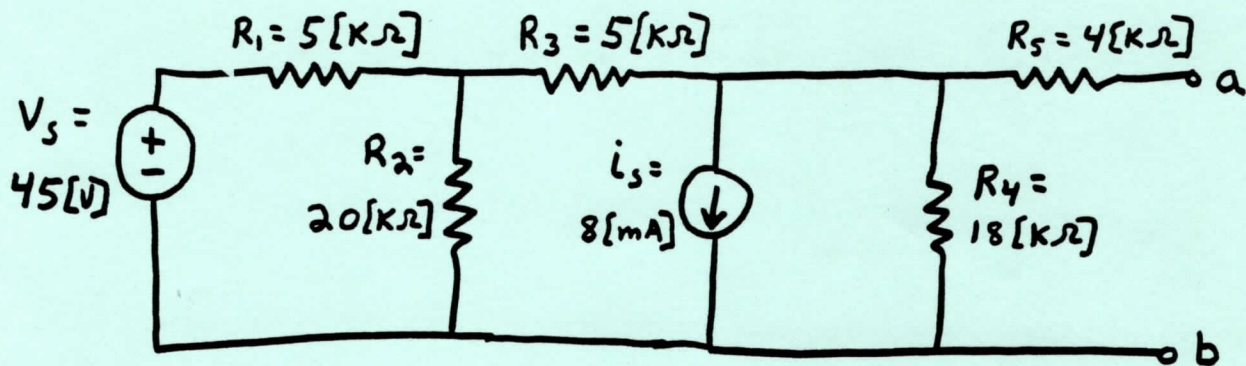3. (15 Points) Apply the source transformations to determine the Thevenin equivalent with respect to terminals a and b for the following circuit.



Transformation steps:

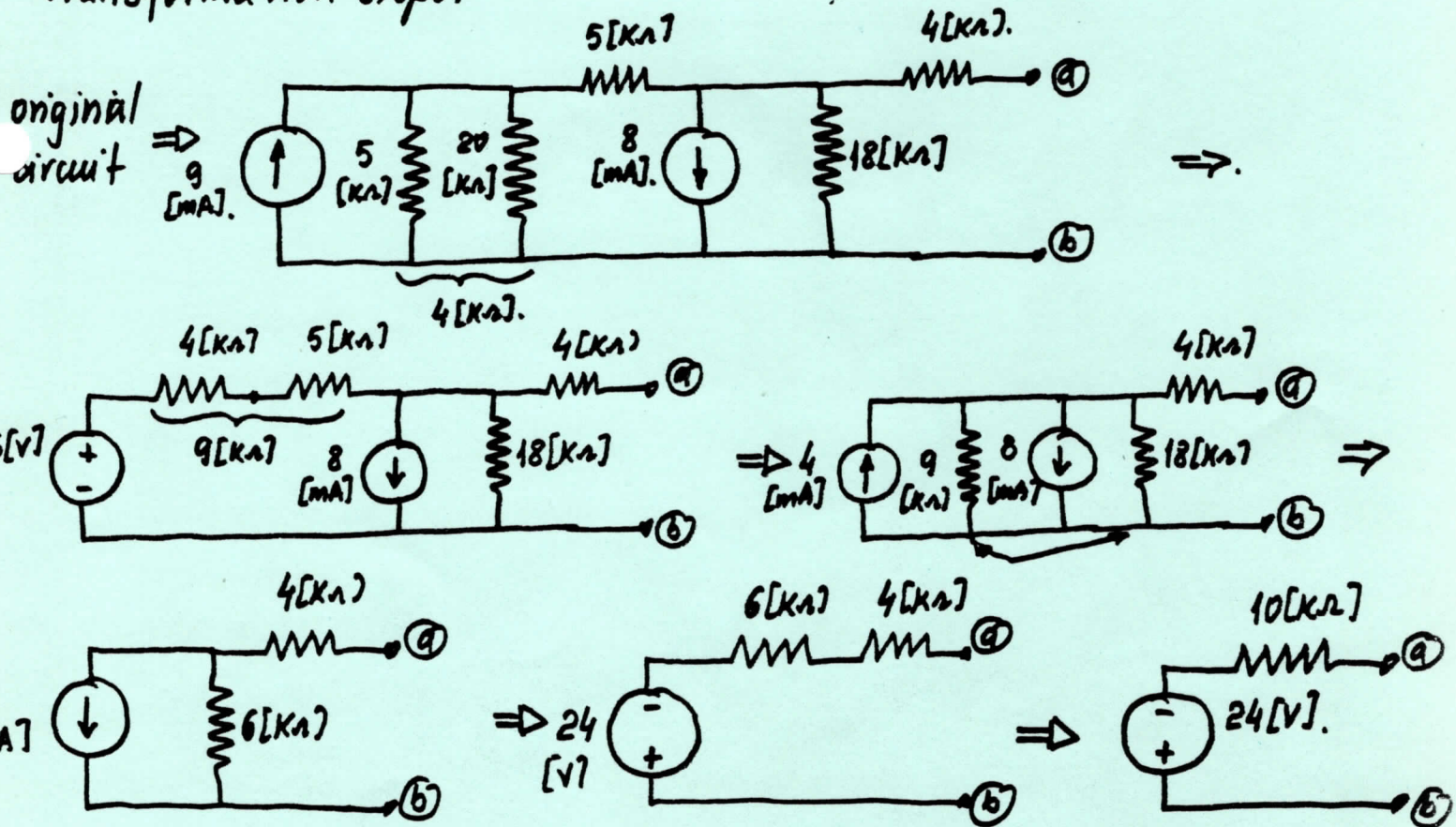

4. (10 Points) A circuit has the following Thevenin equivalent values,

$$V_{TH1} = 30[V]$$

$$R_{TH1} = 300[\Omega],$$





and a second circuit has the following Thevenin equivalent values,

$$V_{TH2} = 25[V]$$


$$R_{TH2} = 500[\Omega].$$

These two equivalent circuits are connected in parallel at their terminals. Find the Thevenin equivalent of one of the possible parallel combinations of these circuits, with respect to the common terminals.


Solutions

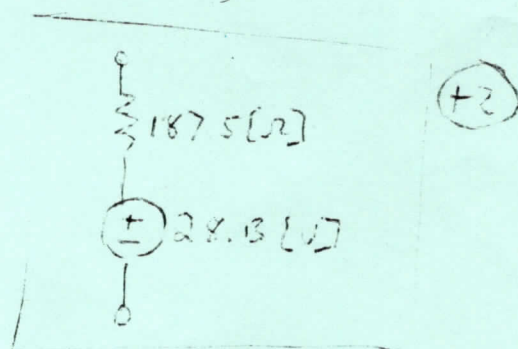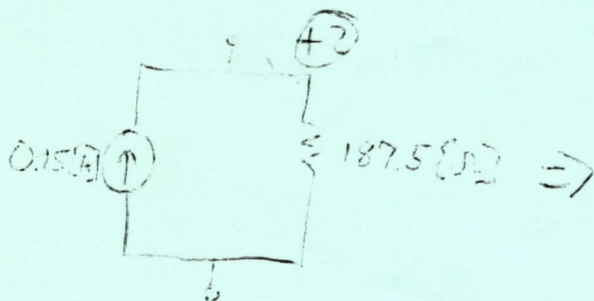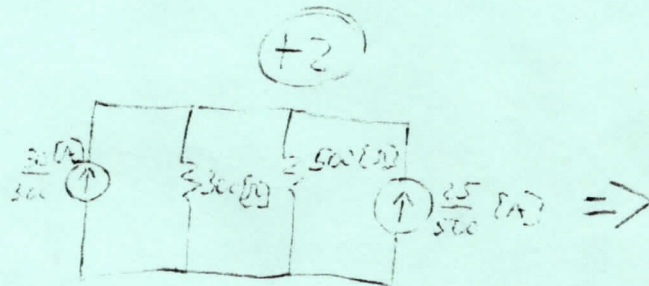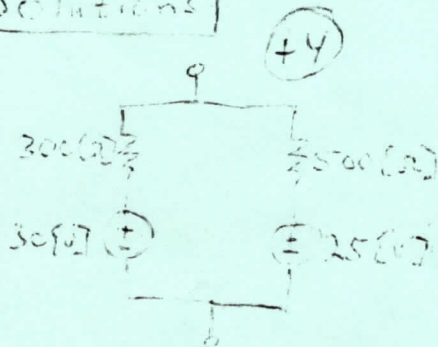


Other possibilities

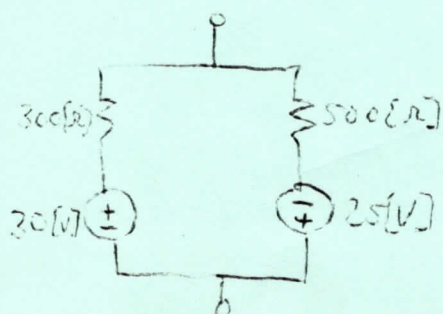

$\Rightarrow$

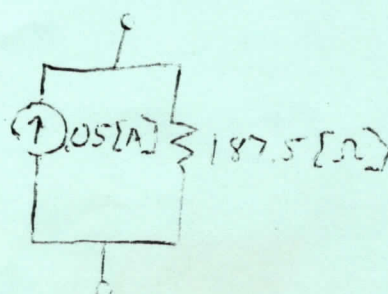


$\Rightarrow$

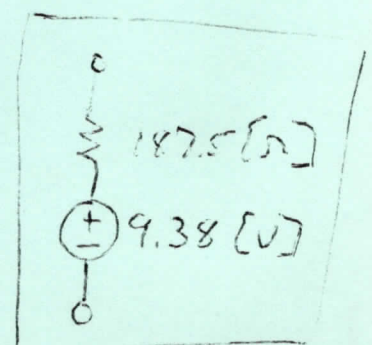

either source could have a minus sign.

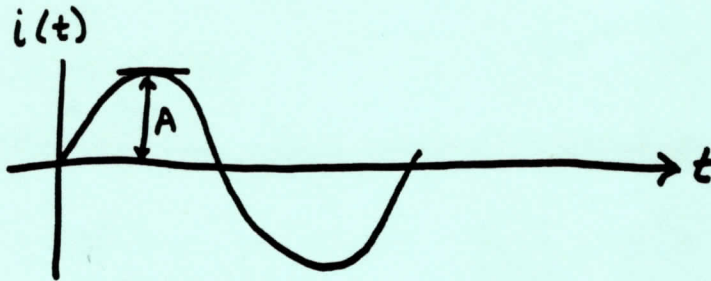5. (10 Points) If the current through a 90[mH] inductor is sinusoidal, as shown in the sketch below, what must the amplitude A be in order to generate an inductor voltage that has an amplitude of 10[kV]?



$$i(t) = A \sin(1000t)$$

$$v(t) = L \frac{di(t)}{dt} = LA 1000 \cos 1000t = 90 \times 10^{-3} \times 10^3 \times A \cdot \cos 1000t :$$

$$V_{\max} = 90 A \Rightarrow 10 \cdot 10^3 [V] : \left[A = \frac{10 \cdot 10^3}{90} = \underline{111.1111 [A]} \right]$$

6. (15 Points) An inductor with inductance $L = 10[\text{mH}]$ has a current at time $t=1[\text{s}]$ which is equal to $5[\text{A}]$. The voltage across the inductor is equal to $5e^{-3t}[\text{V}]$ for the time period $1[\text{s}] < t < 5[\text{s}]$. Find the magnitude of the power absorbed by the inductor at $t=3[\text{s}]$.

$$i_L(t) = \frac{1}{L} \int_{t_0}^t v_L(\tau) d\tau + i_L(t_0) \quad (+4)$$

$$P_i = V_L i_L \quad (+3)$$

$$P(3) = (5e^{-3t}) \left(\frac{1}{L} \int_1^t 5e^{-3\tau} d\tau + i_L(1) \right) \Big|_{t=3} \quad [\text{watts}] \quad (+4)$$

$$P(3) = (5e^{-9}) \left(\frac{1}{10^{-2}} \int_1^3 5e^{-3\tau} d\tau + 5 \right) [\text{watts}]$$

$$P(3) = (5e^{-9}) \left(100 \frac{(5)}{(-3)} e^{-3\tau} \Big|_1^3 + 5 \right) [\text{watts}]$$

$$P(3) = (5e^{-9}) \left(\frac{-500}{3} \{ e^{-9} - e^{-3} \} + 5 \right) [\text{w}]$$

$$P(3) = (6.17 \times 10^{-4}) \left(\frac{-500}{3} \{ -4.97 \times 10^{-2} \} + 5 \right) [\text{w}]$$

$$P(3) = (6.17 \times 10^{-4}) (8.28 + 5) [\text{w}]$$


$$P(3) = (6.17 \times 10^{-4}) (13.28) [\text{w}]$$

$$P(3) = 8.19 [\text{mW}]$$

(+4) work + answer

- 3 for neglecting $i_L(1)$
- 3 for wrong integral limits
- 2 for math error
- 2 for no units

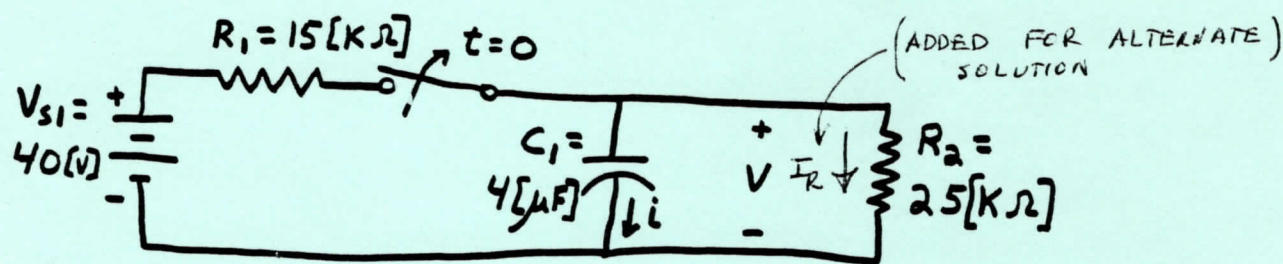7. (15 Points) In the network given, the switch has been closed for a long time. At time $t=0$ the switch is opened.



a) Determine the value of v for all time greater than zero.

SOLUTION: SINCE THE SWITCH HAS BEEN CLOSED FOR A "LONG TIME,"

$$v_c(0^-) = 40 \times \frac{25k}{40k} = 25V = v_c(0^+)$$

AFTER SWITCH IS OPENED, THE EQUATION FOR $v(t) = v_c(t)$ CAN BE WRITTEN AS

$$v_c(t) = A_1 e^{-t/RC} + A_2 \text{ VOLTS}$$

$$RC = 25 \times 10^3 \times 4 \times 10^{-6} = .1 \text{ sec}$$

NOW

$$v_c(0^+) = 25V ; \therefore 25 = A_1 + A_2$$

$$v_c(t \rightarrow \infty) = 0 ; \therefore 0 = A_2$$

$$\text{HENCE } v_c(t) = v(t) = \boxed{25e^{-10t} \text{ VOLTS}}$$

b) Determine the value of i for all time greater than zero.

$$\text{NOW } i_c = i = C \frac{dv_c(t)}{dt} = C [-250e^{-10t}] \text{ A}$$


$$= -4 \times 10^{-6} \times 250 e^{-10t} = \boxed{-1 \times 10^{-3} e^{-10t} \text{ AMPS}}$$

ALTERNATE SOLUTION: (SEE CIRCUIT DIAGRAM)

$$I_R = \frac{v(t)}{R} = \frac{25e^{-10t}}{25 \times 10^3} = 1 \times 10^{-3} e^{-10t} \text{ AMPS}$$

$$\text{BUT } i = -I_R = \boxed{-1 \times 10^{-3} e^{-10t} \text{ AMPS}}$$

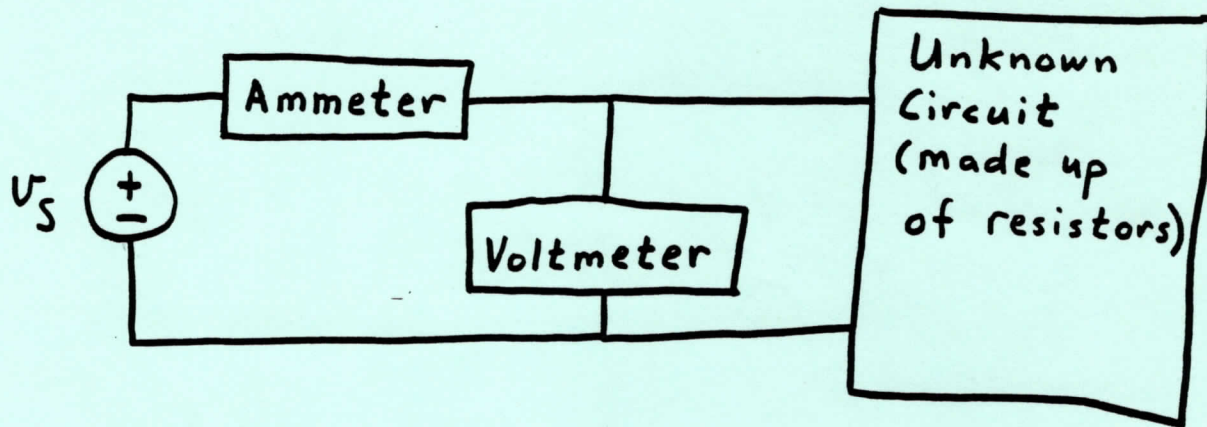Bonus question. (10 points) In the following circuit, the ammeter shown has a resistance of $10[\Omega]$, and the voltmeter shown has a resistance of $20[k\Omega]$. The ammeter reads $2.5[mA]$, and the voltmeter reads $10[V]$. What is the equivalent resistance of the unknown resistive circuit?



The current in the voltmeter is

$$\frac{10[V]}{20[k\Omega]} = 0.5[mA] \quad (+3)$$

so the current in the unknown circuit is

$$2.5 - 0.5 = 2[mA] \quad (+3)$$

$$\text{so } R = \frac{10[V]}{2[mA]} = 5[k\Omega] \quad (+4)$$