



Chapter 6 Transmission Lines

ECE 3317
Dr. Stuart A. Long



p.133

Voltage $V(z) = \alpha_1 \int_{C_t} \mathbf{E} \cdot d\mathbf{s}$ $(C_t \perp z)$ (a)

Current $I(z) = \alpha_2 \oint_{C_0} \mathbf{H} \cdot d\mathbf{s}$ $(C_0 \text{ closed})$ (b)

p.133

Power

$$\frac{1}{2} \operatorname{Re} [V(z) I^*(z)] = \int_A \frac{1}{2} \operatorname{Re} [\mathbf{E} \times \mathbf{H}^*] \cdot \hat{\mathbf{z}} \, dA \quad (c)$$

Characteristic
Impedance

$$Z_0 = \frac{V(z)}{I(z)}$$


infinite line with
with no reflection

Parallel Plate Waveguide (TEM mode)

The Transverse Electromagnetic Fields in a Parallel Waveguide are approximately as follows:

$$\mathbf{E} = \hat{\mathbf{x}} E_0 e^{-jkz} \quad 6.1a$$
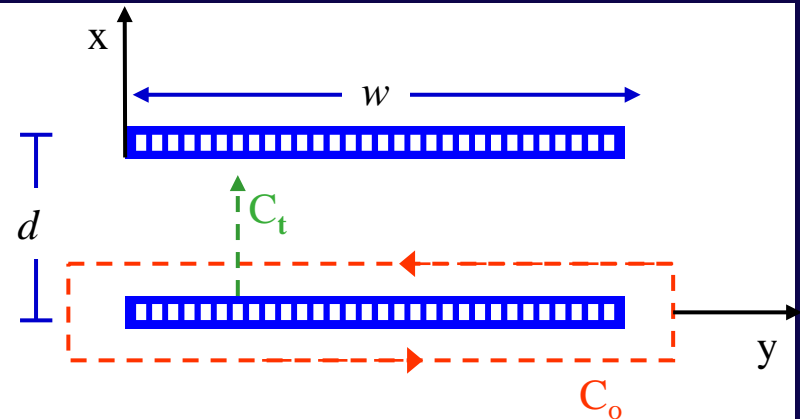
$$\mathbf{H} = \hat{\mathbf{y}} \frac{E_0}{\eta} e^{-jkz} \quad 6.1b$$



Using the
General
Definitions

$$V(z) = \alpha_1 \int_0^d \mathbf{E} \cdot \hat{\mathbf{x}} dx = \alpha_1 E_0 d e^{-jkz} \quad 6.2a$$

$$I(z) = \alpha_2 \int_0^w \mathbf{H} \cdot \hat{\mathbf{y}} dy = \alpha_2 \frac{E_0 w}{\eta} e^{-jkz} \quad 6.2b$$

Parallel Plate Waveguide (TEM mode)

The time-average power transmitted
is given by

$$P_t = \int_A \frac{E_0^2}{2\eta} \hat{z} \circ \hat{z} dA = \frac{E_0^2}{2\eta} wd$$


equate

$$\frac{1}{2} \operatorname{Re} \left[V(z) I(z)^* \right] = \frac{E_0^2}{2\eta} wd$$

$$\frac{1}{2} (\alpha_1 E_0 d) \left(\alpha_2 \frac{E_0}{\eta} w \right) = \frac{E_0^2}{2\eta} wd$$

$$\alpha_1 \alpha_2 \frac{E_0^2}{2\eta} wd = \frac{E_0^2}{2\eta} wd \Rightarrow \alpha_1 \alpha_2 = 1$$


choose $\alpha_1 = 1$ and $\alpha_2 = 1$

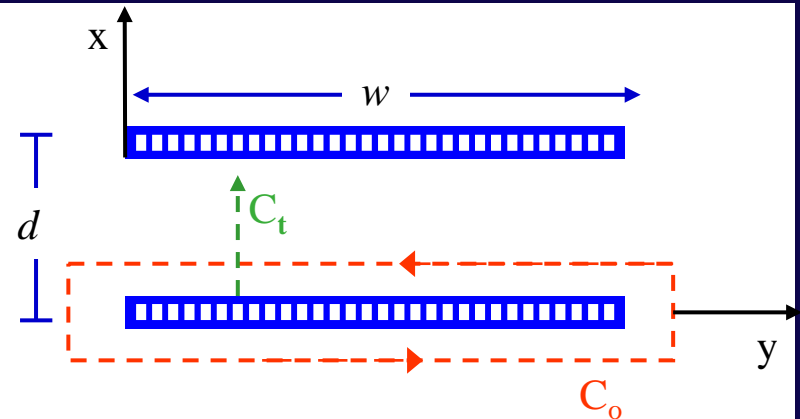


$$V(z) = E_0 d e^{-jkz} \quad 6.3a$$

$$I(z) = \frac{E_0 w}{\eta} e^{-jkz} \quad 6.3b$$
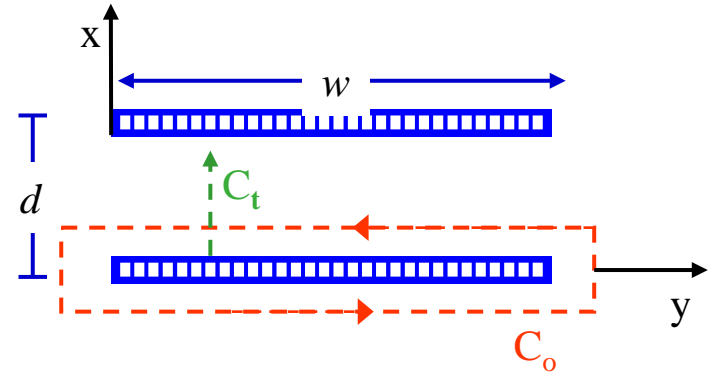
$$Z_0 = \eta \frac{d}{w} \quad [\Omega] \quad 6.4$$



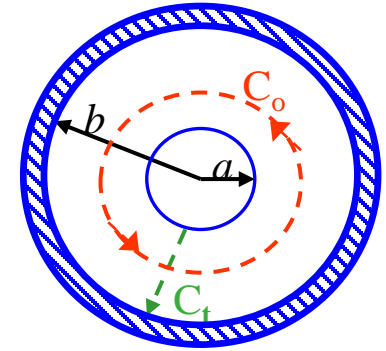The fields inside a coaxial line for the TEM mode are given by



$$\mathbf{E} = \hat{\rho} \frac{V_0}{\rho} e^{-jkz} \quad 6.5a$$

$$\mathbf{H} = \hat{\phi} \frac{V_0}{\eta\rho} e^{-jkz} \quad 6.5b$$

Using the
General
Definitions

$$V(z) = \alpha_1 \int_a^b \mathbf{E} \cdot \hat{\rho} d\rho = \alpha_1 V_0 \ln \frac{b}{a} e^{-jkz} \quad 6.6a$$

$$I(z) = \alpha_2 \oint \mathbf{H} \cdot \hat{\phi} \rho d\phi = \alpha_2 \frac{2\pi V_0}{\eta} e^{-jkz} \quad 6.6b$$

The time-average power transmitted is given by

$$P_t = \frac{\pi V_0^2}{\eta} \ln \frac{b}{a}$$


equate

$$\frac{1}{2} \operatorname{Re} \left[V(z) I(z)^* \right] = \frac{\pi V_0^2}{\eta} \ln \frac{b}{a}$$

$$\frac{1}{2} \left(\alpha_1 V_0 \ln \frac{b}{a} \right) \left(\alpha_2 \frac{2\pi V_0}{\eta} \right) = \frac{\pi V_0^2}{\eta} \ln \frac{b}{a}$$

$$\alpha_1 \alpha_2 \frac{\pi V_0^2}{\eta} \ln \frac{b}{a} = \frac{\pi V_0^2}{\eta} \ln \frac{b}{a} \Rightarrow \alpha_1 \alpha_2 = 1$$

choose $\alpha_1 = 1$ and $\alpha_2 = 1$

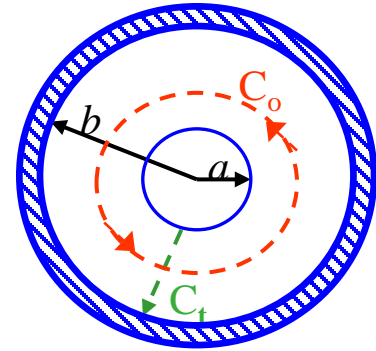


$$V(z) = V_0 \ln \frac{b}{a} e^{-jkz}$$

$$I(z) = \frac{2\pi V_0}{\eta} e^{-jkz}$$

$$Z_0 = \frac{\eta}{2\pi} \ln \frac{b}{a} \quad [\Omega]$$

6.7

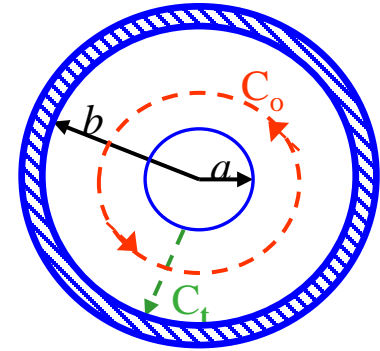

Example: What is the ratio b/a for
an air-filled coax and $50[\Omega]$ line?

$$50 = \frac{377}{2\pi} \ln(b/a)$$

$$\Rightarrow \frac{b}{a} = 2.3$$

Rectangular Waveguide (Dominant TE₁₀ mode)


6-11

The Electromagnetic fields in a Rectangular Waveguide for the are TE₁₀ mode are

$$E_y = E_0 \sin\left(\frac{\pi x}{a}\right) e^{-jk_z z} \quad 6.8a$$

$$H_x = -\frac{k_z}{\omega\mu} E_0 \sin\left(\frac{\pi x}{a}\right) e^{-jk_z z} \quad 6.8b$$

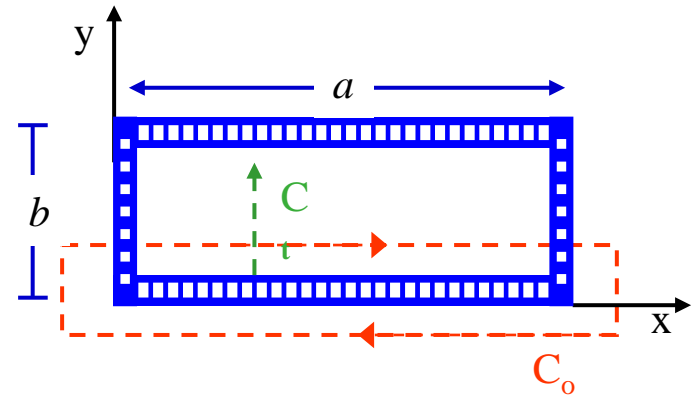
$$H_z = j \frac{\pi/a}{\omega\mu} E_0 \cos\left(\frac{\pi x}{a}\right) e^{-jk_z z} \quad 6.8c$$



Rectangular Waveguide (Dominant TE_{10} mode)

6-12

Using the
General
Definitions

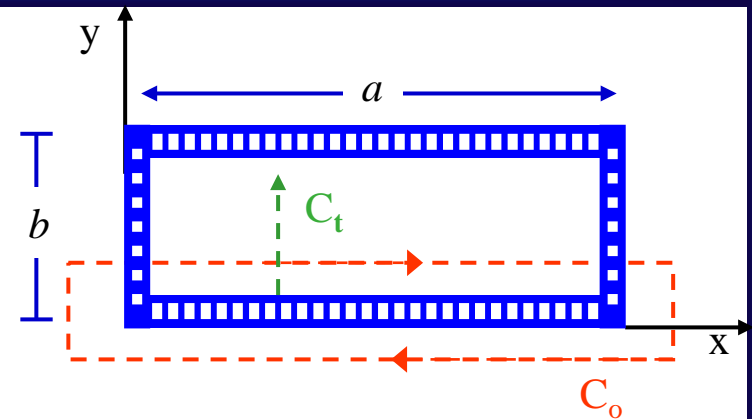

$$\begin{aligned} V(z) &= \alpha_1 \int_0^b E_y \Big|_{x=a/2} dy \\ &= \alpha_1 E_0 b e^{-jk_z z} \end{aligned}$$

6.9a

$$\begin{aligned} I(z) &= \alpha_2 \oint_{C_0} \hat{x} \cdot \mathbf{H} dx \\ &= \alpha_2 \frac{2E_0 a k_z}{\pi \omega \mu} e^{-jk_z z} \end{aligned}$$


6.9b

Rectangular Waveguide (Dominant TE_{10} mode)

6-13

The time-average power transmitted
is given by
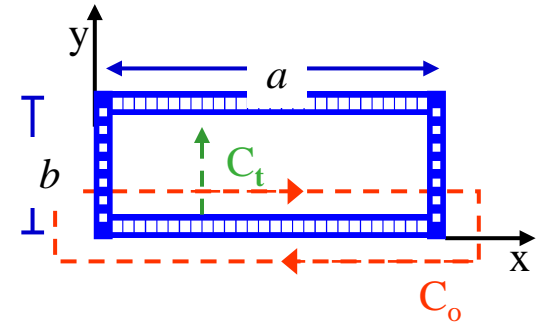
$$P_t = \frac{ab}{4} \frac{k_z}{\omega\mu} E_0^2$$



equate
$$\frac{1}{2} \text{Re} \left[V(z) I(z)^* \right] = \frac{ab}{4} \frac{k_z}{\omega\mu} E_0^2$$

$$\frac{1}{2} (\alpha_1 E_0 b) \left(\alpha_2 \frac{2E_0 a k_z}{\pi \omega\mu} \right) = \frac{ab}{4} \frac{k_z}{\omega\mu} E_0^2$$

$$\alpha_1 \alpha_2 \frac{ab}{\pi} \frac{k_z}{\omega\mu} E_0^2 = \frac{ab}{4} \frac{k_z}{\omega\mu} E_0^2 \Rightarrow \alpha_1 \alpha_2 = \frac{\pi}{4}$$

choose
$$\alpha_1 = \sqrt{\frac{ak_z}{2b\omega\mu}} \text{ and } \alpha_2 = \sqrt{\frac{\pi^2 b\omega\mu}{8ak_z}} \Rightarrow Z_0 = 1$$


Rectangular Waveguide (Dominant TE_{10} mode)

6-14

$$V(z) = \sqrt{\frac{ak_z}{2b\omega\mu}} E_0 b e^{-jk_z z}$$

$$I(z) = \sqrt{\frac{\pi^2 b\omega\mu}{8ak_z}} \frac{2E_0 ak_z}{\pi\omega\mu} e^{-jk_z z}$$

$$Z_0 = 1 \text{ } [\Omega]$$

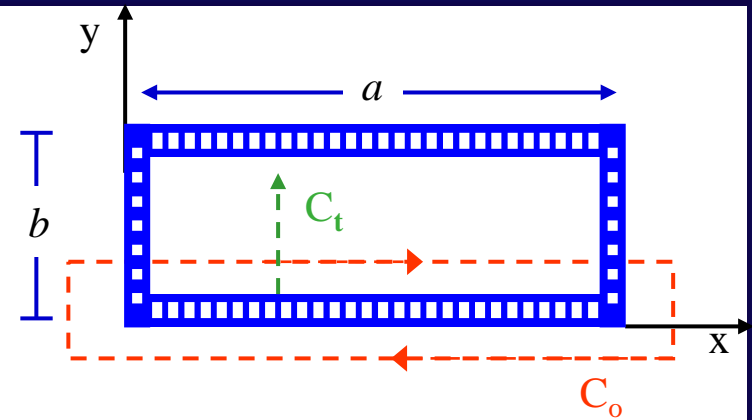

(Parallel plate waveguide)

$$\nabla \times \mathbf{E} = -j\omega\mu\mathbf{H}$$

$$\frac{\partial}{\partial z} E_x = -j\omega\mu H_y$$

$$V(z) = E_0 d e^{-jkz} = d E_x$$

$$\frac{\partial V}{\partial z} = -j\omega L I$$

$$L = \frac{\mu d}{w} \left[\frac{\text{H}}{\text{m}} \right]$$

$$\nabla \times \mathbf{H} = j\omega\varepsilon\mathbf{E}$$

$$-\frac{\partial}{\partial z} H_y = j\omega\varepsilon E_x$$

$$I(z) = \frac{E_0 w}{\eta} e^{-jkz} = w H_y$$

$$\frac{\partial I}{\partial z} = -j\omega C V$$

$$C = \frac{\varepsilon w}{d} \left[\frac{\text{F}}{\text{m}} \right]$$

(Parallel plate waveguide)

$$\frac{\partial^2 V}{\partial z^2} + \omega^2 LC V = 0 \quad \text{wave equation} \quad 6.15$$

$$V = V_+ e^{-jkz} + V_- e^{+jkz} \quad 6.16$$

$$I = \frac{1}{Z_0} \left[V_+ e^{-jkz} - V_- e^{+jkz} \right] \quad 6.17$$

$$k = \omega \sqrt{LC}$$

$$Z_0 = \sqrt{\frac{L}{C}} \quad 6.18$$

$$V(z) = V^+ e^{-jkz} + V^- e^{+jkz} \quad 6.22$$

$$I(z) = \frac{V^+}{Z_0} e^{-jkz} - \frac{V^-}{Z_0} e^{+jkz} \quad 6.23$$

Impedance $Z(z) = \frac{V(z)}{I(z)}$

$$Z_n(z) = \frac{Z(z)}{Z_0} = \frac{V^+ e^{-jkz} + V^- e^{+jkz}}{V^+ e^{-jkz} - V^- e^{+jkz}} \quad 6.24$$


(note $Z(0) = Z_L$)

Reflection coefficient

$$\Gamma_L = \frac{V^-}{V^+}$$

With the reflection coefficient now defined, we can rewrite 6.24 as
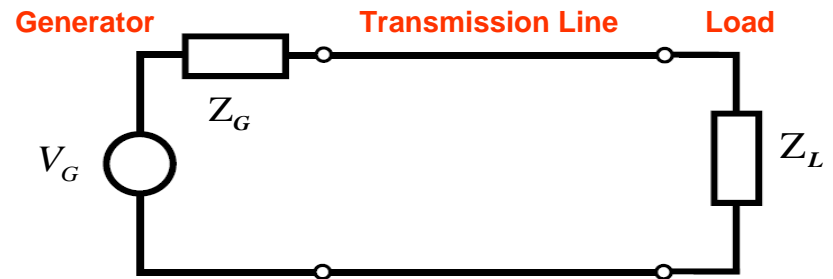
$$Z_n(z) = \frac{e^{-jkz} + \Gamma_L e^{+jkz}}{e^{-jkz} - \Gamma_L e^{+jkz}}$$



Evaluating Z_n at the Load ($z = 0$)

$$Z_{nL}(z = 0) = \frac{Z(z = 0)}{Z_0} = \frac{1 + \Gamma_L}{1 - \Gamma_L} \quad \left(\text{or } \Gamma_L = \frac{Z_{nL} - 1}{Z_{nL} + 1} \right) \quad 6.25$$

Evaluating Z_n at a point along line ($z = -l$)

$$Z_n(z = -l) = \frac{Z(z = -l)}{Z_0} = \frac{Z_L + jZ_0 \tan kl}{Z_0 + jZ_L \tan kl} \quad 6.27$$

$$\left| V_{(z)} \right| = \left| V^+ \right| \left| 1 + \Gamma_L e^{j2kz} \right|$$

with $\Gamma_L = \left| \Gamma_L \right| e^{j\varphi}$

$$\left| V_{(z)} \right| = \left| V^+ \right| \left| 1 + \left| \Gamma_L \right| e^{j(\varphi + 2kz)} \right|$$

V_{\max} when $\varphi + 2kz = 0, -2\pi, \dots$

V_{\min} when $\varphi + 2kz = -\pi, -3\pi, \dots$

$$|V(z)| = |V^+| \left| 1 + |\Gamma_L| e^{j(\varphi + 2kz)} \right|$$

$$\frac{|V(z)|}{|V^+|} = \left| 1 + |\Gamma_L| e^{j(\varphi + 2kz)} \right|$$

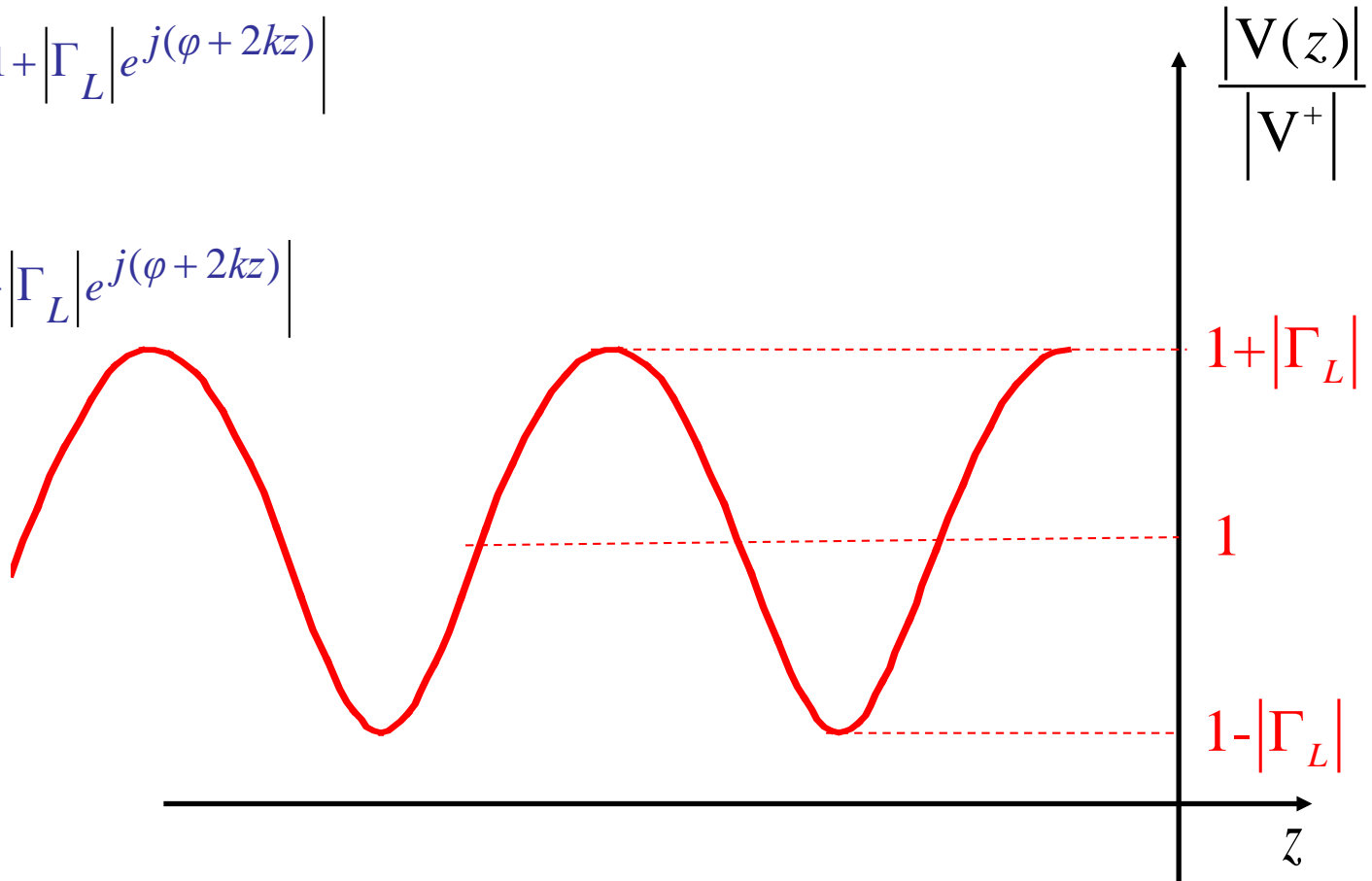


Fig. 6.6

$$|V(z)| = |V^+| \left| 1 + |\Gamma_L| e^{j(\varphi + 2kz)} \right|$$

$$\frac{|V(z)|}{|V^+|} = \left| 1 + |\Gamma_L| e^{j(\varphi + 2kz)} \right|$$


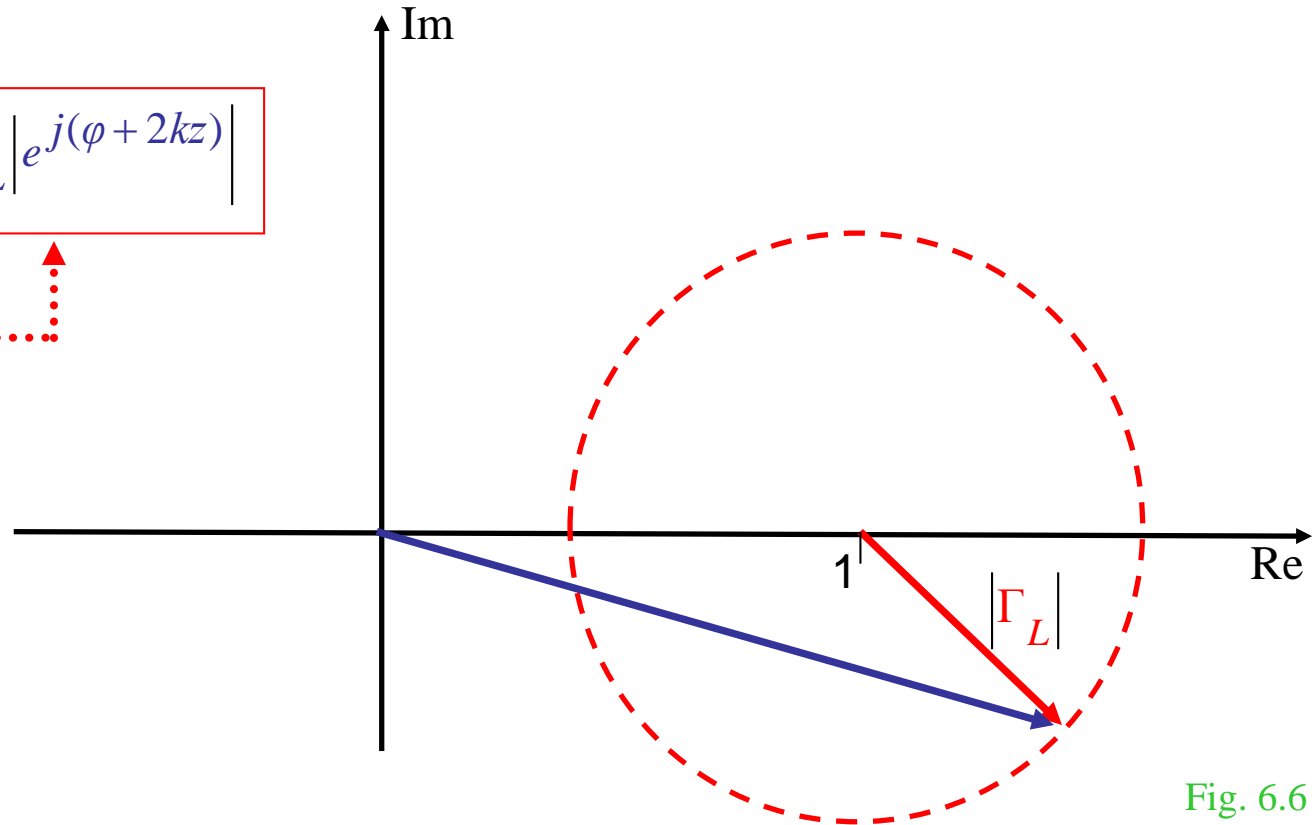


Fig. 6.6

$$\left| 1 + |\Gamma_L| e^{j(\varphi + 2kz)} \right|$$

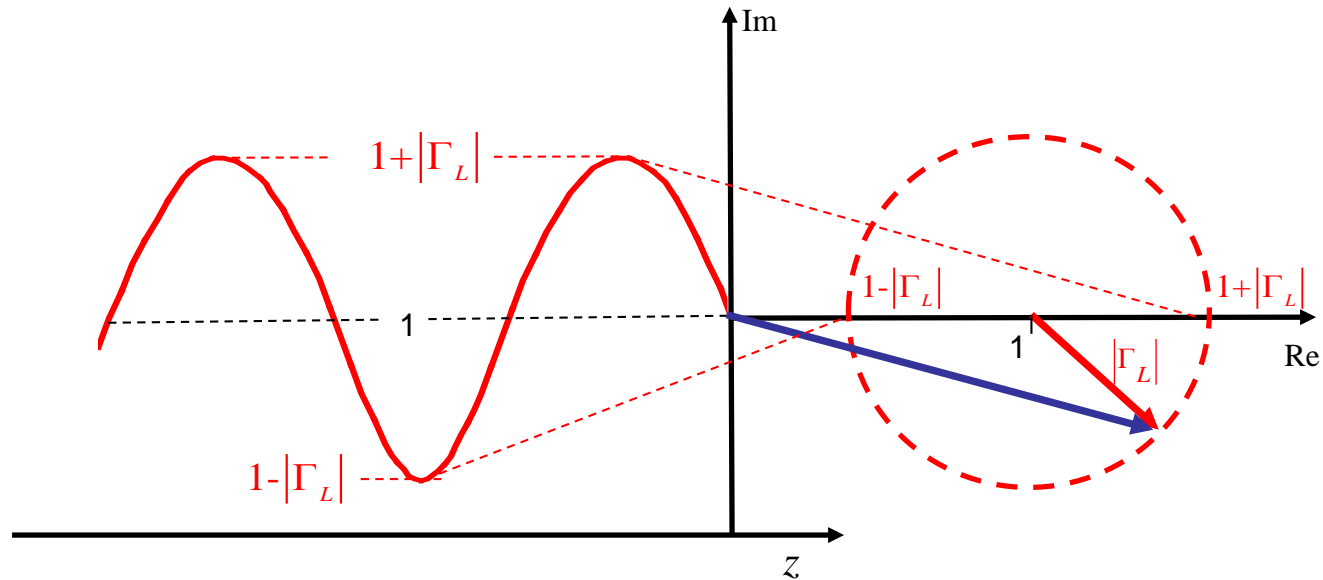

$$\frac{|V(z)|}{|V^+|} = \left| 1 + |\Gamma_L| e^{j(\varphi + 2kz)} \right|$$

$$[\text{VSWR}] = \frac{V_{\max}}{V_{\min}} = \frac{I_{\max}}{I_{\min}}$$

$$[\text{VSWR}] = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad 6.29$$

$$|\Gamma_L| = \frac{[\text{VSWR}] - 1}{[\text{VSWR}] + 1} \quad 6.30$$

To determine ($\angle \Gamma_L$) or Z_L
also need position of V_{\min}

Note:

$$\text{Power} \sim V^2 \Rightarrow \frac{P^-}{P^+} = |\Gamma_L|^2$$

$$\text{Power to load} \sim 1 - |\Gamma_L|^2$$

Ex. 6.6

$$Z_L = 17.4 - j30[\Omega] \quad \text{and} \quad Z_0 = 50[\Omega]$$

$$\Gamma_L = \frac{Z_{nL}^{-1}}{Z_{nL} + 1} = \frac{Z_L - Z_0}{Z_L + Z_0} = -0.24 - j.55$$



or

$$\Gamma_L = 0.6e^{-j1.99}$$

where

$$|\Gamma_L| = 0.6$$

$$\phi = \angle \Gamma_L = 1.99$$

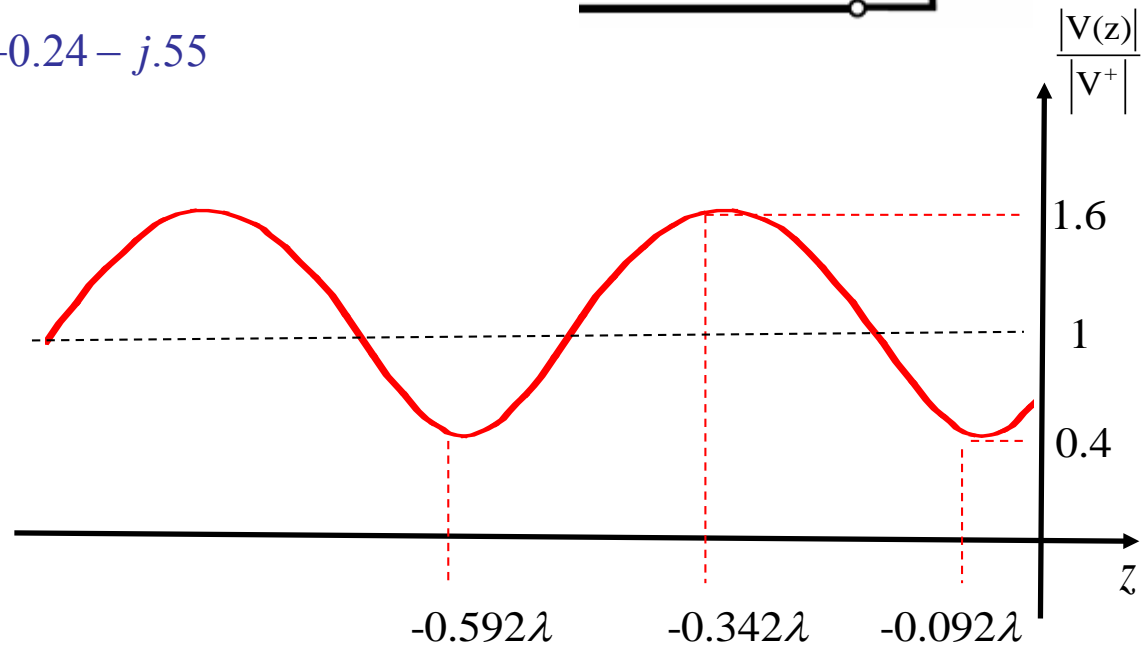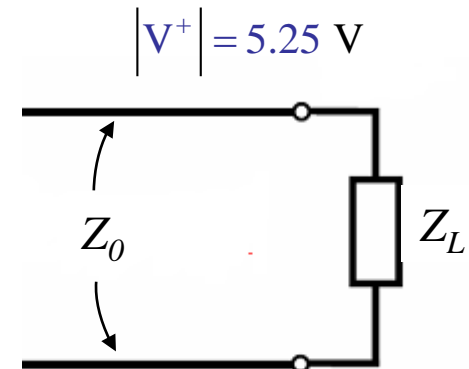


$$V_{\max} \quad \text{when} \quad \varphi + 2kz = 0, -2\pi, \dots$$

$$V_{\min} \quad \text{when} \quad \varphi + 2kz = -\pi, -3\pi, \dots$$

Ex. 6.6 V_{\min} where $\phi + 2k z_m = -\pi$

$$z_m = \frac{-\pi - \phi}{2k} = \frac{(-\pi + 1.99)\lambda}{2(2\pi)} = -.092\lambda$$

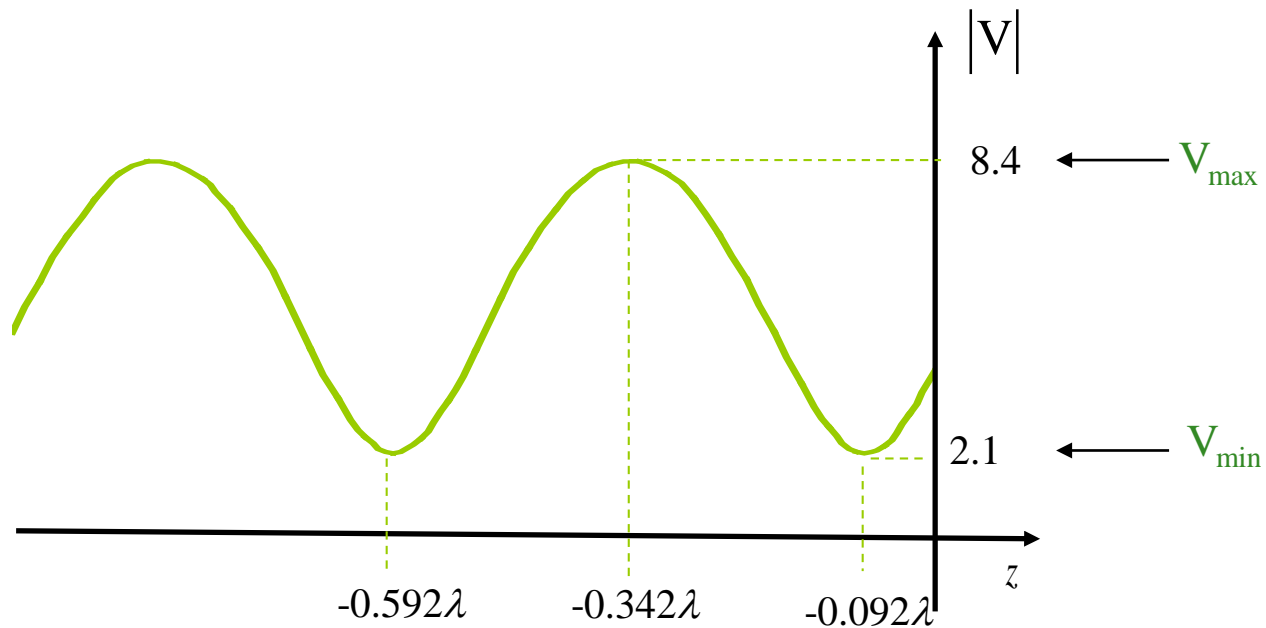

Ex. 6.6

Reverse problem

$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{8.4}{2.1} = 4.0$$



$$|\Gamma_L| = \frac{VSWR-1}{VSWR+1} = \frac{4-1}{4+1} = 0.6$$

To determine ($\angle\Gamma_L$) or Z_L also need position of V_{\min}

$$\angle\Gamma_L = \phi = -\pi - 2kz_m = -\pi - 2\left(\frac{2\pi}{\lambda}\right)(-.092\lambda) = -1.99$$

$$Z_L = Z_0 \left[\frac{1+\Gamma_L}{1-\Gamma_L} \right] = \boxed{17.4 - j30 \quad \Omega}$$
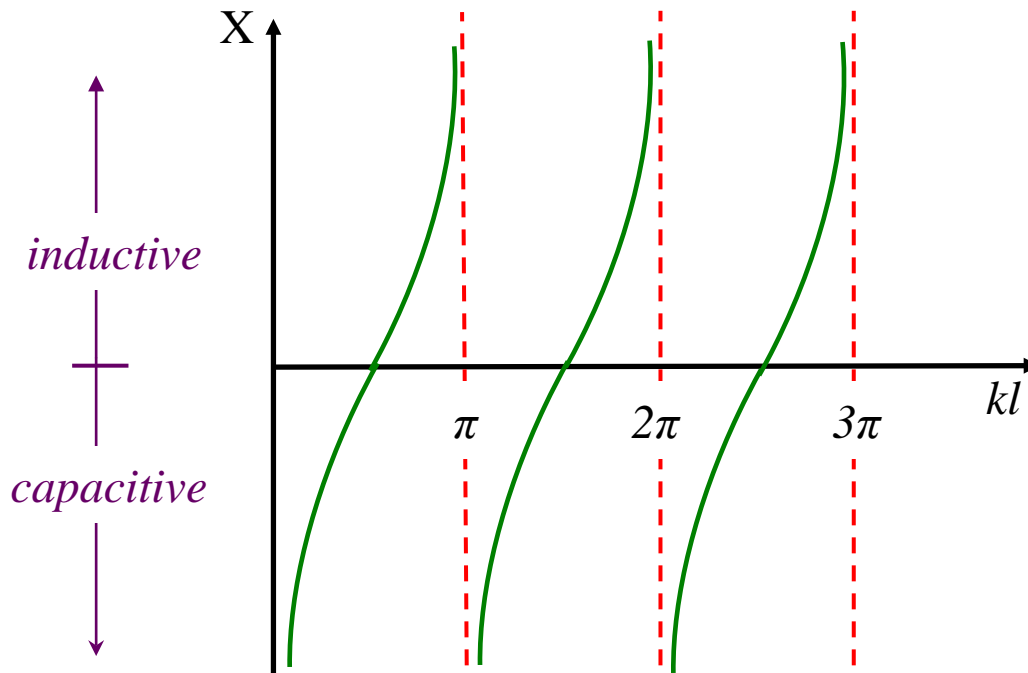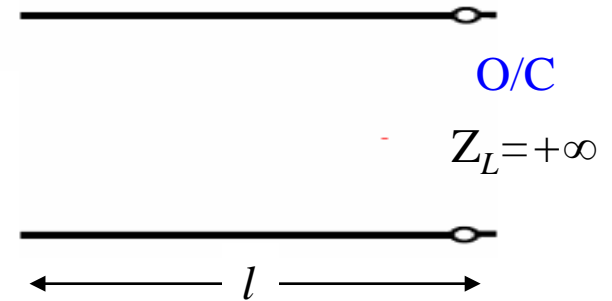
$$Z(-l) = Z_0 \frac{Z_L + jZ_0 \tan kl}{Z_0 + jZ_L \tan kl} = Z_0 \frac{1}{j \tan kl}$$





pure imaginary

$$jX = -jZ_0 \cot kl$$

If the impedance is purely imaginary, $Z = R + jX$ becomes $Z = jX$, where X is called the reactance.

$\lim kl \ll 1$ (small l or low freq)

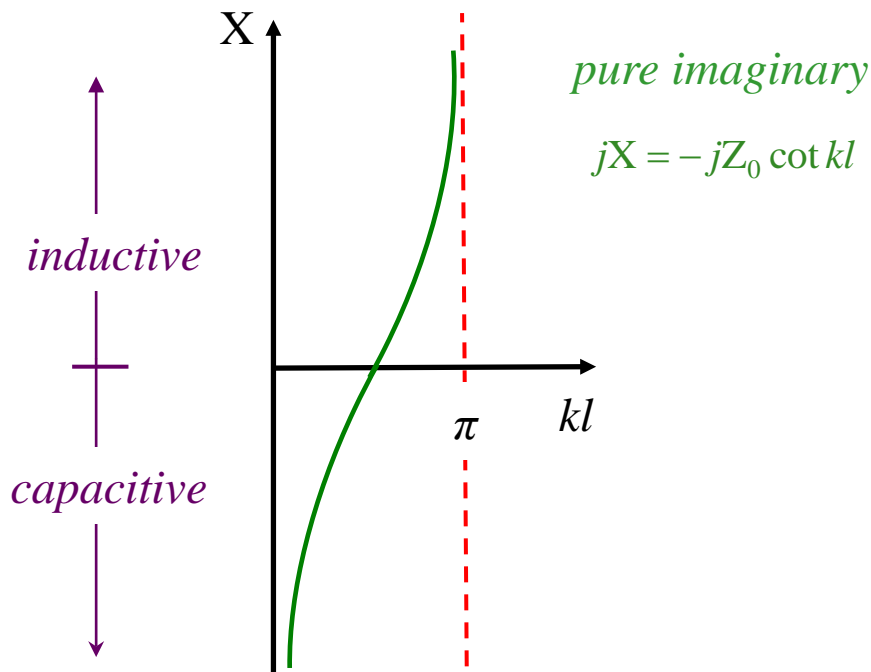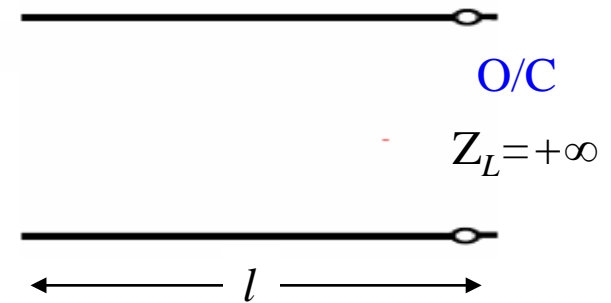

Note: at $kl = \frac{\pi}{2} \Rightarrow \left(l = \frac{\lambda}{4} \right)$


$Z\left(-\lambda/4\right) = 0$ (short circuit)

near $kl \leq \pi$ Z is inductive

near $kl \geq 0$ Z is capacitive



Philip Smith

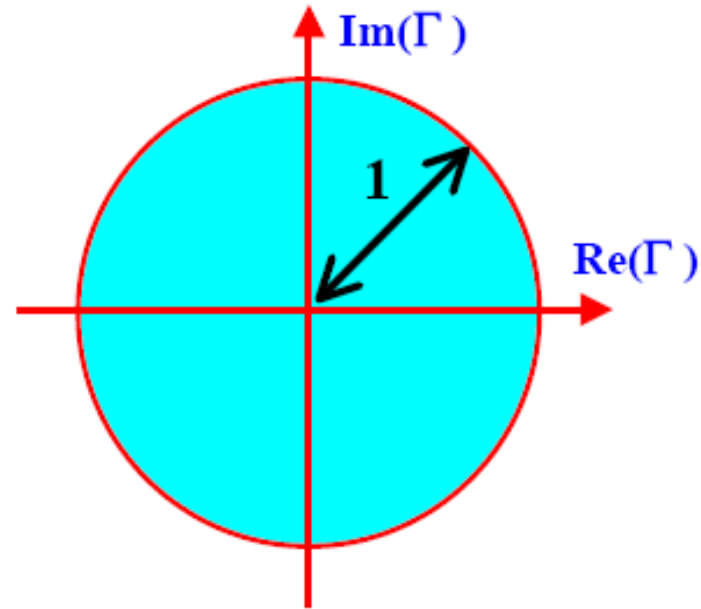


- Shows the entire universe of complex impedances in one convenient circle.
- Invented at Bell Labs by Philip Smith in 1937.
- By 1975 about 9 million copies of his chart sold to microwave engineers all over the world.
- Its usefulness continues to this day as a method of displaying measured and calculated data produced by computer software and modern measurement instruments.



$$Z_{nL} = \frac{1 + \Gamma_L}{1 - \Gamma_L} = R + jX$$
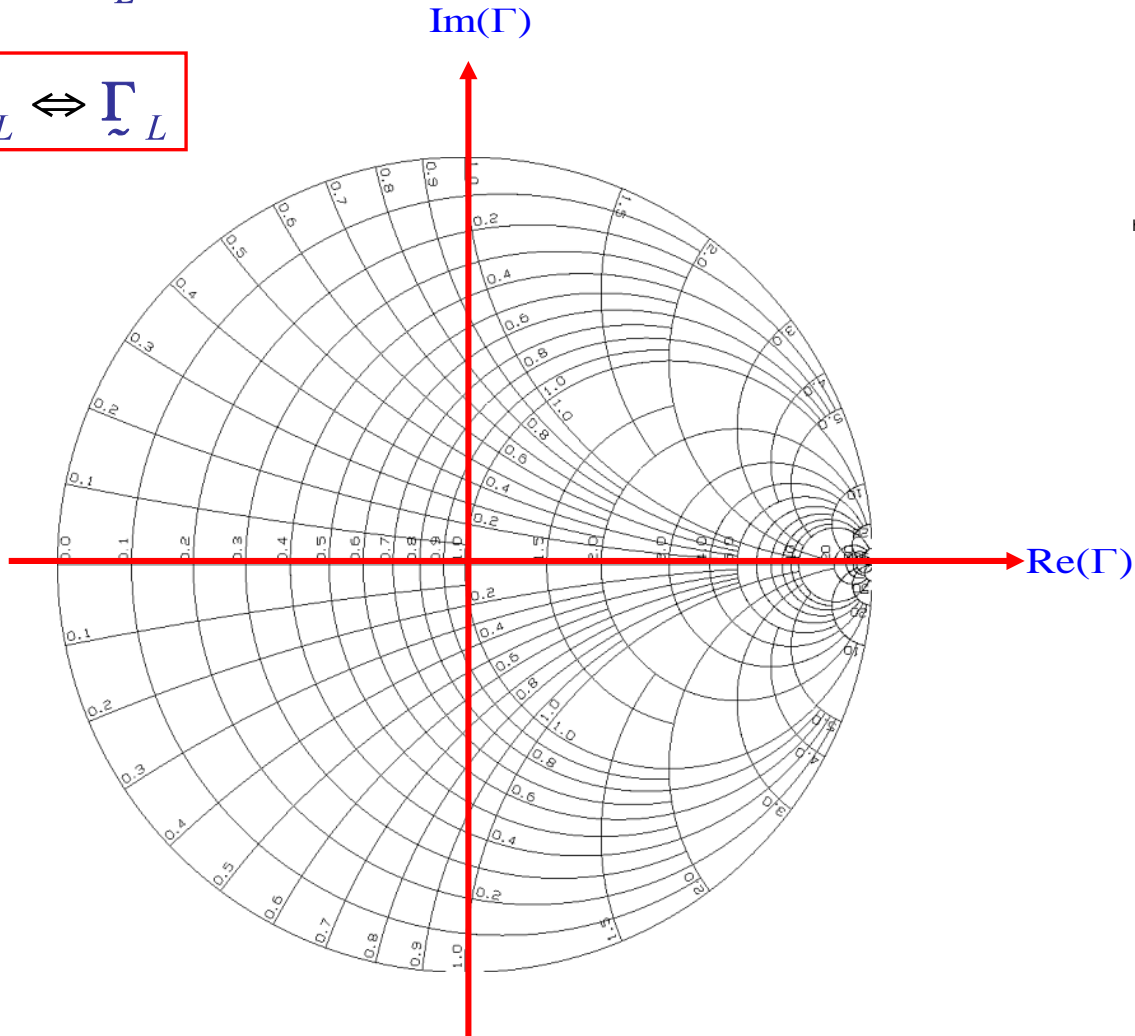
$$\tilde{Z}_{nL} \Leftrightarrow \tilde{\Gamma}_L$$



http://my.ece.ucsb.edu/sanabria/images/chris_tatoo2.jpg

Z Chart

Constant R Circles on Chart


$R_n=0$

$R_n=0.5$

$R_n=1$

$R_n=2$

$R_n=50$

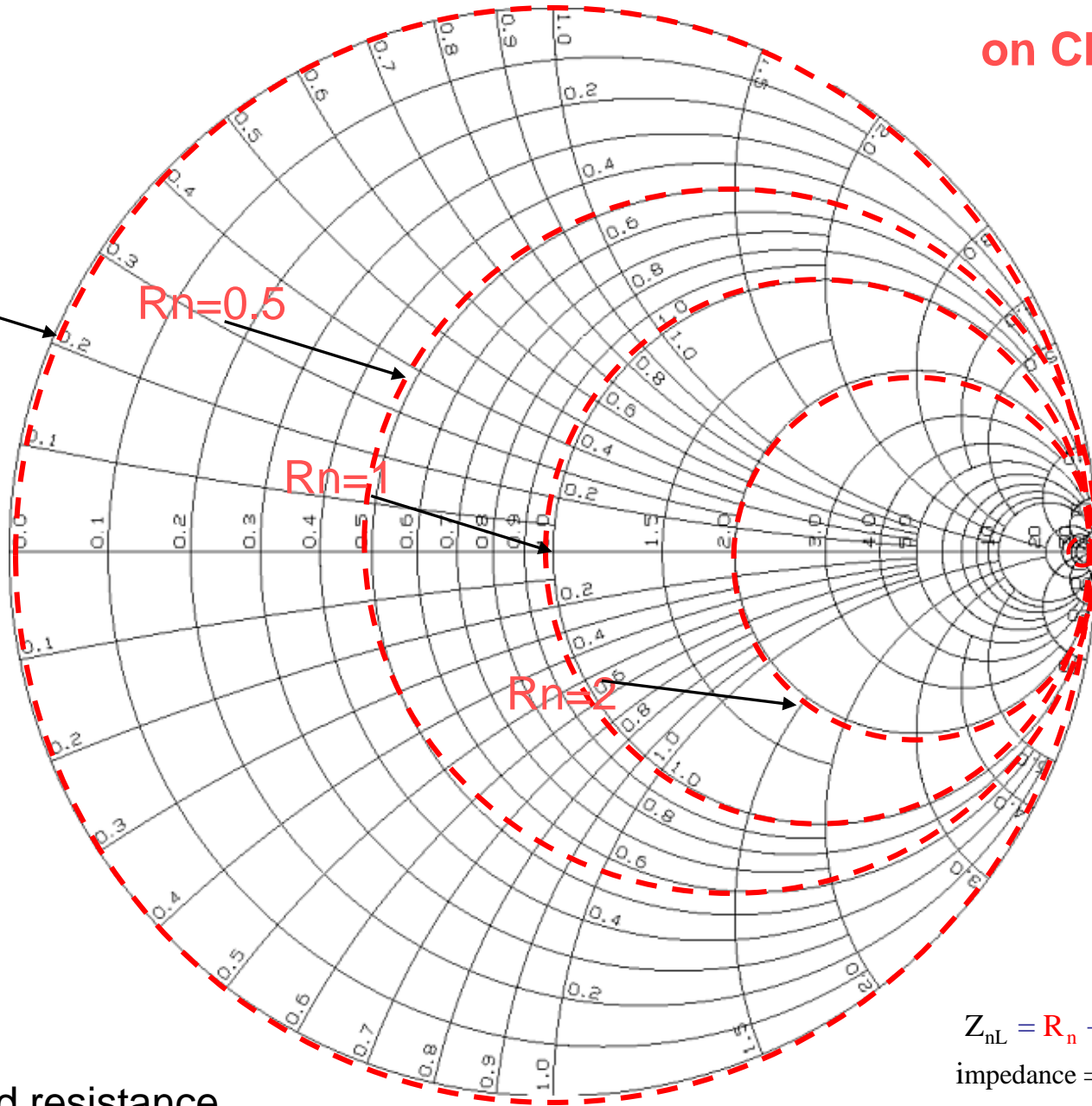


$$Z_{nL} = R_n + jX_n \quad [\Omega]$$

impedance = resistance + j reactance

R_n : normalized resistance

Z Chart

Constant X Arcs on Chart

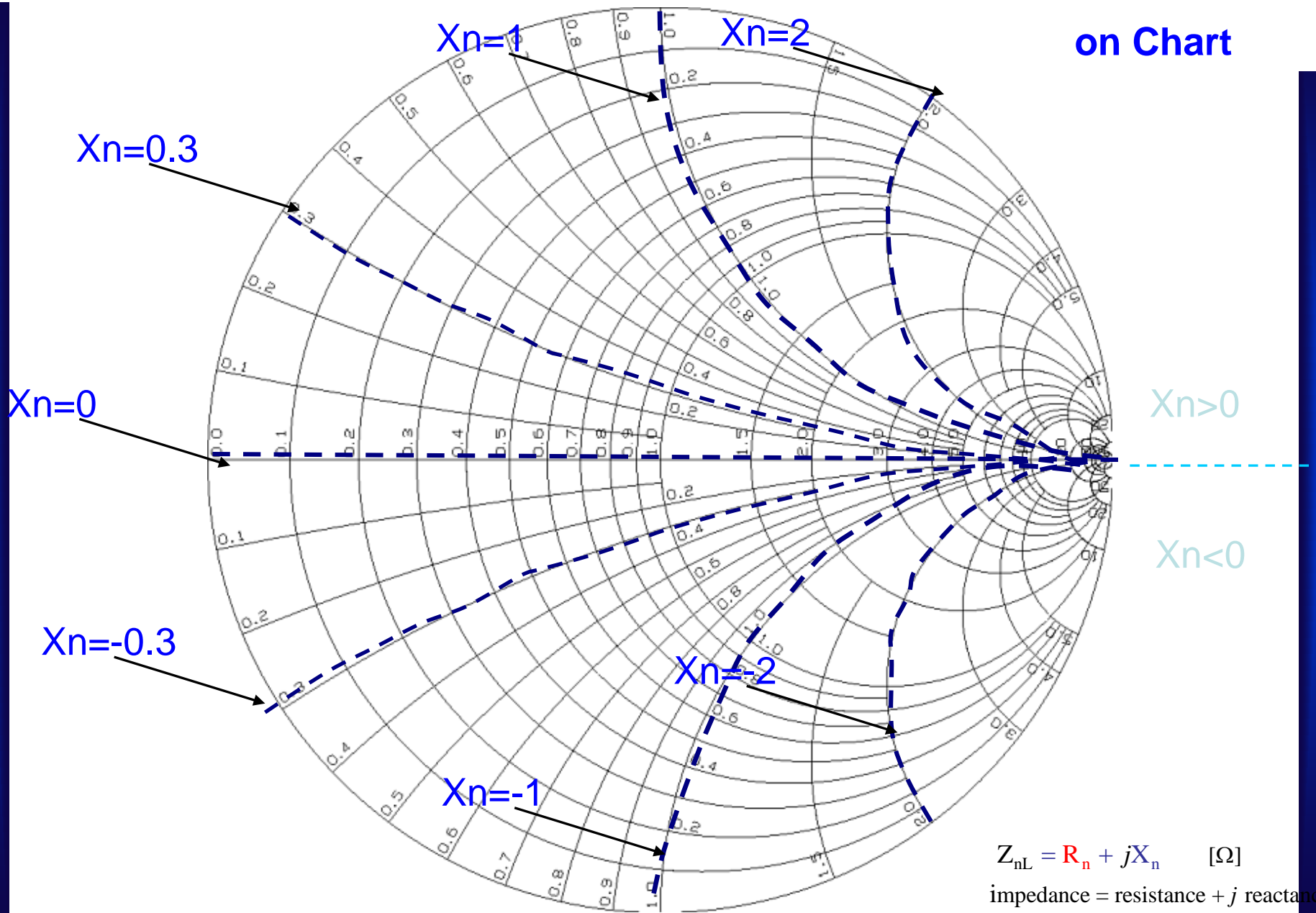

$$Z_{nL} = R_n + jX_n \quad [\Omega]$$


impedance = resistance + j reactance

$$Z_{nL} = R_n + jX_n \quad [\Omega]$$

$$Z_{nL} = 0.2 - j0.3 \quad [\Omega]$$

Rn=0.2 circle

Xn=-0.3 arc

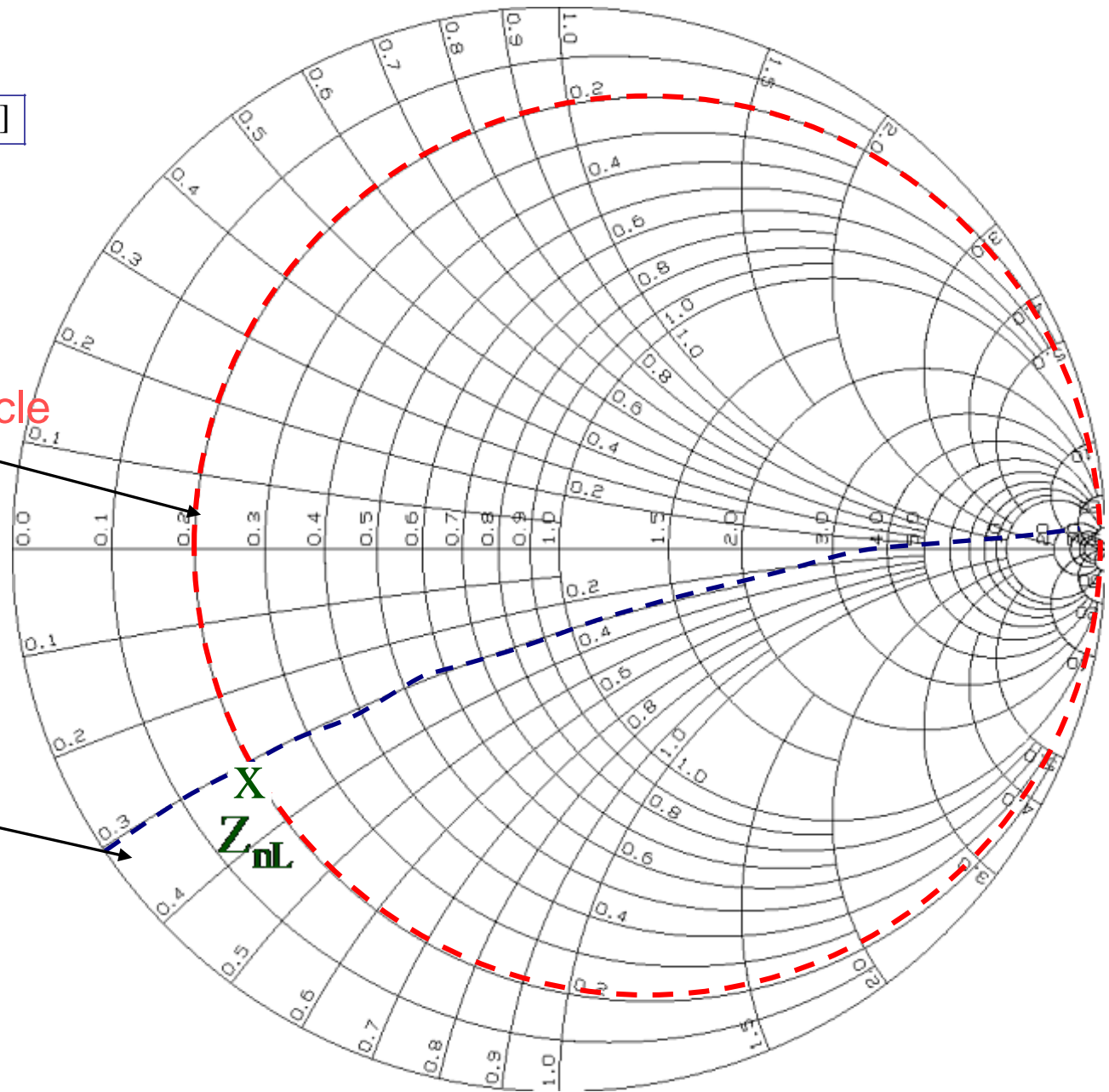


$$Z_{nL} = R_n + jX_n \quad [\Omega]$$

$$Z_{nL} = 0.2 - j0.3 \quad [\Omega]$$

Using your compass draw the $0.2 - j0.3$ circle with center at $z_n = 1$.

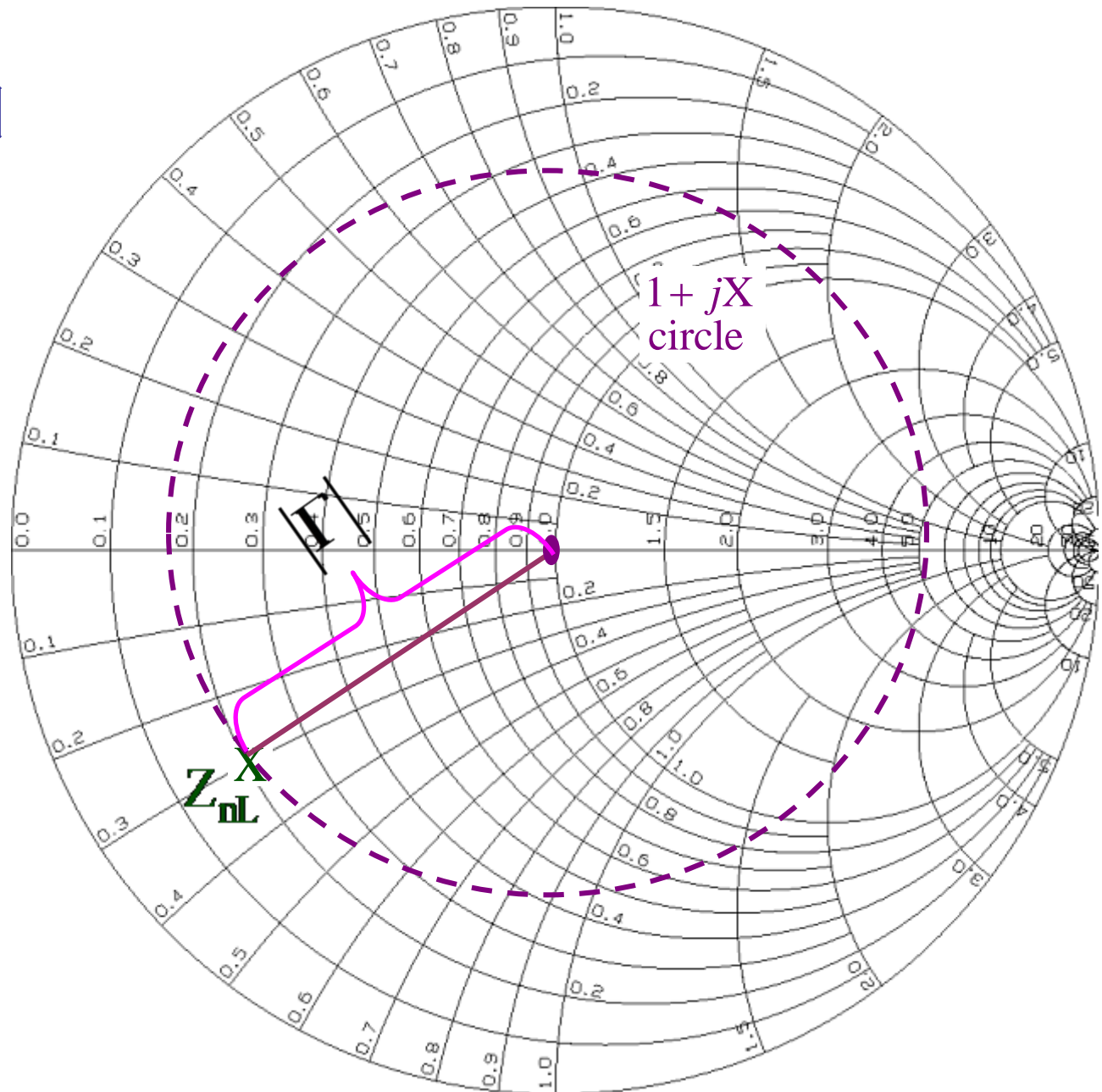
(NOTE: this circle is not on the chart until you draw it.)



Find the value of reflection coefficient

Reflection Coeff PHASE

Reflection Coeff MAGNITUDE

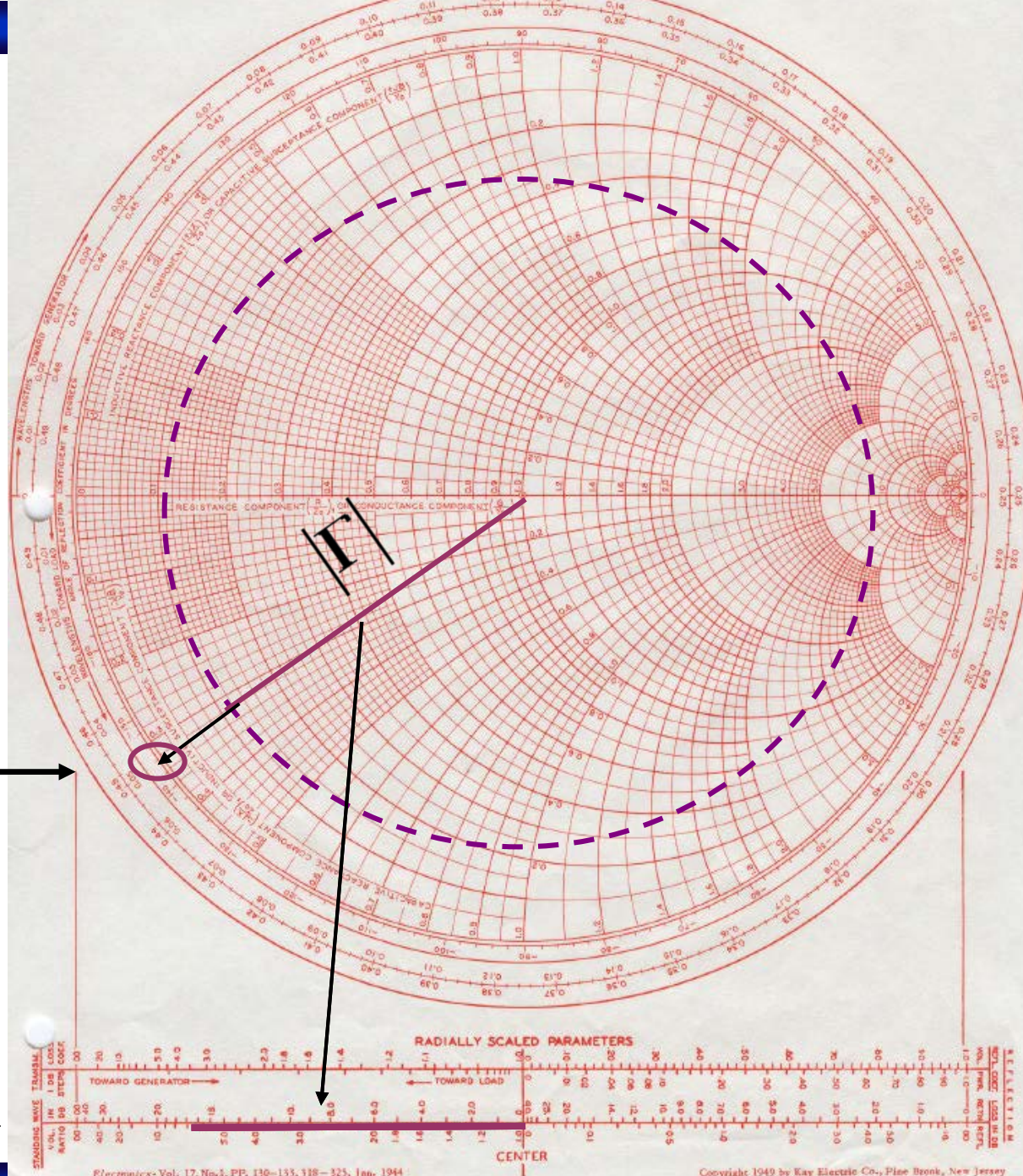

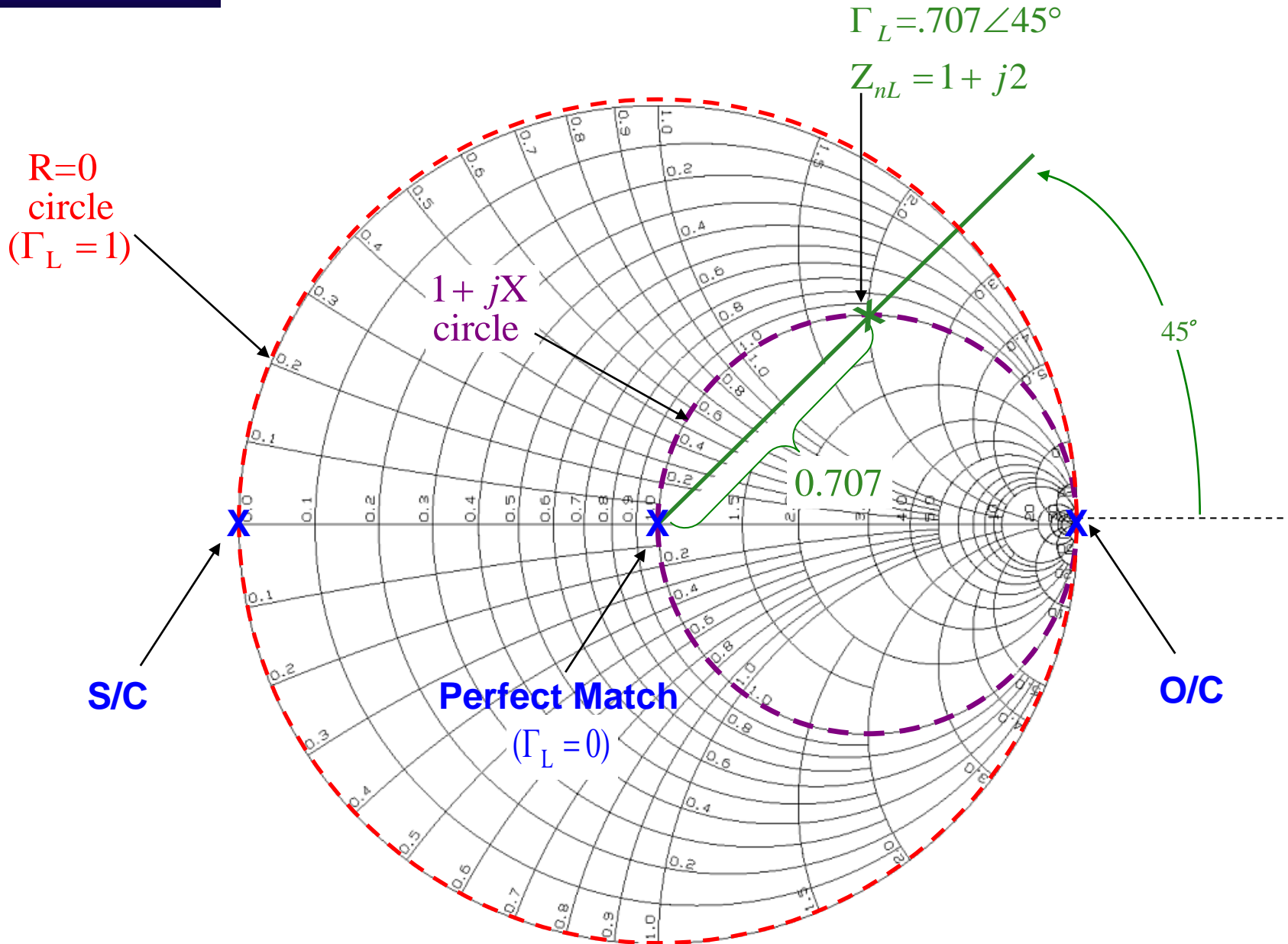




fig 6.13

$$Z(z) = Z_0 \frac{e^{-jkz} + \Gamma_L e^{+jkz}}{e^{-jkz} - \Gamma_L e^{+jkz}} = Z_0 \frac{1 + \Gamma_L e^{+2jkz}}{1 - \Gamma_L e^{+2jkz}}$$


movement in negative \hat{z} direction
(toward generator)



clockwise motion on circle of constant $|\Gamma_L|$

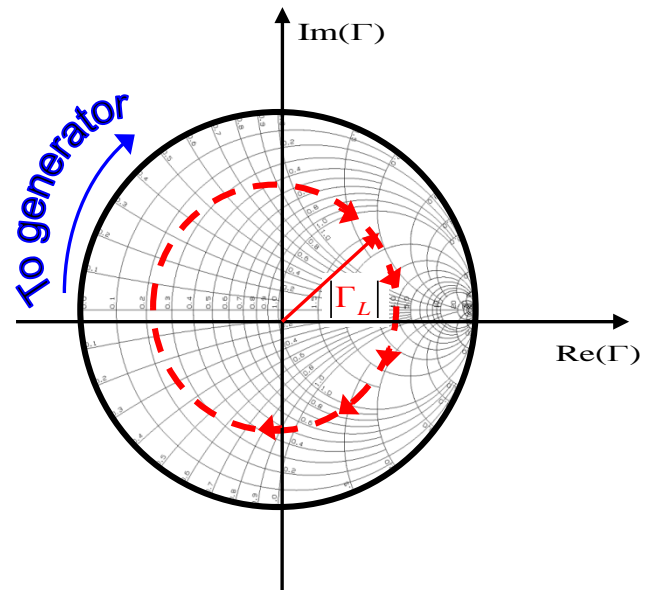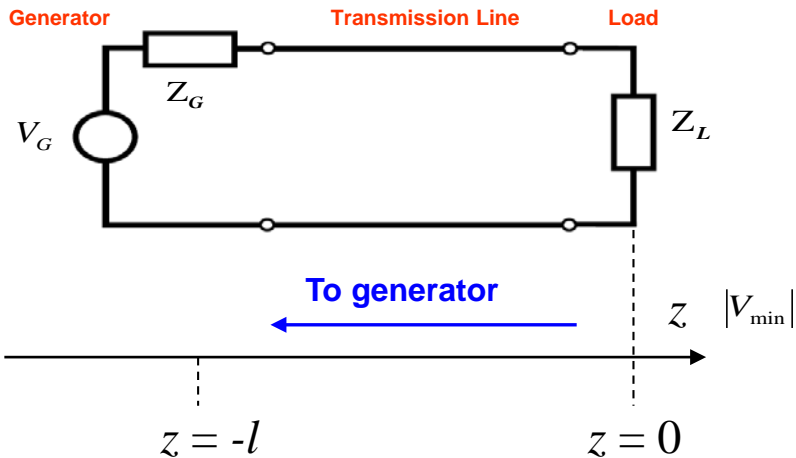

$$\frac{|V(z)|}{|V^+|} = \left| 1 + \Gamma_L e^{j2kz} \right|$$

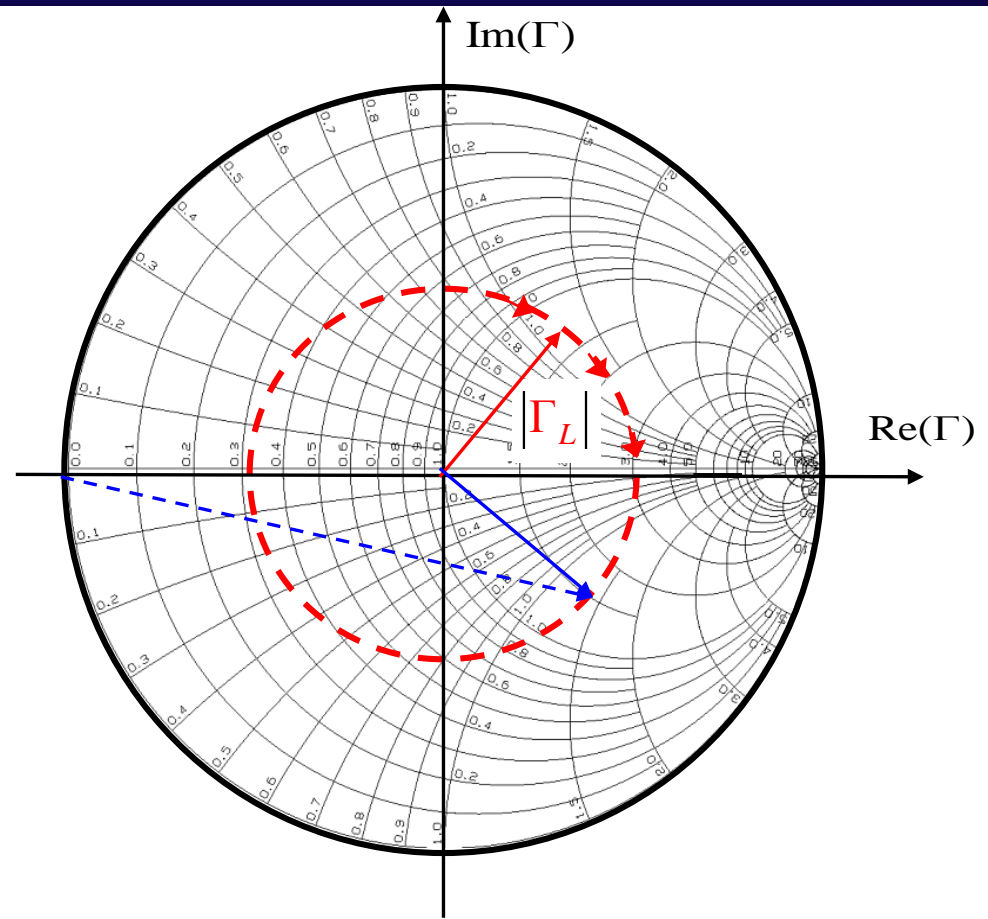

Note:


complete circle ($360^\circ = 2\pi \text{ rad}$) = $\frac{\lambda}{2}$

$Y_n(z) = \frac{1}{Z_n(z)} \Rightarrow$ can just replace Γ_L by $(-\Gamma_L)$



$$|V_{\max}| = 1 + |\Gamma_L| \quad (\text{RH Real axis})$$

$$|V_{\min}| = 1 - |\Gamma_L| \quad (\text{LH Real axis})$$

$$\frac{|V(z)|}{|V^+|} = |1 + \Gamma_L e^{2jkz}|$$

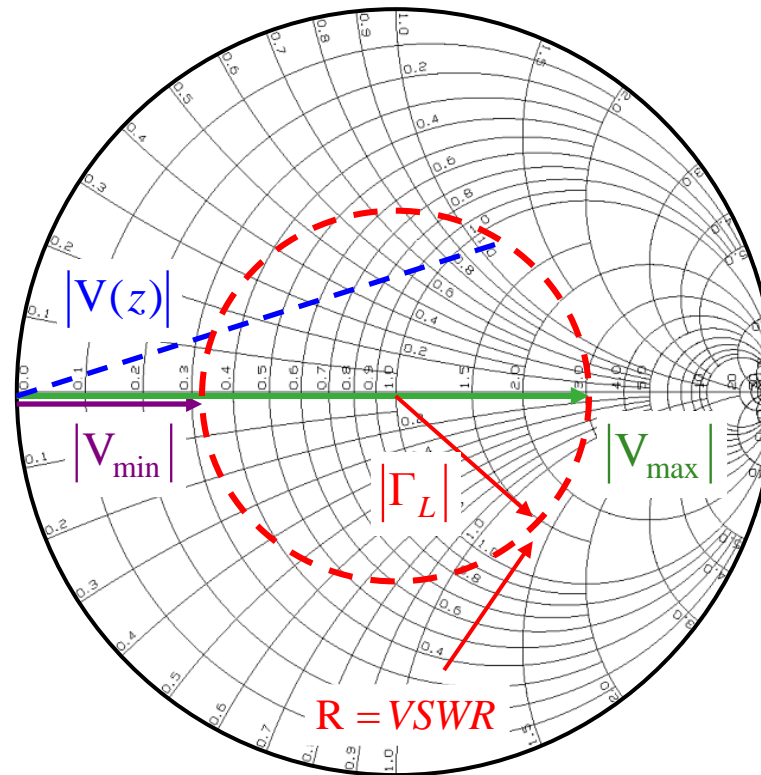

$$Z_{nL} = 1 + j2$$

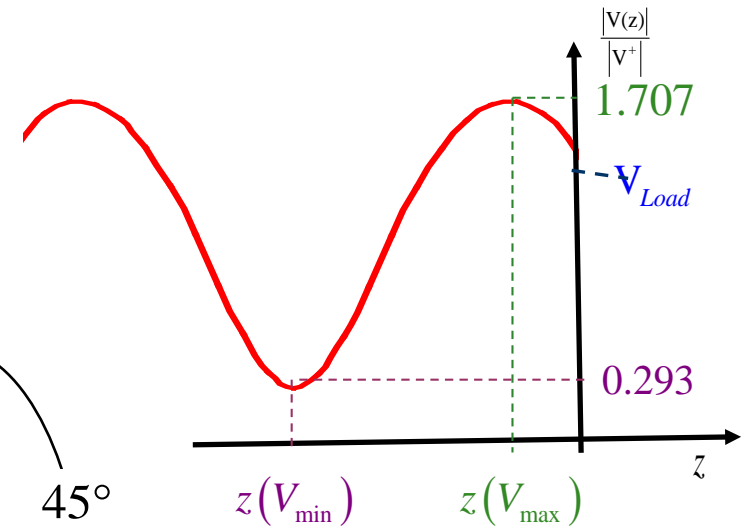
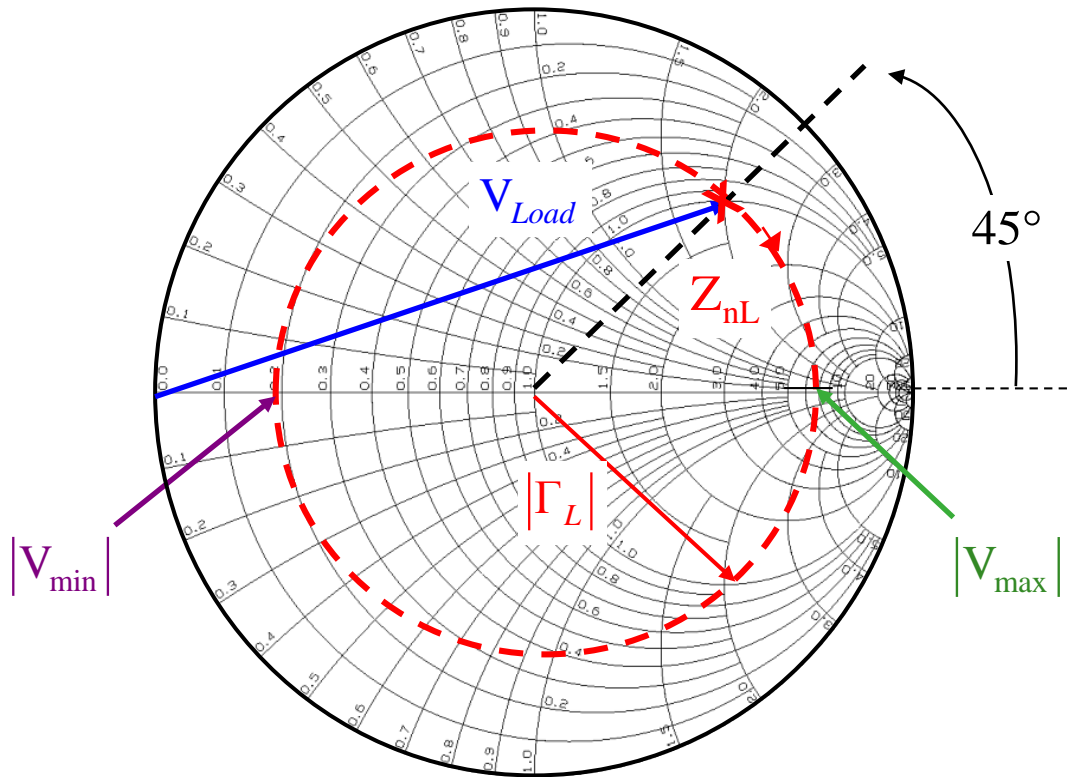


$$Z_{nL} = 1 + j2$$

$$\Gamma = .707 \angle 45^\circ$$



360° on Smith Chart = $\frac{\lambda}{2}$

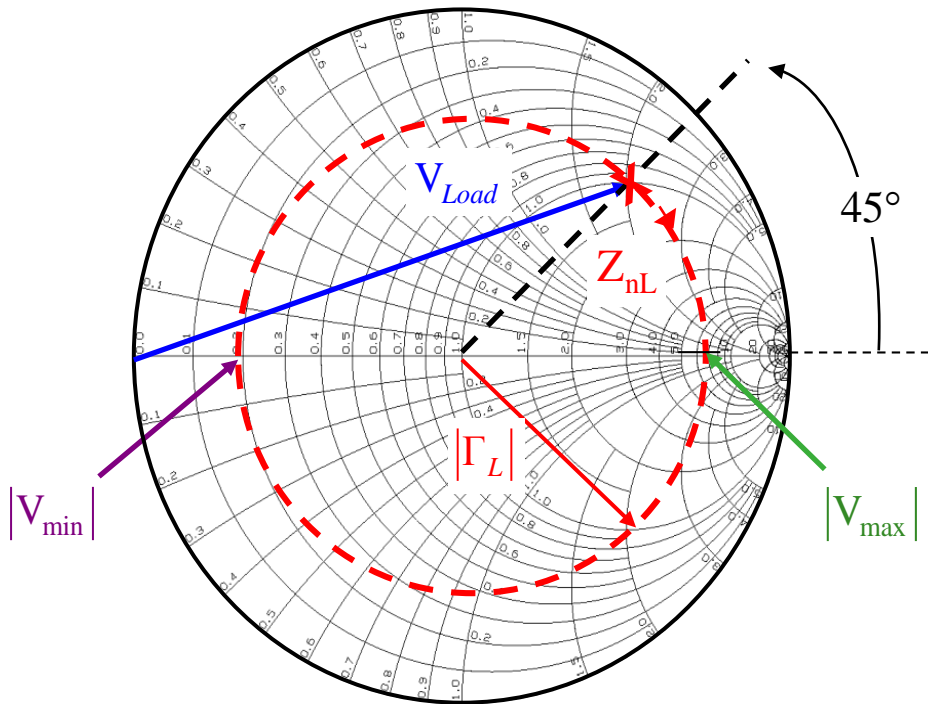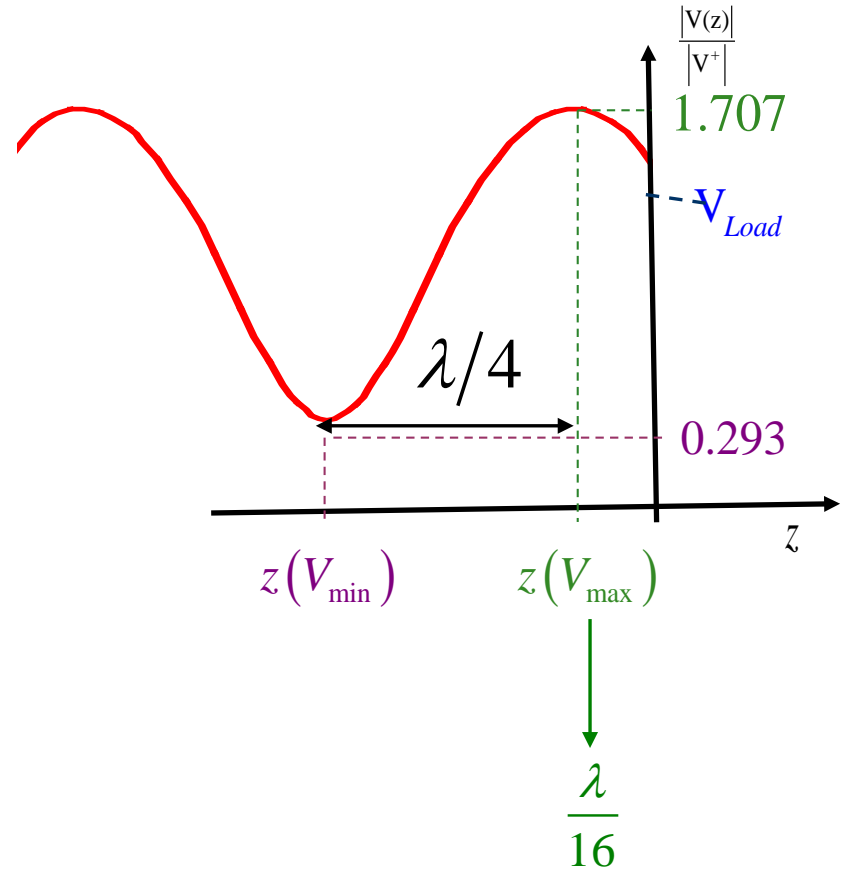180° on Smith Chart = $\frac{\lambda}{4}$




$$Z_{nL} = 1 + j2$$

$$\Gamma = .707 \angle 45^\circ$$

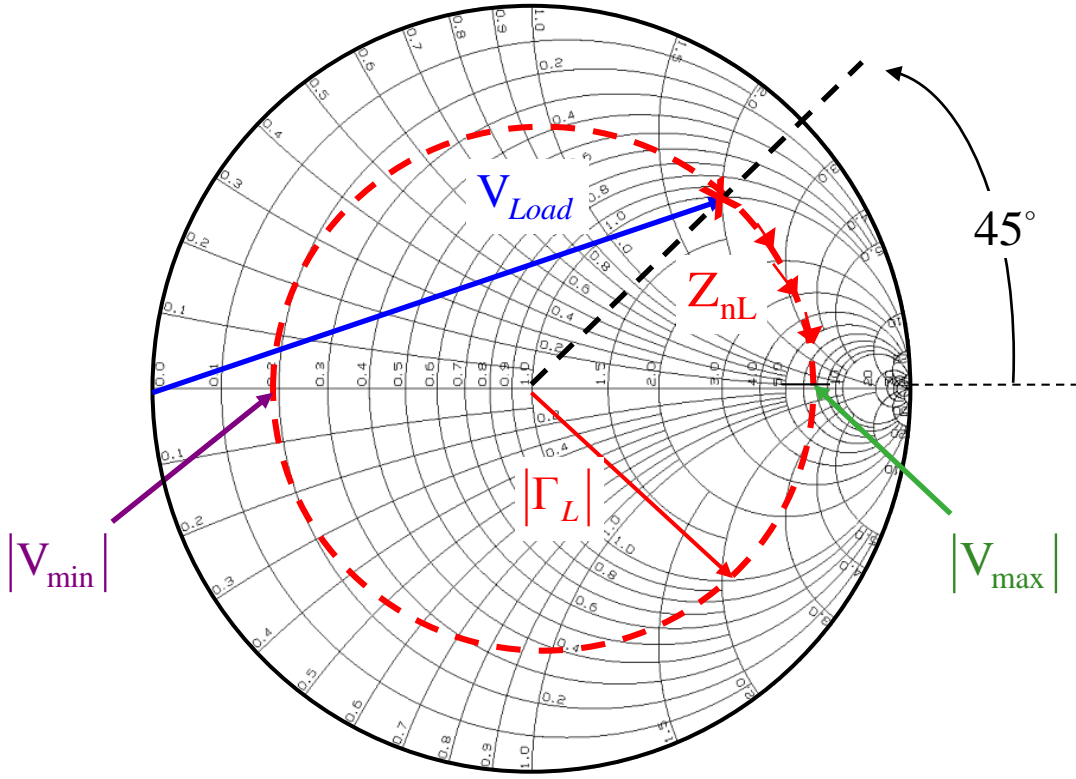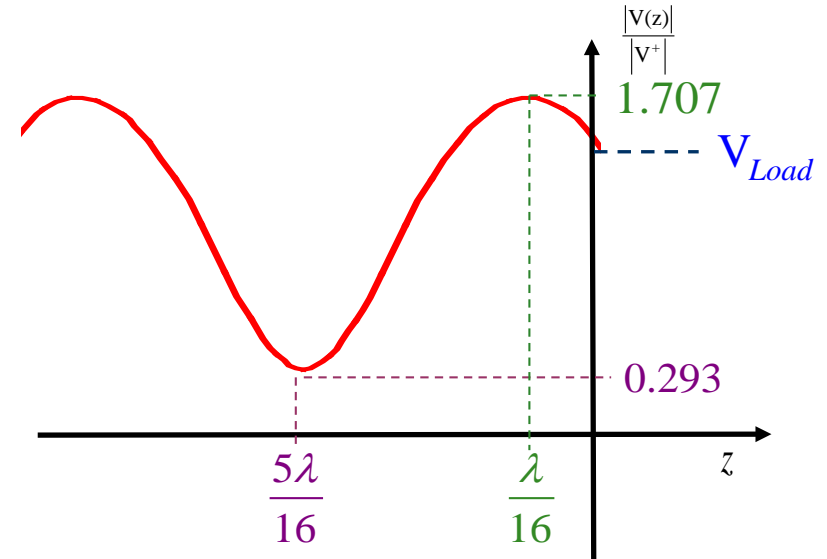

$$0.25\lambda - 0.1875\lambda = 0.0625\lambda$$
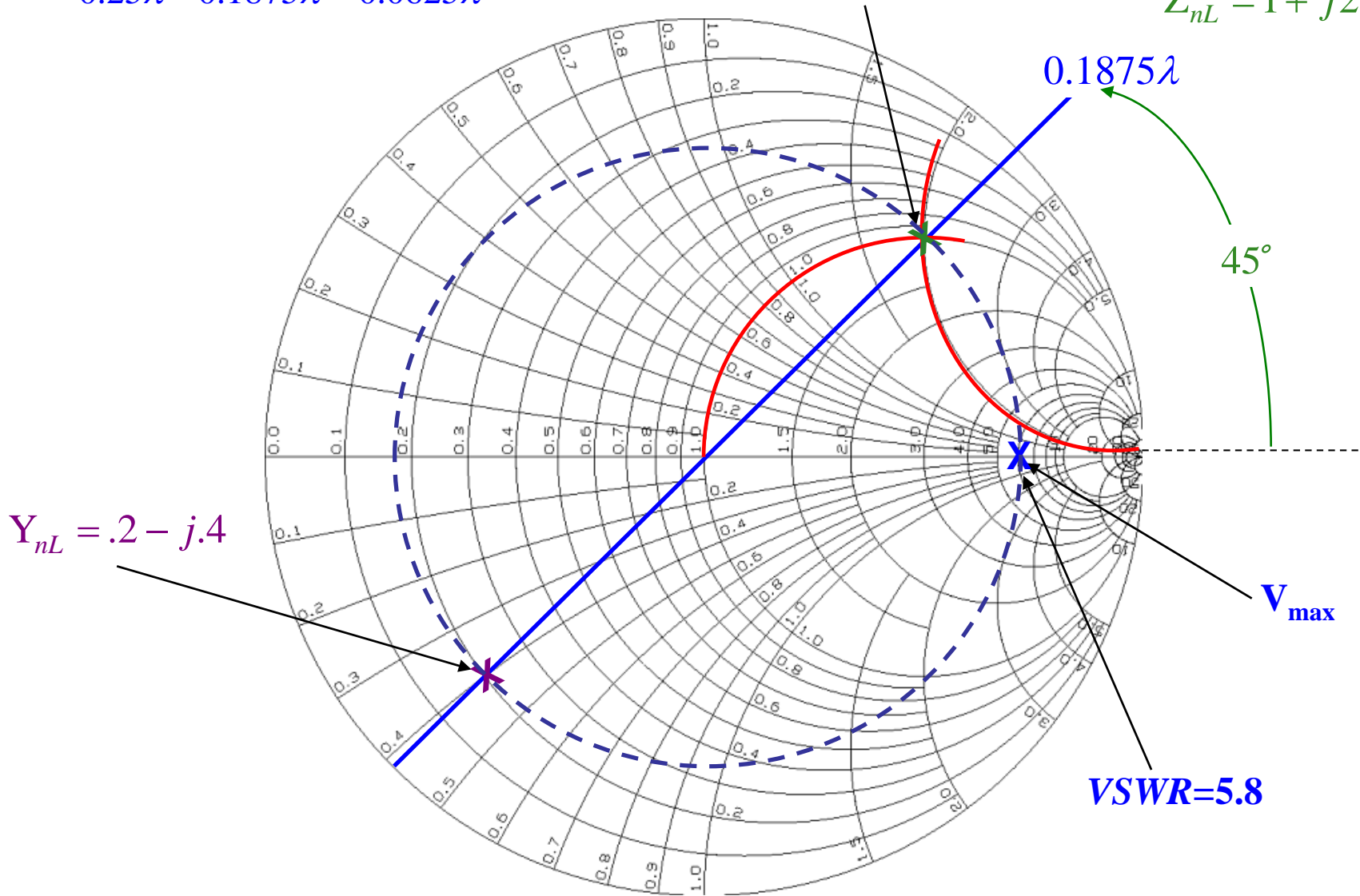
$$\Gamma_L = .707 \angle 45^\circ$$
$$Z_{nL} = 1 + j2$$



Usually want power to be absorbed by load (minimize $|\Gamma_L|^2$).

To do so one adds pure reactances (or susceptances) to tune or match the network.

$$Z = R + jX \quad [\Omega]$$

impedance = resistance + j reactance

$$Y = G + jB \quad [S]$$

admittance = conductance + j susceptance

Note: It is physically easier to add a shunt susceptance than series reactance.

Example: Given $Z_{nL} = 2 + j2 \Rightarrow \Gamma = 0.62 \angle 30^\circ$

$$|\Gamma|^2 = 0.62^2 = 38\% \text{ power reflected}$$

change from $Z_{nL} \Rightarrow Y_{nL} = G_{nL} + jB_{nL}$

$$Y_{nL} = \frac{1}{Z_{nL}} = \frac{1}{2 + j2} = 0.25 - j0.25$$

could add $+j.25$ at load

$$Y_{nL} = 0.25 \Rightarrow \Gamma = 0.6 \angle 0^\circ$$

$$|\Gamma|^2 = 0.6^2 = 36\% \text{ power reflected}$$

instead rotate toward generator to $1 + jB$ circle and add a $-jB$ there.

Smith Chart


Solution:

Add $+j1.57$ at 0.362λ


Or $-j1.57$ at 0.219λ


$$0.041\lambda + 0.178\lambda = 0.219\lambda$$
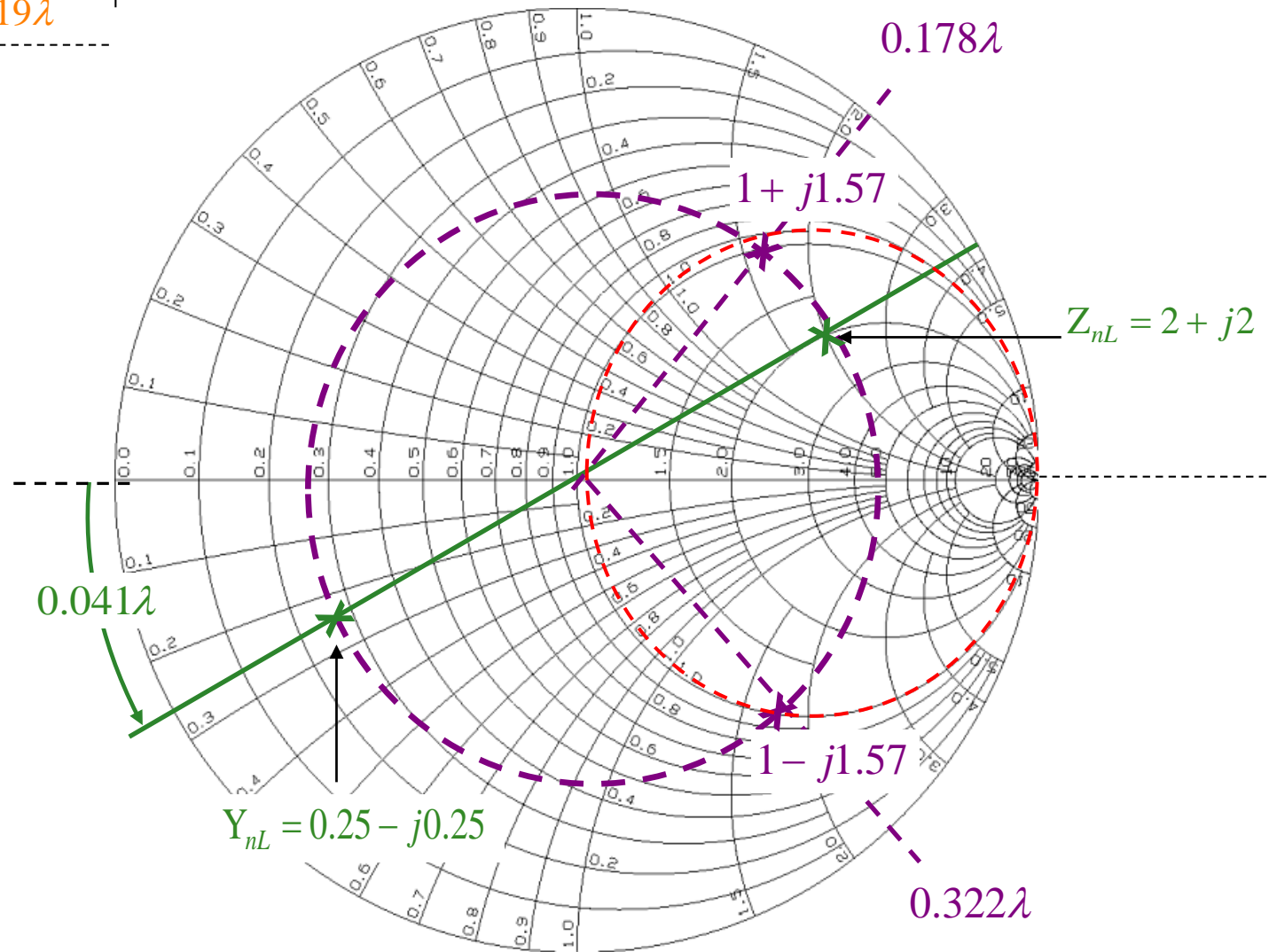
$$0.041\lambda + 0.322\lambda = 0.363\lambda$$


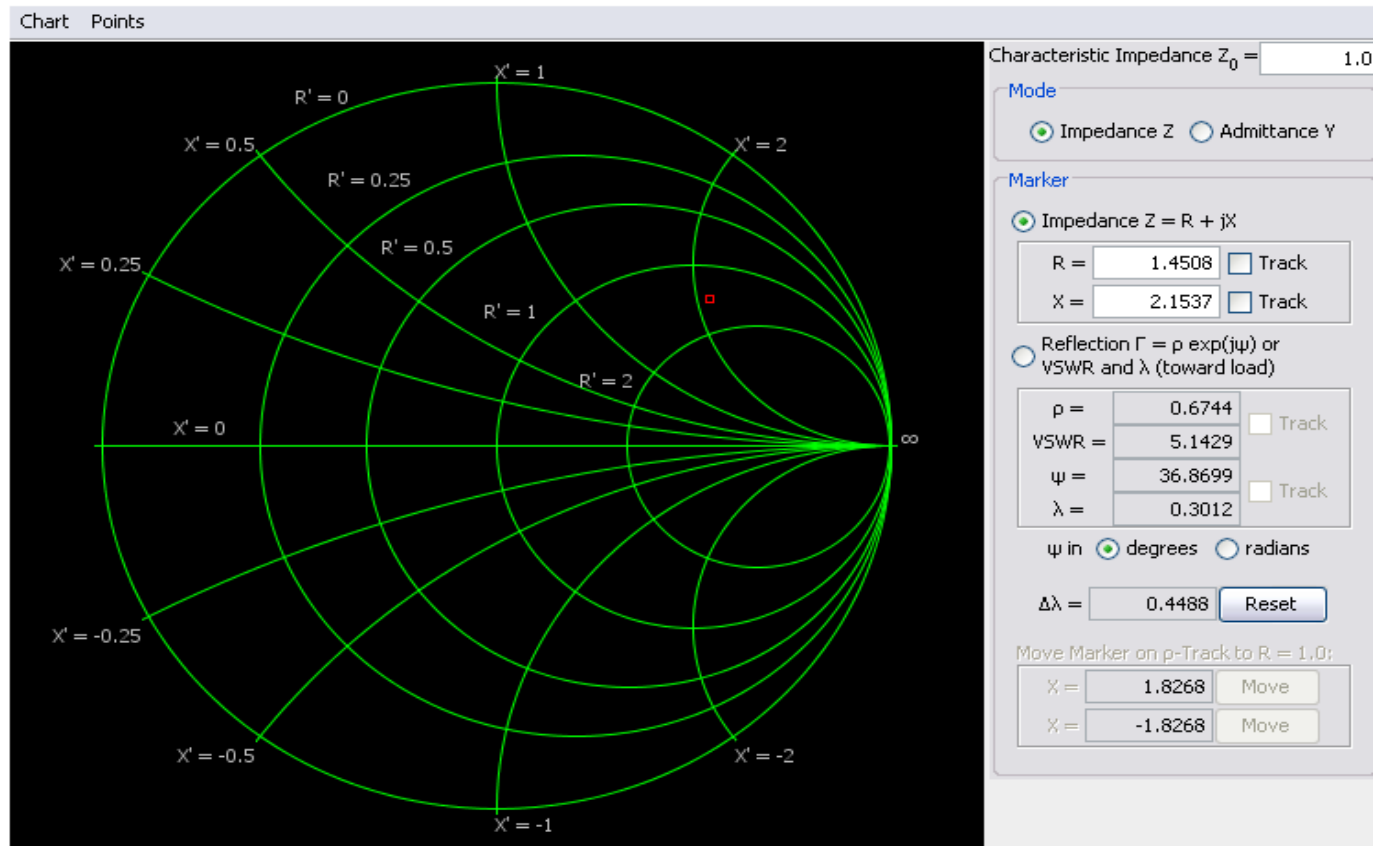
<http://www.ocf.berkeley.edu/~joydip/smithchart/index.html>



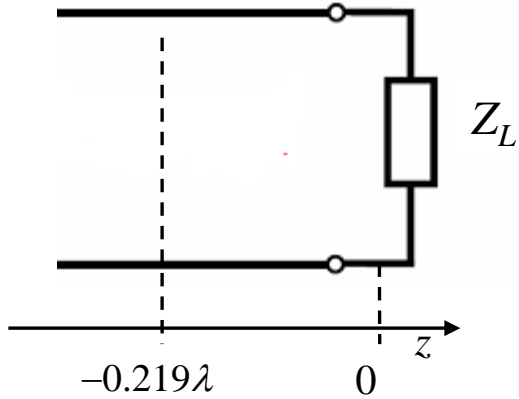


Voltages: Unmatched Line


$$V_{load} = V(0) = 1.55$$

$$V_{max} = 1.62$$

$$V_{min} = 0.38$$

$$V(-0.219\lambda) = 0.78$$

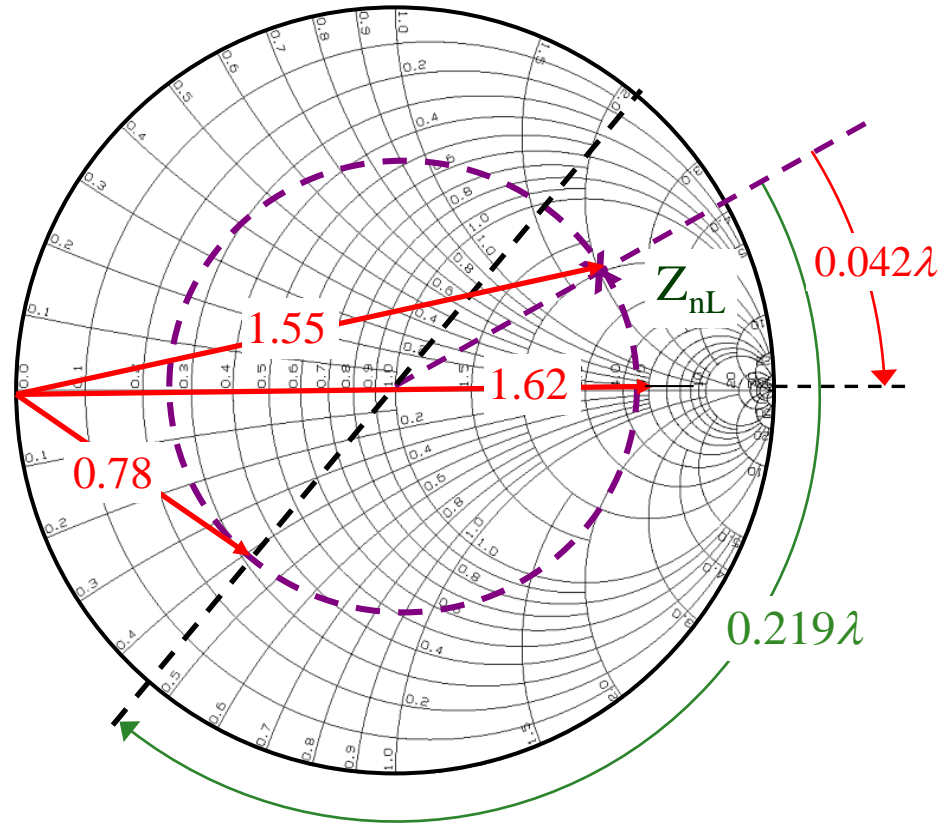

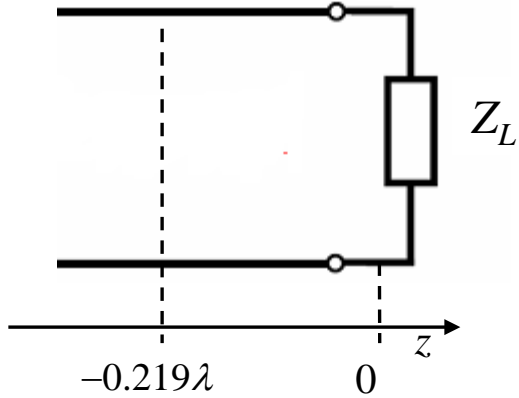


Currents: Unmatched Line


$$I_{load} = 0.55$$

$$I_{max} = 1.62$$

$$I_{min} = 0.38$$


$$I(-0.219\lambda) = 1.45$$

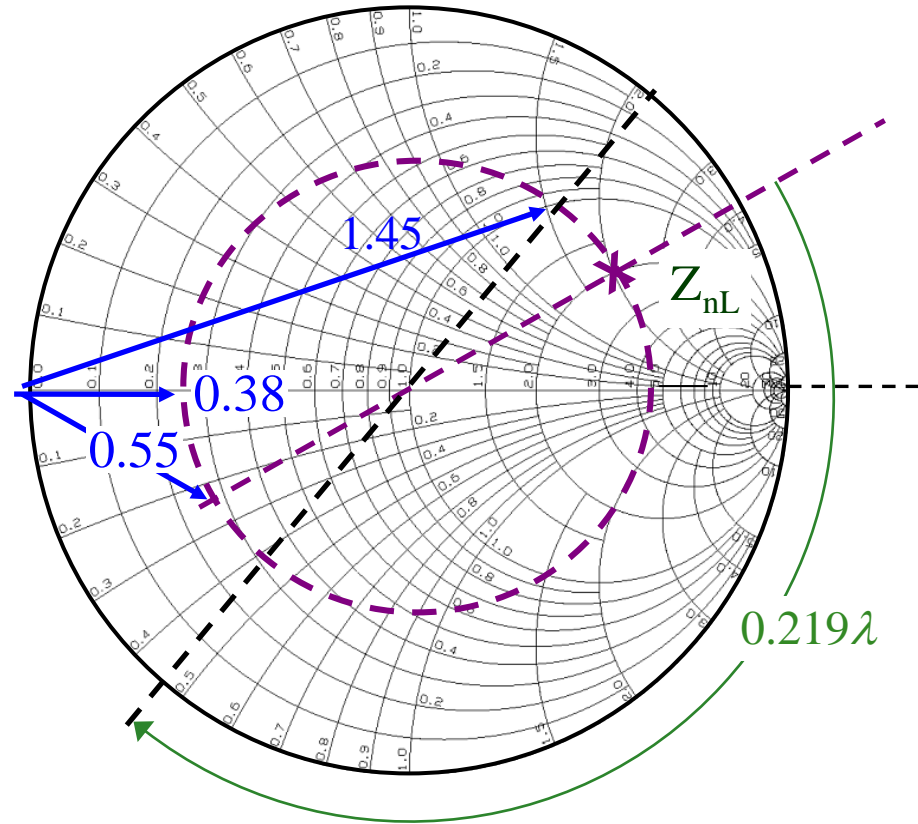

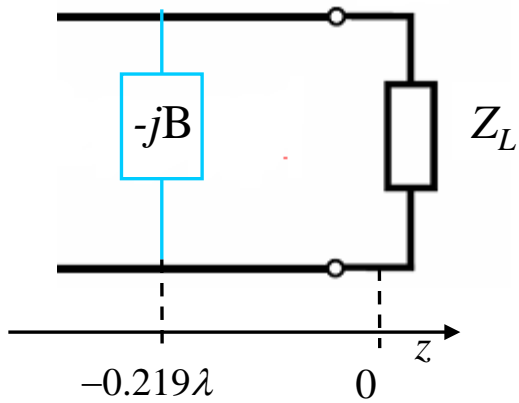



Voltages: Matched Line

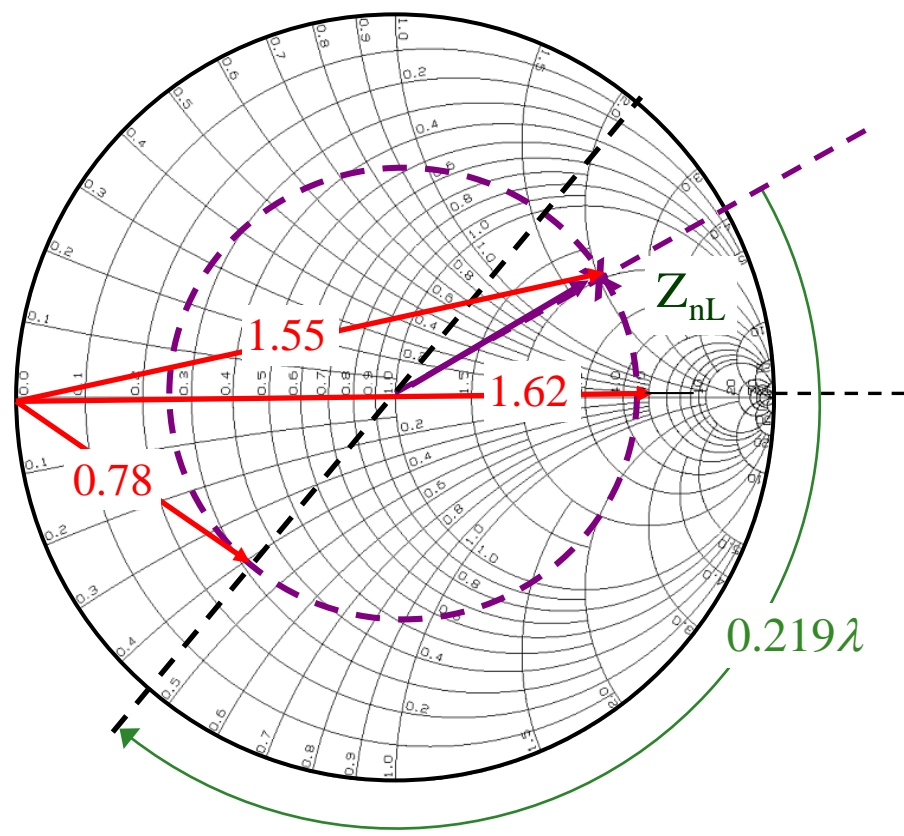- $V_{load} = 1.55$
- $V_{max} = 1.62$
- $V_{min} = 0.38$
- $V(-0.219\lambda) = 0.78$




Standing Wave Pattern

UNMATCHED

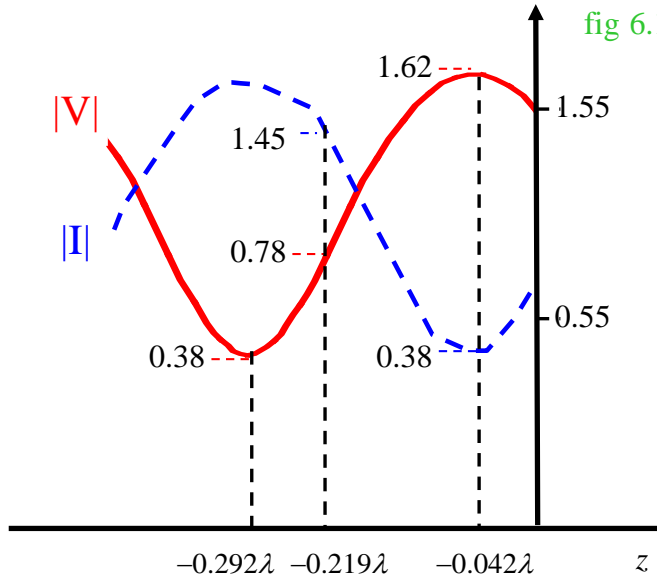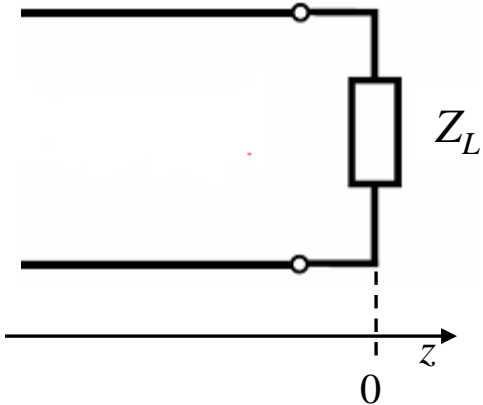

- $V_{load} = 1.55$
- $V_{max} = 1.62$
- $V_{min} = 0.38$
- $V(-0.219\lambda) = 0.78$
- $I_{load} = 0.55$
- $I_{max} = 1.55$
- $I_{min} = 0.38$
- $I(-0.219\lambda) = 1.45$

MATCHED

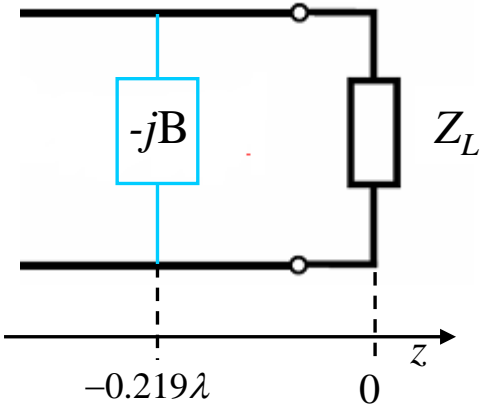


For tuned line


V,I between load and shunt are greater than those for unmatched line

by a factor of $\frac{1}{0.78}$

for the same incident power.

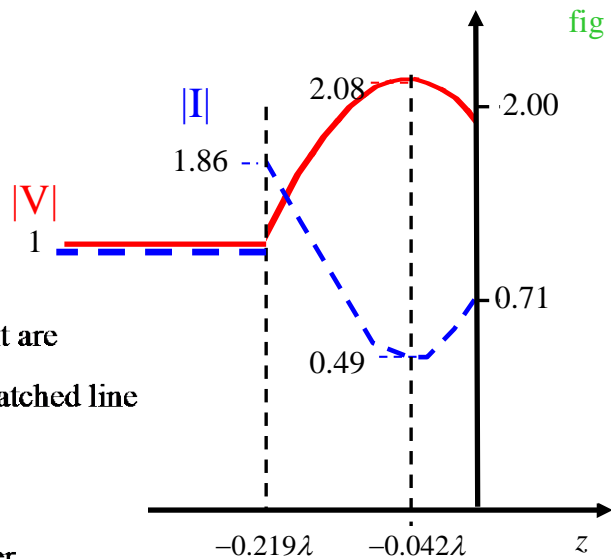

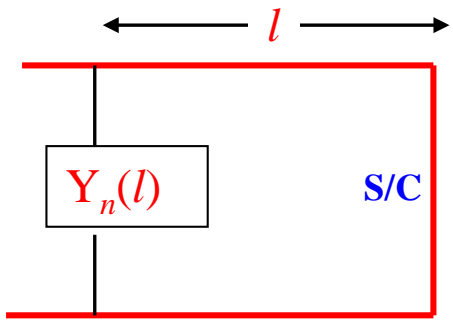For a transmission line \Rightarrow usually add a short circuit section of a line placed perpendicular to the main line.



$$Y_n(l) = -j \cot kl$$

6.36

for kl varying from 0 to π
 \Downarrow
 $0 \leq l \leq \frac{\lambda}{2}$

all possible values
 $-j\infty \leq jB \leq +j\infty$


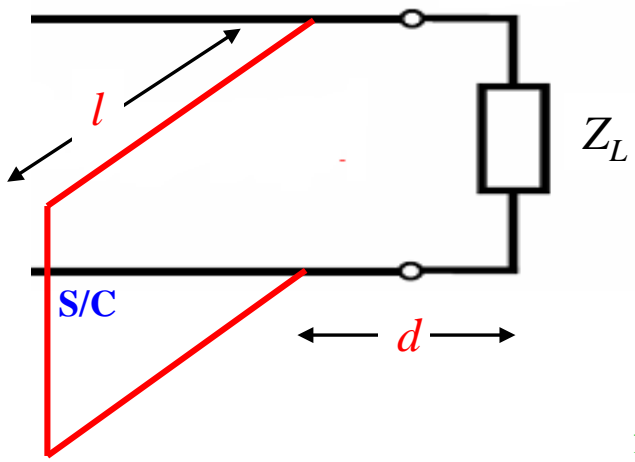



fig 6.20

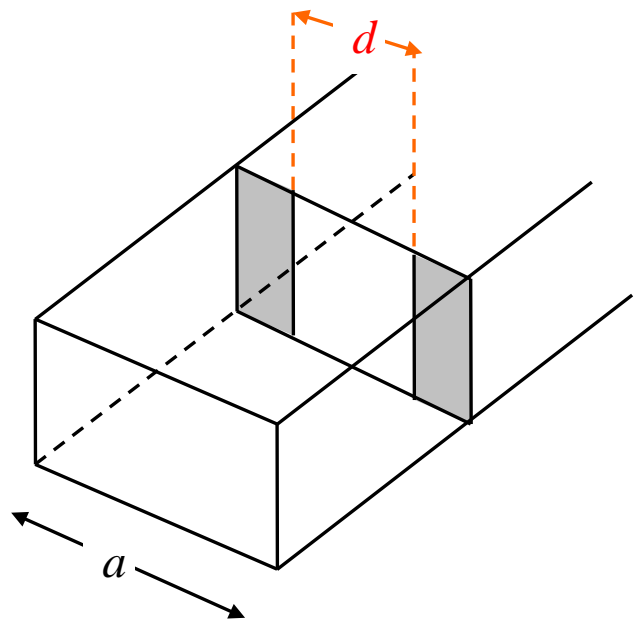For a rectangular waveguide \Rightarrow usually insert a metal iris inside the waveguide.



Inductive Iris

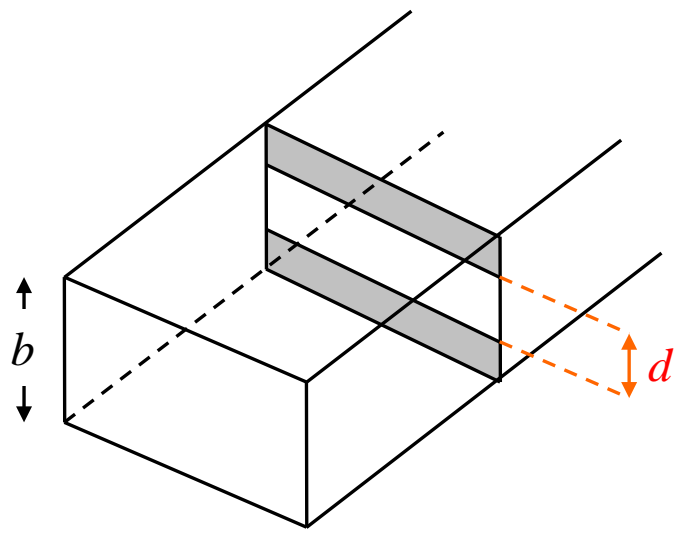
$$B_0 = \frac{-\lambda_g}{a} \cot^2 \left(\frac{\pi d}{2a} \right) \quad 6.37$$



Capacitive Iris

$$B_0 = \frac{4b}{\lambda_g} \ln \left[\csc \left(\frac{\pi d}{2b} \right) \right] \quad 6.38$$

Rotate clockwise from S/C to desired jB

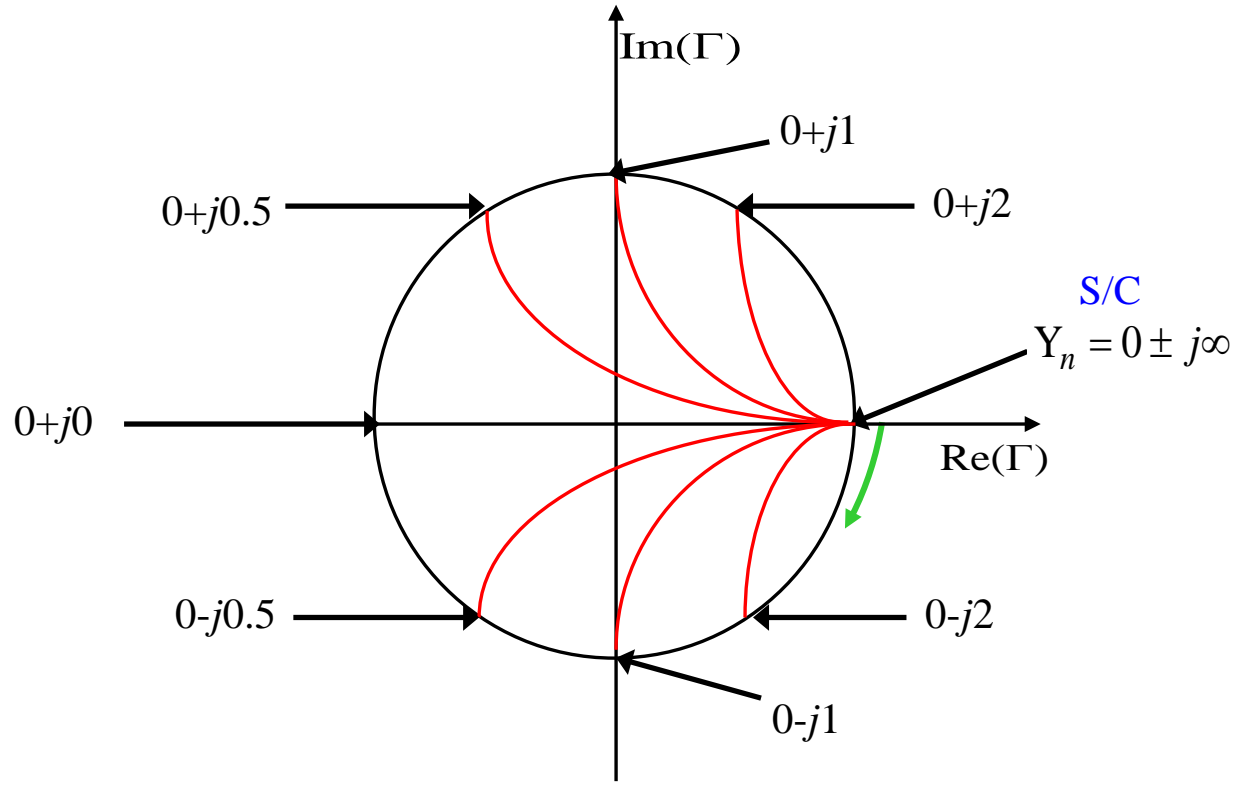

Example: To add

$$jB = -j1.57$$

analytically


$$Y_n = -j \cot kl$$

$$-j1.57 = -j \cot kl$$

$$\cot kl = 1.57 \quad ; \quad \tan kl = \frac{1}{1.57}$$

$$kl = \frac{2\pi}{\lambda} l = 0.567 \text{ [radians]}$$

$$l = 0.0903\lambda$$

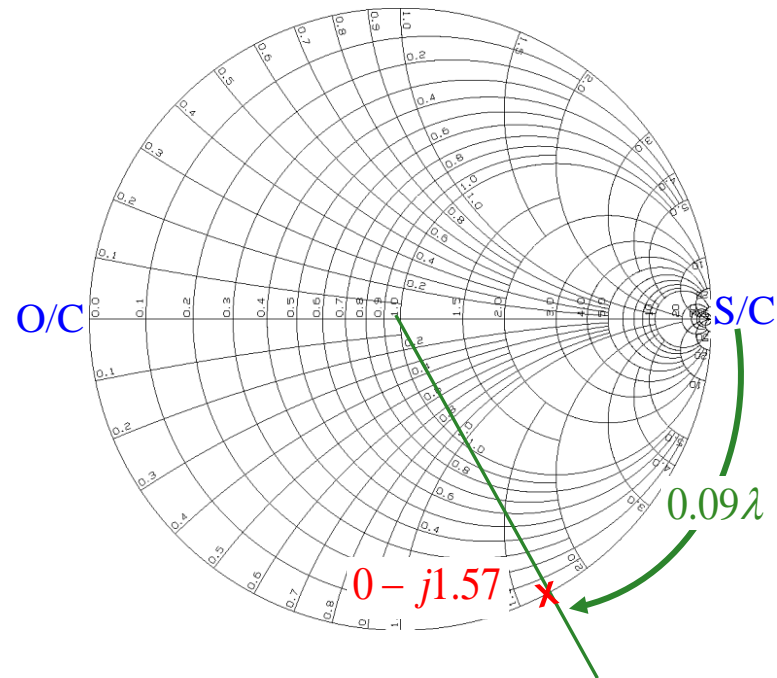

Example: Given $Z_{nL} = 0.5 - j2$ find everything

Smith chart

Analytically

$$\Gamma = 0.82 \angle -51^\circ$$

$$\Gamma = 0.8246 \angle -50.9^\circ$$

$$Y_n = 0.12 + j0.47$$

$$Y_n = 0.1176 + j0.4706$$

$$SWR = 10.5$$

$$SWR = 10.46$$

$$d_1 = 0.131\lambda$$

$$d_1 = 0.1315\lambda$$

$$B_1 = -2.9$$

$$B_1 = -2.915$$


$$l_1 = 0.053\lambda$$

$$l_1 = 0.0526\lambda$$

$$d_2 = 0.227\lambda$$

$$B_2 = +2.9$$

$$l_2 = 0.447\lambda$$

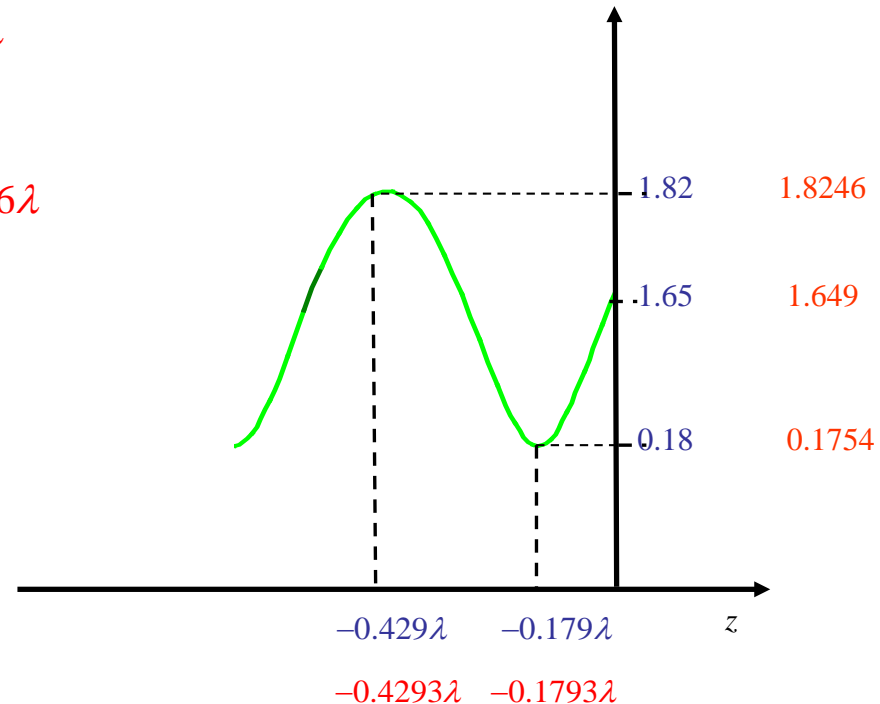


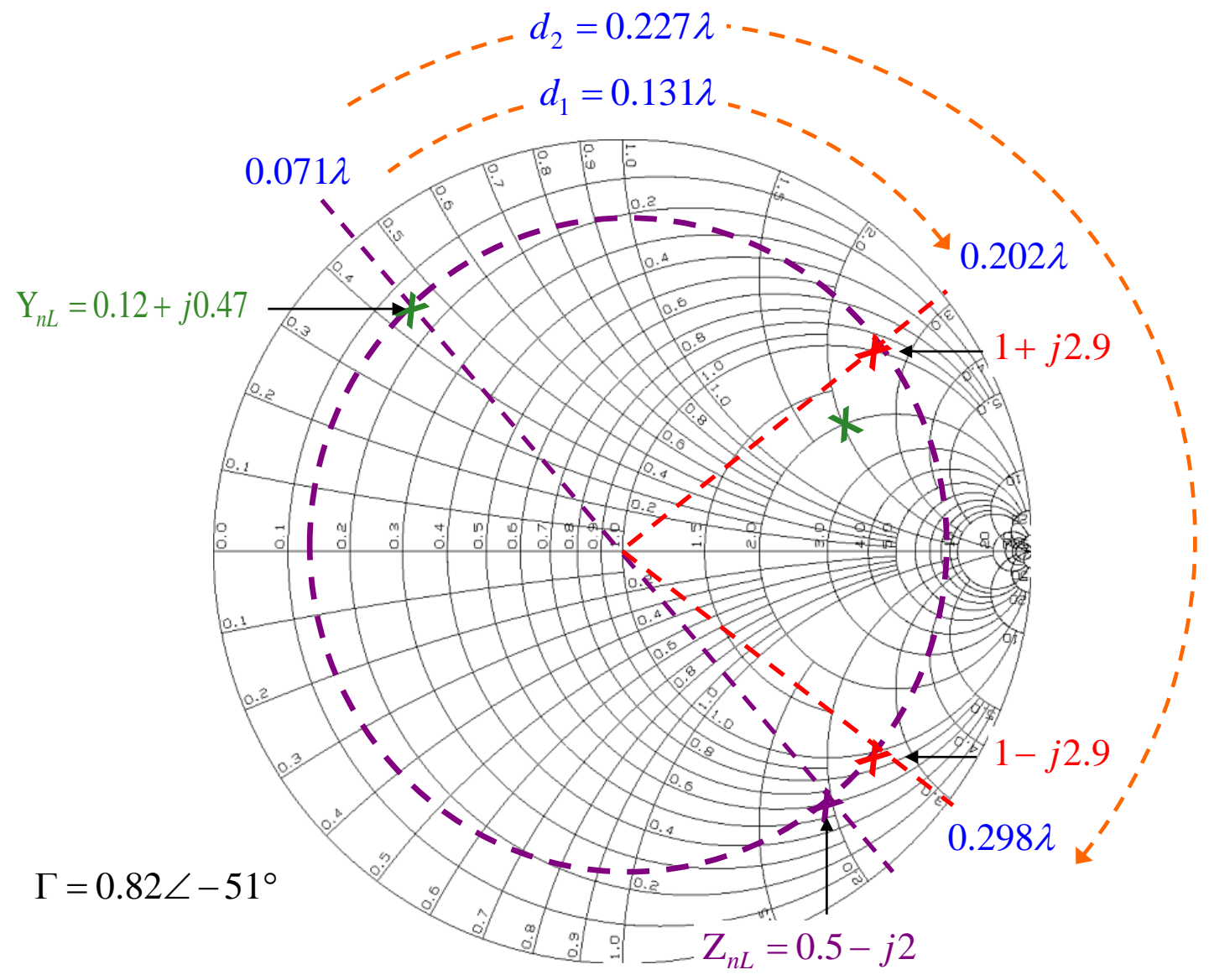


fig 6.18

$$l_1 = (0.303 - 0.25)\lambda$$
$$l_1 = 0.053\lambda$$

Note:
 $l_1 + l_2 = 0.5\lambda$

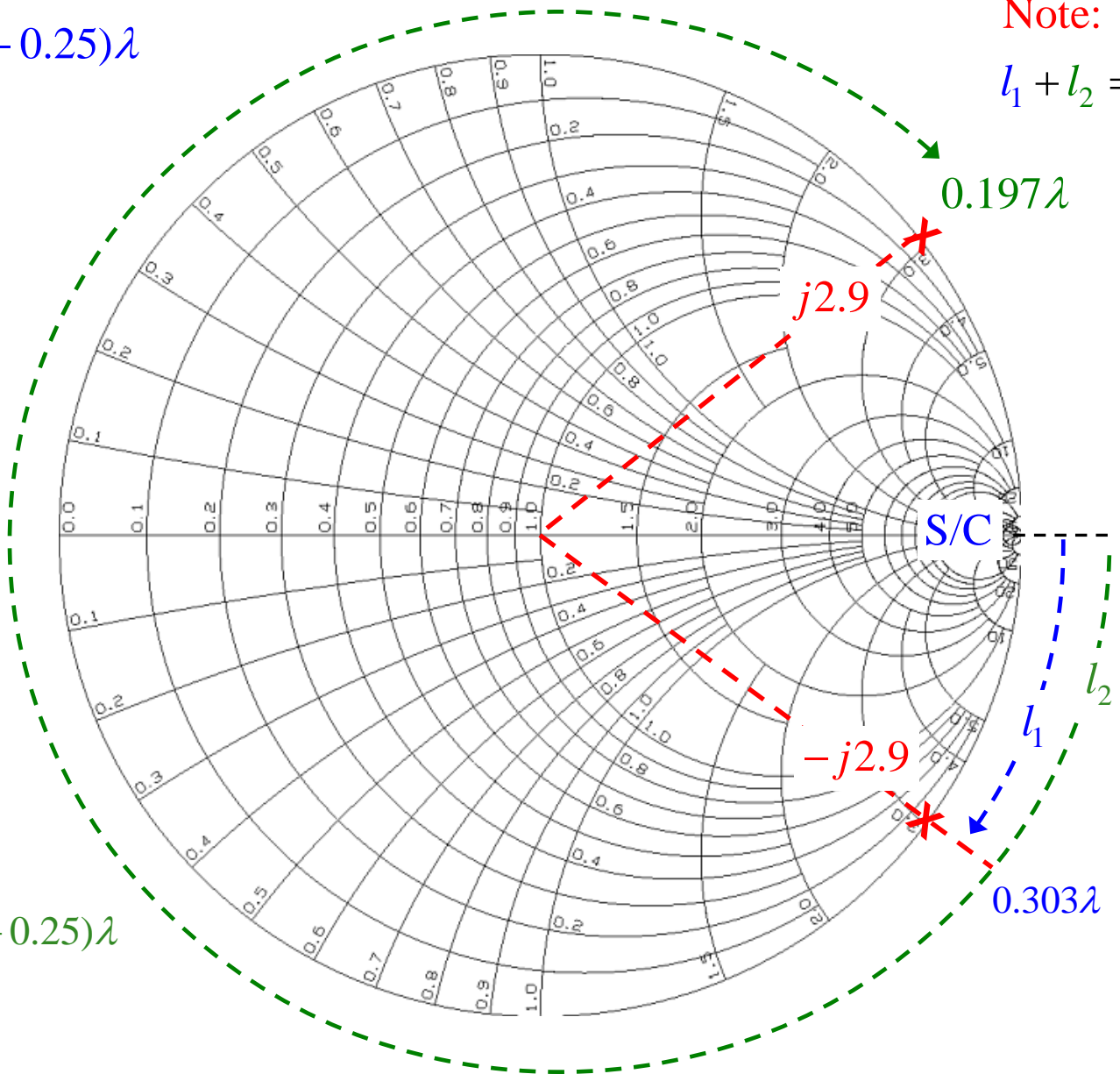

$$l_2 = (0.197 + 0.25)\lambda$$
$$l_2 = 0.447\lambda$$