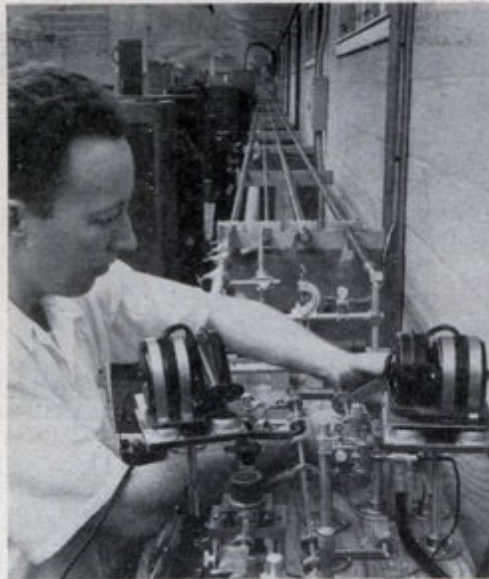


Chapter 6 Transmission Lines

ECE 3317
Dr. Stuart A. Long



Popular Mechanics, 1955



Bell scientist checks test equipment used to bounce microwaves back and forth for 40 miles in metal tubes



The flexibility of the coiled-wire tubing permits it to be laid over long distances and rough terrain

Long-Distance Microwave Pipe Carries Many Television Programs

Tens of thousands of cross-country telephone calls along with hundreds of television programs may someday be carried in a single two-inch metal tube. The long-distance wave guide, developed by Bell, could be buried underground and would funnel extremely short microwaves up hill, down dale and around corners. It is constructed of thin copper wire, tightly

coiled like a spring under pressure and wrapped inside a flexible outer coating which holds the wire in place. In laboratory tests, microwaves have been carried for 40 miles in a metal tube with the same loss of strength encountered when the waves travel 12 miles in a coaxial cable. The system uses microwaves shorter than any previously used in communications.

p.133

Voltage

$$V(z) = \alpha_1 \int_{C_t} \mathbf{E} \cdot d\mathbf{s} \quad (C_t \perp z) \quad (a)$$

Current

$$I(z) = \alpha_2 \oint_{C_0} \mathbf{H} \cdot d\mathbf{s} \quad (C_0 \text{ closed}) \quad (b)$$

p.133

Power

$$\frac{1}{2} \operatorname{Re} [V(z) I^*(z)] = \int_A \frac{1}{2} \operatorname{Re} [\mathbf{E} \times \mathbf{H}^*] \cdot \hat{\mathbf{z}} \, dA \quad (c)$$

Characteristic
Impedance

$$Z_0 = \frac{V(z)}{I(z)}$$

infinite line with
with no reflection

Parallel Plate Waveguide (TEM mode)

6-5

The Transverse Electromagnetic Fields in a Parallel Plate Waveguide are approximately as follows:


$$\mathbf{E} = \hat{\mathbf{x}} E_0 e^{-jkz} \quad 6.1a$$

$$\mathbf{H} = \hat{\mathbf{y}} \frac{E_0}{\eta} e^{-jkz} \quad 6.1b$$

Using the
General
Definitions

$$V(z) = \alpha_1 \int_0^d \mathbf{E} \cdot \hat{\mathbf{x}} dx = \alpha_1 E_0 d e^{-jkz} \quad 6.2a$$
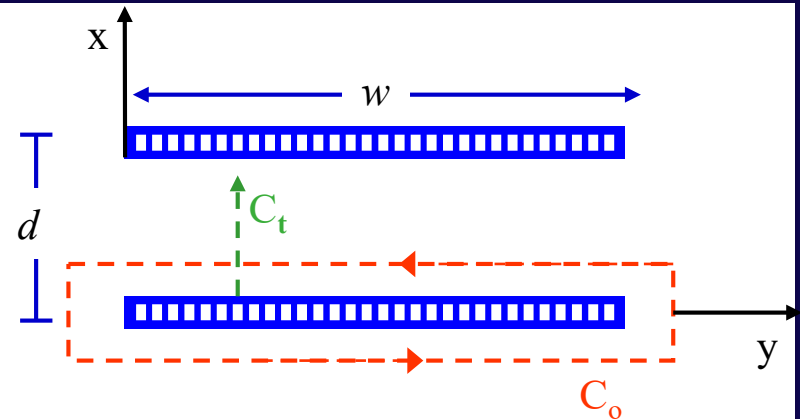
$$I(z) = \alpha_2 \int_0^w \mathbf{H} \cdot \hat{\mathbf{y}} dy = \alpha_2 \frac{E_0 w}{\eta} e^{-jkz} \quad 6.2b$$



Parallel Plate Waveguide (TEM mode)

6-6

The time-average power transmitted
is given by

$$P_t = \int_A \frac{E_0^2}{2\eta} \hat{z} \square \hat{z} dA = \frac{E_0^2}{2\eta} wd$$


equate

$$\frac{1}{2} \operatorname{Re} \left[V(z) I(z)^* \right] = \frac{E_0^2}{2\eta} wd$$

$$\frac{1}{2} (\alpha_1 E_0 d) \left(\alpha_2 \frac{E_0}{\eta} w \right) = \frac{E_0^2}{2\eta} wd$$

$$\alpha_1 \alpha_2 \frac{E_0^2}{2\eta} wd = \frac{E_0^2}{2\eta} wd \Rightarrow \alpha_1 \alpha_2 = 1$$

choose $\alpha_1 = 1$ and $\alpha_2 = 1$

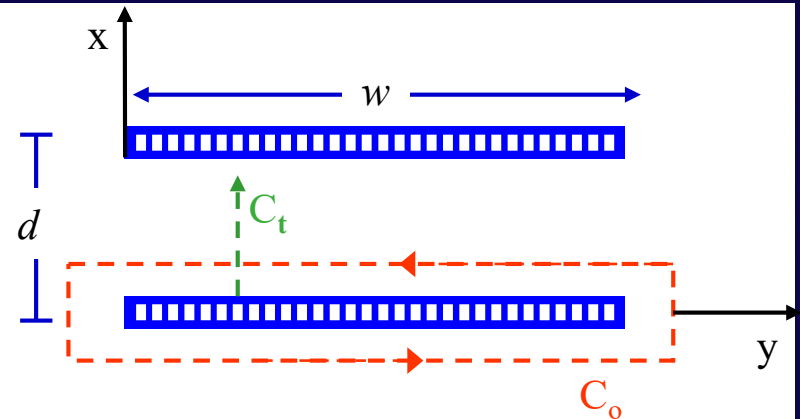


Parallel Plate Waveguide (TEM mode)

6-7

$$V(z) = E_0 d e^{-jkz} \quad 6.3a$$

$$I(z) = \frac{E_0 w}{\eta} e^{-jkz} \quad 6.3b$$
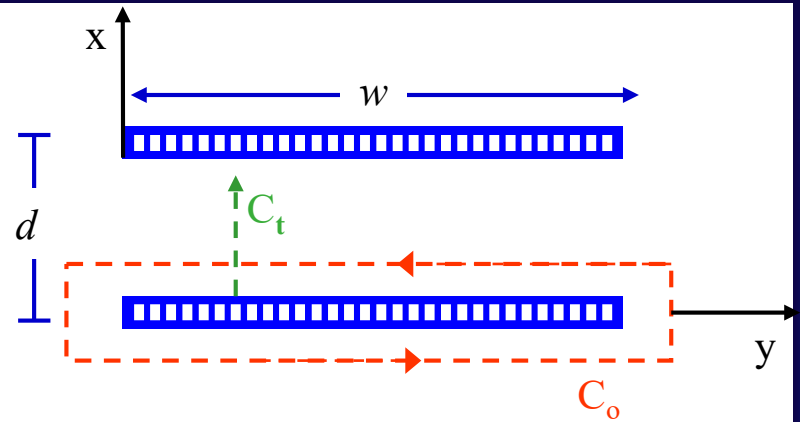
$$Z_0 = \eta \frac{d}{w} \quad [\Omega] \quad 6.4$$




Coaxial Line

The fields inside a coaxial line for the TEM mode are given by

$$\mathbf{E} = \hat{\rho} \frac{V_0}{\rho} e^{-jkz} \quad 6.5a$$
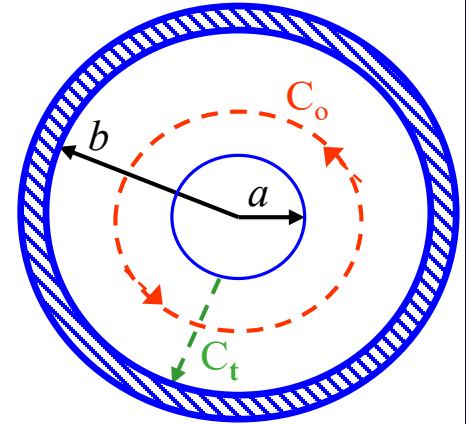
$$\mathbf{H} = \hat{\phi} \frac{V_0}{\eta\rho} e^{-jkz} \quad 6.5b$$



Using the
General
Definitions

$$V(z) = \alpha_1 \int_a^b \mathbf{E} \cdot \hat{\rho} d\rho = \alpha_1 V_0 \ln \frac{b}{a} e^{-jkz} \quad 6.6a$$

$$I(z) = \alpha_2 \oint \mathbf{H} \cdot \hat{\phi} \rho d\phi = \alpha_2 \frac{2\pi V_0}{\eta} e^{-jkz} \quad 6.6b$$

The time-average power transmitted is given by

$$P_t = \frac{\pi V_0^2}{\eta} \ln \frac{b}{a}$$


equate

$$\frac{1}{2} \operatorname{Re} \left[V(z) I(z)^* \right] = \frac{\pi V_0^2}{\eta} \ln \frac{b}{a}$$

$$\frac{1}{2} \left(\alpha_1 V_0 \ln \frac{b}{a} \right) \left(\alpha_2 \frac{2\pi V_0}{\eta} \right) = \frac{\pi V_0^2}{\eta} \ln \frac{b}{a}$$

$$\alpha_1 \alpha_2 \frac{\pi V_0^2}{\eta} \ln \frac{b}{a} = \frac{\pi V_0^2}{\eta} \ln \frac{b}{a} \Rightarrow \alpha_1 \alpha_2 = 1$$

choose $\alpha_1 = 1$ and $\alpha_2 = 1$

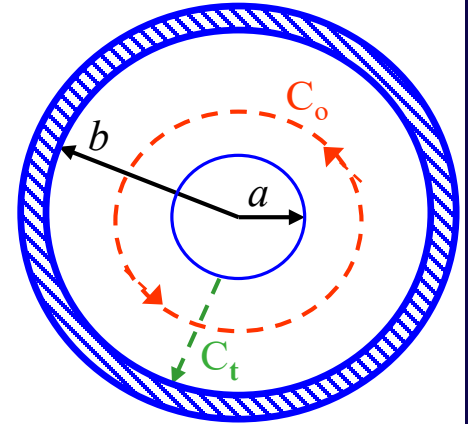


$$V(z) = V_0 \ln \frac{b}{a} e^{-jkz}$$

$$I(z) = \frac{2\pi V_0}{\eta} e^{-jkz}$$

$$Z_0 = \frac{\eta}{2\pi} \ln \frac{b}{a} \quad [\Omega]$$

6.7

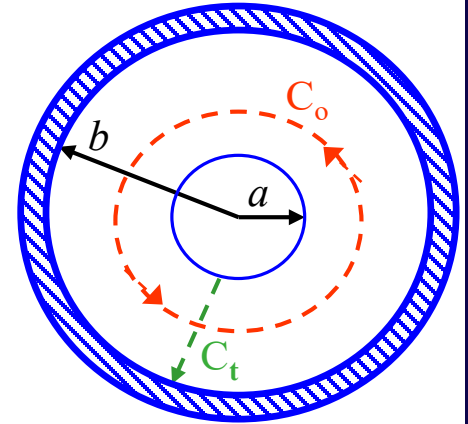

Example: What is the ratio b/a for
an air-filled coax and $50[\Omega]$ line?

$$50 = \frac{377}{2\pi} \ln(b/a)$$

$$\Rightarrow \frac{b}{a} = 2.3$$

Rectangular Waveguide (Dominant TE₁₀ mode)


6-11

The Electromagnetic fields in a Rectangular Waveguide for the are TE₁₀ mode are

$$E_y = E_0 \sin\left(\frac{\pi x}{a}\right) e^{-jk_z z} \quad 6.8a$$

$$H_x = -\frac{k_z}{\omega\mu} E_0 \sin\left(\frac{\pi x}{a}\right) e^{-jk_z z} \quad 6.8b$$

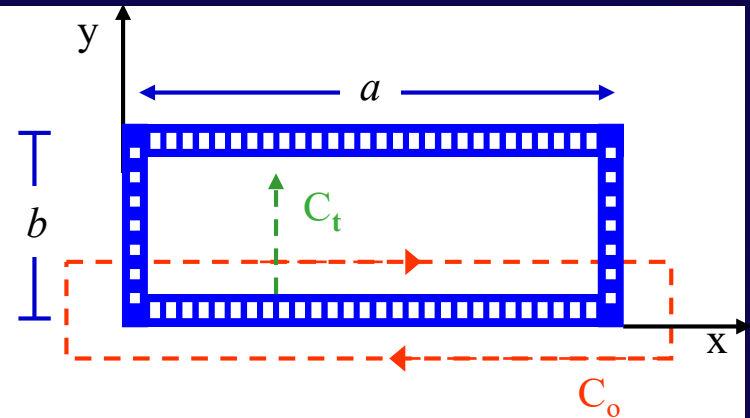
$$H_z = j \frac{\pi/a}{\omega\mu} E_0 \cos\left(\frac{\pi x}{a}\right) e^{-jk_z z} \quad 6.8c$$



Rectangular Waveguide (Dominant TE_{10} mode)

6-12

Using the
General
Definitions

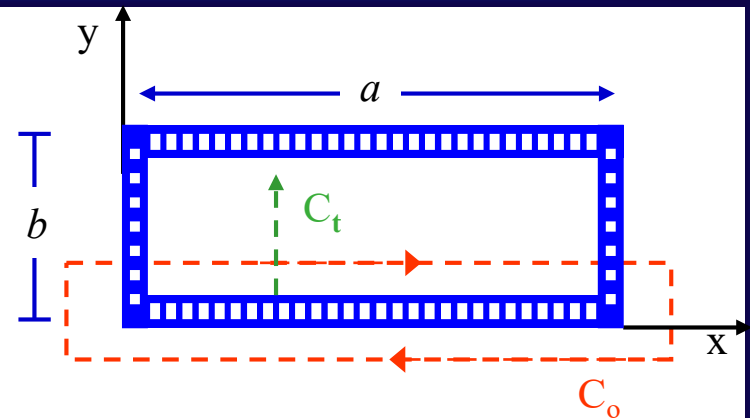

$$\begin{aligned} V(z) &= \alpha_1 \int_0^b E_y \Big|_{x=a/2} dy \\ &= \alpha_1 E_0 b e^{-jk_z z} \end{aligned}$$

6.9a

$$\begin{aligned} I(z) &= \alpha_2 \oint_{C_0} \hat{x} \cdot \mathbf{H} dx \\ &= \alpha_2 \frac{2E_0 a k_z}{\pi \omega \mu} e^{-jk_z z} \end{aligned}$$


6.9b

Rectangular Waveguide (Dominant TE_{10} mode)

6-13

The time-average power transmitted
is given by
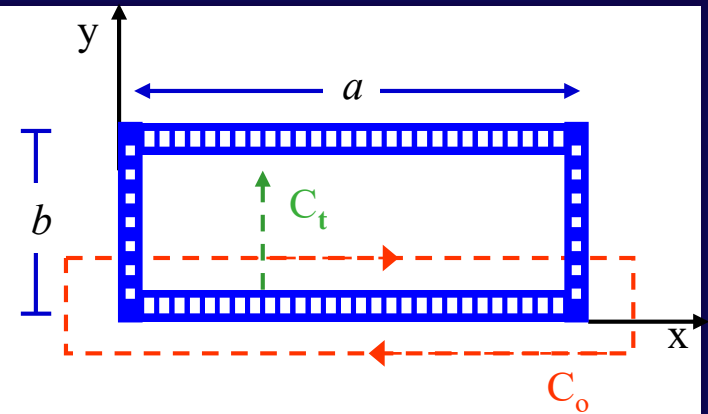
$$P_t = \frac{ab}{4} \frac{k_z}{\omega\mu} E_0^2$$



equate

$$\frac{1}{2} \operatorname{Re} \left[V(z) I(z)^* \right] = \frac{ab}{4} \frac{k_z}{\omega\mu} E_0^2$$

$$\frac{1}{2} (\alpha_1 E_0 b) \left(\alpha_2 \frac{2E_0 a k_z}{\pi \omega\mu} \right) = \frac{ab}{4} \frac{k_z}{\omega\mu} E_0^2$$

$$\alpha_1 \alpha_2 \frac{ab}{\pi} \frac{k_z}{\omega\mu} E_0^2 = \frac{ab}{4} \frac{k_z}{\omega\mu} E_0^2 \Rightarrow \alpha_1 \alpha_2 = \frac{\pi}{4}$$

$$\text{choose } \alpha_1 = \sqrt{\frac{ak_z}{2b\omega\mu}} \text{ and } \alpha_2 = \sqrt{\frac{\pi^2 b\omega\mu}{8ak_z}} \Rightarrow Z_0 = 1$$



Rectangular Waveguide (Dominant TE_{10} mode)

6-14

$$V(z) = \sqrt{\frac{ak_z}{2b\omega\mu}} E_0 b e^{-jk_z z}$$

$$I(z) = \sqrt{\frac{\pi^2 b\omega\mu}{8ak_z}} \frac{2E_0 ak_z}{\pi\omega\mu} e^{-jk_z z}$$

$$Z_0 = 1 \text{ } [\Omega]$$

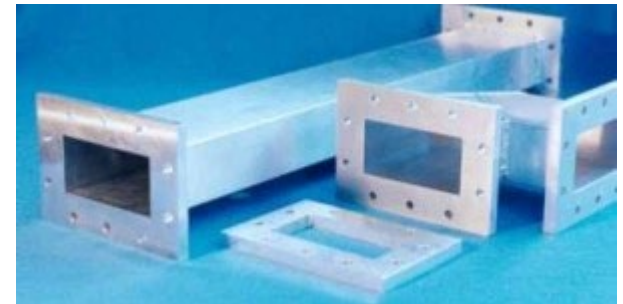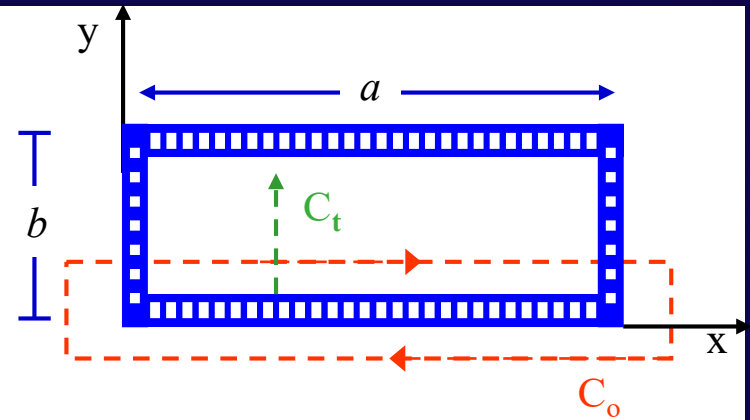

(Parallel plate waveguide)

$$\nabla \times \mathbf{E} = -j\omega\mu\mathbf{H}$$

$$\frac{\partial}{\partial z} E_x = -j\omega\mu H_y$$

$$V(z) = E_0 d e^{-jkz} = d E_x$$

$$\frac{\partial V}{\partial z} = -j\omega L I$$

$$L = \frac{\mu d}{w} \left[\frac{\text{H}}{\text{m}} \right]$$

$$\nabla \times \mathbf{H} = j\omega\varepsilon\mathbf{E}$$

$$-\frac{\partial}{\partial z} H_y = j\omega\varepsilon E_x$$

$$I(z) = \frac{E_0 w}{\eta} e^{-jkz} = w H_y$$

$$\frac{\partial I}{\partial z} = -j\omega C V$$

$$C = \frac{\varepsilon w}{d} \left[\frac{\text{F}}{\text{m}} \right]$$

(Parallel plate waveguide)

$$\frac{\partial^2 V}{\partial z^2} + \omega^2 LC V = 0 \quad \text{wave equation} \quad 6.15$$

$$V = V_+ e^{-jkz} + V_- e^{+jkz} \quad 6.16$$

$$I = \frac{1}{Z_0} \left[V_+ e^{-jkz} + V_- e^{+jkz} \right] \quad 6.17$$

$$k = \omega \sqrt{LC}$$

$$Z_0 = \sqrt{\frac{L}{C}} \quad 6.18$$

$$V(z) = V^+ e^{-jkz} + V^- e^{+jkz} \quad 6.22$$

$$I(z) = \frac{V^+}{Z_0} e^{-jkz} - \frac{V^-}{Z_0} e^{+jkz} \quad 6.23$$

Impedance $Z(z) = \frac{V(z)}{I(z)}$

$$Z_n(z) = \frac{Z(z)}{Z_0} = \frac{V^+ e^{-jkz} + V^- e^{+jkz}}{V^+ e^{-jkz} - V^- e^{+jkz}} \quad 6.24$$


(note $Z(0) = Z_L$)

Reflection coefficient

$$\Gamma_L = \frac{V^-}{V^+}$$

With the reflection coefficient now defined, we can rewrite 6.24 as
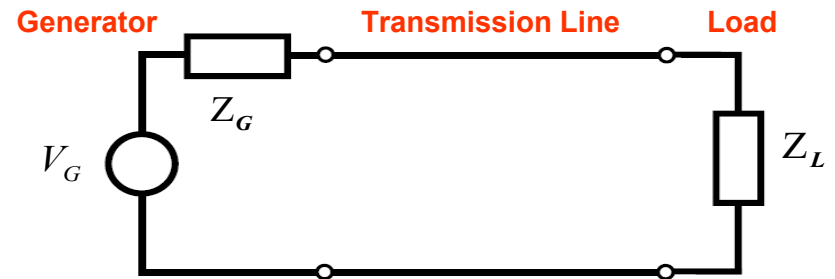
$$Z_n(z) = \frac{e^{-jkz} + \Gamma_L e^{+jkz}}{e^{-jkz} - \Gamma_L e^{+jkz}}$$



Evaluating Z_n at the Load ($z = 0$)

$$Z_{nL}(z = 0) = \frac{Z(z = 0)}{Z_0} = \frac{1 + \Gamma_L}{1 - \Gamma_L} \quad \left(\text{or } \Gamma_L = \frac{Z_{nL} - 1}{Z_{nL} + 1} \right) \quad 6.25$$

Evaluating Z_n at a point along line ($z = -l$)

$$Z_n(z = -l) = \frac{Z(z = -l)}{Z_0} = \frac{Z_L + jZ_0 \tan kl}{Z_0 + jZ_L \tan kl} \quad 6.27$$

$$\left| V_{(z)} \right| = \left| V^+ \right| \left| 1 + \Gamma_L e^{j2kz} \right|$$

with $\Gamma_L = \left| \Gamma_L \right| e^{j\varphi}$

$$\left| V_{(z)} \right| = \left| V^+ \right| \left| 1 + \left| \Gamma_L \right| e^{j(\varphi + 2kz)} \right|$$

V_{\max} when $\varphi + 2kz = 0, -2\pi, \dots$

V_{\min} when $\varphi + 2kz = -\pi, -3\pi, \dots$

$$|V(z)| = |V^+| \left| 1 + |\Gamma_L| e^{j(\varphi + 2kz)} \right|$$

$$\frac{|V(z)|}{|V^+|} = \left| 1 + |\Gamma_L| e^{j(\varphi + 2kz)} \right|$$

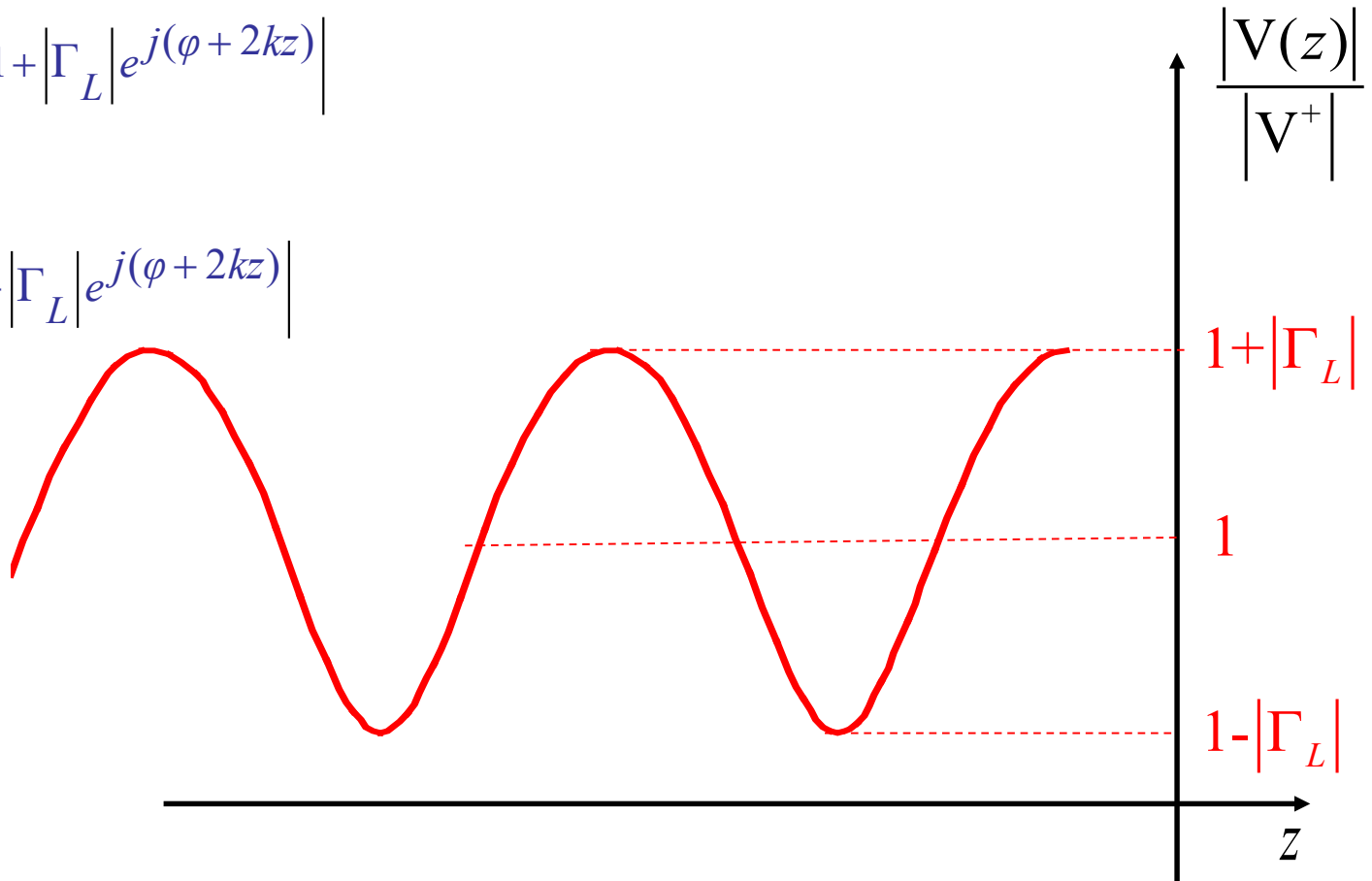


Fig. 6.6

$$|V(z)| = |V^+| \left| 1 + |\Gamma_L| e^{j(\varphi + 2kz)} \right|$$

$$\frac{|V(z)|}{|V^+|} = \left| 1 + |\Gamma_L| e^{j(\varphi + 2kz)} \right|$$


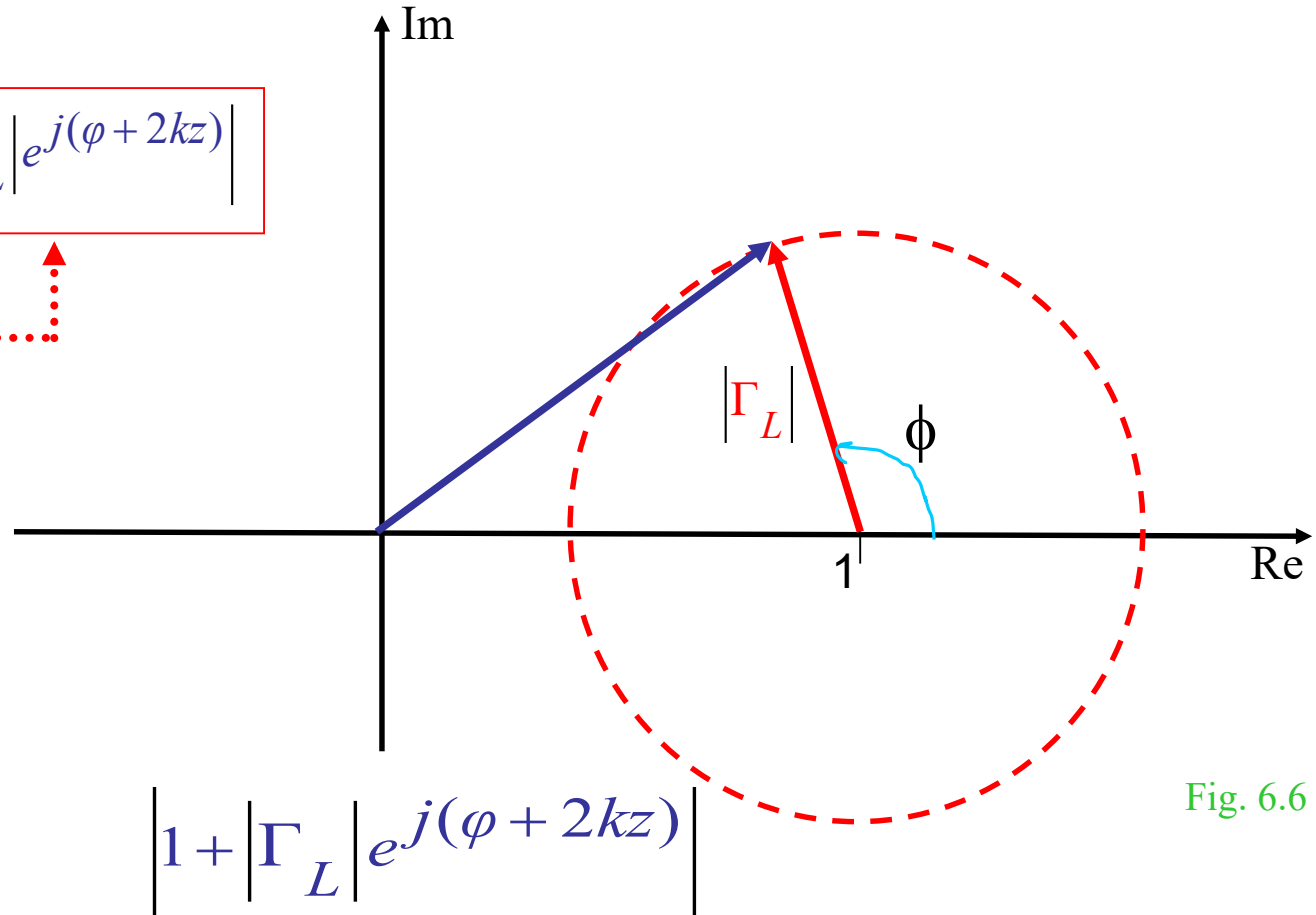


Fig. 6.6

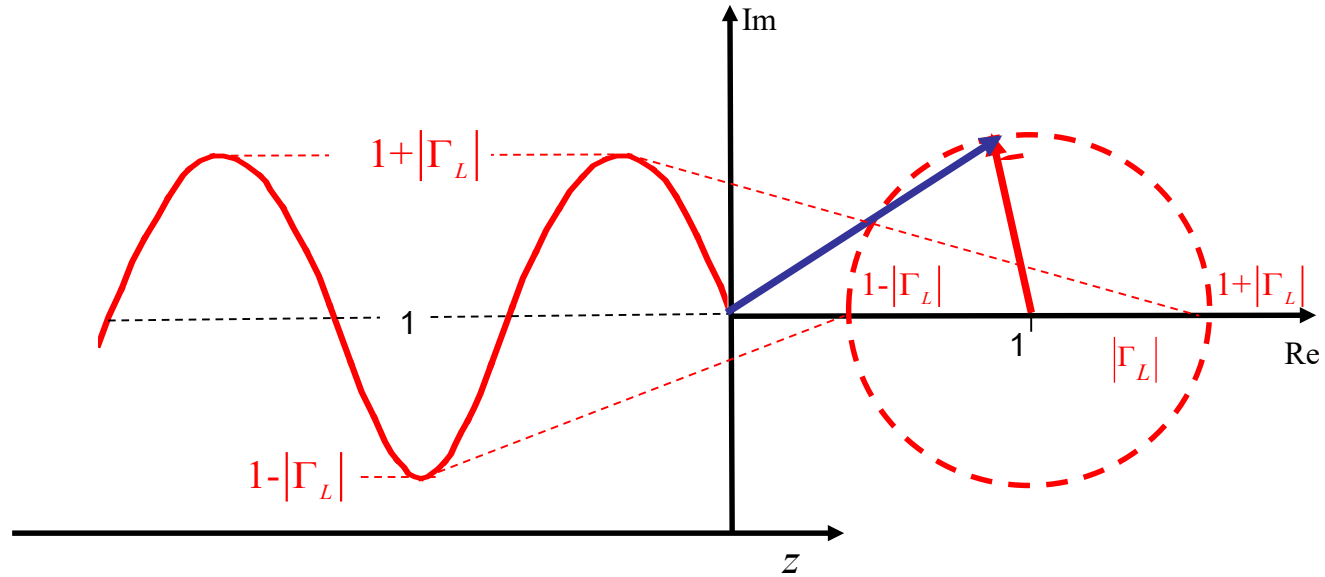

$$\frac{|V(z)|}{|V^+|} = \left| 1 + |\Gamma_L| e^{j(\varphi + 2kz)} \right|$$

$$[\text{VSWR}] = \frac{V_{\max}}{V_{\min}} = \frac{I_{\max}}{I_{\min}}$$

$$[\text{VSWR}] = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad 6.29$$

$$|\Gamma_L| = \frac{[\text{VSWR}] - 1}{[\text{VSWR}] + 1} \quad 6.30$$

To determine ($\angle \Gamma_L$) or Z_L
also need position of V_{\min}

Note:

$$\text{Power} \sim V^2 \Rightarrow \frac{P^-}{P^+} = |\Gamma_L|^2$$

$$\text{Power to load} \sim 1 - |\Gamma_L|^2$$

Ex. 6.6

$Z_L = 17.4 - j30[\Omega]$ and $Z_0 = 50[\Omega]$

$$\Gamma_L = \frac{Z_{nL}^{-1}}{Z_{nL} + 1} = \frac{Z_L - Z_0}{Z_L + Z_0} = -0.24 - j.55$$



or

$\Gamma_L = 0.6e^{-j1.99}$

where

$$|\Gamma_L| = 0.6$$
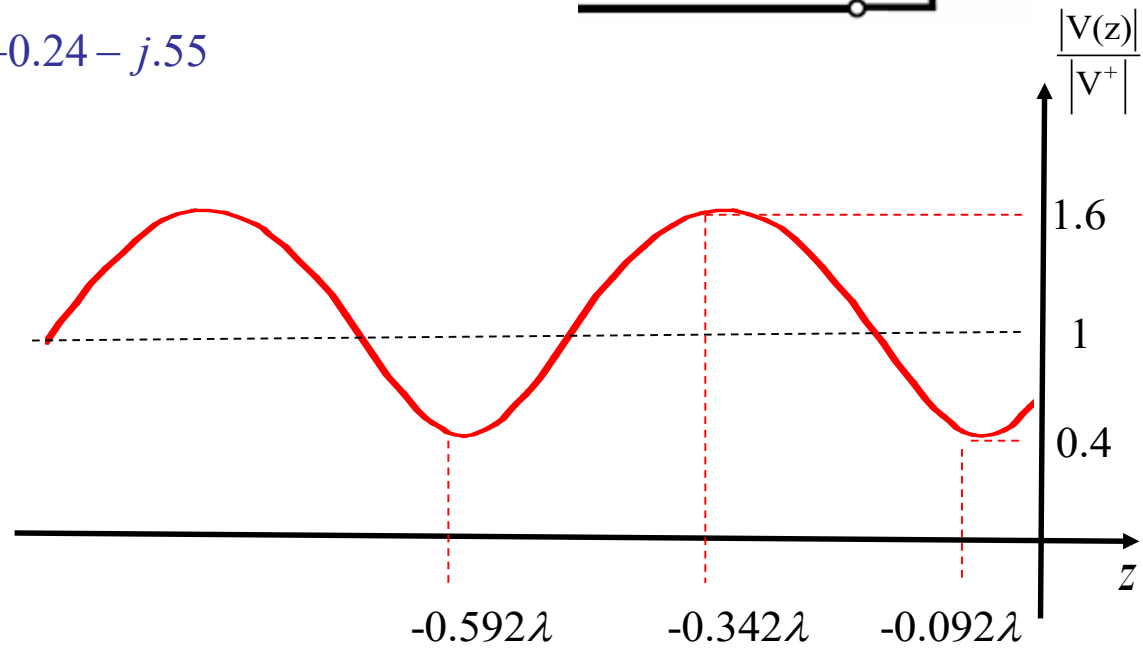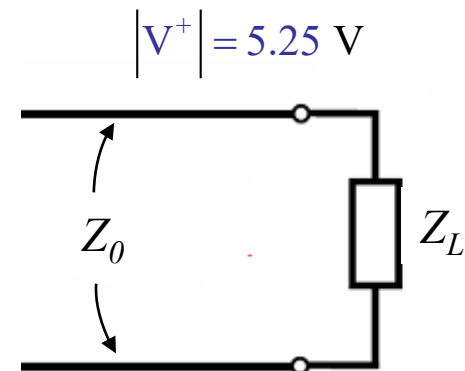
$$\phi = \angle \Gamma_L = -1.99 \text{ [rad]}$$




V_{\max} when $\phi + 2kz = 0, -2\pi, \dots$

V_{\min} when $\phi + 2kz = -\pi, -3\pi, \dots$

Ex. 6.6 V_{\min} where $\phi + 2k z_m = -\pi$

$$z_m = \frac{-\pi - \phi}{2k} = \frac{(-\pi + 1.99)\lambda}{2(2\pi)} = -.092\lambda$$

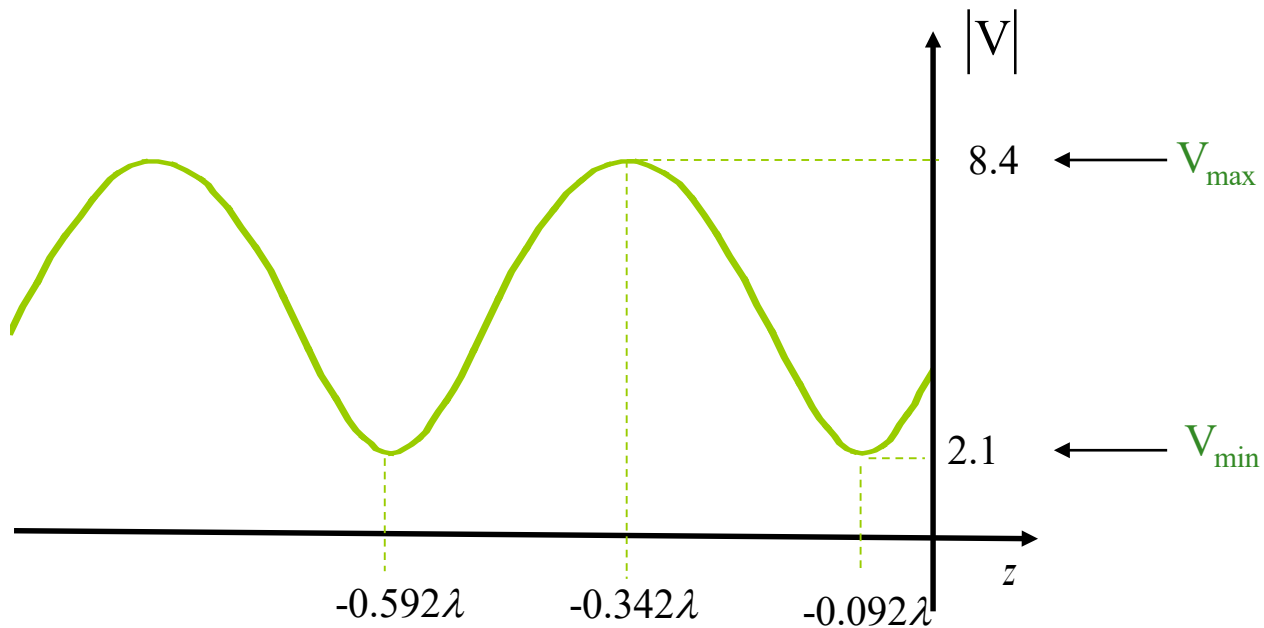

Ex. 6.6

Reverse problem

$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{8.4}{2.1} = 4.0$$



$$|\Gamma_L| = \frac{VSWR-1}{VSWR+1} = \frac{4-1}{4+1} = 0.6$$

To determine ($\angle\Gamma_L$) or Z_L also need position of V_{\min}

$$\angle\Gamma_L = \phi = -\pi - 2kz_m = -\pi - 2\left(\frac{2\pi}{\lambda}\right)(-.092\lambda) = -1.99$$

$$Z_L = Z_0 \left[\frac{1+\Gamma_L}{1-\Gamma_L} \right] = \boxed{17.4 - j30 \quad \Omega}$$
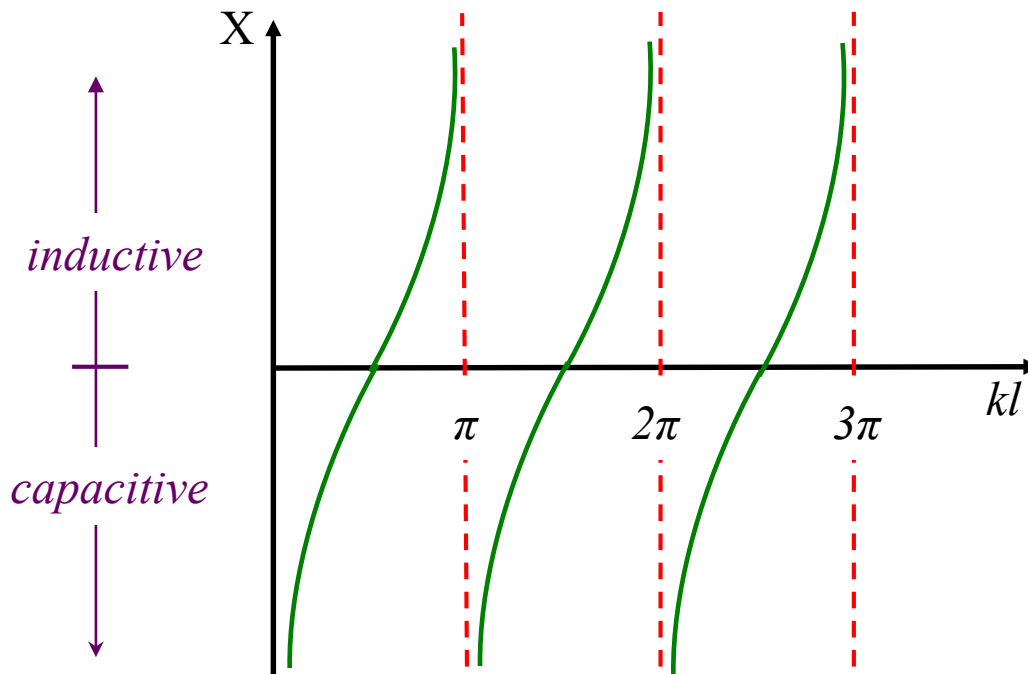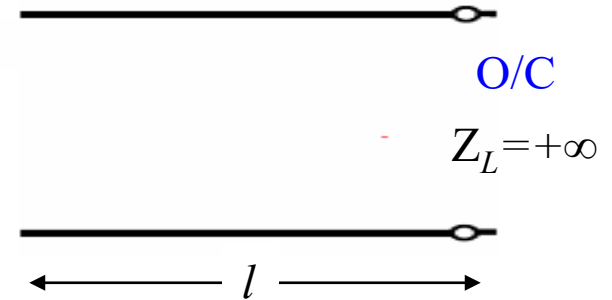
$$Z(-l) = Z_0 \frac{Z_L + jZ_0 \tan kl}{Z_0 + jZ_L \tan kl} = Z_0 \frac{1}{j \tan kl}$$





pure imaginary

$$jX = -jZ_0 \cot kl$$

If the impedance is purely imaginary, $Z = R + jX$ becomes $Z = jX$, where X is called the reactance.

$\lim kl \ll 1$ (small l or low freq)

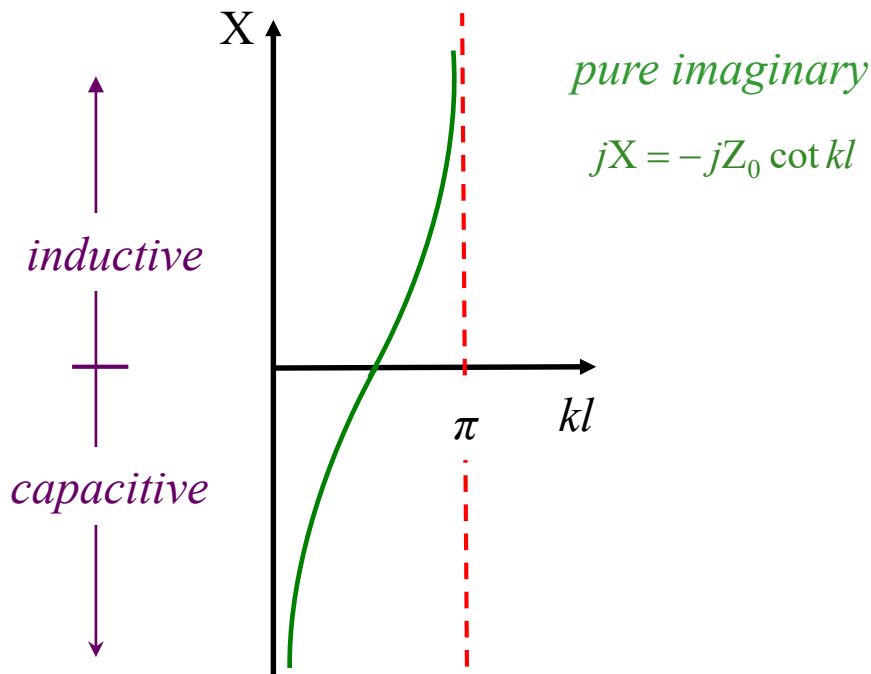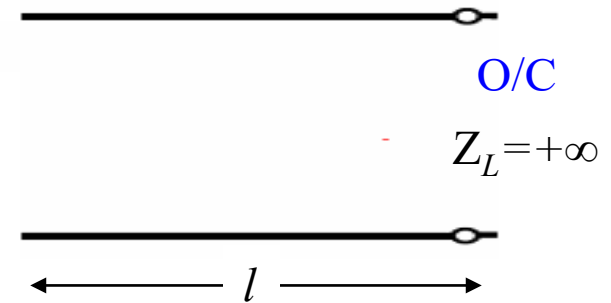

Note: at $kl = \frac{\pi}{2} \Rightarrow \left(l = \frac{\lambda}{4} \right)$


$Z\left(-\lambda/4\right) = 0$ (short circuit)

near $kl \leq \pi$ Z is inductive

near $kl \geq 0$ Z is capacitive



Philip Smith

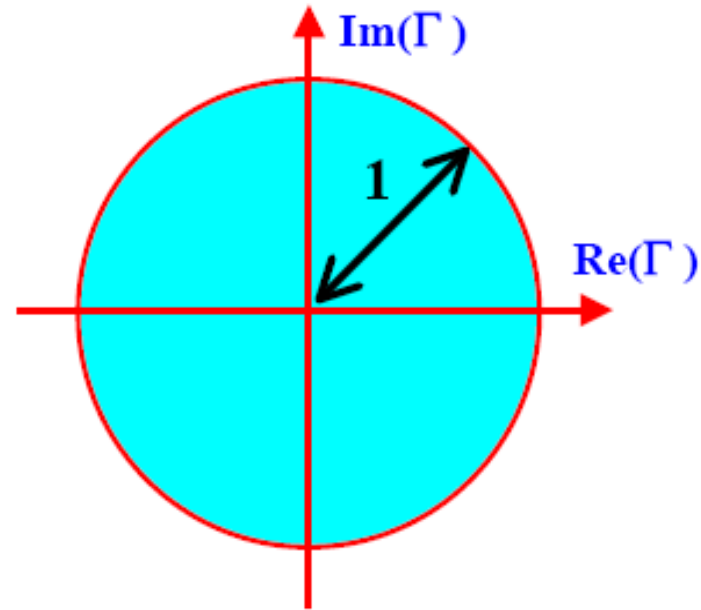


- Shows the entire universe of complex impedances in one convenient circle.
- Invented at Bell Labs by Philip Smith in 1937.
- By 1975 about 9 million copies of his chart sold to microwave engineers all over the world.
- Its usefulness continues to this day as a method of displaying measured and calculated data produced by computer software and modern measurement instruments.



$$Z_{nL} = \frac{1 + \Gamma_L}{1 - \Gamma_L} = R + jX$$

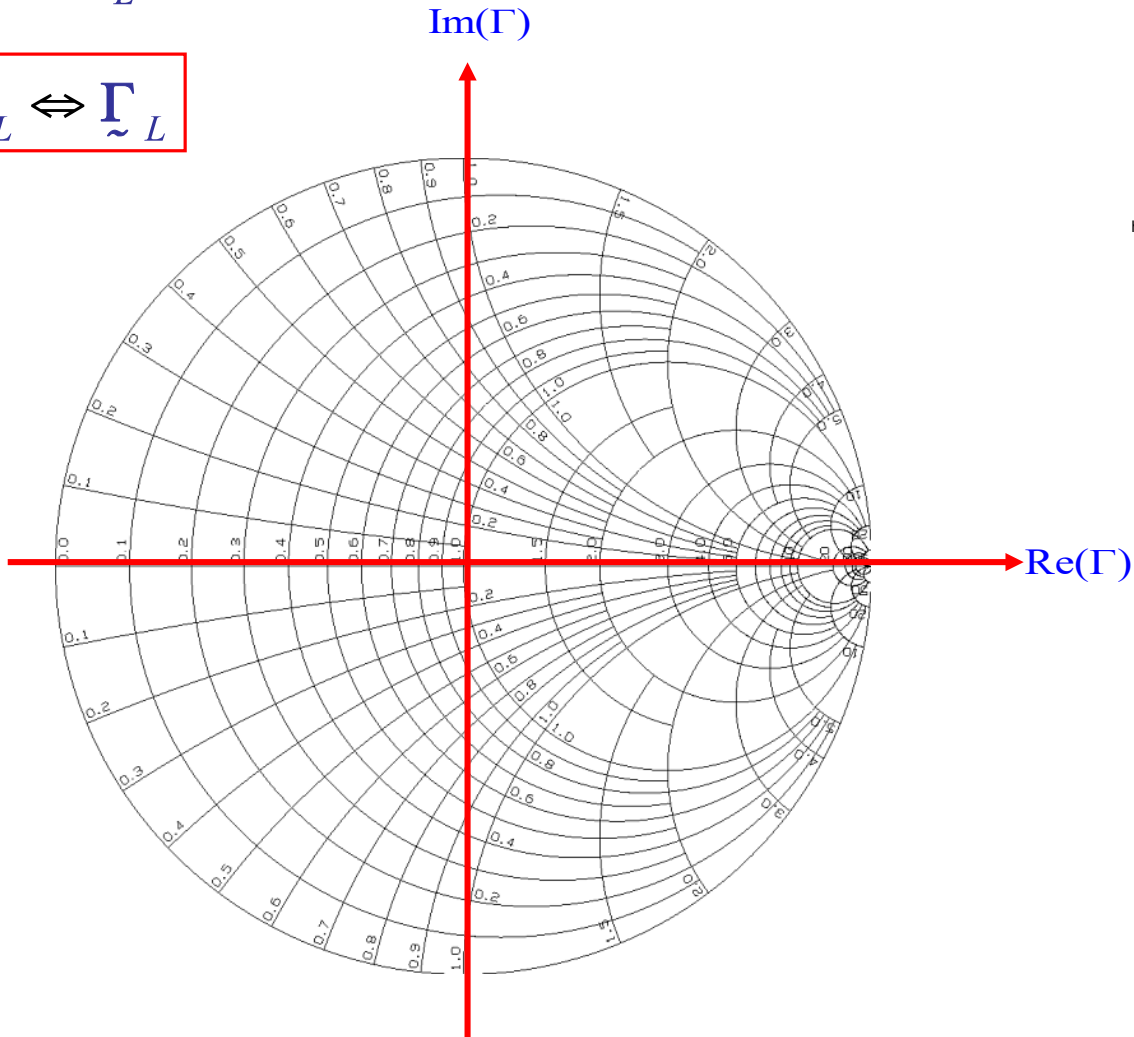
$$\tilde{Z}_{nL} \Leftrightarrow \tilde{\Gamma}_L$$



http://my.ece.ucsb.edu/sanabria/images/chris_tattoo2.jpg

Z Chart


Constant R Circles on Chart

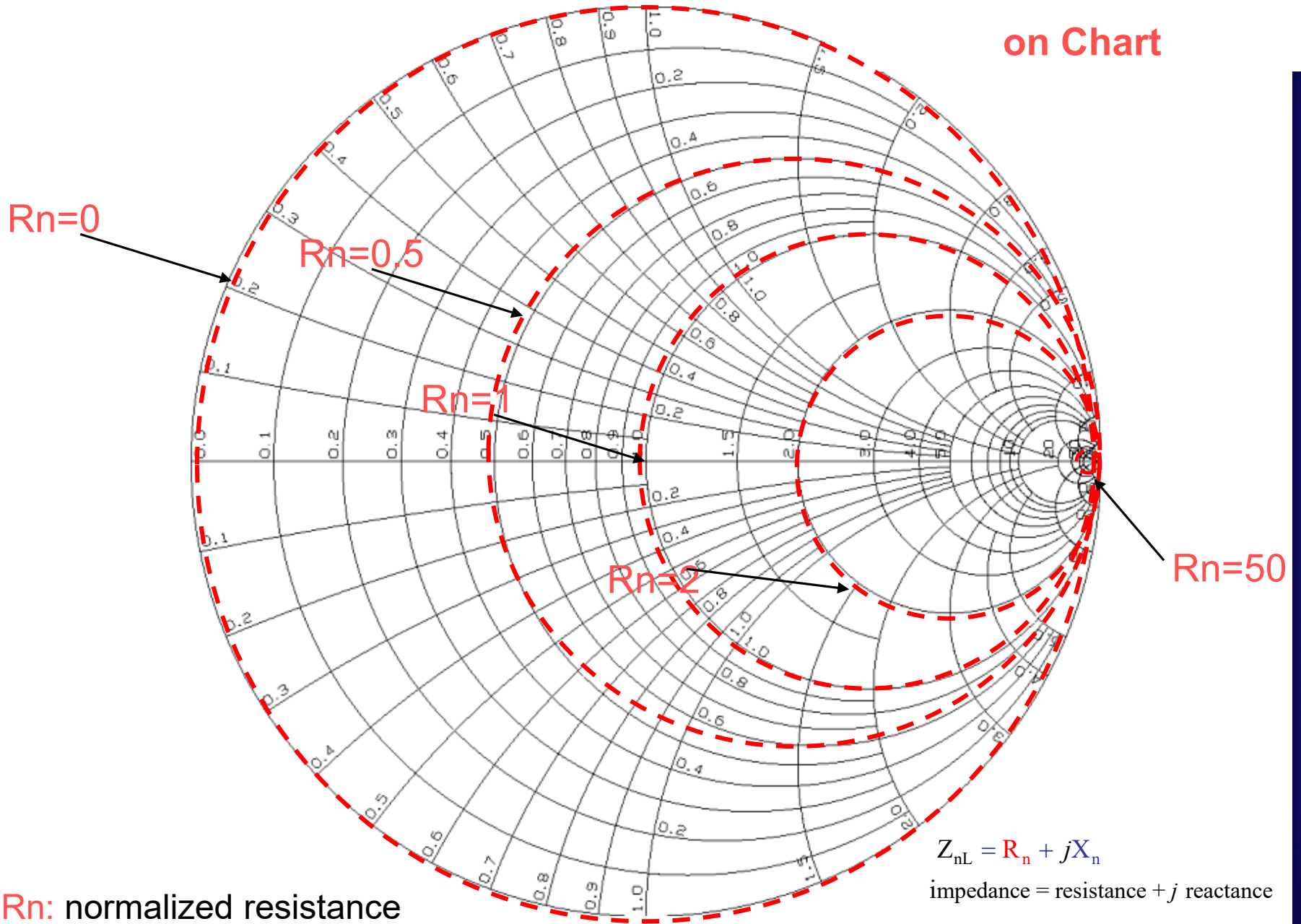

R_n : normalized resistance

Z Chart

Constant X Arcs on Chart

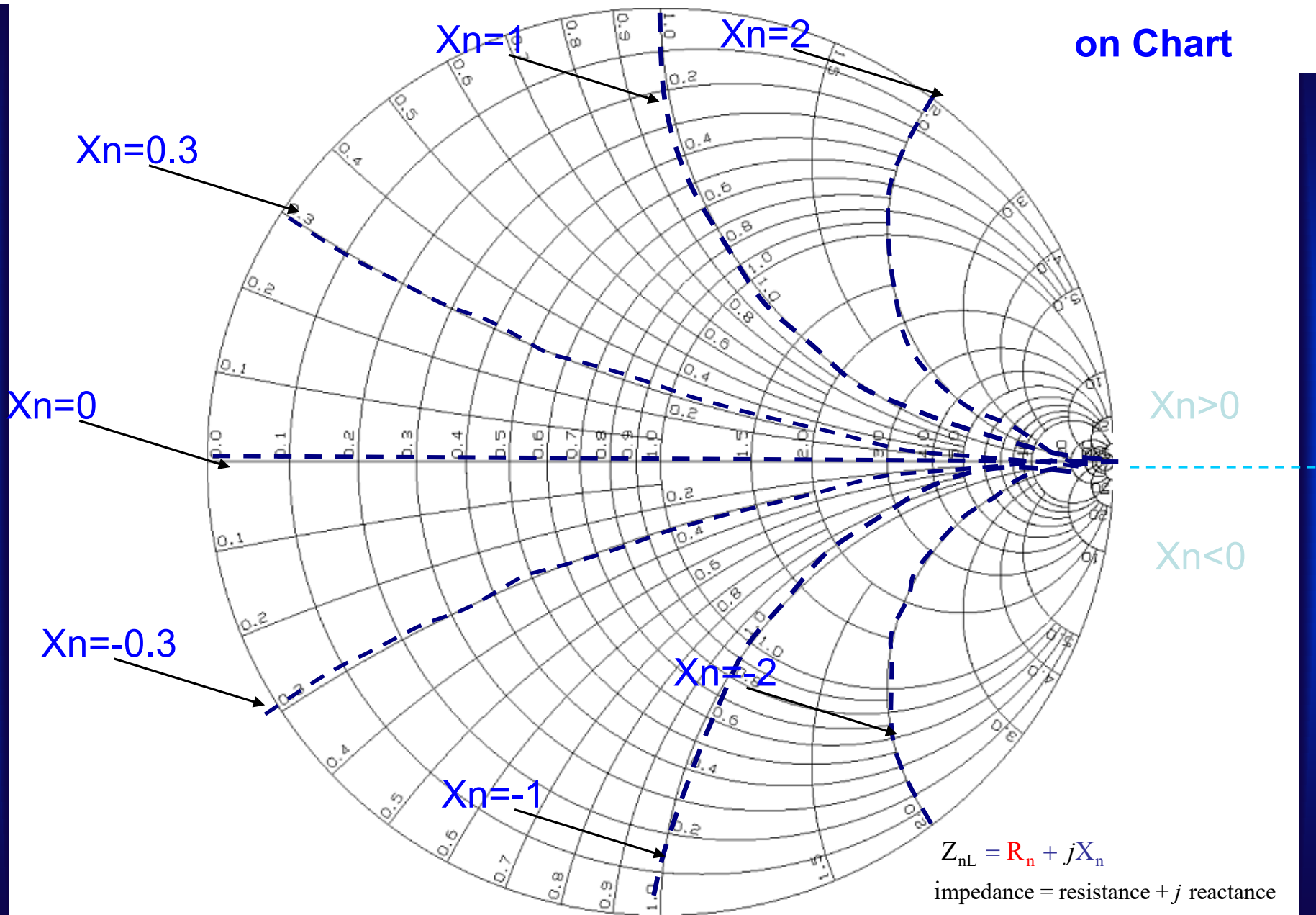

$$Z_{nL} = R_n + jX_n$$


impedance = resistance + j reactance

$$Z_{nL} = R_n + jX_n$$

$$Z_{nL} = 0.2 - j0.3$$

$R_n=0.2$ circle

$X_n=-0.3$ arc

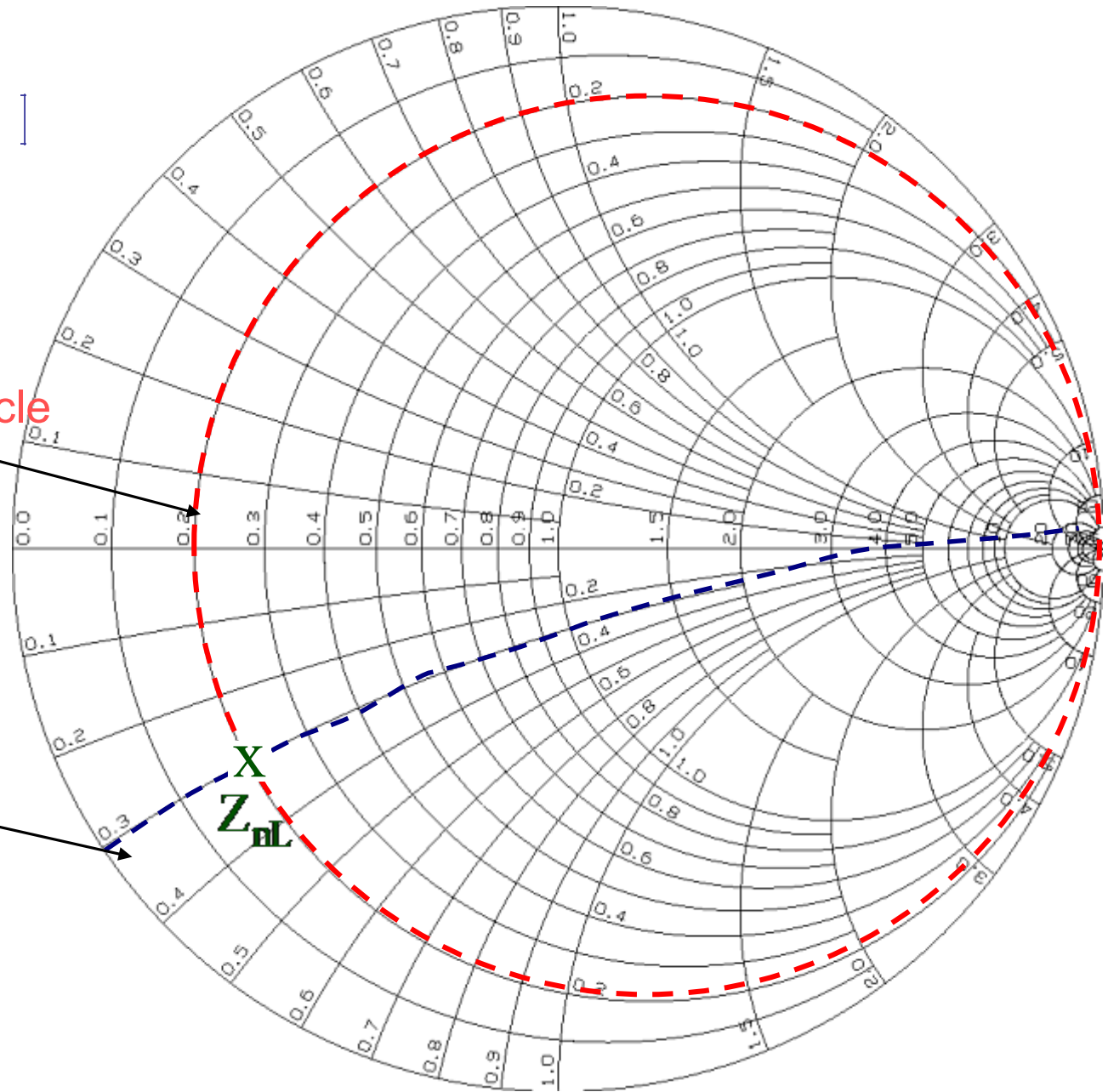


$$Z_{nL} = R_n + jX_n \quad [\Omega]$$

$$Z_{nL} = 0.2 - j0.3 \quad [\Omega]$$

Using your compass draw the $0.2 - j0.3$ circle with center at $z_n = 1$.

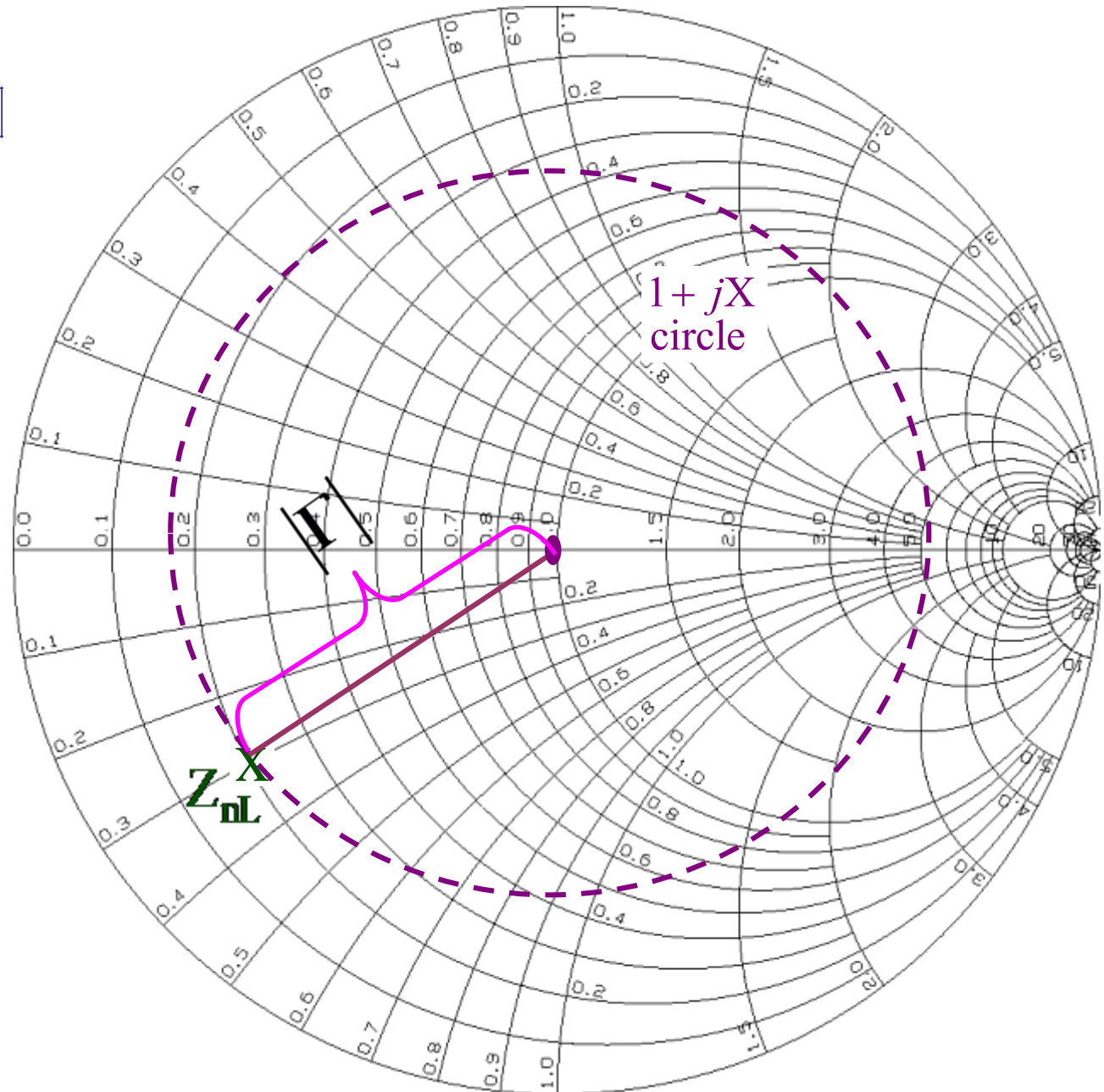(NOTE: this circle is not on the chart until you draw it.)




Find the value of reflection coefficient for $Z_n L = 0.2 - j0.3$

Reflection Coefficient PHASE = -145.4 degrees


Reflection Coeff MAGNITUDE = 0.691

VSWR = 5.47

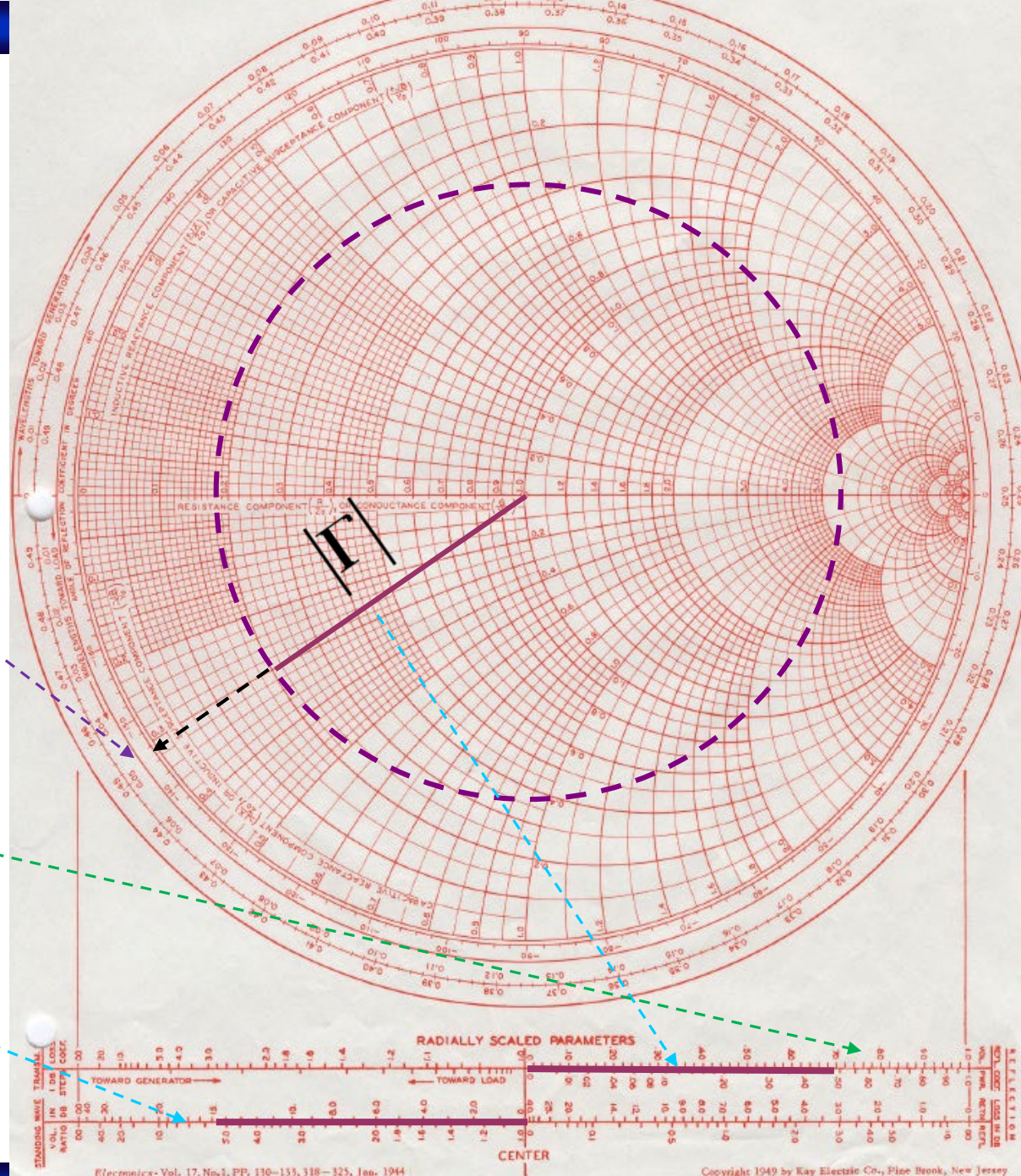



SCALED PARAMETERS

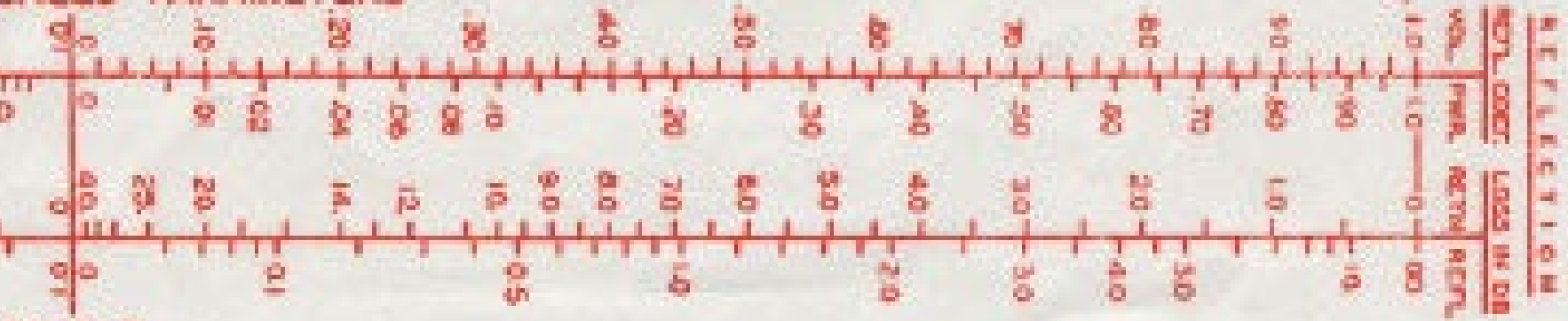

CENTER

Copyright 1949 by Kay Electric Co., Pine Brook, New Jersey

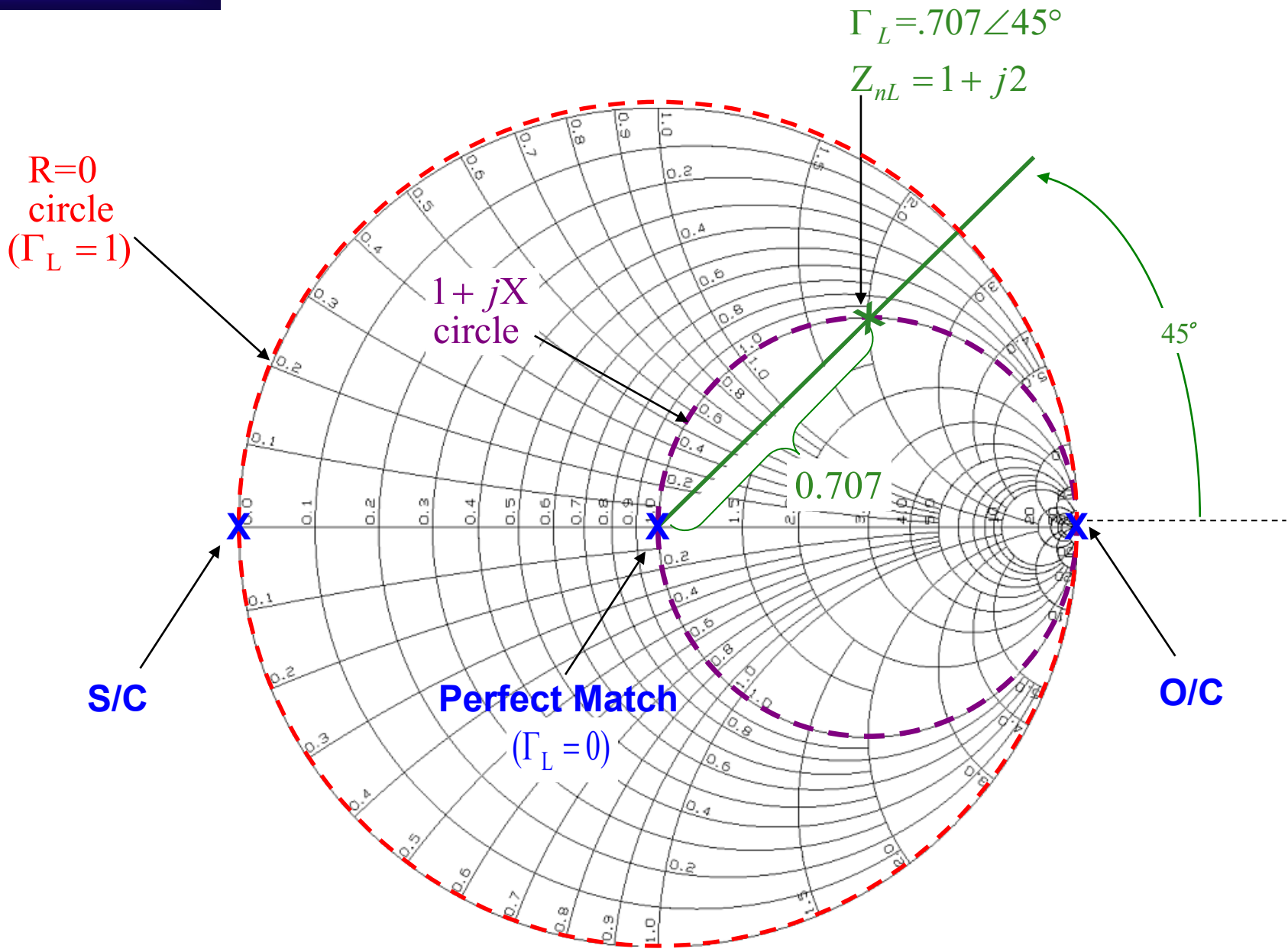




fig 6.13

$$Z(z) = Z_0 \frac{e^{-jkz} + \Gamma_L e^{+jkz}}{e^{-jkz} - \Gamma_L e^{+jkz}} = Z_0 \frac{1 + \Gamma_L e^{+2jkz}}{1 - \Gamma_L e^{+2jkz}}$$


movement in negative \hat{z} direction
(toward generator)



clockwise motion on circle of constant $|\Gamma_L|$

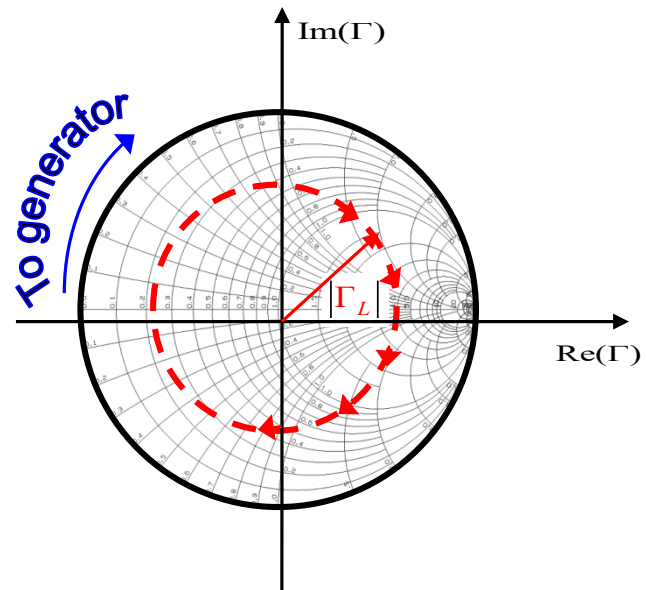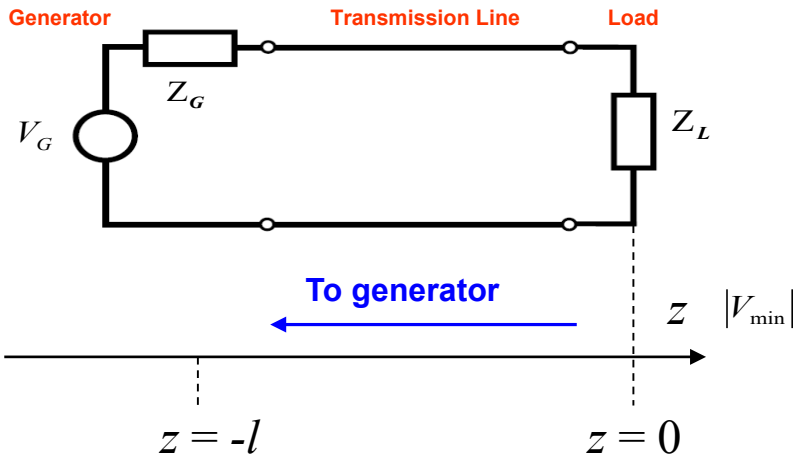

$$\frac{|V(z)|}{|V^+|} = \left| 1 + \Gamma_L e^{j2kz} \right|$$

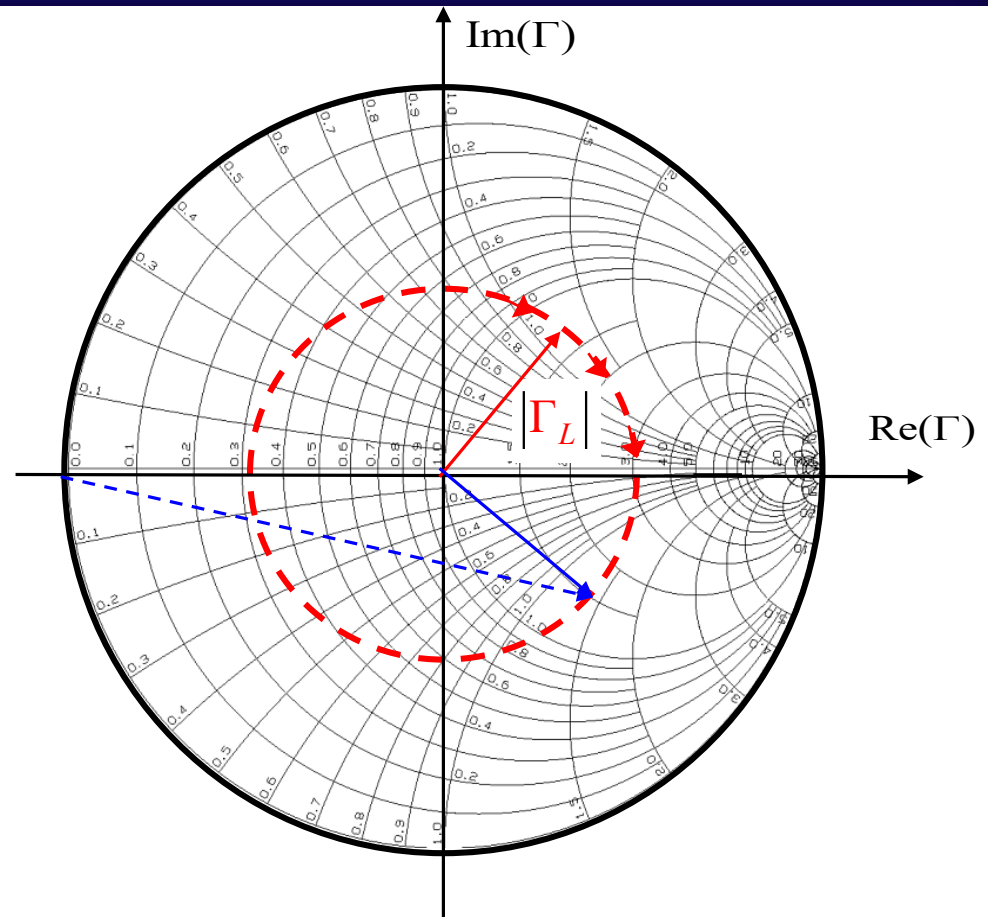

Note:


complete circle ($360^\circ = 2\pi \text{ rad}$) = $\frac{\lambda}{2}$

$Y_n(z) = \frac{1}{Z_n(z)} \Rightarrow$ can just replace Γ_L by $(-\Gamma_L)$



$$|V_{\max}| = 1 + |\Gamma_L| \quad (\text{RH Real axis})$$

$$|V_{\min}| = 1 - |\Gamma_L| \quad (\text{LH Real axis})$$

$$\frac{|V(z)|}{|V^+|} = |1 + \Gamma_L e^{2jkz}|$$

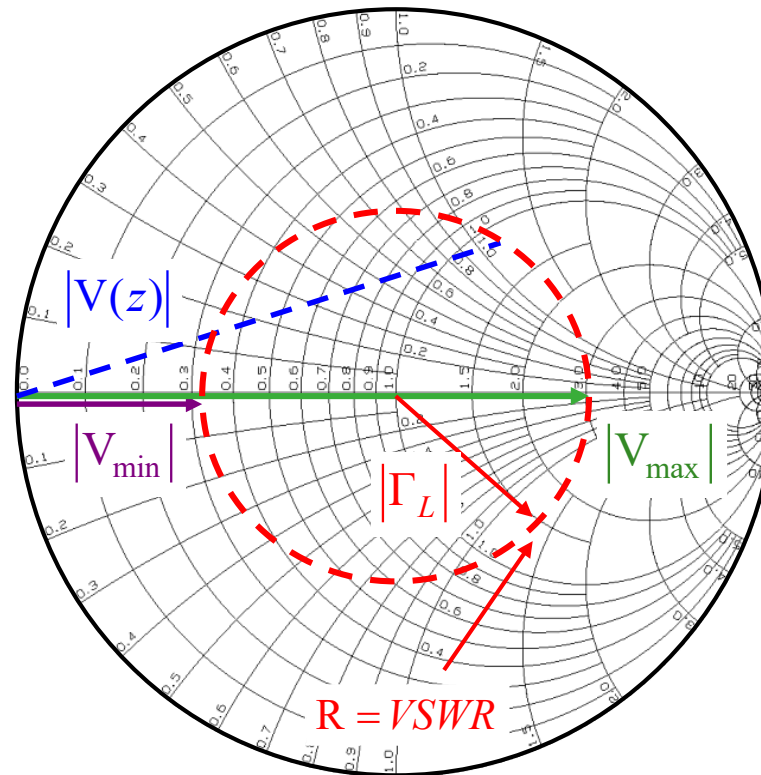

$$Z_{nL} = 1 + j2$$

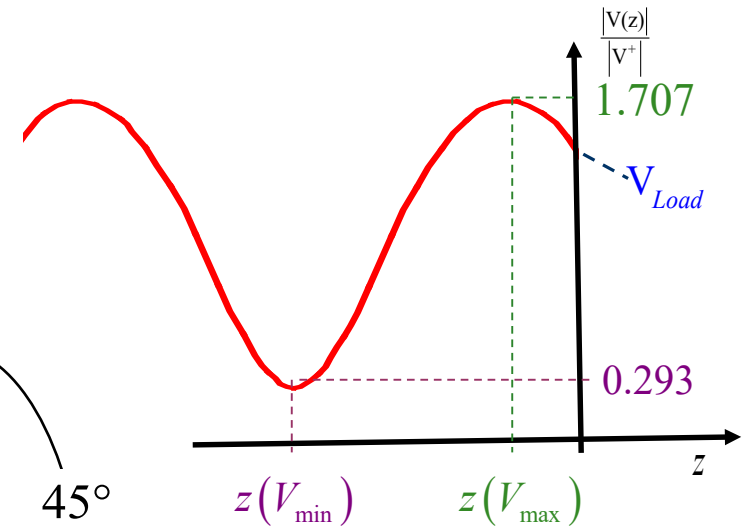
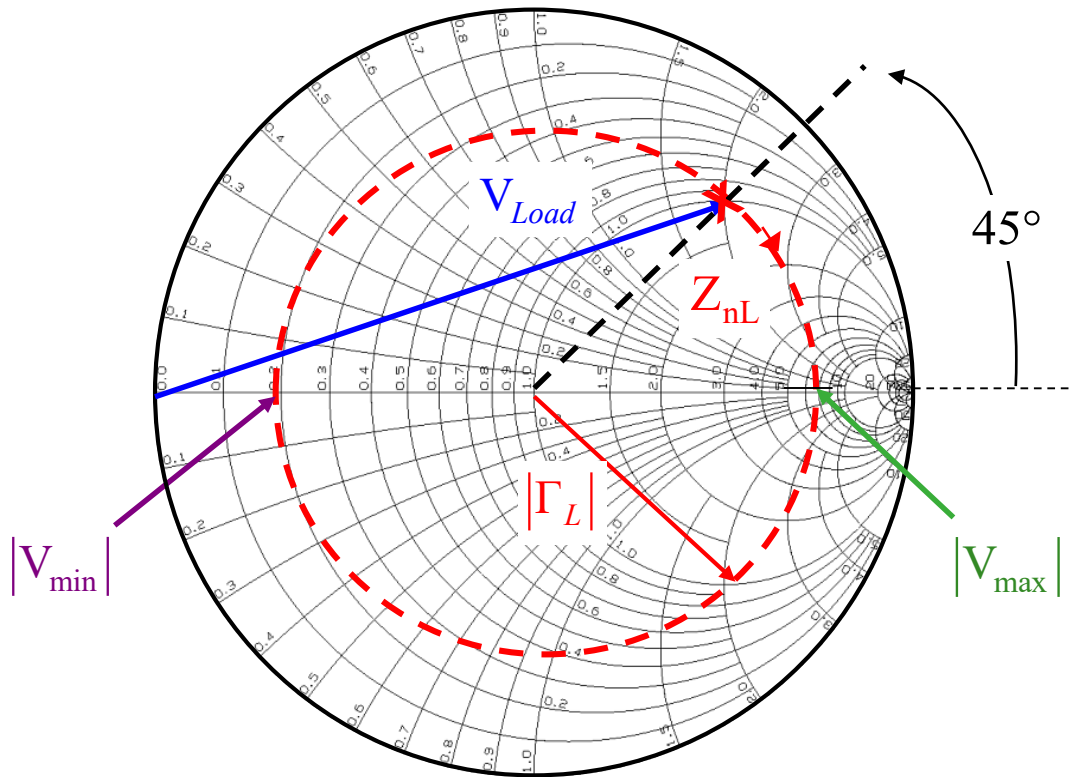


$$Z_{nL} = 1 + j2$$

$$\Gamma = .707 \angle 45^\circ$$



$$360^\circ \text{ on Smith Chart} = \frac{\lambda}{2}$$
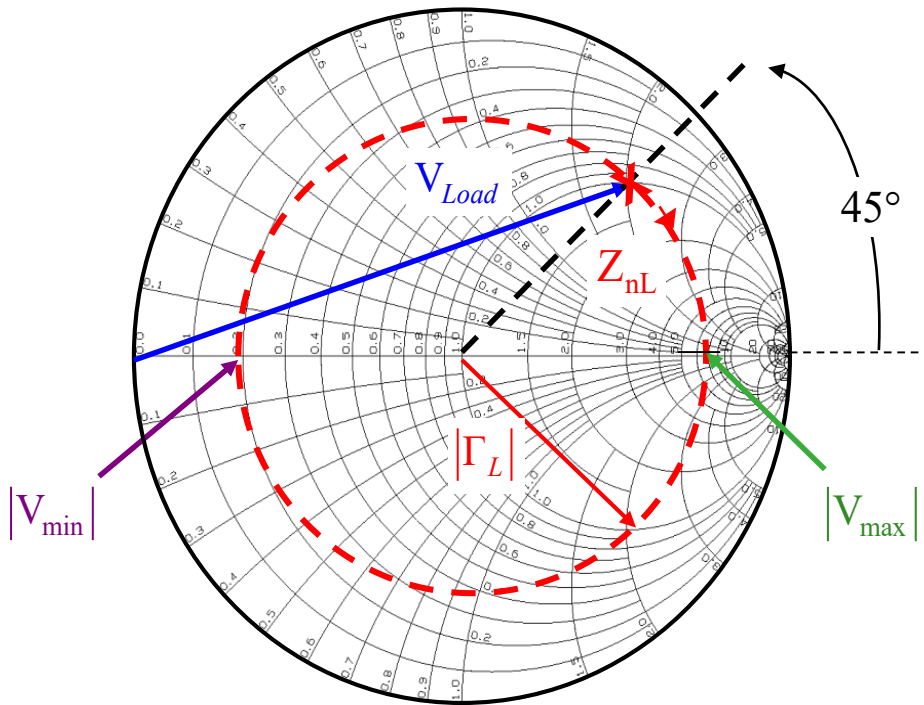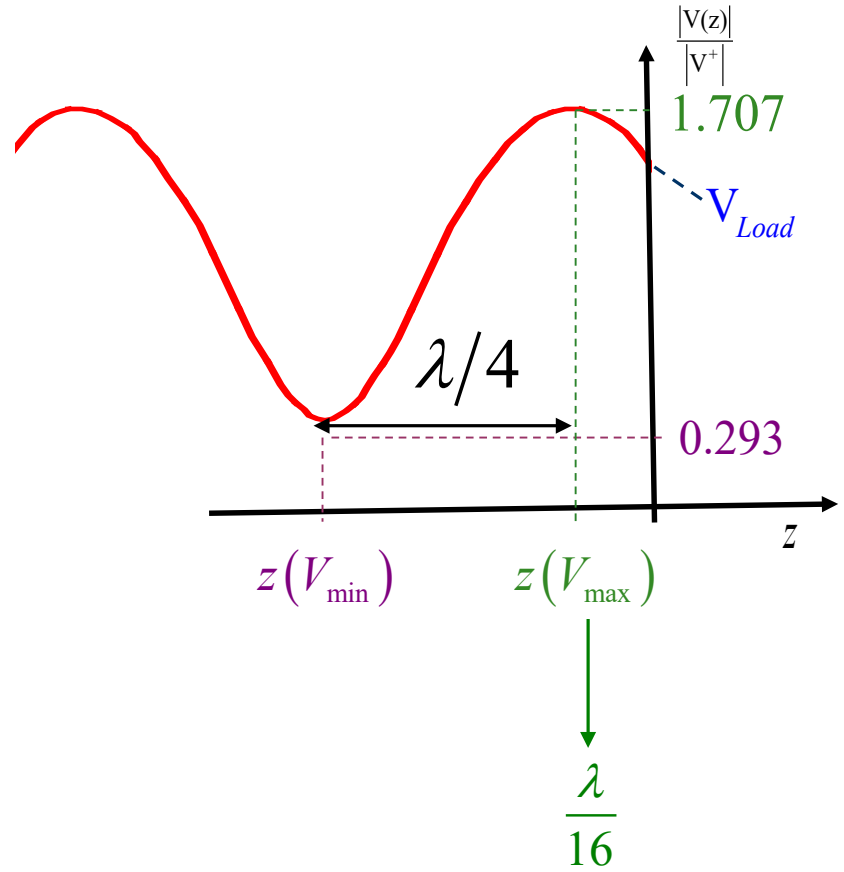
$$180^\circ \text{ on Smith Chart} = \frac{\lambda}{4}$$



$$Z_{nL} = 1 + j2$$


$$\Gamma = .707 \angle 45^\circ$$

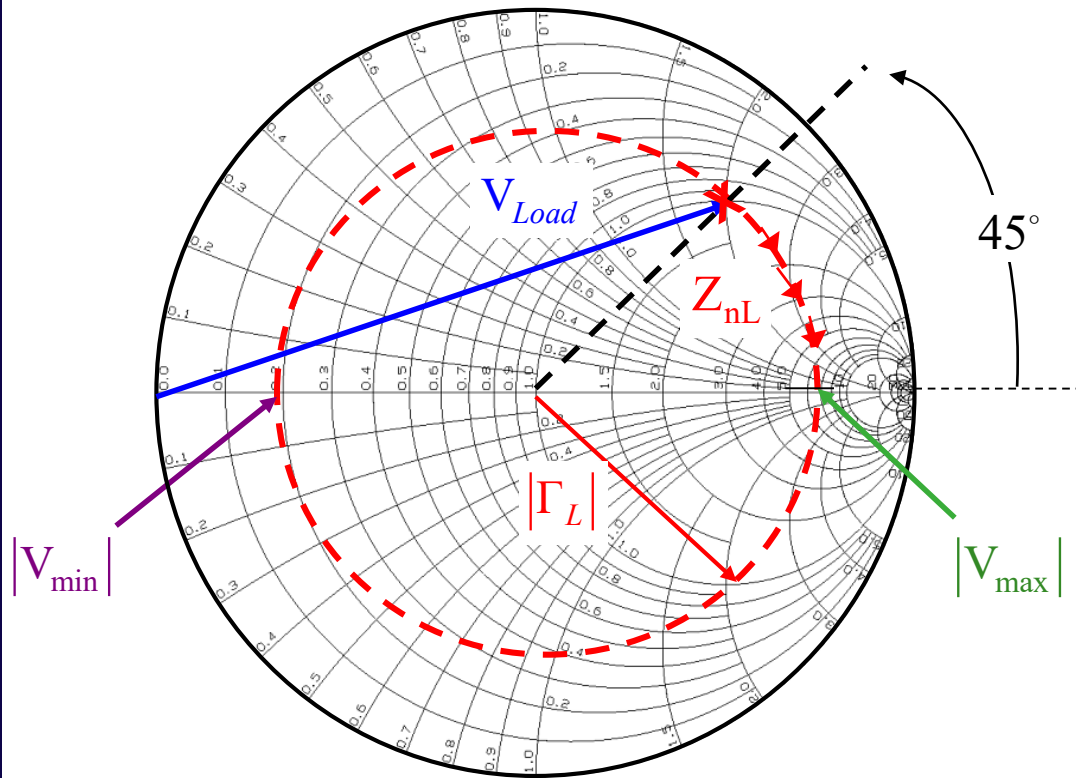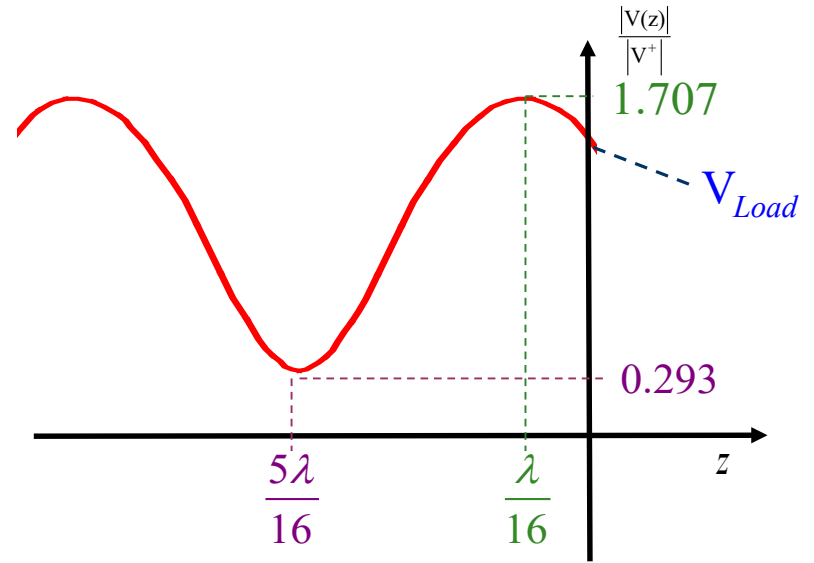

$$0.25\lambda - 0.1875\lambda = 0.0625\lambda$$

$$\Gamma_L = .707 \angle 45^\circ$$

$$Z_{nL} = 1 + j2$$

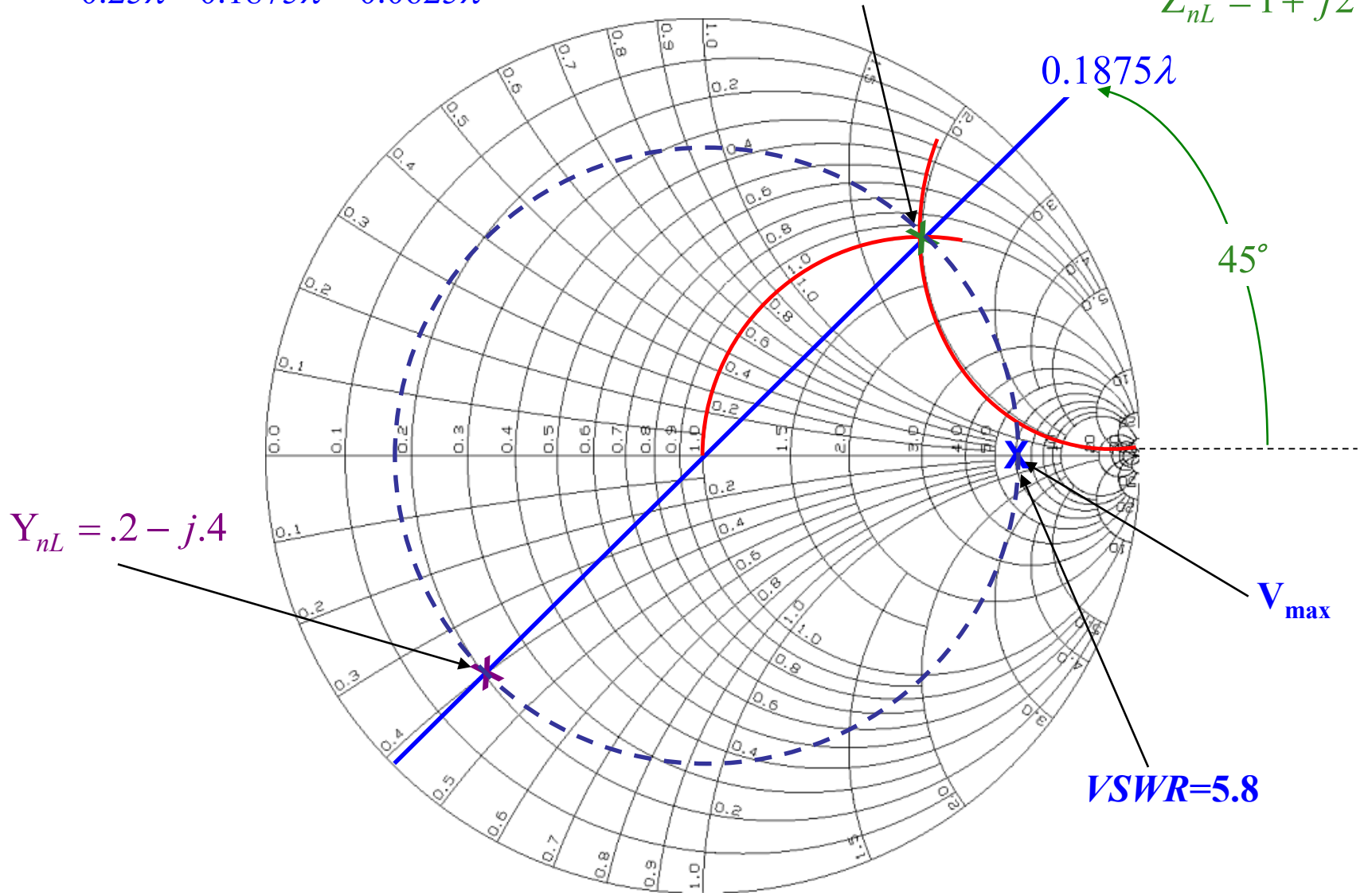

Usually want power to be absorbed by load (minimize $|\Gamma_L|^2$).

To do so one adds pure reactances (or susceptances) to tune or match the network.

$$Z = R + jX \quad [\Omega]$$

impedance = resistance + j reactance

$$Y = G + jB \quad [S]$$

admittance = conductance + j susceptance

Note: It is physically easier to add a shunt susceptance than series reactance.

Example: Given $Z_{nL} = 2 + j2 \Rightarrow \Gamma = 0.62 \angle 30^\circ$

$$|\Gamma|^2 = 0.62^2 = 38\% \text{ power reflected}$$

change from $Z_{nL} \Rightarrow Y_{nL} = G_{nL} + jB_{nL}$

$$Y_{nL} = \frac{1}{Z_{nL}} = \frac{1}{2 + j2} = 0.25 - j0.25$$

could add $+j.25$ at load

$$Y_{nL} = 0.25 \Rightarrow \Gamma = 0.6 \angle 0^\circ$$

$$|\Gamma|^2 = 0.6^2 = 36\% \text{ power reflected}$$

instead rotate toward generator to $1 + jB$ circle and add a $-jB$ there.

Smith Chart


Solution:

Add $+j1.57$ at 0.362λ

Or $-j1.57$ at 0.219λ

$$0.041\lambda + 0.178\lambda = 0.219\lambda$$
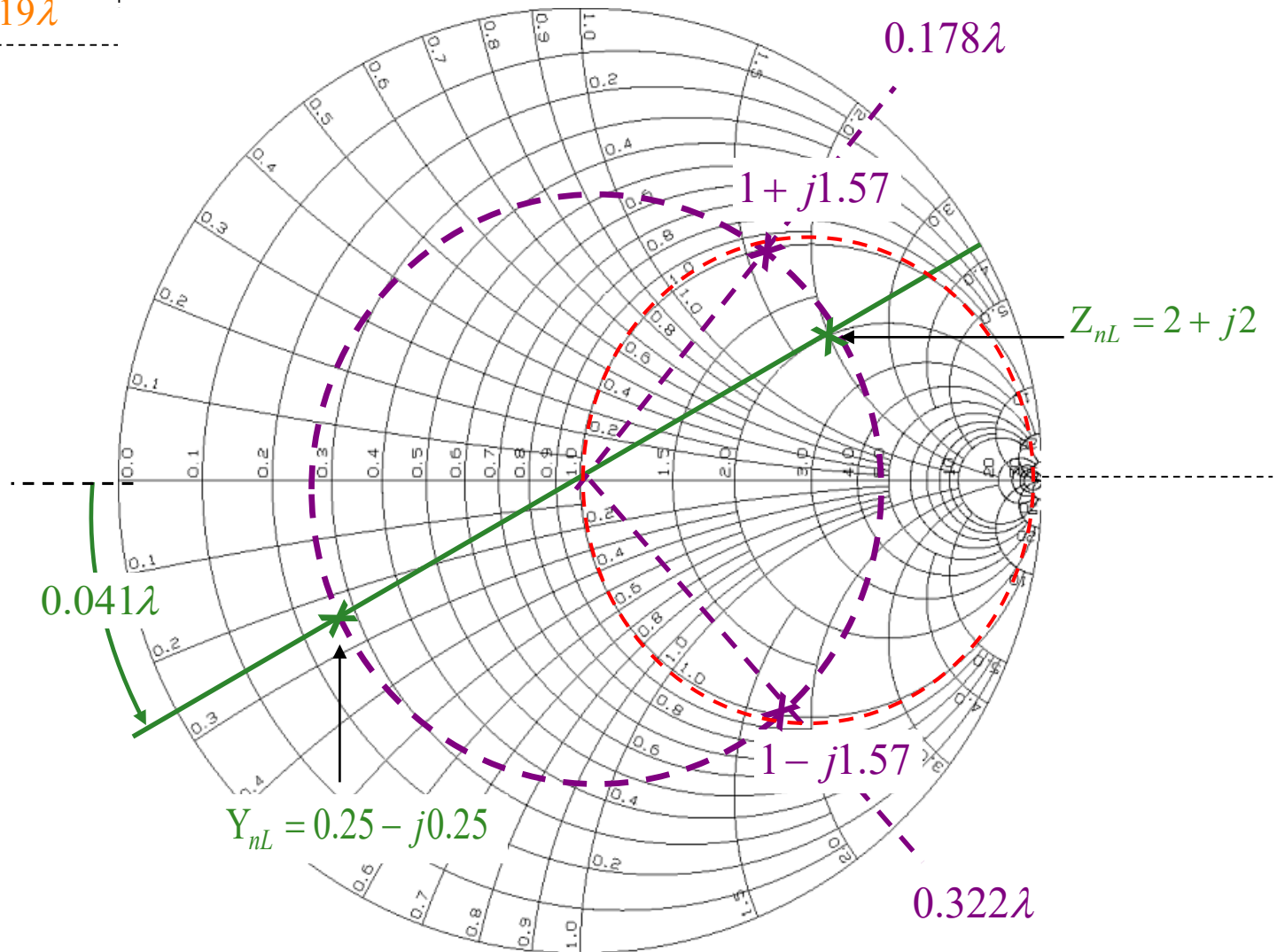
$$0.041\lambda + 0.322\lambda = 0.363\lambda$$



Smith Chart


Solution:

Add $+j1.57$ at 0.362λ


Or $-j1.57$ at 0.219λ


$$0.041\lambda + 0.178\lambda = 0.219\lambda$$
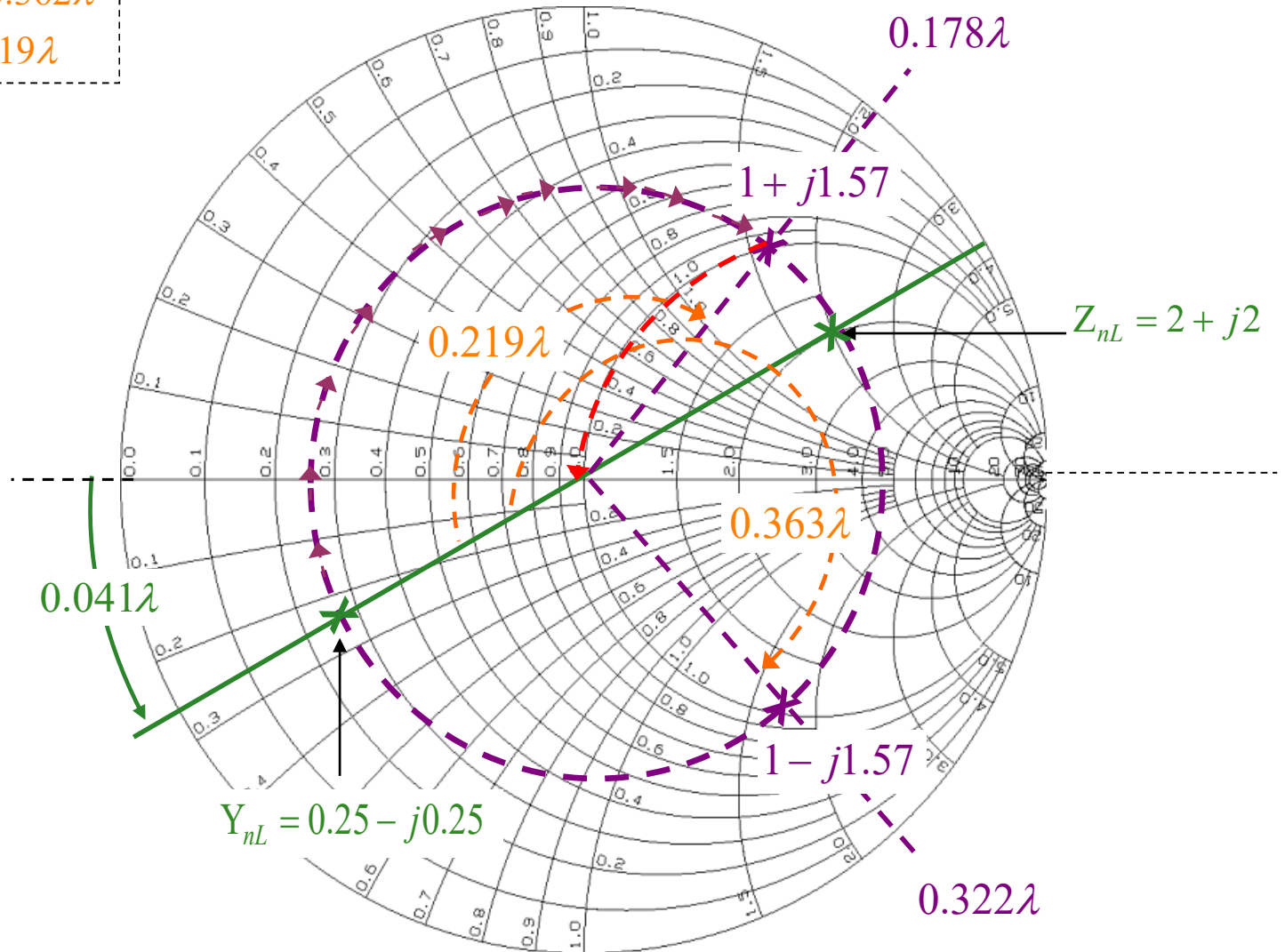
$$0.041\lambda + 0.322\lambda = 0.363\lambda$$


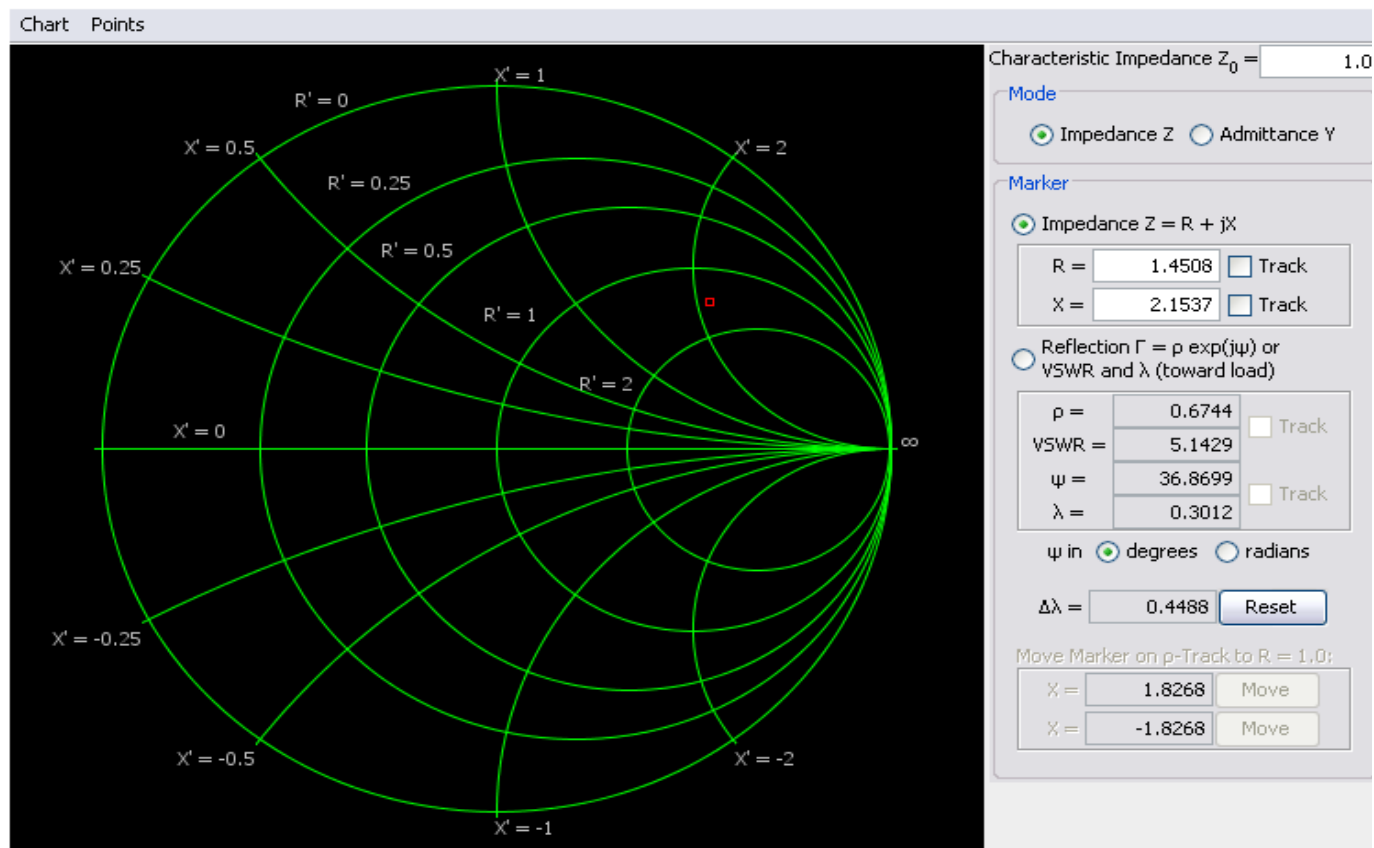
<http://www.ocf.berkeley.edu/~joydip/smithchart/index.html>



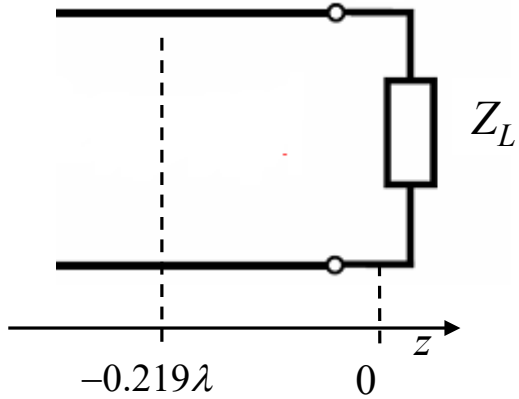


Voltages: Unmatched Line


$$V_{load} = V(0) = 1.55$$

$$V_{max} = 1.62$$

$$V_{min} = 0.38$$

$$V(-0.219\lambda) = 0.78$$

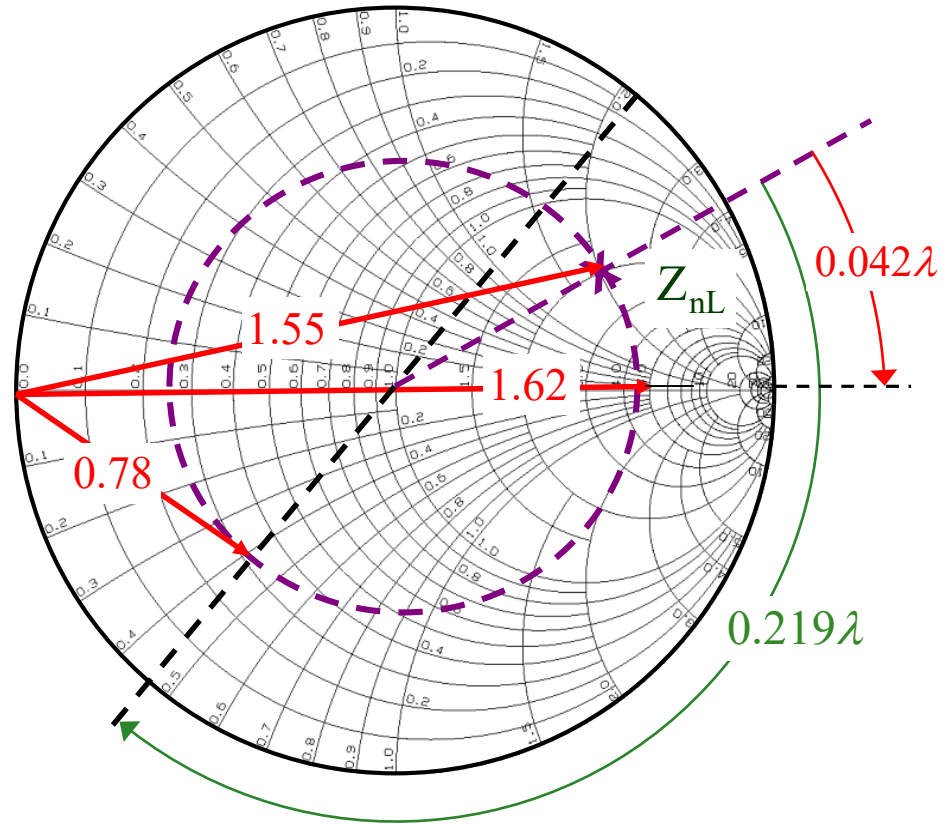

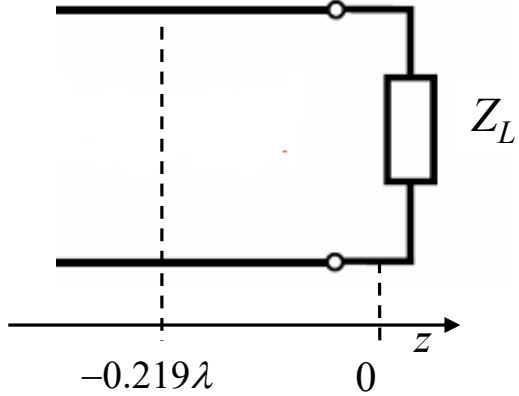


Currents: Unmatched Line


$$I_{load} = 0.55$$

$$I_{max} = 1.62$$

$$I_{min} = 0.38$$


$$I(-0.219\lambda) = 1.45$$

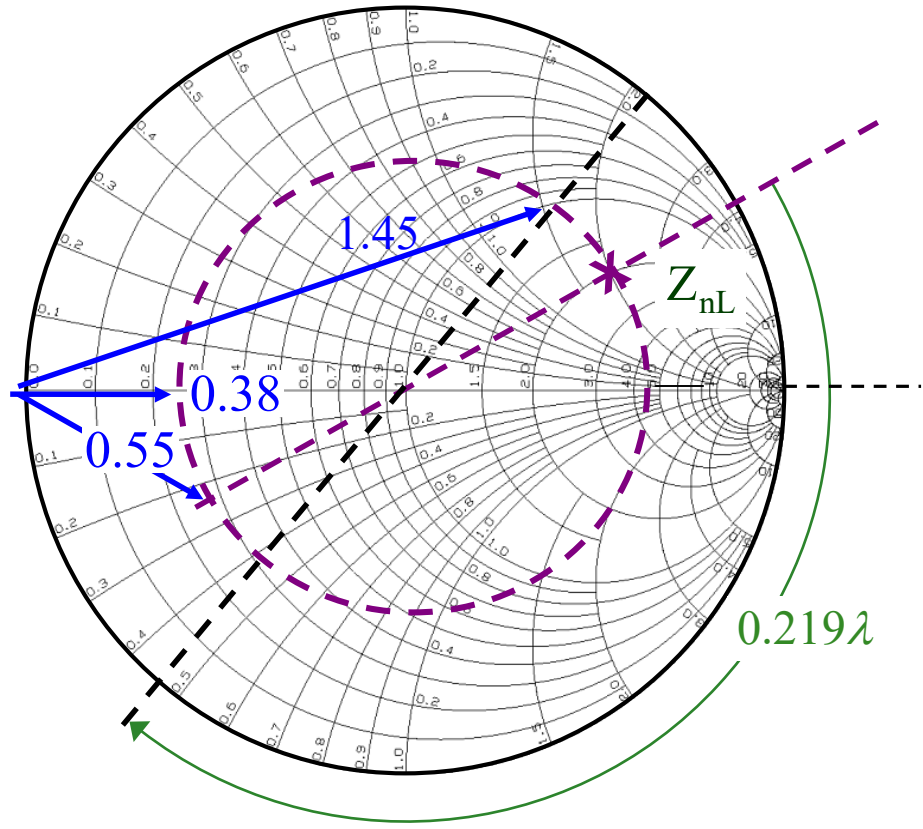


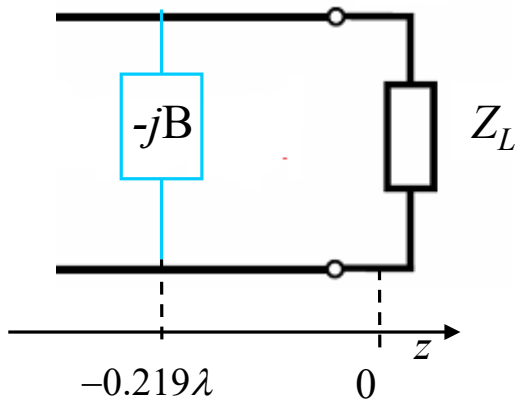


Voltages: Matched Line

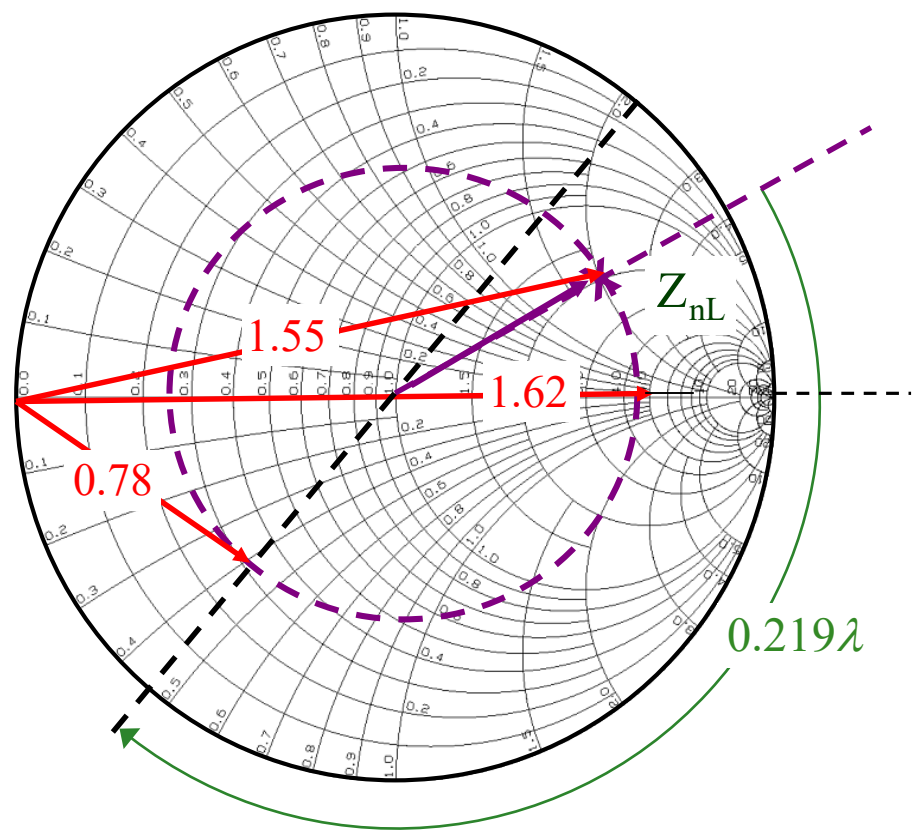
- $V_{load} = 1.55$
- $V_{max} = 1.62$
- $V_{min} = 0.38$
- $V(-0.219\lambda) = 0.78$




Standing Wave Pattern

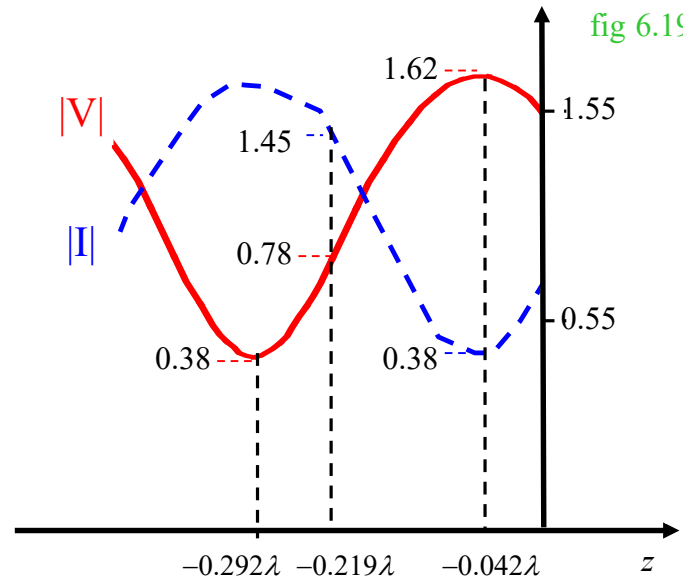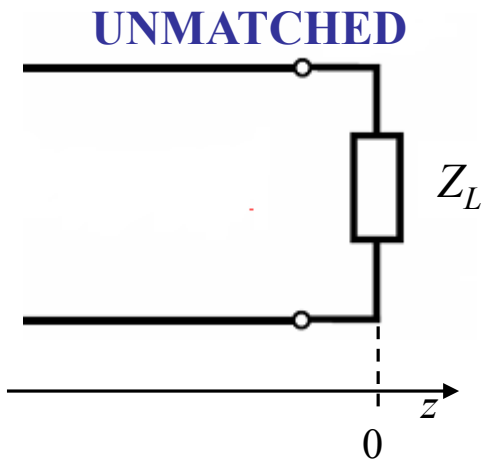

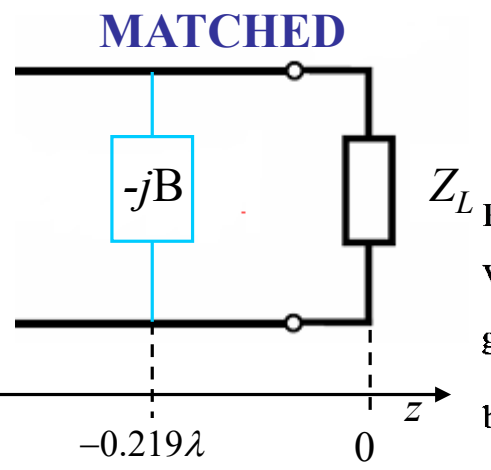
- $V_{load} = 1.55$
- $V_{max} = 1.62$
- $V_{min} = 0.38$
- $V(-0.219\lambda) = 0.78$
- $I_{load} = 0.55$
- $I_{max} = 1.55$
- $I_{min} = 0.38$
- $I(-0.219\lambda) = 1.45$



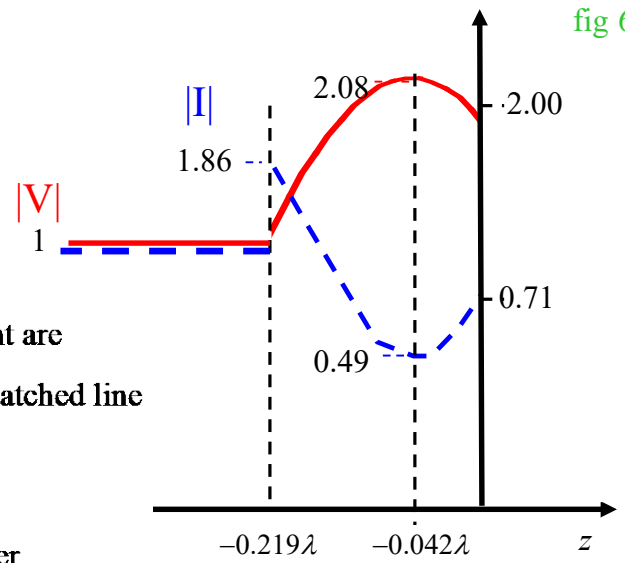For tuned line
 V, I between load and shunt are
 greater than those for unmatched line
 by a factor of $\frac{1}{0.78}$
 for the same incident power.



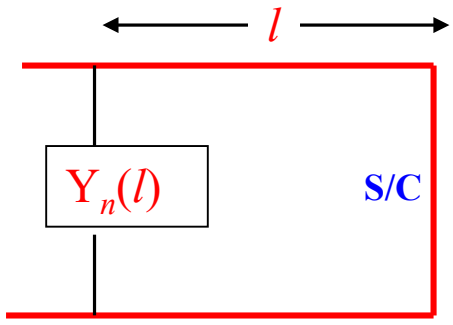For a transmission line \Rightarrow usually add a short circuit section of a line placed perpendicular to the main line.



$$Y_n(l) = -j \cot kl$$

6.36

for kl varying from 0 to π
 \Downarrow
 $0 \leq l \leq \frac{\lambda}{2}$

all possible values
 $-j\infty \leq jB \leq +j\infty$


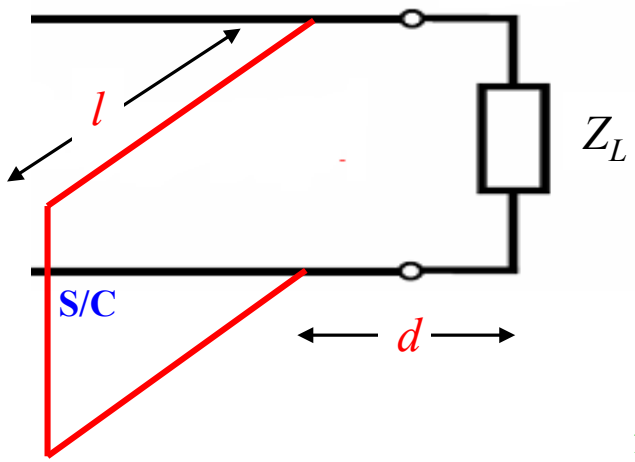



fig 6.20

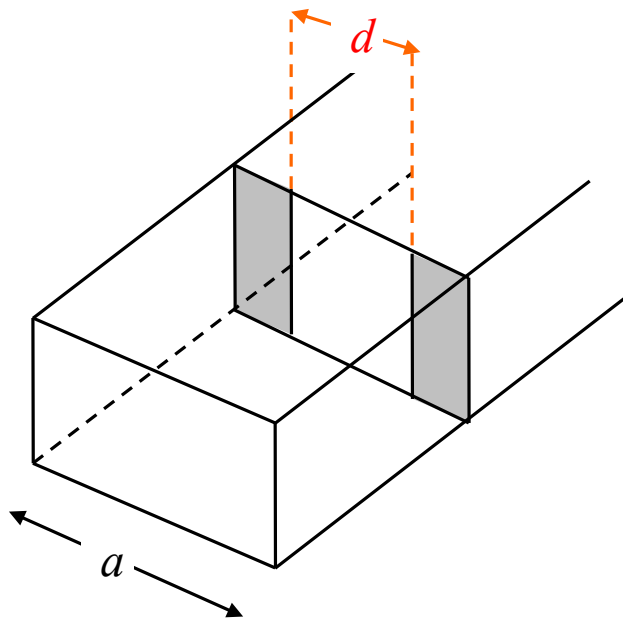For a rectangular waveguide \Rightarrow usually insert a metal iris inside the waveguide.



Inductive Iris

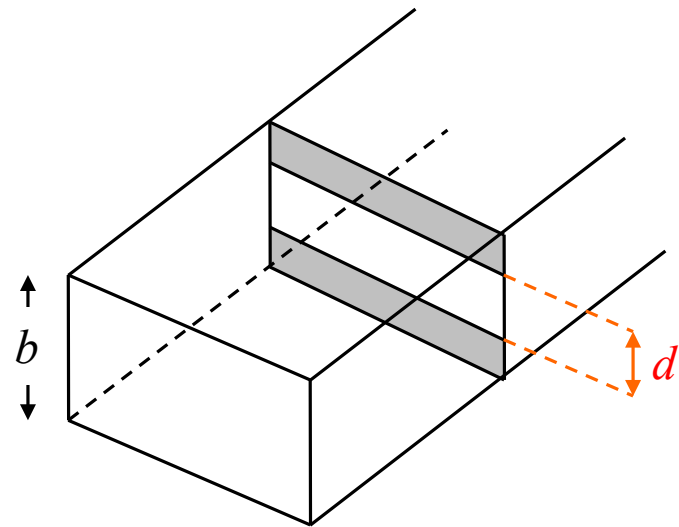
$$B_0 = \frac{-\lambda_g}{a} \cot^2 \left(\frac{\pi d}{2a} \right) \quad 6.37$$



Capacitive Iris

$$B_0 = \frac{4b}{\lambda_g} \ln \left[\csc \left(\frac{\pi d}{2b} \right) \right] \quad 6.38$$

Rotate clockwise from S/C to desired jB

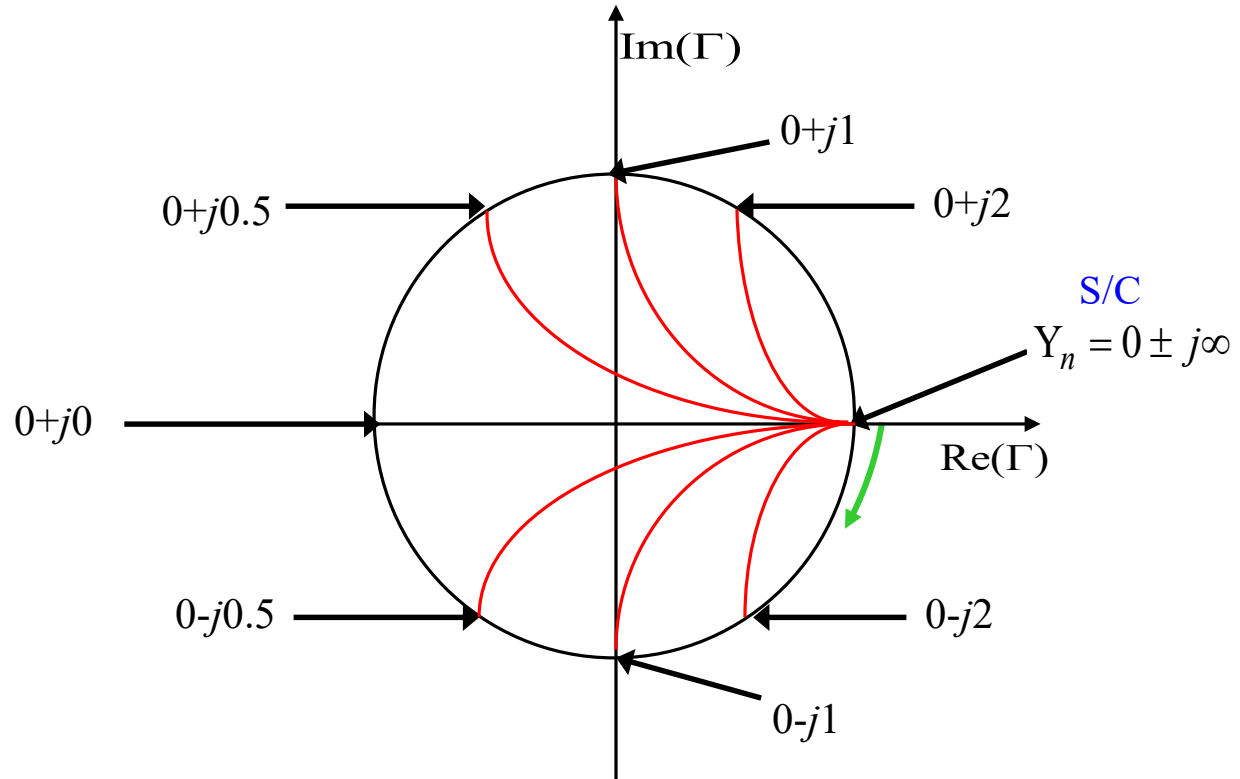

Example: To add

$$jB = -j1.57$$

analytically


$$Y_n = -j \cot kl$$

$$-j1.57 = -j \cot kl$$

$$\cot kl = 1.57 \quad ; \quad \tan kl = \frac{1}{1.57}$$

$$kl = \frac{2\pi}{\lambda} l = 0.567 \text{ [radians]}$$

$$l = 0.0903\lambda$$

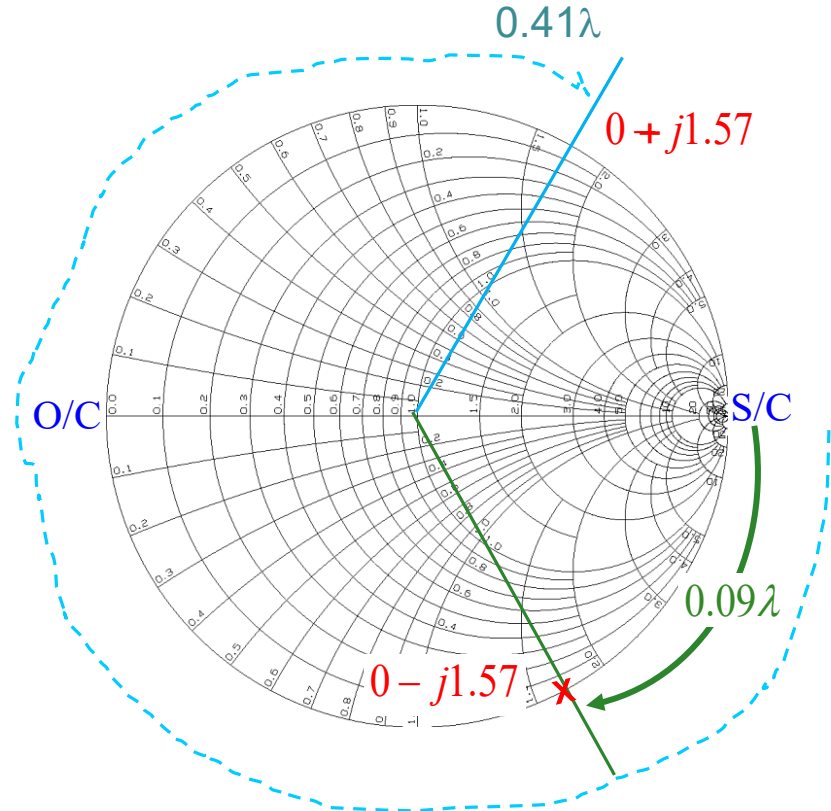

Example: Given $Z_{nL} = 0.5 - j2$ find everything

Smith chart

Analytically

$$\Gamma = 0.82 \angle -51^\circ$$

$$\Gamma = 0.8246 \angle -50.9^\circ$$

$$Y_n = 0.12 + j0.47$$

$$Y_n = 0.1176 + j0.4706$$

$$SWR = 10.5$$

$$SWR = 10.46$$

$$d_1 = 0.131\lambda$$

$$d_1 = 0.1315\lambda$$

$$B_1 = -2.9$$

$$B_1 = -2.915$$


$$l_1 = 0.053\lambda$$

$$l_1 = 0.0526\lambda$$

$$d_2 = 0.227\lambda$$

$$B_2 = +2.9$$

$$l_2 = 0.447\lambda$$

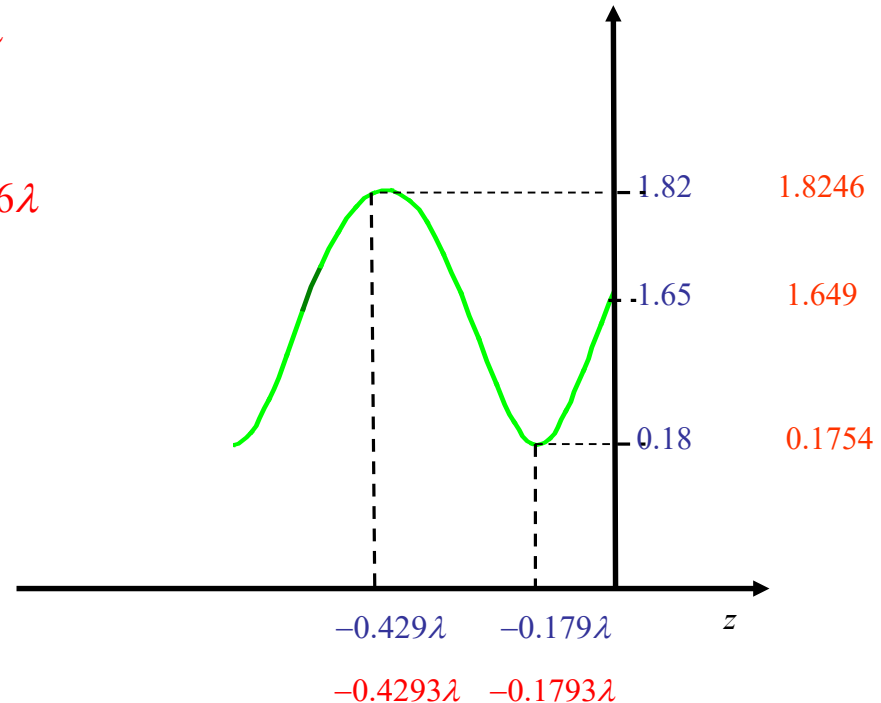


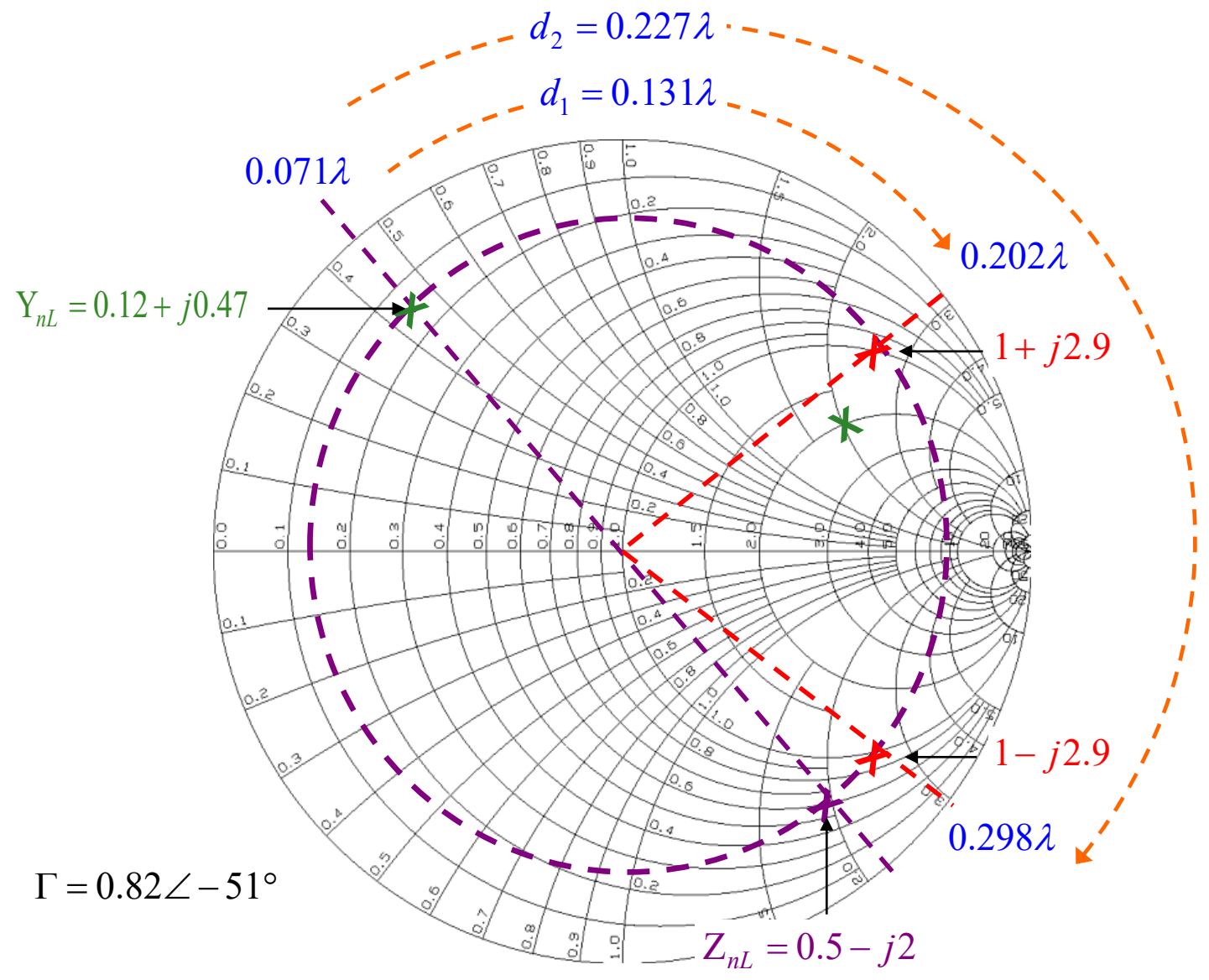


fig 6.18

$$l_1 = (0.303 - 0.25)\lambda$$
$$l_1 = 0.053\lambda$$

Note:
 $l_1 + l_2 = 0.5\lambda$

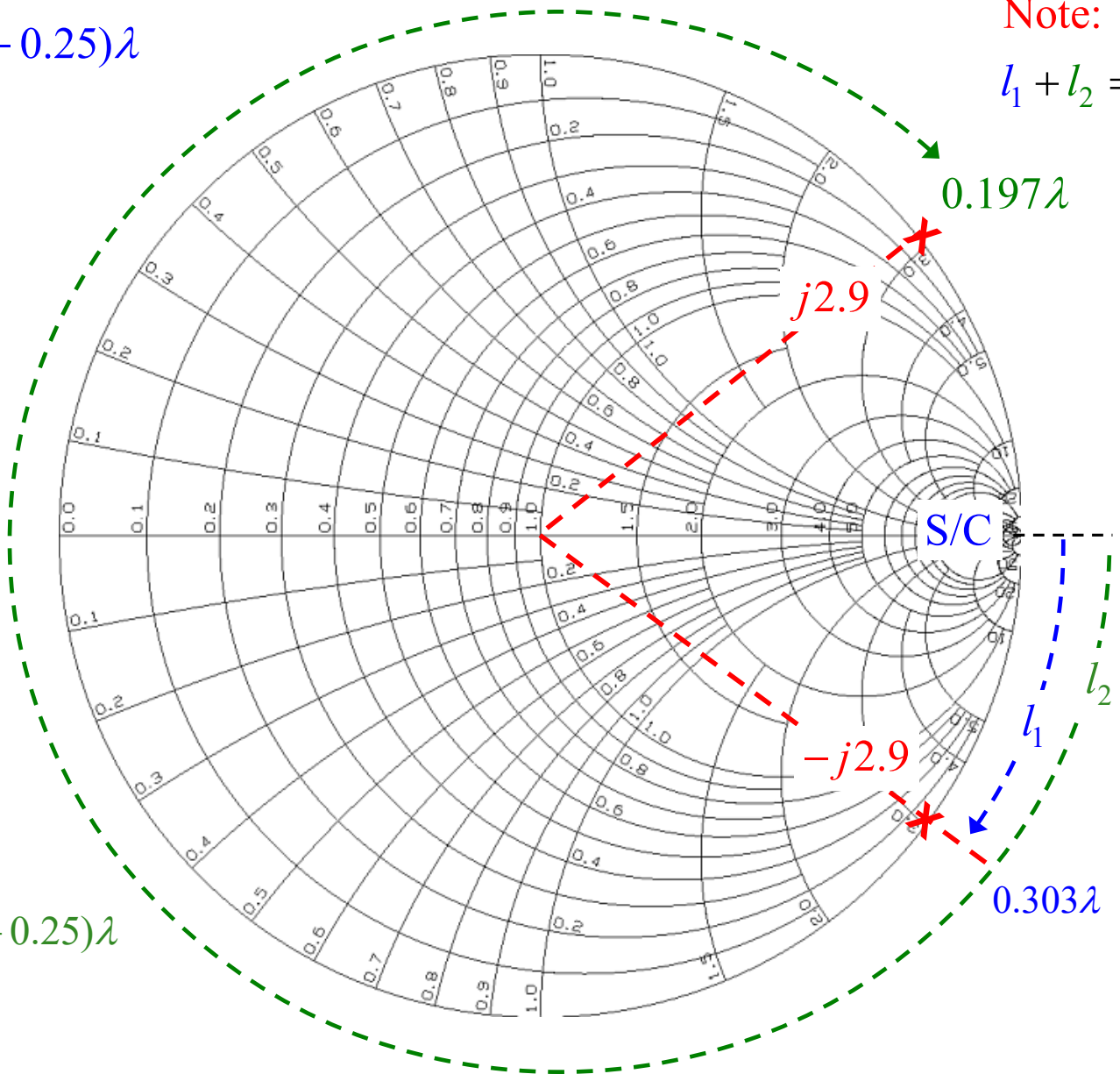

$$l_2 = (0.197 + 0.25)\lambda$$
$$l_2 = 0.447\lambda$$