




Blast From the Past!



Exam 1 Spring 2013

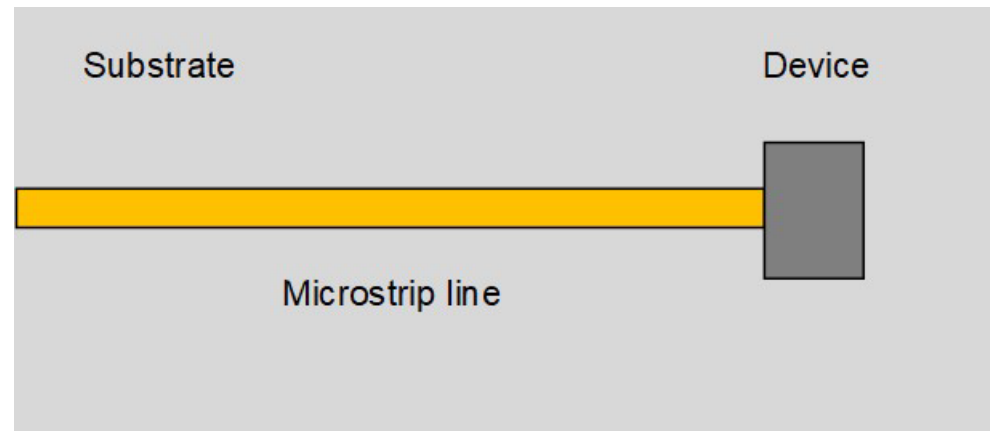Problem 3 (40 pts.)

A transmission line is connected to a certain device on a printed circuit board, operating at 10.0 GHz (a top view is shown below). The device is located at $z = 0$. The microstrip line has a characteristic impedance of 50 $[\Omega]$. The effective relative permittivity of the microstrip line is 1.5.




Blast From the Past!



Exam 1 Spring 2013

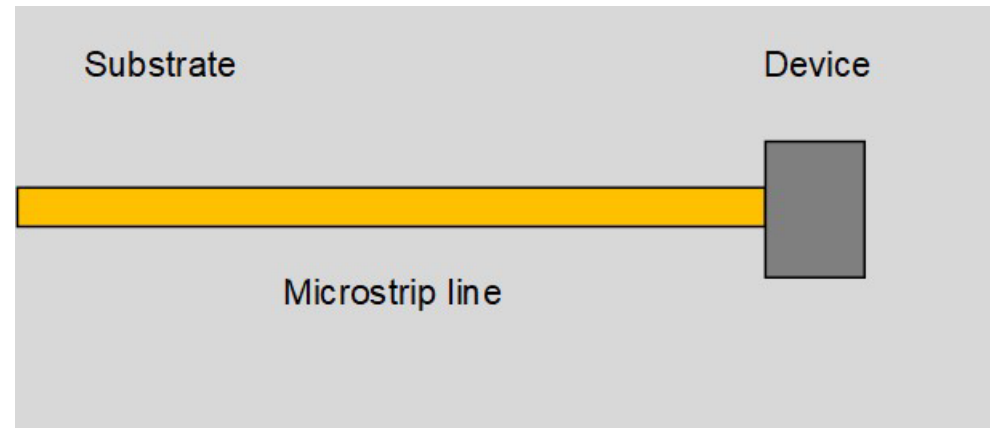- (a) By probing the line, it is found that the voltage on the line has a maximum magnitude of 1.5 volts and a minimum magnitude of 0.5 volts. A voltage minimum occurs at a distance of 0.75 [cm] from the device. Determine the input impedance of the device. Do the calculation exactly (do not use the Smith chart).





Blast From the Past!



Exam 1 Spring 2013

Part (a) At 10.0 GHz we have: $\lambda_0 = 2.9979$ [cm] $\lambda_g = \frac{\lambda_0}{\sqrt{\epsilon_r^{\text{eff}}}} = 2.4478$ [cm]

$$Z_{\text{in}} = Z_0 \left(\frac{1 + \Gamma_L}{1 - \Gamma_L} \right)$$

Therefore: $\Gamma_L = 0.5 e^{j(0.70875)}$

$$\Gamma_L = |\Gamma_L| e^{j\phi}$$

$$Z_{\text{in}} = 50 \left(\frac{1 + 0.5 e^{j(0.70875)}}{1 - 0.5 e^{j(0.70875)}} \right)$$


$$\text{SWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad \Rightarrow \quad |\Gamma_L| = \frac{\text{SWR} - 1}{\text{SWR} + 1}$$

$$Z_{\text{in}} = 76.402 + j(66.305) \text{ } [\Omega]$$

$$\Rightarrow |\Gamma_L| = \frac{3 - 1}{3 + 1} = \frac{1}{2}$$

$$\phi + 2 \left(2\pi \frac{z_{\text{min}}}{\lambda_g} \right) = \pi + 2\pi n \quad (z_{\text{min}} = -0.75 \text{ [cm]})$$
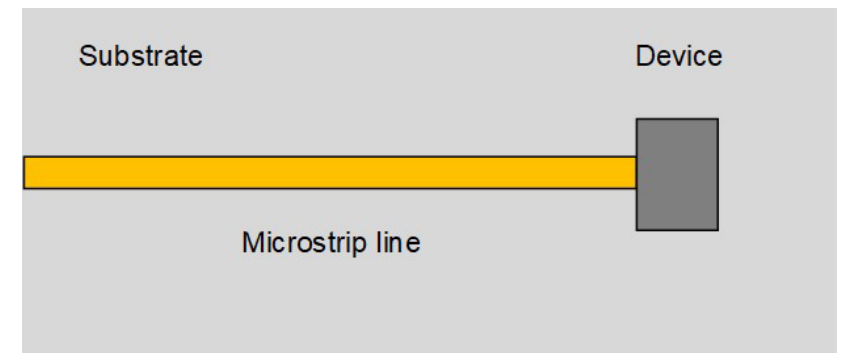
$$\Rightarrow \phi = 0.70875 \text{ [rad]} \quad (\text{any multiple of } 2\pi \text{ can be added on})$$




Blast From the Past!



Exam 1 Spring 2013

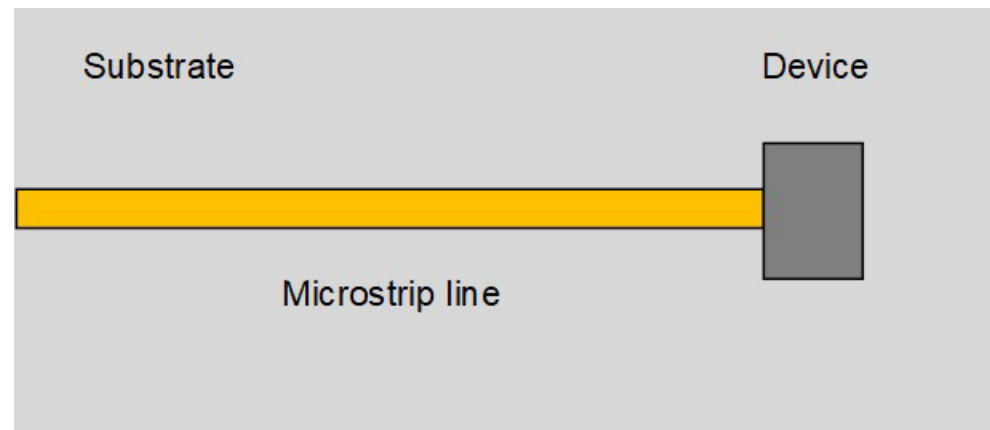- (b) Assume now that a new device is connected to the end of the line, which has an input impedance of $Z_{in} = 100 + j100 \text{ } [\Omega]$. An open-circuited stub line having characteristic impedance of $50 \text{ } [\Omega]$ and an effective permittivity of 1.5 is added at a distance d from the load. Find the distance d and the length of the open-circuited stub line (in cm) to obtain a perfect match seen by an incoming wave that arrives from a generator on the left (not shown). Use the shortest distance d possible. Use the Smith chart to do all calculations. (A Smith chart is included at the end of this problem.)



Blast From the Past!




Exam 1 Spring 2013

Part (b) At 10.0 GHz we have: $\lambda_0 = 2.9979$ [cm] $\lambda_g = \frac{\lambda_0}{\sqrt{\epsilon_r^{\text{eff}}}} = 2.4478$ [cm]

From the Smith chart:

$$d = 0.220\lambda_g = 0.530 \text{ [cm]}$$
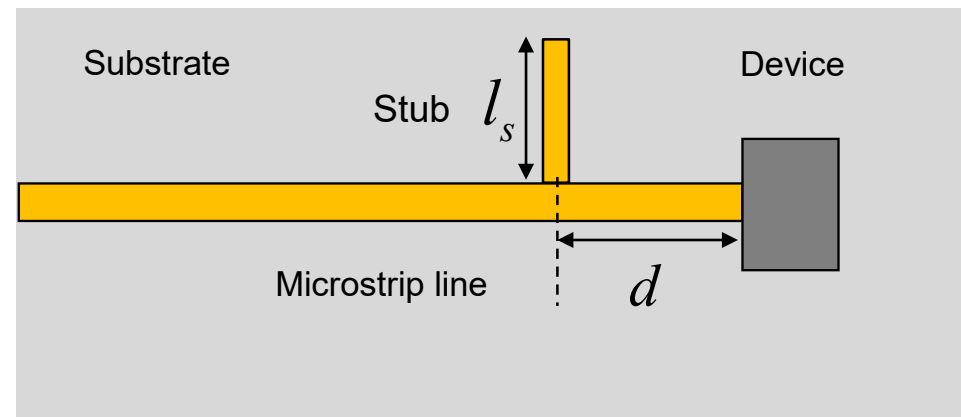
$$l_s = 0.342\lambda_g = 0.837 \text{ [cm]}$$






The Complete Smith Chart

Black Magic Design



Part (b)
Calculation for d

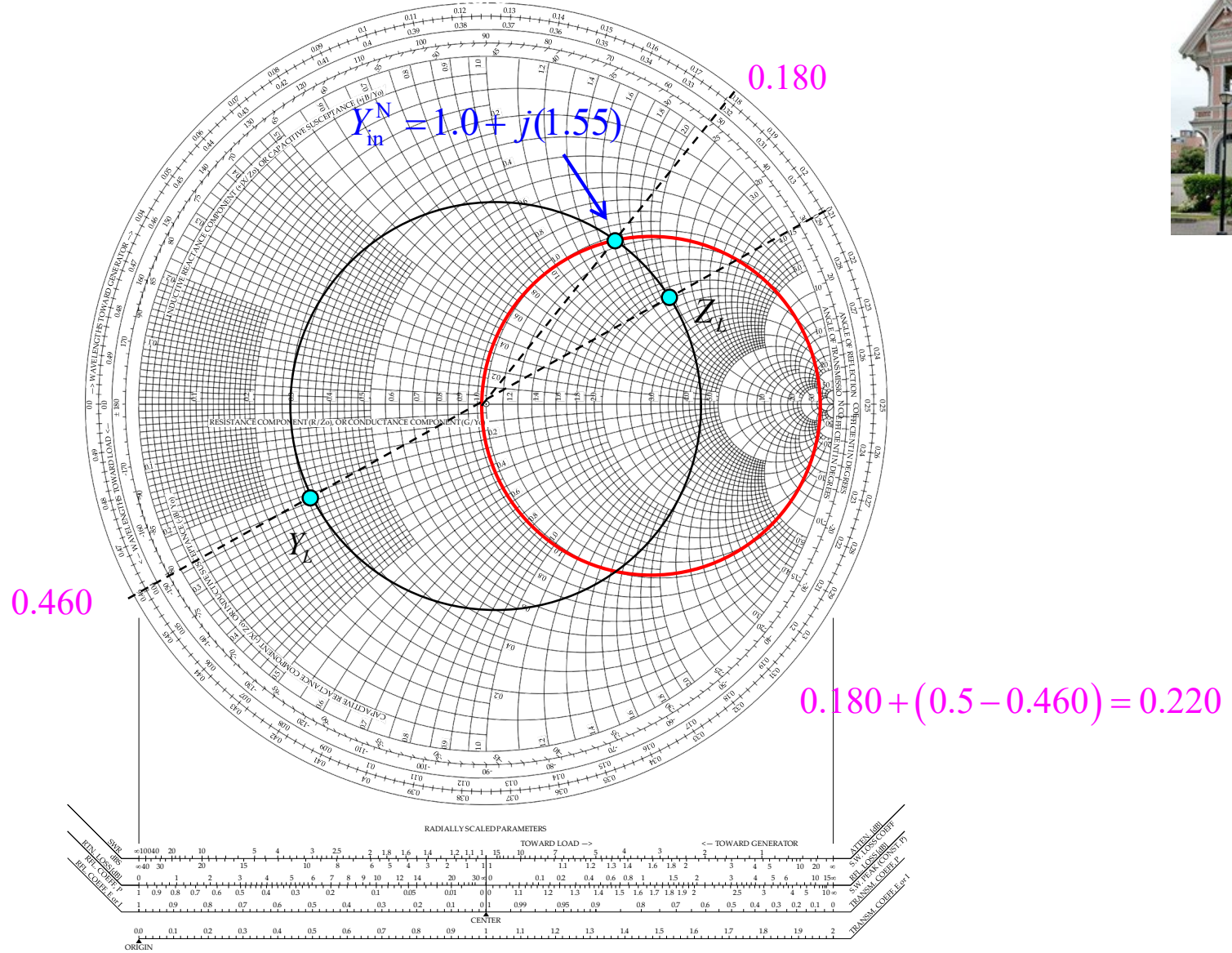




The Complete Smith Chart

Black Magic Design



Part (b)
Calculation for I_s

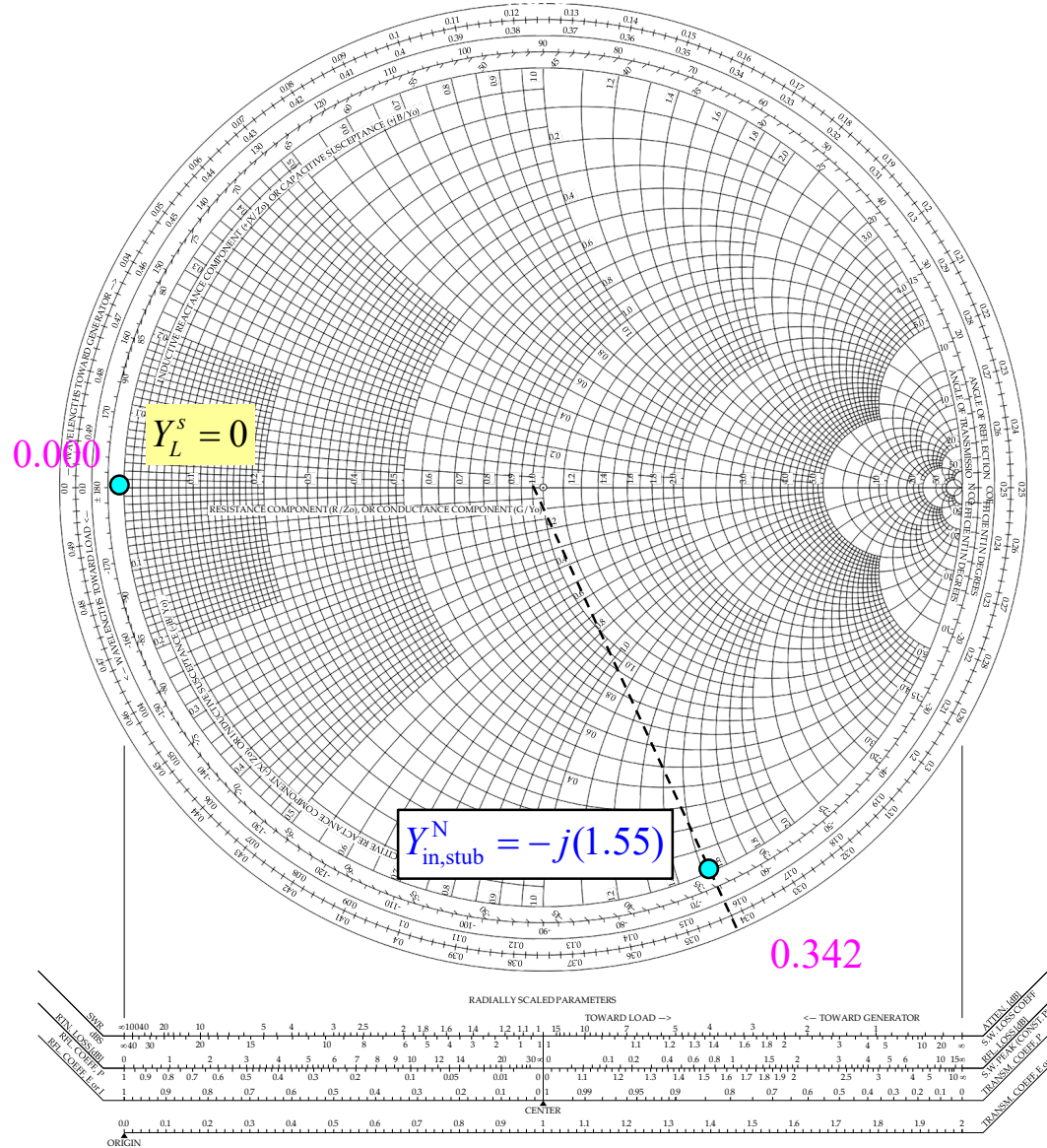


Note:
We are using the Smith chart as an admittance calculator here.

Blast From the Past!



Exam 1
Spring 2013

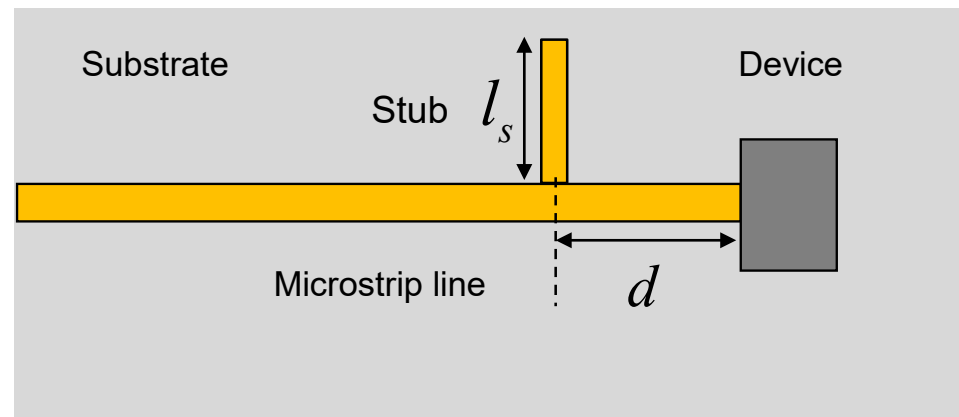- (c) As a continuation of part (b), what is the SWR on the main line between the device and the open-circuited stub? What is the SWR on the open-circuited stub line? What is the SWR on the main line to the left of the open-circuited stub? Do the calculations exactly (do not use the Smith chart).





Blast From the Past!



Exam 1
Spring 2013


Part (c)

SWR between device and stub:

$$\Gamma_L = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = 0.538 + j(0.308)$$

$$SWR = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

$$SWR = 4.26$$

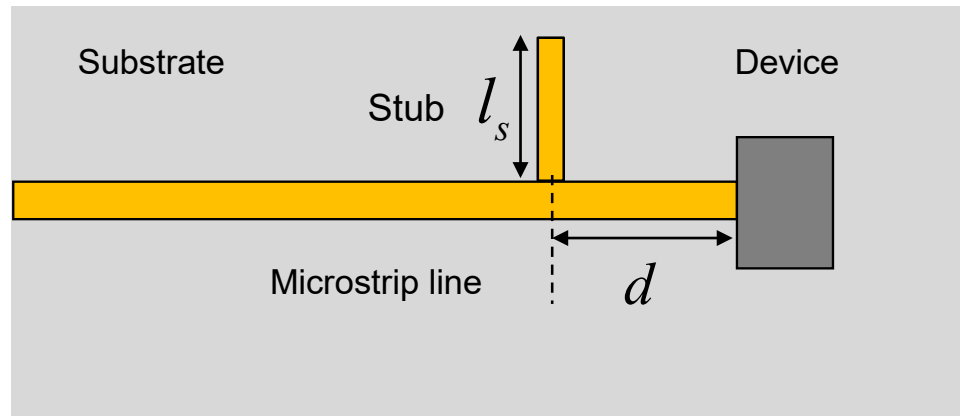


Blast From the Past!



Exam 1
Spring 2013

Part (c)

SWR on stub: $SWR = \infty$

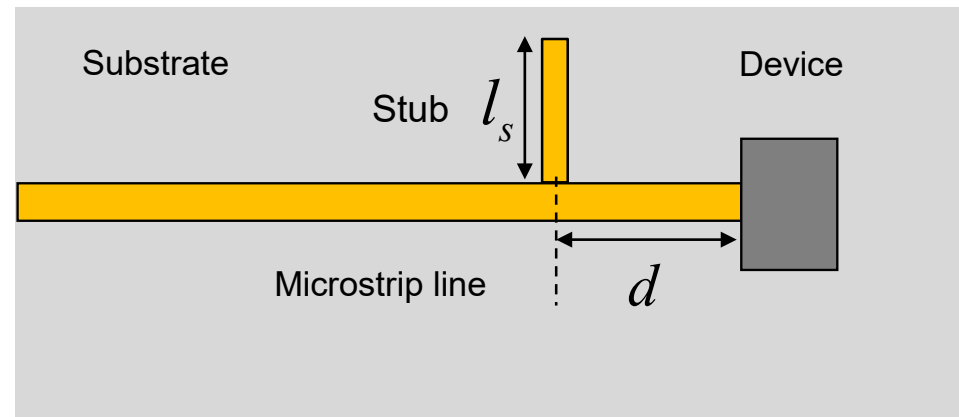

Blast From the Past!



Exam 1
Spring 2013

Part (c)

SWR on feed line: **SWR = 1**

