



Blast From the Past!





Exam 1 Fall 2021

A voltage source is applied at the left end of a transmission line as shown below. The transmission line meets a second transmission line, which is then terminated by a load. At the junction between the two transmission lines a fault occurs, which is modeled by a parallel (shunt) resistor R_F .

A plot of the generator voltage $v_g(t)$ is shown below. The pulse peak is $V_0 = 8$ [V] and the width of the pulse is $W = 3$ [ns].

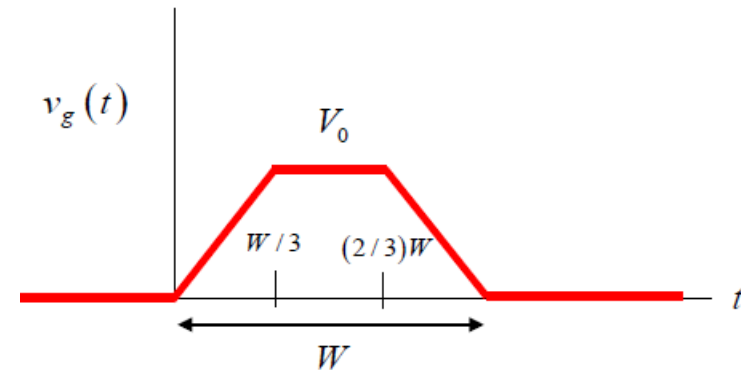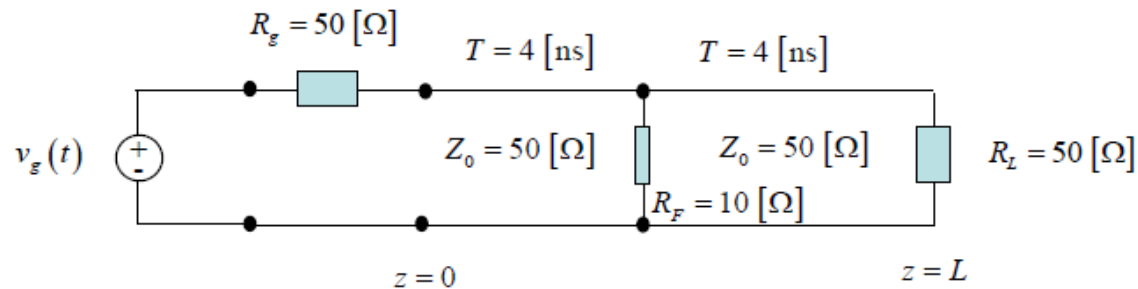
Plot the voltage $v(t)$ measured by an oscilloscope that is connected to the first (left) line at a point halfway down the first line (halfway between the generator and the fault). Plot to a time of 10 [ns]. Use the graph on the next page to make your plot. Label all voltage values on your plot.



Blast From the Past!



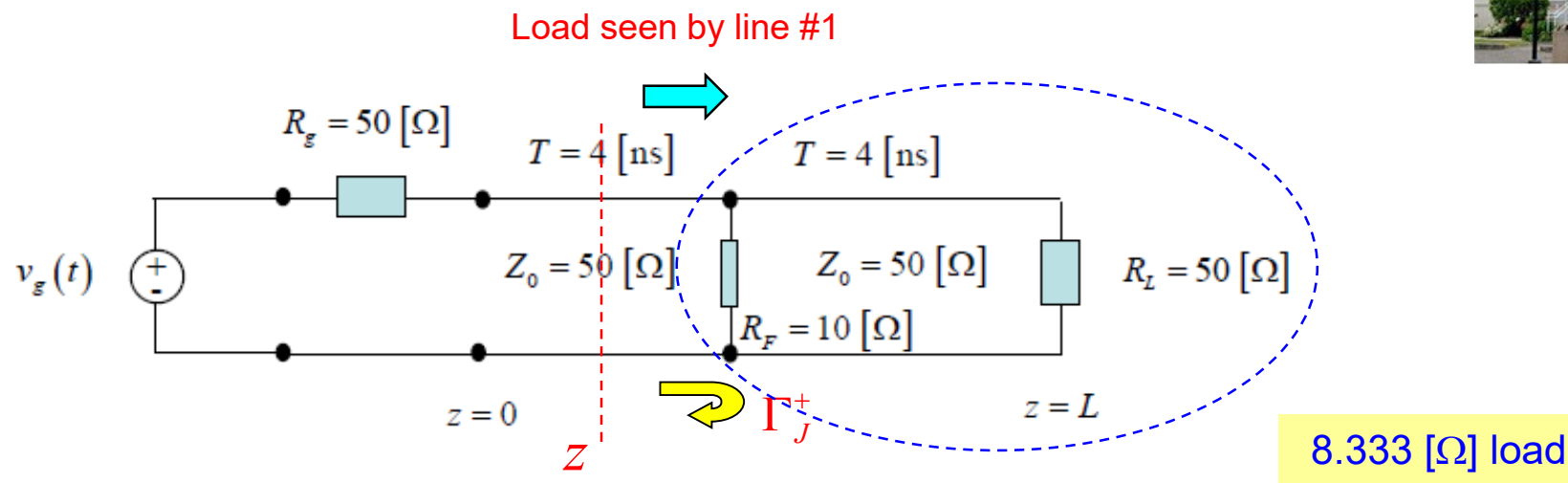Line #1 sees a load of 50 [Ω] in parallel with 10 [Ω], which gives 8.333 [Ω].



$$\Gamma_J^+ = \frac{8.333 - 50}{8.333 + 50} = -0.71429$$


$$\Gamma_g = 0$$

$$A = \frac{1}{2}$$

$$v(z, t) = Av_g(t - z/c_d) + \Gamma_J^+ Av_g(t - L/c_d - (L - z)/c_d) + \cancel{\Gamma_g} \Gamma_J^+ Av_g(t - 2L/c_d - z/c_d) + \cancel{\Gamma_g} \Gamma_J^{+2} Av_g(t - 3L/c_d - (L - z)/c_d) + \dots$$



Blast From the Past!

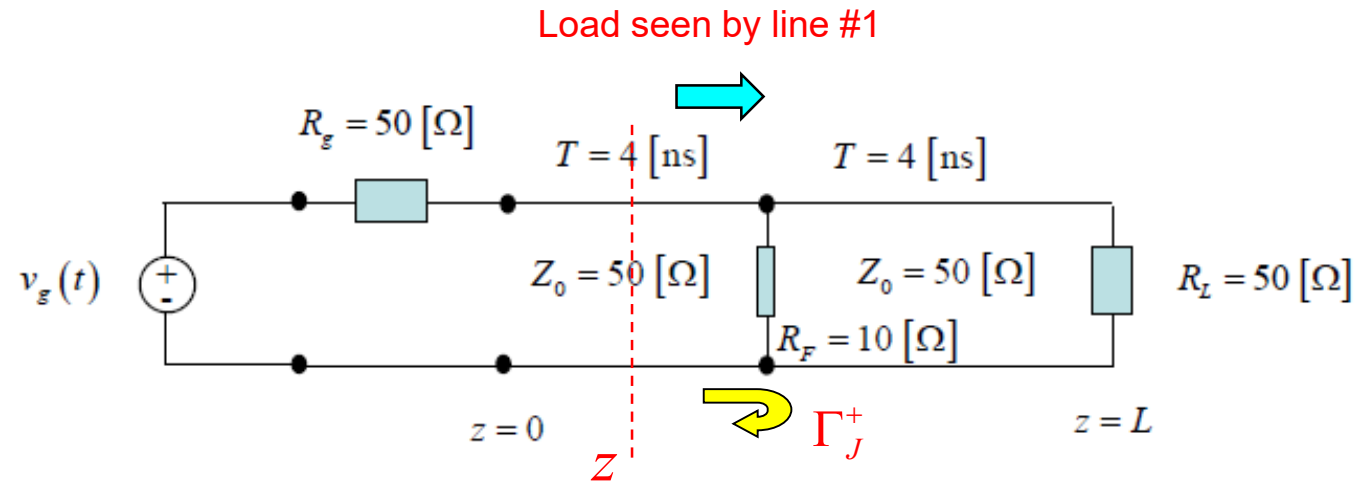

$$v(z, t) = 0.5v_g(t - 2.0[\text{nS}]) + (-0.71429)(0.5)v_g(t - 4.0[\text{nS}] - 2.0[\text{nS}])$$

Blast From the Past!



Plot of voltage

