


Blast From the Past!

Final Exam
Spring 2013

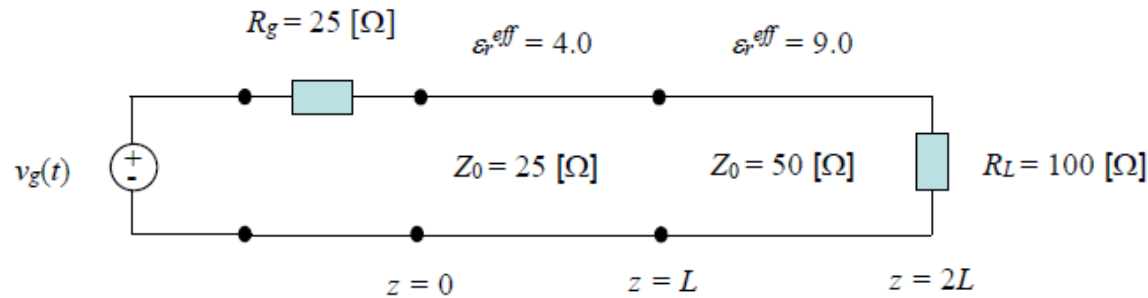Problem 1 (40 pts.)


A step function of amplitude $V_0 = 2.0$ [V] is applied at the input to the transmission line circuit shown below. Each of the two transmission lines has a length L that is 3.0 [m]. Each line has a different effective relative permittivity, however.

- Construct a bounce diagram that extends to a time of 50 [ns], labeling with 10 [ns] divisions on your time scale. (Make your bounce diagram on the next page.)
- Make an accurate “snapshot” trace of the voltage on the line at $t = 35$ [ns]. Make your snapshot trace on the graph shown below, plotting out to $2L$. Label all voltage values on your plot as well as all z values at which the voltage on your plot changes. Also, indicate in which direction (to the left or right) each “wavefront” (point of voltage discontinuity) is moving.





Blast From the Past!

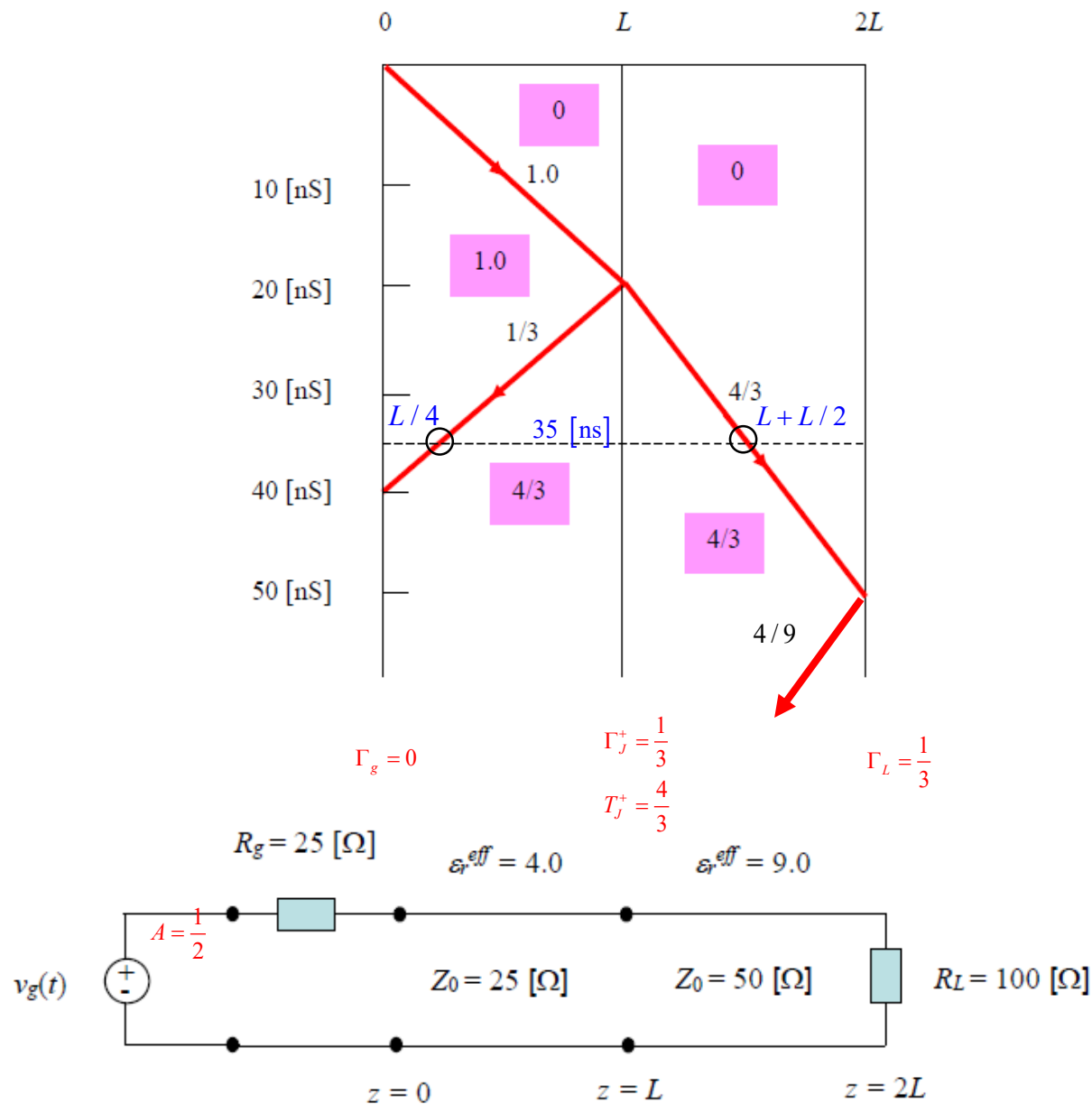

$$c_{d1} = c / \sqrt{4} = 1.5 \times 10^8 \text{ [m/s]}$$

$$c_{d2} = c / \sqrt{9} = 1.0 \times 10^8 \text{ [m/s]}$$

$$T_1 = L / c_{d1} = 20 \text{ [nS]}$$


$$T_2 = L / c_{d2} = 30 \text{ [nS]}$$



Blast From the Past!



Generator voltage

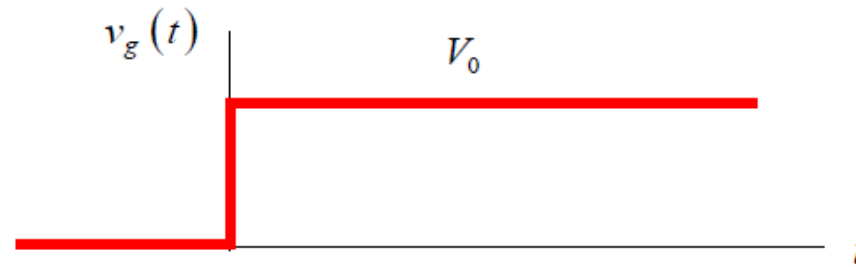

Snapshot of voltage

