

# Blast From the Past!


## Final Exam Fall 2018

### Problem 1 (20 pts.)

A Time Domain Reflectometer (TDR) is being used to determine a fault on a transmission line. The TDR has a voltage generator  $v_g(t)$  that applies a voltage step function with an amplitude of  $V_0 = 2.0$  [V] at the input to the transmission line circuit shown below. The transmission line has a relative permittivity of 2.1. The voltage waveform  $v_0(t)$  that is recorded by the TDR at  $z = 0$  is shown below. A partial short on the line (the fault) is modeled as a parallel resistance  $R_p$  as shown.

Determine the unknown resistance  $R_p$  and the distance  $d$  between the short and the TDR.

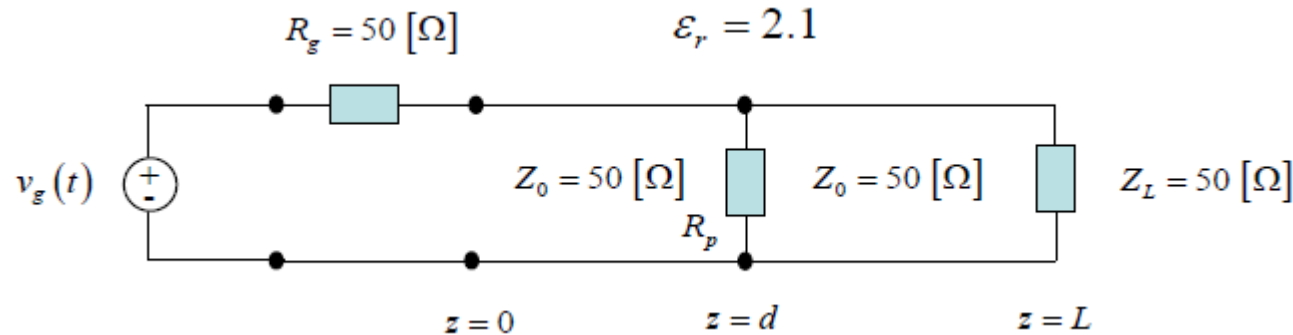Support your answer by constructing a bounce diagram and using it to get the voltage  $v_0(t)$  in terms of  $d$  and  $R_p$ .





# Blast From the Past!




## Measured Waveform

( $z = 0$ )

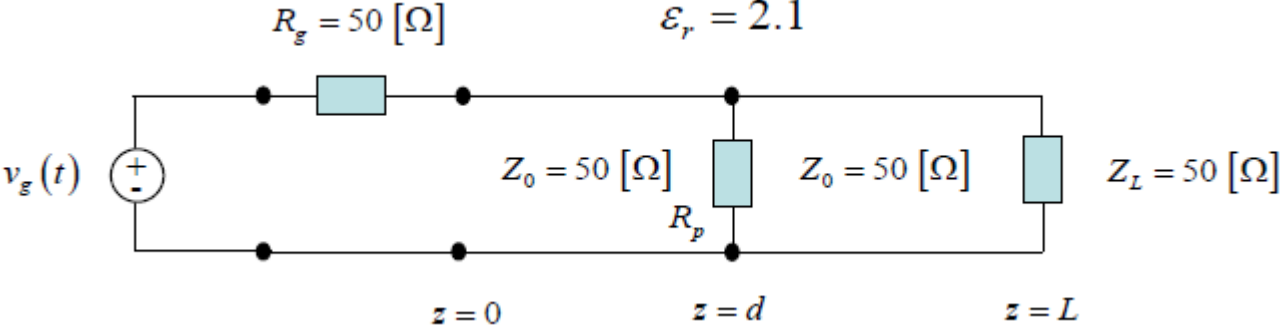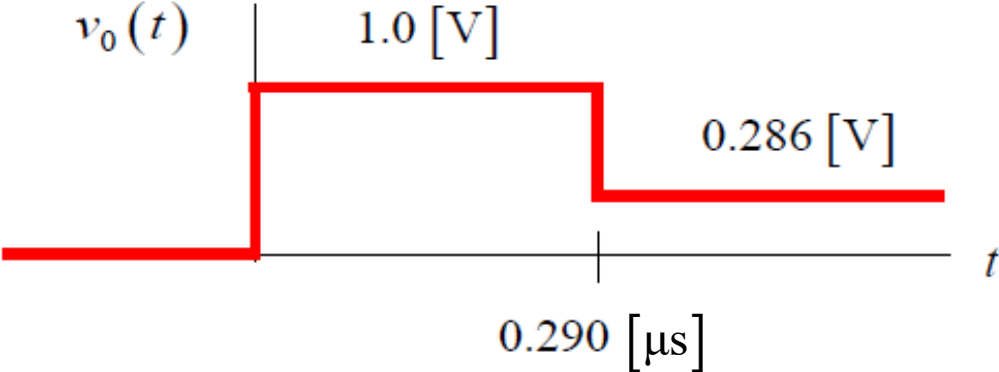




# Blast From the Past!

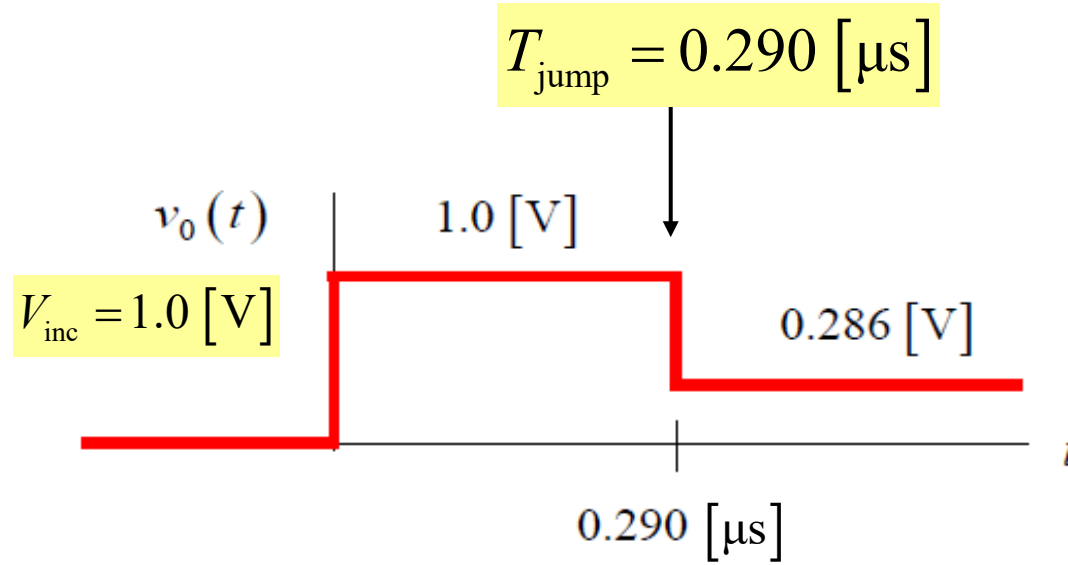

$$T_{\text{jump}} = \frac{2d}{c_d} = \frac{2d}{c/\sqrt{\epsilon_r}} = d \left( \frac{2}{c} \sqrt{\epsilon_r} \right) = d (9.6676 \times 10^{-9}) \quad (\text{solve for } d)$$

$$d = 30.0 \text{ } [\text{m}]$$

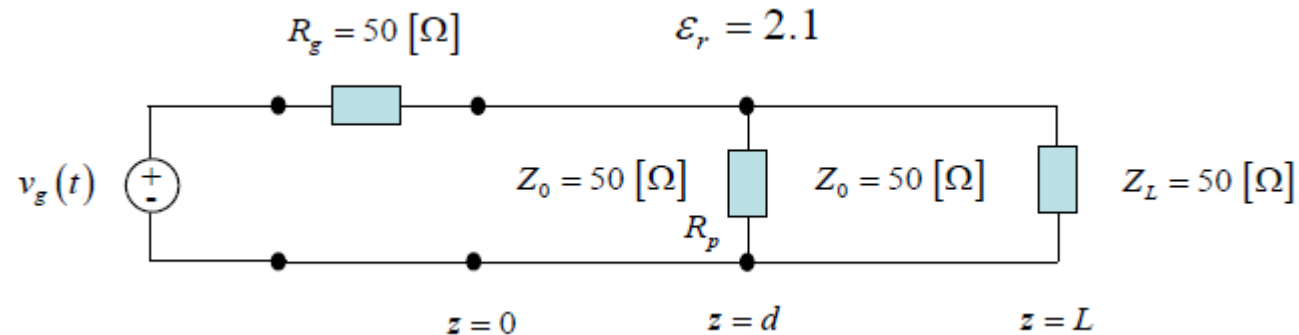

# Blast From the Past!



(See next slide for bounce diagram.)

$$(V_{\text{inc}})(1.0 + \Gamma_J^+) = 0.286$$



$$(1.0)(1.0 + \Gamma_J^+) = 0.286$$





$$\Gamma_J^+ = -0.714$$

$$\Gamma_J^+ = \frac{(50 \parallel R_p) - 50}{(50 \parallel R_p) + 50}$$


$$50 \parallel R_p = \frac{50R_p}{50 + R_p}$$

$$\frac{\left(\frac{50R_p}{50 + R_p}\right) - 50}{\left(\frac{50R_p}{50 + R_p}\right) + 50} = -7.14 \quad (\text{solve for } R_p)$$

$$R_p = 10 \text{ } [\Omega]$$

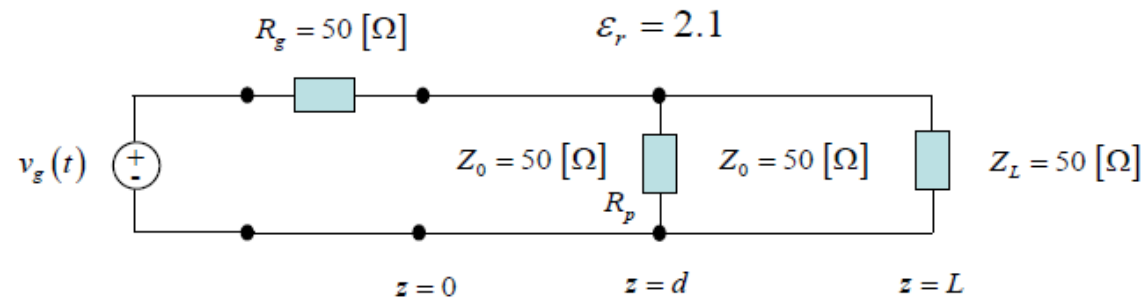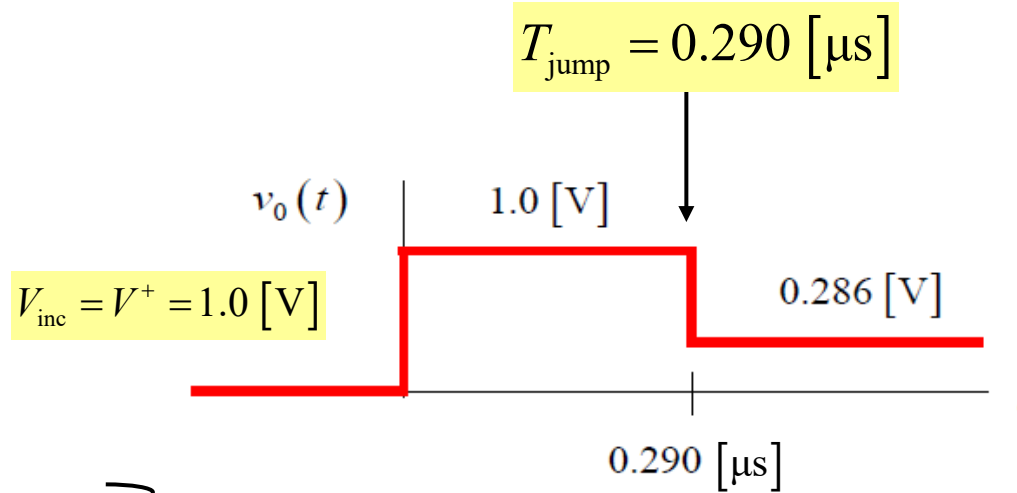

# Blast From the Past!

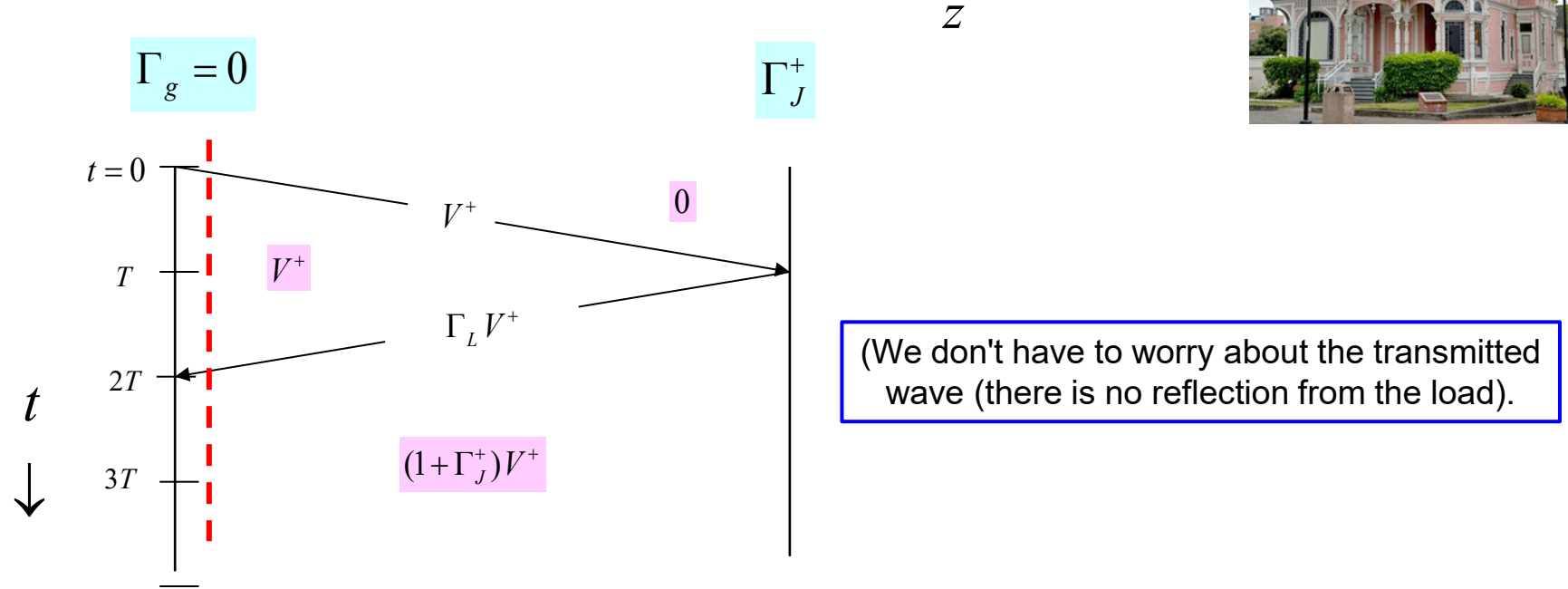

$T_{\text{jump}} = 2T$

