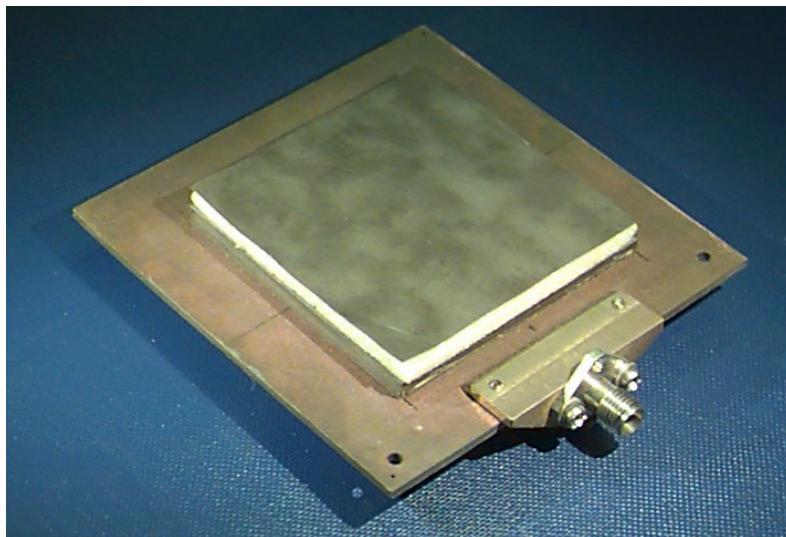


# ECE 6345

## Fall 2024

Prof. David R. Jackson  
ECE Dept.




## Notes 2

# Overview

In this set of notes we discuss the CAD circuit model of the microstrip antenna.


- Discuss complex resonance frequency
- Derive formula for  $Q$
- Derive formula for input impedance
- Derive formula for impedance bandwidth

# CAD Model of Microstrip Antennas

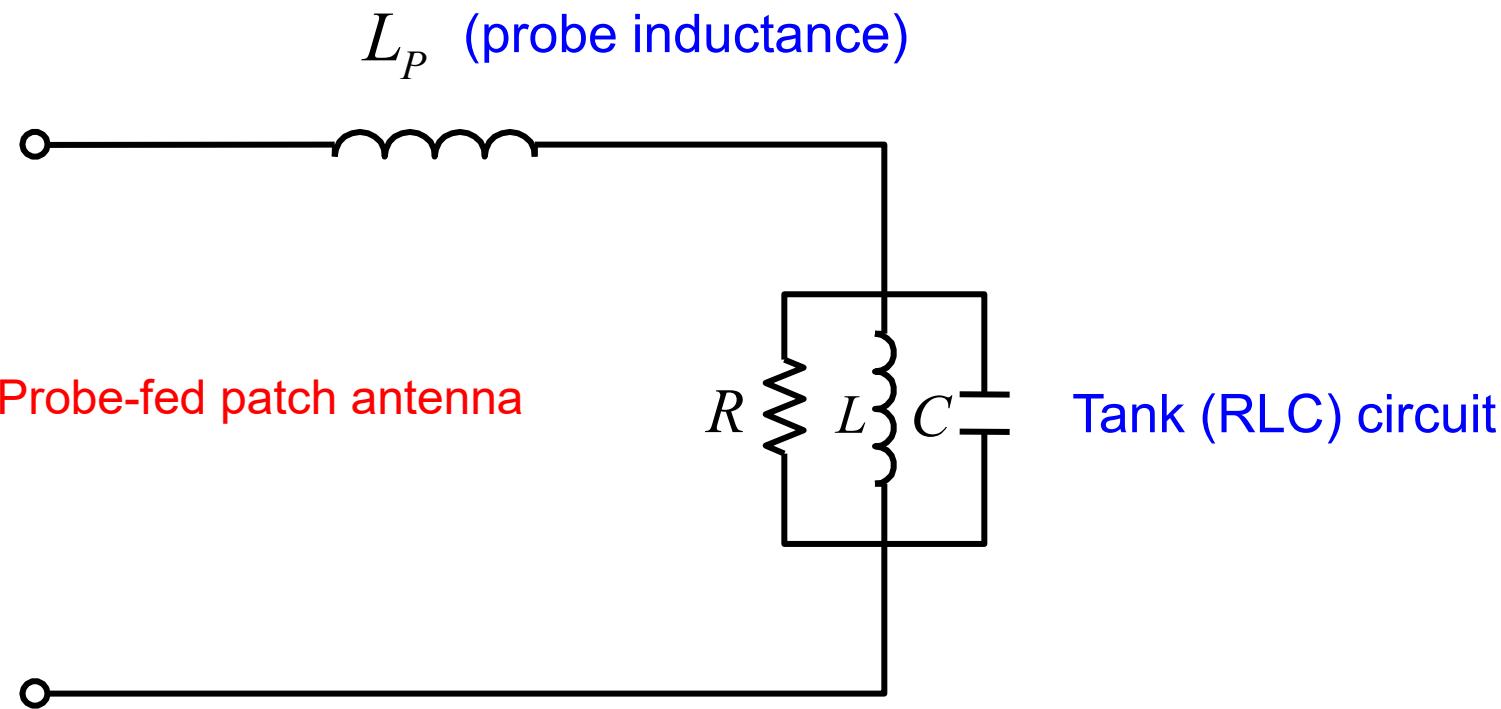

The circuit model is justified from the eigenfunction method in the cavity model, discussed later.
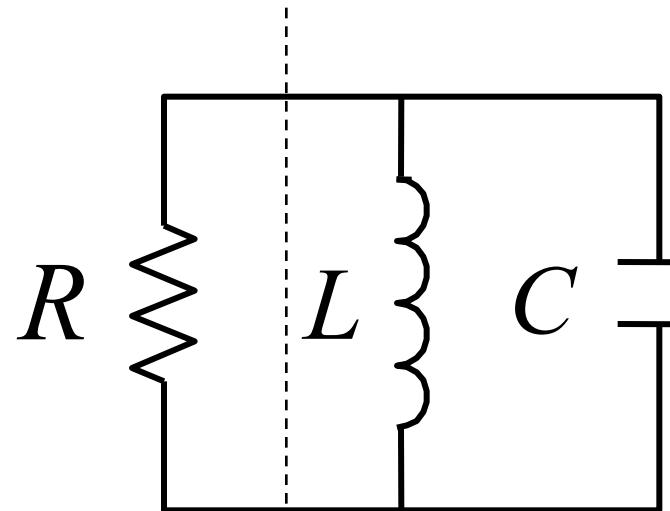
# Tank Circuit: complex resonance frequency



+  
 $V$   
-

$$G \equiv \frac{1}{R}$$

$$\overleftarrow{Y} \quad \longleftrightarrow \quad \overrightarrow{Y}$$

Transverse Resonance Equation (TRE):

$$\overleftarrow{Y} = -\overrightarrow{Y}$$

The complex resonance frequency is denoted as  $\omega_0$ .

# Complex Resonance Frequency (cont.)

TRE:

$$G = - \left[ j\omega_0 C + \frac{1}{j\omega_0 L} \right]$$

$$\Rightarrow j\omega_0 L G = \omega_0^2 L C - 1$$

$$\Rightarrow \omega_0^2 (LC) + \omega_0 (-jLG) + (-1) = 0$$

$$\rightarrow \omega_0 = \frac{jLG \pm \sqrt{-L^2 G^2 + 4LC}}{2LC}$$

$$G \rightarrow 0, \quad \omega_0 \rightarrow \frac{1}{\sqrt{LC}} \quad \text{so choose + sign}$$

# Complex Resonance Frequency (cont.)

$$\omega_0 = j \frac{1}{2} \left( \frac{1}{RC} \right) + \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{1}{4} \frac{L}{R^2 C}}$$

Denote:  $\omega_0 = \omega'_0 + j\omega''_0$

$$\omega'_0 = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{1}{4} \frac{L}{R^2 C}}$$

$$\omega''_0 = \frac{1}{2} \left( \frac{1}{RC} \right)$$

# Complex Resonance Frequency (cont.)

$$\omega'_0 = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{1}{4} \frac{L}{R^2 C}}$$
$$\omega''_0 = \frac{1}{2} \left( \frac{1}{RC} \right)$$


Assume  $R \gg \sqrt{\frac{L}{C}}$  (a good resonator)

We then have:

$$\omega'_0 \approx \frac{1}{\sqrt{LC}}$$

$$\omega''_0 = \frac{1}{2} \left( \frac{1}{RC} \right)$$

# Natural Response (no source)

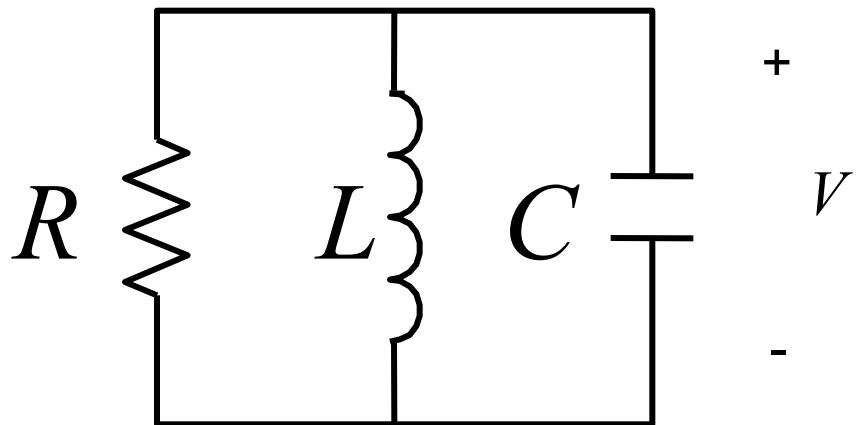

The complex resonance frequency is  $\omega_0$ .

$$\omega_0 = \omega'_0 + j\omega''_0$$


In the time domain:  $v(t) = \text{Re}(V e^{j\omega_0 t})$  (Assume phasor voltage  $V = 1$ )

so


$$v(t) = \text{Re}(e^{j\omega'_0 t} e^{-\omega''_0 t}) = e^{-\omega''_0 t} \cos(\omega'_0 t)$$
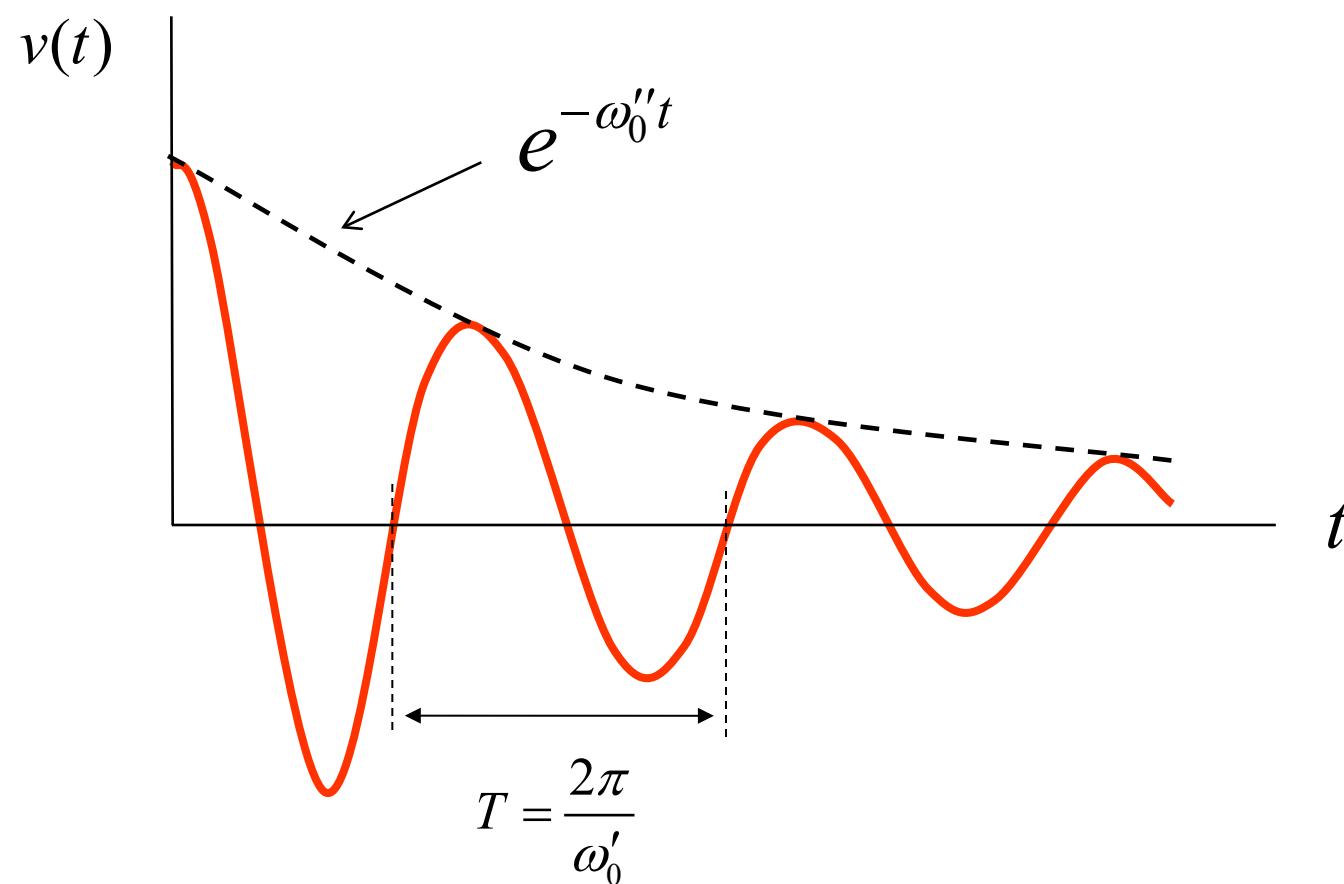
# Natural Response (cont.)

$$v(t) = e^{-\omega_0'' t} \cos(\omega_0' t)$$



# Stored Energy

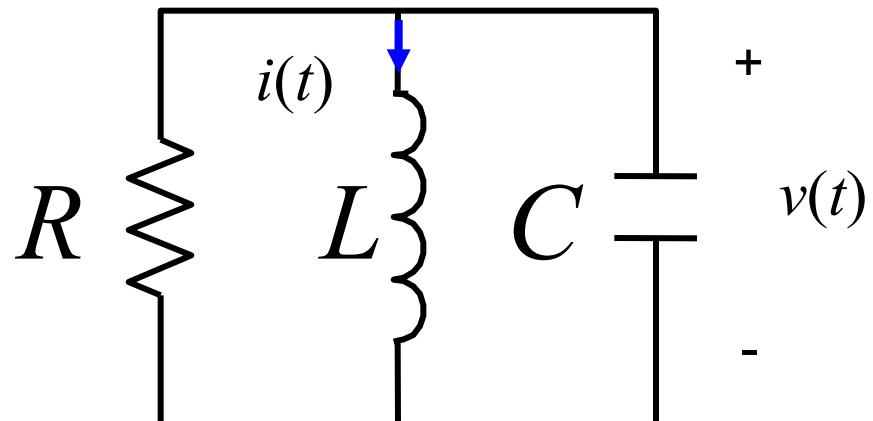

For the capacitor:

$$\begin{aligned} U_E(t) &= \frac{1}{2} Cv^2(t) \\ &= \frac{1}{2} Ce^{-2\omega_0''t} \cos^2(\omega_0't) \end{aligned}$$

(Assume  $V = 1$ )


For the inductor:

$$I = \frac{V}{j\omega_0 L} = \frac{1}{j\omega_0 L} \approx \frac{1}{j\omega'_0 L}$$

Therefore,

$$i(t) = \operatorname{Re}(I e^{j\omega_0 t}) \approx \frac{1}{\omega'_0 L} \operatorname{Re}\left(\frac{1}{j} e^{-\omega_0'' t} e^{+j\omega_0' t}\right) = \frac{1}{\omega'_0 L} e^{-\omega_0'' t} \sin(\omega_0' t)$$

# Stored Energy (cont.)

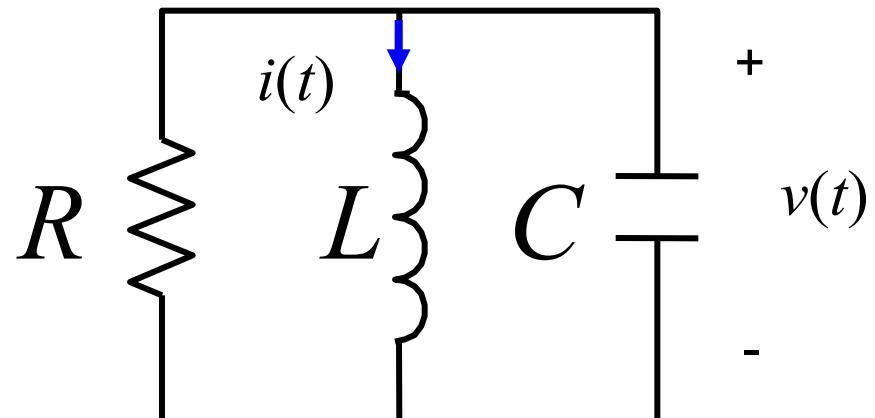

$$\begin{aligned} U_H(t) &= \frac{1}{2} L i^2(t) \\ &= \frac{1}{2} L \left( \frac{1}{\omega'_0 L} \right)^2 e^{-2\omega''_0 t} \sin^2(\omega'_0 t) \\ &= \frac{1}{2} C e^{-2\omega''_0 t} \sin^2(\omega'_0 t) \end{aligned}$$

Note:  $\langle U_E(t) \rangle = \langle U_H(t) \rangle = \frac{1}{4} C e^{-2\omega''_0 t}$


Also, note that

$$U_S(t) = U_E(t) + U_H(t) = \frac{1}{2} C e^{-2\omega''_0 t}$$

# Stored Energy (cont.)

Hence, we have:

$$U_S(t) = U_S(0) e^{-2\omega_0'' t}$$

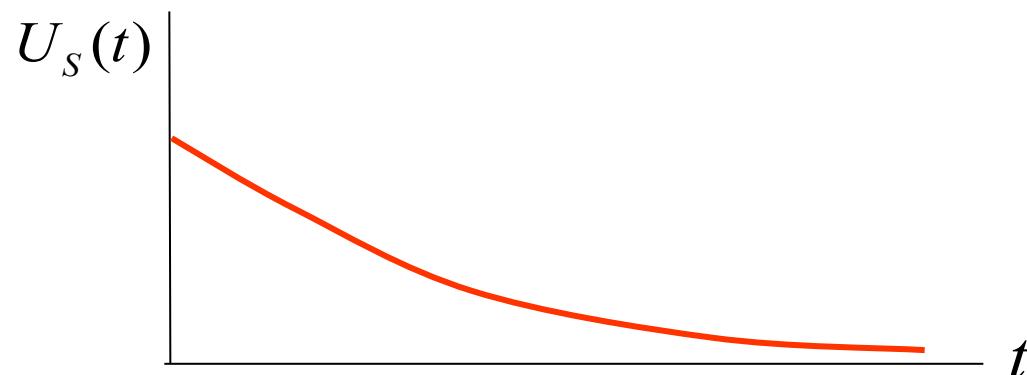

# *Q* of Cavity

$$Q \equiv 2\pi \left( \frac{U_S}{U_D^T} \right)$$

$U_S$  = stored energy

$U_D^T$  = energy dissipated per cycle

$$Q = \frac{2\pi}{T} \left( \frac{U_S}{U_D^T / T} \right) \quad \text{or}$$

$$Q \equiv \omega_0' \left( \frac{U_S}{P_D^{\text{ave}}} \right)$$

$P_D^{\text{ave}}$  = average power dissipated

(This includes radiation loss.)

# ***Q* of Cavity (cont.)**

Power dissipation in circuit:  $P_D(t) = G v(t)^2$

$$Q = \omega'_0 \left( \frac{\frac{1}{2} C e^{-2\omega''_0 t}}{\langle G v(t)^2 \rangle} \right) = \omega'_0 \left( \frac{\frac{1}{2} C e^{-2\omega''_0 t}}{G \langle e^{-2\omega''_0 t} \cos^2(\omega'_0 t) \rangle} \right)$$

$$= \omega'_0 \left( \frac{\frac{1}{2} C e^{-2\omega''_0 t}}{\frac{1}{2} G e^{-2\omega''_0 t}} \right)$$

$$= \frac{\omega'_0 C}{G}$$

$$= \omega'_0 R C$$

**Note :**

$$\begin{aligned} & \langle e^{-2\omega''_0 t} \cos^2(\omega'_0 t) \rangle \\ & \approx e^{-2\omega''_0 t} \langle \cos^2(\omega'_0 t) \rangle \\ & = e^{-2\omega''_0 t} \left( \frac{1}{2} \right) \end{aligned}$$

# *Q* of Cavity (cont.)

We then have:

$$Q = \omega'_0 RC = \frac{1}{\omega'_0} \left( \frac{R}{L} \right) = R \sqrt{\frac{C}{L}}$$

Recall that  $\omega'_0 \approx \frac{1}{\sqrt{LC}}$        $\omega''_0 = \frac{1}{2} \left( \frac{1}{RC} \right)$

Hence

$$\omega_0 = \omega'_0 + j\omega''_0 \approx \omega'_0 \left( 1 + j \frac{1}{2} \left( \frac{1}{RC} \right) \frac{1}{\omega'_0} \right)$$

Next, put this in terms of  $Q$ .

# *Q* of Cavity (cont.)

$$\omega_0 = \omega'_0 + j\omega''_0 = \omega'_0 \left( 1 + j \frac{1}{2} \left( \frac{1}{RC} \right) \frac{1}{\omega'_0} \right) \approx \omega'_0 \left( 1 + j \frac{1}{2} \left( \frac{1}{RC} \right) \sqrt{LC} \right) = \omega'_0 \left( 1 + j \frac{1}{2} \left( \frac{1}{R} \right) \sqrt{\frac{L}{C}} \right)$$

Hence

$$\omega_0 \approx \omega'_0 \left( 1 + j \frac{1}{2Q} \right) \quad \left( \text{Recall: } Q = \omega'_0 RC = \frac{1}{\omega'_0} \left( \frac{R}{L} \right) = R \sqrt{\frac{C}{L}} \right)$$

so

$$\omega''_0 = \frac{1}{2Q} \omega'_0$$

or

$$Q = \frac{1}{2} \frac{\omega'_0}{\omega''_0}$$

# *Q* of Cavity (Cont.)

We can thus write

$$v(t) = e^{-\left(\frac{\omega_0'}{2Q}\right)t} \cos(\omega_0' t)$$


$$U_S(t) = U_S(0) e^{-\left(\frac{\omega_0'}{Q}\right)t}$$

# Input Impedance

$$Y_{RLC} = G + j\omega C + \frac{1}{j\omega L}$$

$$\begin{aligned} Z_{RLC} &= \frac{1}{G + j\omega C + \frac{1}{j\omega L}} \\ &= \frac{R}{1 + j\omega RC + \frac{R}{j\omega L}} \\ &= \frac{R}{1 + j\left(\omega RC - \frac{R}{\omega L}\right)} \end{aligned}$$

The probe inductance is neglected here.

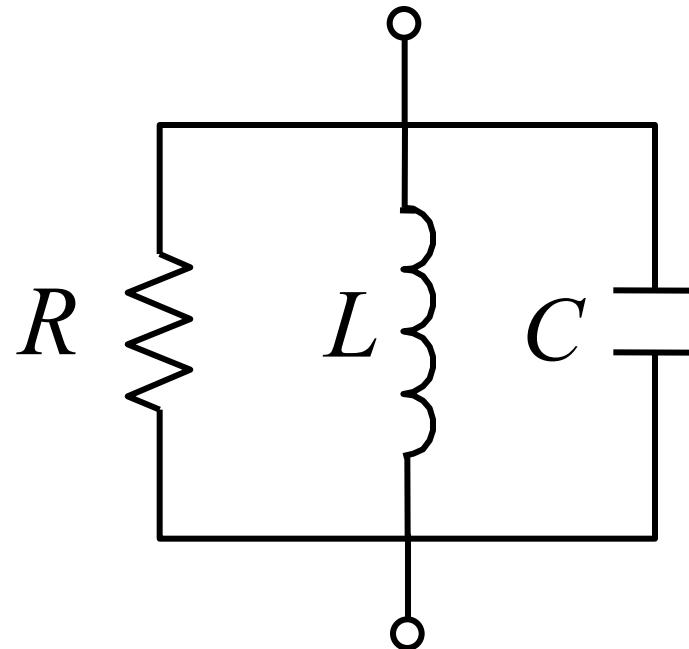

# Input Impedance (cont.)

We can write this as:

$$\begin{aligned} Z_{RLC} &= \frac{R}{1 + j \left( \frac{\omega}{\omega'_0} (\omega'_0 R C) - \frac{R}{\omega'_0 L} \left( \frac{\omega'_0}{\omega} \right) \right)} \\ &= \frac{R}{1 + j \left( \frac{\omega}{\omega'_0} Q - Q \left( \frac{\omega'_0}{\omega} \right) \right)} \end{aligned}$$

Define

$$f_r \equiv \frac{f}{f_0} = \frac{\omega}{\omega'_0}$$

where

$$f_0 \equiv \frac{\omega'_0}{2\pi}$$

(real resonance frequency)

Then we have:

$$Z_{RCL} = \frac{R}{1 + j Q \left( f_r - \frac{1}{f_r} \right)}$$

# Input Impedance (cont.)

Define:

$$F \equiv f_r - \frac{1}{f_r}$$

$$\begin{aligned} F &= \frac{1}{f_r} (f_r^2 - 1) \\ &= \frac{1}{f_r} (f_r - 1)(f_r + 1) \\ &\approx 2(f_r - 1) \text{ for } f_r \approx 1 \end{aligned}$$

Hence, we have:

$$Z_{RLC} = \frac{R}{1 + jQF} = \frac{R}{1 + jQ\left(f_r - \frac{1}{f_r}\right)} \approx \frac{R}{1 + j2Q(f_r - 1)}$$

# Input Impedance (cont.)

$$Z_{RLC} = R \left[ \frac{1}{1 + jQF} \right]$$

Define:

$$x \equiv QF = Q \left( f_r - \frac{1}{f_r} \right) \approx 2Q(f_r - 1)$$

$$\bar{Z}_{RLC} \equiv \frac{Z_{RLC}}{R}$$

We then have:


$$\bar{Z}_{RLC} = \frac{1}{1 + jx}$$

$$\bar{R}_{RLC} = \frac{1}{1 + x^2}$$


$$\bar{X}_{RLC} = \frac{-x}{1 + x^2}$$

# Input Impedance (cont.)


Frequency domain:

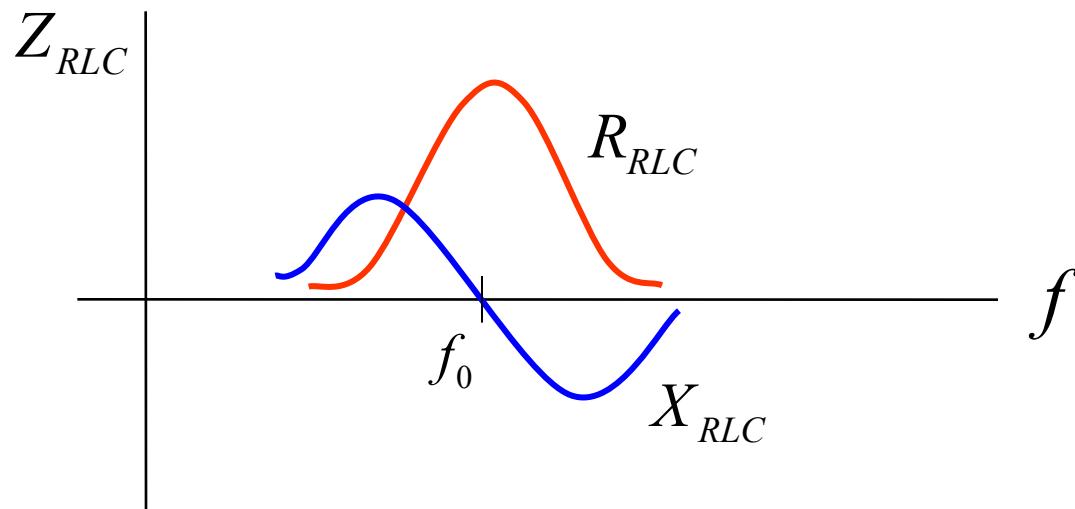

Normalized frequency ( $x$ ) domain:

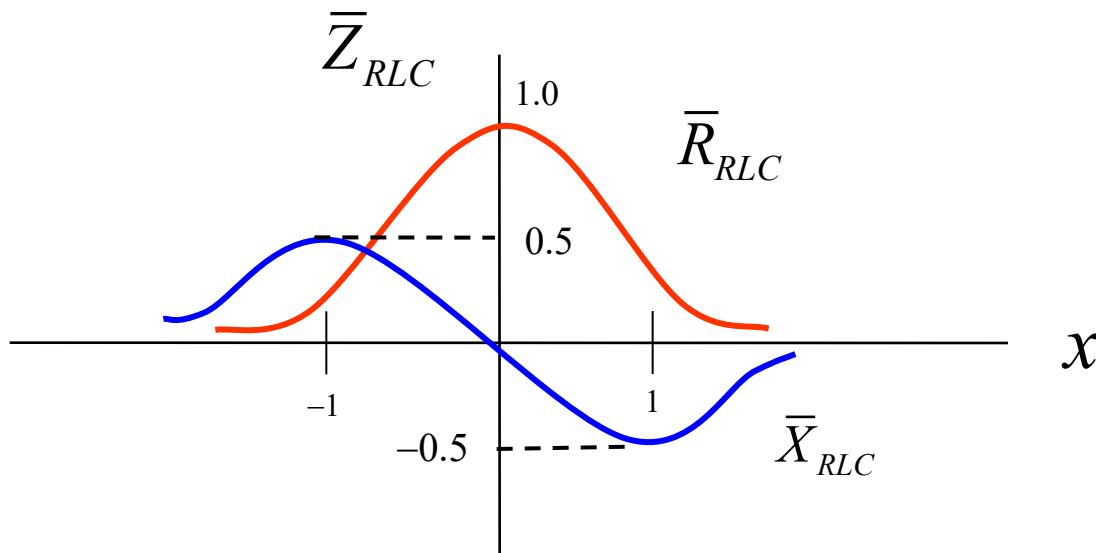

# Reflection Coefficient

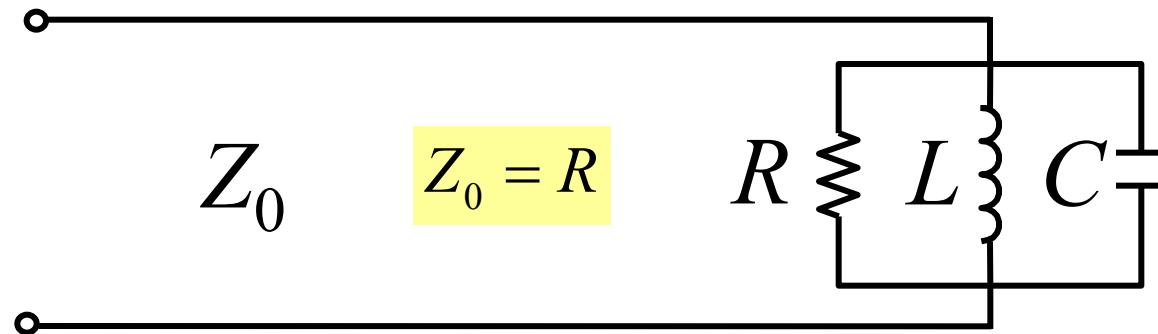

$$\begin{aligned}\Gamma &= \frac{Z_{RLC} - Z_0}{Z_{RLC} + Z_0} = \frac{\bar{Z}_{RLC} - 1}{\bar{Z}_{RLC} + 1} \\ &= \frac{1 - \bar{Y}_{RLC}}{1 + \bar{Y}_{RLC}} = \frac{1 - (1 + jx)}{1 + (1 + jx)} \\ &= \frac{-jx}{2 + jx}\end{aligned}$$



# Bandwidth

$$|\Gamma| = \frac{|x|}{\sqrt{4+x^2}}$$

$$S = \text{SWR} = \frac{1+|\Gamma|}{1-|\Gamma|}$$

Bandwidth definition is based on  $\text{SWR} < S_0$

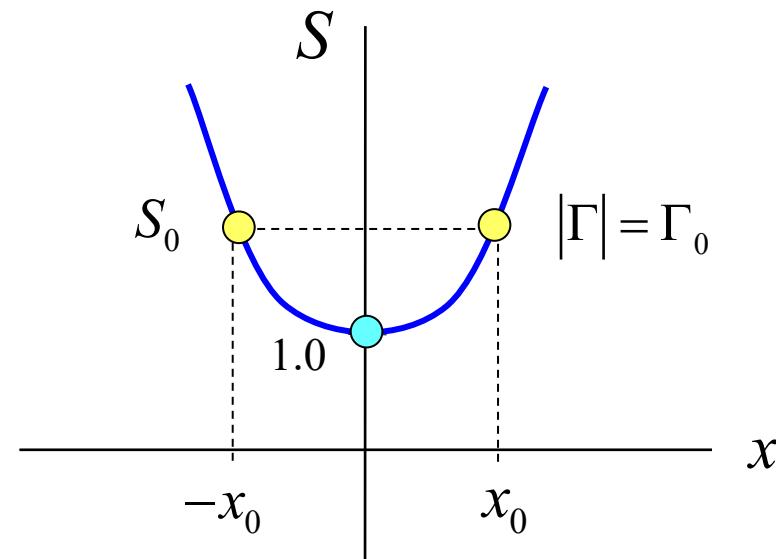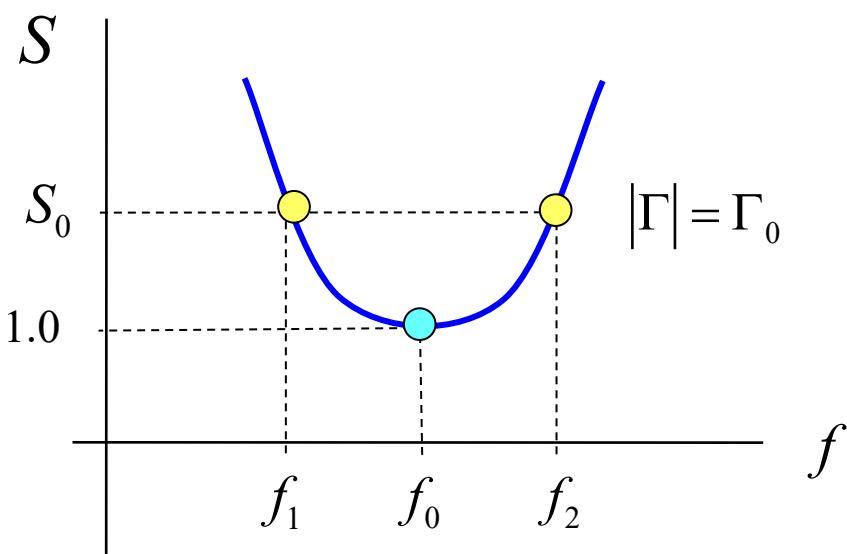(The value  $S_0$  is often chosen as 2.0.)



# Bandwidth (cont.)

Fractional (relative) bandwidth:  $BW = \frac{f_2 - f_1}{f_0} = f_{r2} - f_{r1}$

Recall that  $x \equiv QF = Q\left(f_r - \frac{1}{f_r}\right)$

We can solve for  $f_r$  in terms of  $x$ :

$$f_r - \frac{1}{f_r} = \frac{x}{Q} \quad \Rightarrow \quad f_r^2 - f_r \left( \frac{x}{Q} \right) - 1 = 0$$

so

$$f_r = \frac{\frac{x}{Q} \pm \sqrt{\frac{x^2}{Q^2} + 4}}{2}$$

# Bandwidth (cont.)

To determine correct sign, enforce that  $x \rightarrow 0, f_r \rightarrow 1$

(Therefore, choose the plus sign.)

Hence

$$f_r = \frac{\frac{x}{Q} + \sqrt{\frac{x^2}{Q^2} + 4}}{2}$$

Therefore

$$f_{r2} = \frac{\frac{x_0}{Q} + \sqrt{\frac{x_0^2}{Q^2} + 4}}{2}$$

$$f_{r1} = \frac{-\frac{x_0}{Q} + \sqrt{\frac{x_0^2}{Q^2} + 4}}{2}$$

# Bandwidth (cont.)

Hence,  $BW = f_{r2} - f_{r1} = \frac{x_0}{Q}$

Now we need to solve for  $x_0$ :

$$S_0 = \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|} \quad \text{so} \quad |\Gamma_0| = \frac{S_0 - 1}{S_0 + 1}$$

Also,  $|\Gamma| = \frac{|x|}{\sqrt{4 + x^2}} \Rightarrow |\Gamma_0| = \frac{|x_0|}{\sqrt{4 + {x_0}^2}} = \frac{x_0}{\sqrt{4 + {x_0}^2}}$

# Bandwidth (cont.)

Therefore

$$\frac{x_0}{\sqrt{4+x_0^2}} = \frac{S_0 - 1}{S_0 + 1}$$

so

$$\frac{x_0^2}{4+x_0^2} = \left( \frac{S_0 - 1}{S_0 + 1} \right)^2 \equiv A$$

Thus, we have  $4A + x_0^2 A = x_0^2$

or

$$x_0^2 (1 - A) = 4A$$

# Bandwidth (cont.)

The solution is:

$$\begin{aligned}x_0 &= 2\sqrt{\frac{A}{1-A}} \\&= 2\frac{\left(\frac{S_0-1}{S_0+1}\right)}{\sqrt{1-\left(\frac{S_0-1}{S_0+1}\right)^2}} \\&= 2\frac{S_0-1}{\sqrt{(S_0+1)^2-(S_0-1)^2}} \\&= 2\left(\frac{S_0-1}{\sqrt{4S_0}}\right)\end{aligned}$$

**Recall:**  $A \equiv \left(\frac{S_0-1}{S_0+1}\right)^2$

# Bandwidth (cont.)

Hence,

$$x_0 = \frac{S_0 - 1}{\sqrt{S_0}}$$

We then have


$$\text{BW} = \frac{1}{Q} \left( \frac{S_0 - 1}{\sqrt{S_0}} \right)$$

For  $S_0 = 2$  we have:


$$\text{BW} = \frac{1}{\sqrt{2}Q}$$

# Bandwidth (cont.)


Assume  $S_0 = \text{SWR} = 2.0$

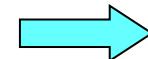

$$|\Gamma| = |S_{11}| = \frac{\text{SWR} - 1}{\text{SWR} + 1} = \frac{1}{3}$$
$$20 \log_{10} |S_{11}| = -9.5 \text{ [dB]}$$

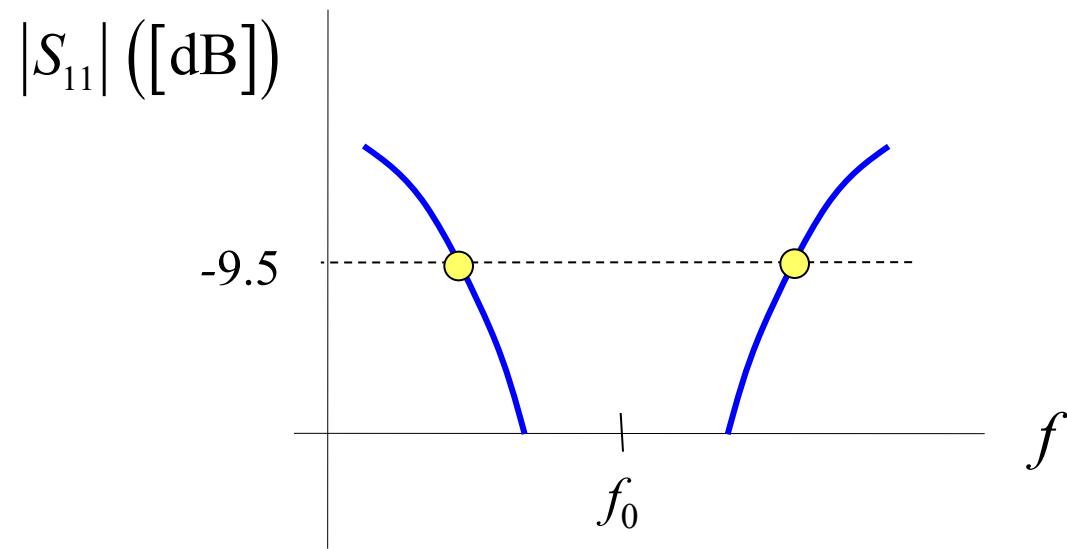


# Complete Model (with Probe Inductance)

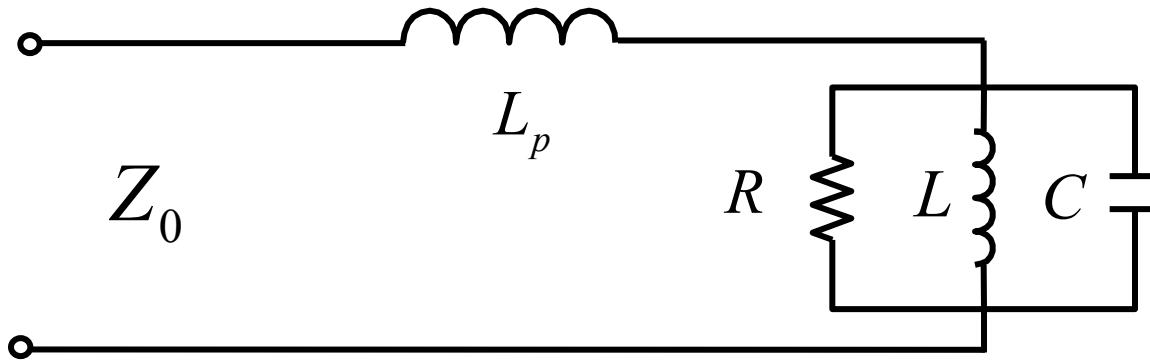

$$X_p = \omega L_p \approx \omega'_0 L_p$$
$$Z_{\text{in}} = jX_p + Z_{RLC}$$

$$\frac{\Delta f}{f_0} \approx (\text{BW}) \left( \frac{1}{\sqrt{2}} \right) \left( \frac{X_p}{R} \right)$$

(This will be derived in a HW problem.)

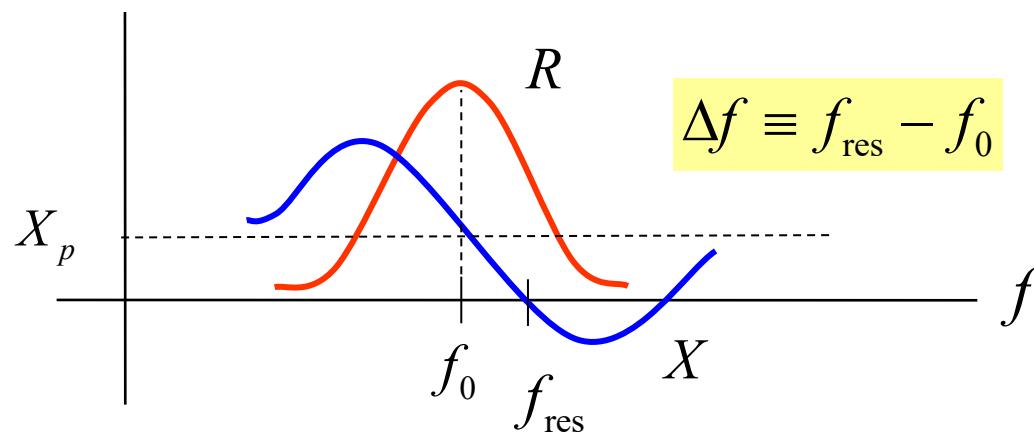

# Complete Model (with Probe Inductance) (cont.)

Outline of Derivation of Formula for  $\Delta f$

Define  $\bar{X}_p \equiv X_p / R$

In terms of the normalized frequency variable  $x$ , the resonance frequency  $f_{\text{res}}$  where the input impedance is purely real, corresponds to

$$x_{\text{res}} = \frac{1 - \sqrt{1 - 4\bar{X}_p^2}}{2\bar{X}_p}$$

(This will be derived in a HW problem.)

If  $X_p \ll R$  then  $x_{\text{res}} \approx \bar{X}_p$

(This follows from a binomial expansion of the square-root term in the numerator.)


Recall:  $f_r = \frac{\frac{x}{Q} + \sqrt{\frac{x^2}{Q^2} + 4}}{2}, \quad f_r \equiv f / f_0$

$$f_r^{\text{res}} = \frac{\frac{x_{\text{res}}}{Q} + \sqrt{\frac{x_{\text{res}}^2}{Q^2} + 4}}{2} \approx 1 + \frac{x_{\text{res}}}{2Q} \approx 1 + \frac{\bar{X}_p}{2Q} \quad (x_{\text{res}} \ll Q)$$
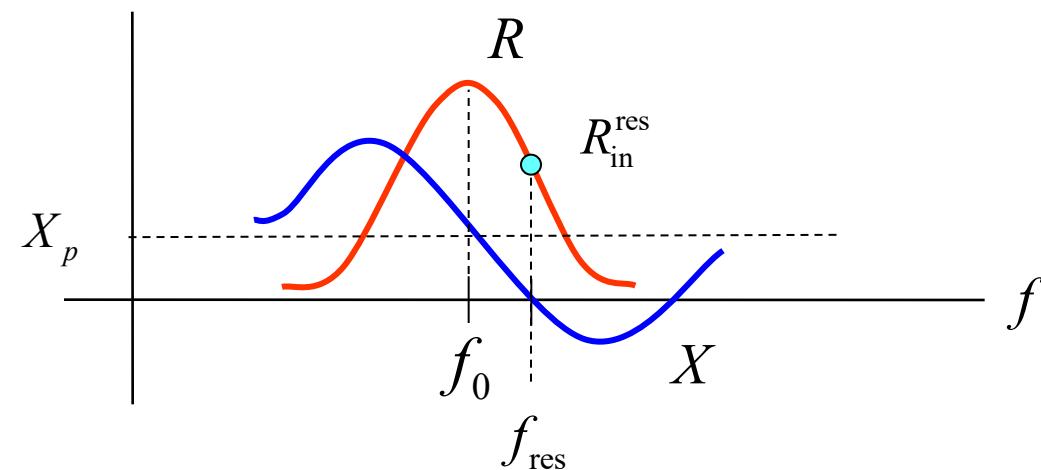
# Complete Model (with Probe Inductance) (cont.)

At the resonance frequency, the input resistance is then:

$$\bar{R}_{RLC} = \frac{1}{1+x^2} \quad \rightarrow \quad R_{in}^{res} = \frac{R}{1+x_{res}^2} \quad \rightarrow \quad R_{in}^{res} \approx \frac{R}{1+\left(\frac{X_p}{R}\right)^2}$$



# Complete Model (with Probe Inductance) (cont.)

$$R_{\text{in}}^{\text{res}} \approx \frac{R}{1 + \left( \frac{X_p}{R} \right)^2}$$

Note that the probe reactance changes the input resistance at resonance.

Given a specified value of the input resistance at resonance (e.g.,  $R_{\text{in}}^{\text{res}} = 50 \Omega$ ), we wish to solve for the corresponding value of  $R$ .

Note that the CAD formula for resonant input resistance (in the short-course notes) gives us the value of  $R$  in terms of the feed location.

# Complete Model (with Probe Inductance) (cont.)

To solve for  $R$ , use

$$R = R_{\text{in}}^{\text{res}} + R_{\text{in}}^{\text{res}} \left( \frac{X_p^2}{R^2} \right)$$

and solve iteratively:

$$R^{(i)} = R_{\text{in}}^{\text{res}} + R_{\text{in}}^{\text{res}} \left( \frac{X_p^2}{(R^{(i-1)})^2} \right)$$

Zero iteration:

$$R = R_{\text{in}}^{\text{res}}$$

First iteration:

$$R = R_{\text{in}}^{\text{res}} + \left( \frac{X_p^2}{R_{\text{in}}^{\text{res}}} \right)$$

Second iteration:

$$R = R_{\text{in}}^{\text{res}} + R_{\text{in}}^{\text{res}} \left( \frac{X_p^2}{\left( R_{\text{in}}^{\text{res}} + \frac{X_p^2}{R_{\text{in}}^{\text{res}}} \right)^2} \right)$$